

ELECTRONICS

Australia

SEPTEMBER, 1978

AUST. \$1.25* NZ \$1.25

COVERING
HI-FI, CB
AMATEUR RADIO
COMPUTERS
AND MORE

HYBRID ELECTRIC CAR



IS LOW COST SOLAR POWER ON THE WAY? ★ HOW TO
TRACK AMATEUR RADIO SATELLITES ★ NEW MIXER FOR
SOUND MOVIES & RECORDING ★ FET-INPUT VOLTMETER

THE LOGICAL CHOICE



SONY'S NEW TC-K7II REDUCING WOW & FLUTTER TO LESS THAN 0.045%

Introducing the King of Sony's new K series cassette decks. The outstanding TC-K7 II with Sony's most advanced electronic and mechanical engineering.

This is a deck that not only has specifications that are superior to many open reel decks but features easy to operate, gentle touch, logic controls in all tape transport modes. There is no need to push the stop bar when changing modes and should the wrong mode be selected accidentally, no damage can occur to your tapes or your deck. All modes including "record mute" can be activated from the optional remote control unit (RM 30).

How do Sony achieve that incredibly low wow and flutter figure (0.045% WRMS). Firstly by using a two motor system, each designed to do a specific job. One motor is for reel drive and Sony's New Tri-Duty Motor handles the capstan drive. The Tri-Duty Motor is a superb piece of engineering and with its servo system, speed variations caused by either line voltage fluctuations or tape load are virtually eliminated.

The TC-K7 II features a "Double" integrated, recording and play back level indication system. Dual, high quality VU meters are augmented by three instant reacting LED peak level indicators, set at "0" and at +4 and +8 dB, so that the oversaturation of recording circuits can be prevented.

Naturally the TC-K7 II has Dolby but it also has an MPX filter defeat (Filter off) mode, a record mute facility and a three position memory rewind and replay facility. The tape select system has three step bias and three step equalisation selectors, giving nine possible positions, for optimum performance from a wide variety of tapes.

At the heart of this deck there's Sony's Ferrite and Ferrite head, hard and highly polished, like black diamond, to give years of head life.

The combination of Sony engineering and research with logic controls and Sony's new Tri Duty Motor produces a cassette deck that must be the choice of discerning Hi-Fi enthusiasts: A sound logical choice.

CHECK THESE EXCEPTIONAL SPECIFICATIONS

Frequency Response	20 Hz — 18,000 Hz (FeCr)
	20 Hz — 17,000 Hz (CrO2)
S/N Ratio	60 dB (FeCr, Dolby off, peak)
Wow and Flutter	0.045% WRMS
Harmonic Distortion	1.3%

SONY
Research makes the difference.

GAC S 9655

ELECTRONICS


Australia

Australia's largest selling electronics & hi-fi magazine


On sale the first Monday of each month

VOL. 40 No. 6

SEPTEMBER, 1978

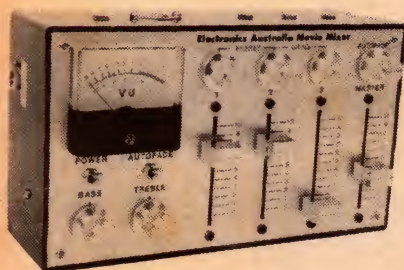

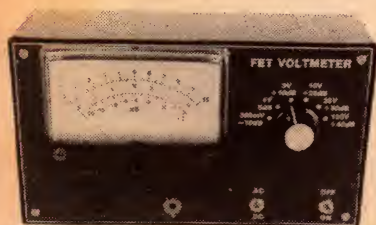Our new 3-input audio mixer design features tone controls, a level meter, a headphone monitoring output, and auto-fading. Full construction details start on p42.



High input impedance and wide frequency response are the main features of this compact new meter which employs a single IC. Details on p74.

On the cover

This new British hybrid electric car has a system that recharges its own batteries. In the "boot" is a petrol generator, designed to replace a conventional engine, and adjacent to it are four 12V heavy duty car batteries. The batteries and a 1.86kW electric motor fitted over each of the rear wheels are charged and driven in parallel by the generator. The method could cut fuel consumption in half for a 2-litre sized car. (Photo courtesy British Information Service). See also Forum, p17.

FEATURES

- THE NATURAL EFFECTS OF ELECTRO-ACOUSTICS *Multi-purpose halls* 8
- SOLAR POWER: CUTTING THE COSTS *Amorphous silicon solar cells* 10
- THE WORLD OF THE PIEZOELECTRIC POLYMER *New, lightweight transducers* 12
- ANDREW DARBYSHIRE: APPRENTICE AT STATION 3DB
Radio apprentice training 20
- A TRIP THROUGH 'SILICON VALLEY' *Jim Rowe reports on his USA trip* 22
- HOW TO PICK UP THE AMATEUR SATELLITES *Keeping track of OSCARs 7 & 8* 52
- PARAMETERS/EA GRAND INSTRUMENT CONTEST NO. 5 *Win an oscilloscope* ... 127

HIFI NEWS AND REVIEWS

- THE CHICAGO CES: FROM THE WAY AHEAD TO THE WAY OUT
New hifi products 31
- REVIEW: SANSUI G-5000 STEREO RECEIVER *3-page in-depth review* 38

PROJECTS AND CIRCUITS

- MIXER FOR HOME MOVIES *Unit has tone controls, 3 inputs & auto-fading* 42
- UPGRADED 200MHz DIGITAL FREQUENCY METER PT 2
Completing construction 60
- ADAPTING THE VNG-DERIVED REFERENCE FOR ASTRONOMY
Some basic changes 70
- SENSITIVE FET-INPUT AC-DC VOLT METER *Low cost and easy to build* 74
- SOFTWARE ROUTINES FOR THE ULTRA-LOW COST VDU *Using DMA* 82
- ALTERNATIVE KEYBOARD FOR THE LOW COST VDU
Interfacing the KBD-5 keyboard 92

AMATEUR RADIO, CB SCENE, DX

- CB SCENE: THE LOGICAL NEXT STEP FOR THE KEEN CBER
Novice amateur exam 95
- AMATEUR RADIO: *Strong amateur reaction to proposed 5A expansion* 106
- REVIEW: FDK MULTI-800D 2-METRE TRANSCEIVER *A good performer* 111
- SHORTWAVE SCENE *Radio Nederland links relay bases via satellite* 122
- REVIEW: YAESU FRG-7000 COMMUNICATIONS RECEIVER *A desirable unit* 126
- REVIEW: TRIO CO-1303G 75mm CRO *Ideal for the amateur "shack"* 127

COLUMNS

- EDITORIAL *The channel 5A problem* 3
- FORUM *Bits and pieces month, but first the Boeing satellite power source* 16
- THE SERVICEMAN *More than an intermittent — a real challenge* 64
- RECORD REVIEWS *Classical* 114
- RECORD REVIEWS *Devotional, popular and jazz* 117

DEPARTMENTS

NEWS HIGHLIGHTS 4 — CIRCUIT & DESIGN IDEAS 68 — MICROCOMPUTER
NEWS & PRODUCTS 90 — NEW PRODUCTS 122 — BOOKS & LITERATURE 129 —
INFORMATION CENTRE 133 — MARKETPLACE 134 — INDEX TO ADVERTISERS
136 — NOTES & ERRATA 133

Now. Two 3-way 40 watt speakers with nine tonal choices Save about \$50 per hour while you assemble them

Even if you didn't know them by number, you probably heard about the Philips AD12K12 MK11 Speaker Kits.

Because they are now a no.1 best-seller.

And here is the compact AD8K30, 8" 3-way compact system, with fine electronic and acoustic components (1" domed tweeters, 5" mid-range, super 8" bass drivers). Brilliant clean sound, with a frequency response closely following the ideal Bruel & Kjaer curve for hi-fi equipment measured in an actual listening room, using the "Third Octave Pink Noise Method".

Plus 9 combination tonal choices to adjust to the acoustics of your own listening-room.

You can assemble the AD8K30's in about two hours. You will get a professional result and save about \$100 per pair over a comparable system. Phone or send coupon now for full details of this and all our kits.

PHILIPS ELECTRONIC COMPONENTS AND MATERIALS

Sydney 427 0888 • Melbourne 699 0300 • Brisbane 277 3332
• Adelaide 45 0211 • Perth 65 4199



ELCOMA

Philips Electronic Components and Materials
P.O. Box 50, Lane Cove, NSW 2066

Please send me full details and brochures on your loud speaker kits and a list of retailers who stock them.

NAME _____

ADDRESS _____

STATE _____ P/CODE _____

EA



**Electronic
Components
and Materials**

PHILIPS



Editorial Viewpoint

The channel 5A problem . . .

EDITOR-IN-CHIEF

Neville Williams
M.I.R.E.E. (Aust.) (VK2XV)

EDITOR

Jamieson Rowe
B.A. (Sydney), B.Sc. (Technology, NSW)
M.I.R.E.E. (Aust.) (VK2ZLO/T)

ASSISTANT EDITOR

Phillip Watson
A.M.I.R.E.E. (Aust.) (VK2ZPW)

SCIENCE FEATURES

Greg Swain, B.Sc. (Hons, Sydney)

PRODUCT REVIEWS

Leo Simpson

TECHNICAL PROJECTS

David Edwards, B.E. (Hons, Tasmania)
Ian Pogson (VK2AZN/T)

GRAPHICS

Robert Flynn

PRODUCTION

Danny Hooper

ADVERTISING MANAGER

Selwyn Sayers

CIRCULATION MANAGER

Alan Parker

During recent weeks, there has been vigorous protest from the amateur fraternity over reported Government plans to make greater use of TV channel 5A. Amateurs fear that, since Channel 5A is immediately adjacent to their own 144-148MHz band, interference problems could lead to a restriction of amateur activity on that band.

While there is undoubtedly some ground for such fears, amateur protests have been weakened by a tendency to substitute emotive statements for hard, proven fact. For example, one correspondent rounded off his letter to us by suggesting that we needed only to ask any amateur in the Wollongong area to discover how serious the problem was.

This last observation surprised us because, despite all the 146MHz traffic between Sydney and the South Coast, we had never as much as heard mention of interference problems. And, when we started asking questions, it seemed that few South Coast amateurs had heard of them either! Even the local radio inspector had to rack his brains to remember any complaints from TV viewers involving 146MHz interference.

Faced with that kind of evidence, the authorities might be forgiven for concluding that the amateurs were "crying wolf". As someone remarked to me: if there is a real interference problem with channel 5A, the amateurs should surely be in a position to demonstrate and document it in the field.

In fact, it would appear that the greatest potential problem is not in the normal service area of a main regional 5A transmitter, because its direct signal can usually over-ride possible interference from amateur stations. It concerns, rather, possible penetration of amateur signal into translators tuned to the regional transmitter. This would affect, not just the isolated viewer, but every receiver tuned to the particular translator!

Assuming that greater use does have to be made of channel 5A to help clear the FM band, the critical thing is therefore to pressure the authorities to do what they have already done for many other translators: to feed them via UHF.

A further and logical step would be to instal, not just a UHF link, but a UHF service in parallel with the main 5A regional. Viewers could be encouraged to use the UHF signal to reduce dependance on 5A, and to hasten the day when it could be phased down and out.

Indeed, it should be possible, as funds permit, to parallel other troublesome VHF channels with a UHF service, so that our spectrum problems will gradually wind down rather than up!

— Neville Williams

Registered for posting as a publication — Category B.

Printed by Magazine Printers Pty Ltd, of Regent Street, Sydney and Masterprint Pty Ltd of Dubbo, NSW, for Sungravure Pty Ltd, of Regent St, Sydney.

*Recommended and maximum price only.

Editorial Office

57 Regent St, Sydney 2008.
Phone (02) 699 3622
Postal Address: PO Box 163, Beaconsfield 2014.

Advertising Offices

Sydney — 57 Regent St, Sydney 2008.
Phone (02) 699 3622

Representative: Narcisco Pimental.
Melbourne — 392 Little Collins St, Melbourne 3000. Phone (03) 602 3033

Representative: Steve Deadman

Adelaide — Charles F. Brown & Associates Ltd,
168 Melbourne St, North Adelaide 5008
Representative: Tom Duffy, (08) 267 4377.

Perth — 454 Murray Street, Perth 6000
Representative: Ashley Croft, (09) 21 8217.

Subscriptions

Subscription Dept, John Fairfax & Sons Ltd, GPO Box 506, Sydney 2001.

Enquiries: Phone (02) 20944, ext 2589.

Circulation Office

21 Morley Ave, Rosebery, Sydney 2018
Phone (02) 663 3911.


Distribution

Distributed in NSW by Sungravure Pty Ltd, 57 Regent St, Sydney; in Victoria by Sungravure Pty Ltd, 392 Little Collins Street, Melbourne; in South Australia by Sungravure Pty Ltd, 101-105

Weymouth St, Adelaide; in Western Australia by Sungravure Pty Ltd, 454 Murray Street, Perth; in Queensland by Gordon and Gotch (A'asia) Ltd; in Tasmania by Ingle Distributors, 93 Macquarie St, Hobart; in New Zealand by Gordon and Gotch (NZ) Ltd, Adelaide Rd, Wellington.

Copyright. All rights reserved

Devices or arrangements shown or described herein may embody patents. Information is furnished without responsibility for its use and without prejudice for patent rights. All manuscripts, photographs and other material submitted to Electronics Australia for publication must be accompanied by a stamped, addressed envelope. Contributions are submitted at the sender's risk, and responsibility for loss cannot be accepted by Electronics Australia.

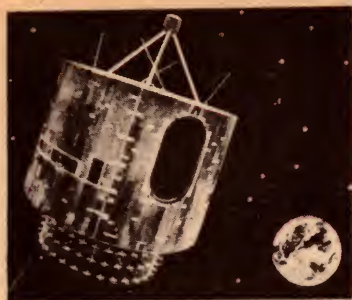

News Highlights

Tokamak for Sydney University

Imagine a flash, a bit longer than the flash from a camera, a deep pinkish red in colour, happening once a second for most of the day and night. This is what the new tokamak at the School of Physics, Sydney University, will be emitting when it is completed next year.

Incidentally, a tokamak is a doughnut-shaped plasma confinement device for research into the problems associated with nuclear fusion.


Nuclear fusion (the fusing together of atomic nuclei, as opposed to the splitting, or fission of nuclei) holds out the exciting prospect of providing a pollution-free and inexhaustible source of electrical power.

Large research projects costing hundreds of millions of dollars are in progress overseas, and many scientists are optimistic that fusion will become feasible within the first decades of the next century. Countries like Australia can assist with small, inexpensive projects which can supply vital data despite their small size and cost.

Sydney University's tokamak will be about 1½ metres in diameter and will stand about 2 metres high. It will be, in the words of Mr Hugh Kirbie, a "real crowd pleaser". The machine will be built with 24 diagnostic ports, at least 6 of which will be available to look inside at the glowing plasma.

The tokamak is a busy machine. Before each experiment it needs to spend from 7-15 hours discharging once a second. This cleans out impurities which gather on the walls inside the doughnut-shaped device. The impurities, consisting of oxygen and carbon, occur because of air leaks or oil impregnation.

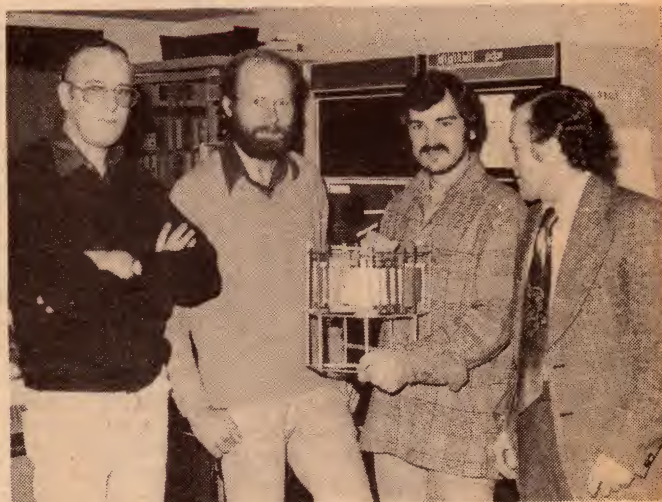The impurities could cause difficulties when the



From left to right: Dr Rodney Cross, Dr Brian James, Mr Hugh Kirbie, and Associate Professor John Lehane with a model of the proposed tokamak.

hydrogen gas inside is repeatedly heated up to 1 million degrees or so for short periods to experiment on plasma containment and diagnosis. In discharge cleaning, the hydrogen combines with the carbon and oxygen to produce methane which is pumped out of the system.

First trials for wave energy rafts

Shown in the accompanying photograph is an artist's impression of articulated wave energy rafts, designed by hovercraft inventor Sir Christopher Cockerell. Such a system could eventually convert power from the waves into electricity in sufficient quantities to feed into Britain's national grid. One is already undergoing trials off the coast of Britain.


The Cockerell Raft consists of a series of pontoons linked together and designed to take advantage of the alternating crest and trough of each wave, the relative movement of the adjacent pontoons producing a motion from which energy can be extracted. This is done either by a gearing system or via

hydraulic rams (see lower diagram) which in turn drive electrical alternators.

Trials off the coast of England using one tenth scale models of the Raft were set up recently to verify results obtained in small scale tank testing of the device. The trials were held in wave conditions approximately one tenth the height of those found in the Western Isles of Scotland and the Western Approaches to the English Channel.

Experts calculate that a 965km stretch of wave energy machines set in those areas could, in principle, provide about one half of the UK's present electricity demand.

Britain is among world leaders in

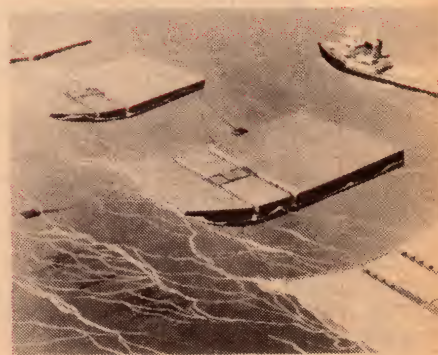

wave energy extraction research at a time when fossil fuels are becoming increasingly scarce.

IBA tunes to satellite TV

British engineers at the Independent Broadcasting Authority (IBA), Crawley Court, Winchester, are now receiving super-high-frequency (SHF) beacon transmissions from the new European Orbital Test Satellite.

The short-term objective of IBA space research is to prepare for Eurovision program exchange via satellite in the early '80s; and in the longer-term to prepare for possible direct broadcasting to homes from space satellites.

The Orbital Test Satellite (OTS) of the European Space Agency was successfully launched from Florida on May 11, 1978 and has now been manoeuvred into position at approximately 11° east.

The objectives of the current European space experiments are to gain experience of television working with satellites; to obtain detailed knowledge of the depolarisation and other effects of weather on SHF signals; to assess the performance of future satellite systems for television distribution and direct broadcasting to homes; and to assess the performance of different forms of modulation, including frequency and digital modulation systems.

New Tandy stores


Tandy Electronics recently announced the opening of three new stores to bring its Australian tally to 117. The new store locations are: 525 Brighton Rd, Brighton, South Australia; Shop 85, Belconnen Mall, Benjamin Way, Belconnen, ACT; and Shop 26, Woodridge Plaza, Wembley Rd, Woodridge, Brisbane. 1978 is Tandy's fifth year of retailing in Australia.

Cordless soldering iron



Released around two years ago by Scope Laboratories (Melbourne), this 60W cordless soldering iron is powered by a pair of NiCd D cells and can reach operating temperature in 6-10 seconds. It can solder over 100 light electrical joints between recharges, and can be recharged between jobs and overnight with a car or workshop recharge accessory. For further information, contact Scope Laboratories, 3 Walton St, Airport West 3042.

Kits for EA Projects

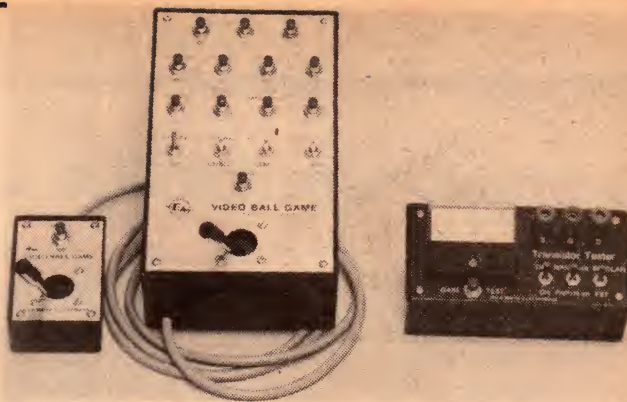

Dick Smith Electronics has produced kits for two recent EA projects: the Video Ball Game and the Transistor Tester. Both were featured in the July 1978 issue of EA.

The kits contain all parts needed to build the projects, except batteries. In addition to electronic parts and hardware, they contain prepunched and anodised front


panels which give the projects a "professionally-made" appearance.

The Video Ball Game Kit (catalog number K-3491) is priced at \$49.50 and the Transistor Tester Kit (catalog number K-3052) \$17.90. They are available at Dick Smith stores or by mail order (post and packing extra) from PO Box 747, Crows Nest, NSW 2065.

Neutron "gun" fights cancer growths

This £1 million cyclotron unit at the Western General Hospital in Edinburgh, Scotland bombards a cancerous tumour with a rapid stream of neutrons that can reach the 'target' without damaging surrounding healthy tissue.

It is the first unit to be based entirely on the new fast neutron therapy treatment of cancer in place of conventional radiotherapy methods. It is also the first unit in the world to be fitted with a steerable beam which can fire its concentrated high speed neutron stream at a patient's body from all angles. This is expected to increase considerably the success rate in treating cancerous tumours that have resisted conventional treatment.

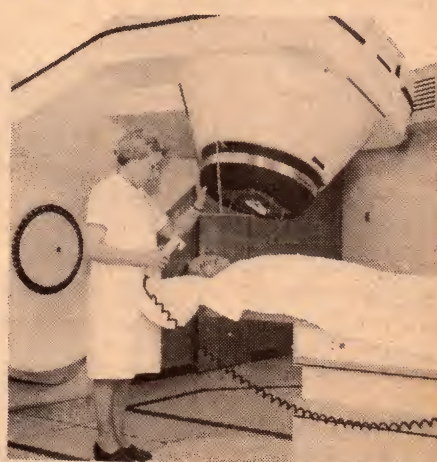

Teletext tests in Sydney & Melbourne

A series of Teletext test transmissions has been carried out in Sydney and Melbourne under the supervision of the P & T Department. The tests, which took place on 29th June last, were conducted to determine the interference effects of Teletext transmissions on domestic television receivers under a wide range of conditions.

Tests were carried out to determine the effects of:

- varying the number of Teletext lines transmitted;
- varying the line positions of the Teletext signal; and
- varying the percentage level of the Teletext signal.

In addition, a number of other tests were carried out to assess the performance of a number of specially fitted Teletext decoders. The tests will help

determine Australian standards for a possible Teletext service.

More than 1000 people took part in the survey, most generally associated with the local TV industry in one way or another. The tests originated in Sydney, and were put to air simultaneously by ABN-2, ATN-7, and TEN-10. Telecom bearer circuits were used to relay the signals to Melbourne for transmission by ABV-2, ATV-0, and HSV-7.

Signals were also relayed to ABAV-1 for transmission in the Albury-Wodonga area.

Developed by BBC and IBA engineers in Britain, Teletext is a technique whereby data is transmitted during the vertical blanking periods of a normal TV transmission. This information can be called up and displayed on the screen by the home TV viewer.

Computer-controlled editing of TV programs

The editing of special visual effects into television programs by manual instructions and switching is a thing of the past at Video Tape Corporation, Sydney's largest television tape and film post-production complex. A computer is now doing the job.

The company's recently installed \$500,000 computerised electronic editing complex is proving a very effective new technical aid, not only for producers of episodic-type programs but also for producers of television commercials, of which VTC processes a large share.

Previously, a producer editing videotape or film footage had to list all the cuts, colour variations, wipes, and fades he wanted in the job. He indicated the exact spot in the footage he wanted this done, and then left it to a control room technician to do this with split-second timing as he viewed the tape or film.

Now technical and editing instructions are prepared in the form of code numbers and fed into the memory of a CMX 340X computer editing system. This in turn is linked to a Control Dynamics Vision Switcher and a bank of four VPR-1 Ampex 1-inch videotape recorders.

The tape or film is run, and the computer does the rest. The visual effect or



Picture shows the heart of Video Tape Corporation's new editing system. The vision switcher is situated at left, while the computer terminal is at right.

editing is exact and achieved more efficiently than human hands operating a bewildering array of control switches.

Roger Weatherstone, Manager of Video Tape Corporation, explained that the new complex cuts down the time involved in post-production,

besides permitting a greater range of visual effects with either videotape or film. And, it will enable Video Tape Corporation to provide a faster turnaround of work to producers and production companies and free its technical staff for other urgent duties.

Dutch buy Viewdata know-how

The Netherlands has recently signed a contract to buy British Post Office know-how on the Viewdata system. Viewdata is a revolutionary communications system that enables people to call up information from computer data banks via the telephone network and have that information displayed on their TV sets.

The Netherlands is the second country to decide to acquire software for Viewdata, the first overseas sale going to West Germany in August last year. The contracts with Germany and the Netherlands are of the two-fold value: they will help ensure a common Viewdata standard; and will enable the development of one basic IC chip for international application.

New VCRs launched in Australia

With VCR sales in Europe and the USA booming, three new long-play VCR models have recently been released in Australia to compete with the previously released Philips N1700 unit. The new models, from Akai, Sony and Grundig, feature playing times of 3 hours, 3¼ hours, and 5 hours respectively. They were recently demonstrated to the technical press by Mr Derry Weis, owner of Consolidated Video Industries, 2 Guilfoyle Ave, Double Bay, 2028.

Prices of the three models vary in ac-

cordance with playing time and facilities. The Akai VS 9200EA unit is the cheapest of the three at around \$1295. Main features are a 24 hour timer and a memory rewind facility. The Sony Betamax, at \$1399, costs a little more than the Akai unit, but offers a 3-day timer and 15 minutes longer playing time.

The Grundig 4004 is the most advanced of the three units. It features 5 hours of playing time, a 10-day timer, remote control, and a facility to set the unit to record more than one program



Retailer Derry Weis demonstrates the Sony Betamax VCR. His company sells most of the major VCR brands.

in advance. Retail price is around \$1695.

All the models listed are capable of recording both VHF and UHF transmissions, and all have 24-hour LED digital time indicators and built-in tuners.



A WORLD OF ENERGY CONSERVATION

Think of how much energy is wasted in the production of millions of zinc or alkaline batteries. Once their energy supply has been used up, they are discarded.

The General Electric rechargeable battery system is the answer to power conservation. The G.E. battery is rechargeable and thus recyclable. Conservation of energy is the essence of this product. Don't throw away batteries. G.E.'s nickel cadmium rechargeable batteries can be recharged up to a thousand times. They last for years.

The features of the G.E. rechargeable battery are:-

- Constant voltage throughout the discharge period.

- Available in all standard sizes.
- Special heavy duty versions for industrial use.
- The heavy duty rechargeable batteries are designed to withstand high ambient temperatures and continuous discharge overload.

Be part of the energy conservation movement. Look into the General Electric Rechargeable Battery System.

For information on the G.E. nickel cadmium rechargeable battery system and list of stockists, fill in the coupon and return to Australian General Electric Battery Division, 86-90 Bay Street, Ultimo, N.S.W. 2007.

Name

Address

.....Post Code

GENERAL  **ELECTRIC**

The natural effects of electro-acoustics

By using modern electronic techniques, it is possible to tailor the acoustic response of concert halls or auditoria to suit the occasion. This article briefly outlines the electro-acoustic methods that have made multi-purpose halls a reality.

At one extreme, a multi-purpose hall must respond like a concert hall, warmly and sympathetically, to the infinite riches of a full symphony orchestra; and at the other it must permit every member of an audience to hear each syllable spoken by an actor as though he were only a few metres away.

Those are conflicting requirements. The sounds of orchestra, choir or organ must not be rudely hurried away: they must be permitted to linger a little while, just long enough for the diminishing glory of each sound to colour the succeeding sounds. That's what the composer had in mind when he wrote the music, because that's how he was (or is) accustomed to hearing music. But the sound of speech is not to be changed; it must be conveyed without converting it, because that's

how our ears were made to hear it.

We may express the varied requirements quite simply: any sound which is to be heard in the hall must sound natural. Unfortunately, there is no hall in the world which, in its natural state, will allow all kinds of sounds to be heard naturally. That is where the latest developments in electro-acoustics come in: they impart the desired naturalness to whatever kind of sound is being made, enhancing, overcoming, or not interfering with, the natural acoustics of the hall.

If a loud sharp noise is made in the hall — the engineer shown in the new Oslo Concert Hall is doing it professionally with a pistol — the direct sound of it will be followed by a gradually diminishing indirect sound, lasting up to two or more seconds. This phenomenon is known as reverberation, and the time for it to die away is known as the reverberation time. The professionals measure this time precisely with instruments, because it is the critical factor in designing an electro-acoustic system.


Reverberation is caused by the sound waves being reflected from walls, ceiling and floor. In the large volume of a cathedral, with hard surfaces which absorb very little of the sound striking them, a sound may take as much as five seconds to die away. In that time it will have travelled about 1700 metres. It is doubtful whether such a long reverberation time really suits any kind of music at all, though of course it creates an incredibly colourful tapestry of sound of cathedral choir and organ. The human speaking voice, however, is hopelessly and unintelligibly jumbled up in such an acoustic environment; in five seconds, there are ten or more spoken words!

In general, the reverberation time of an enclosed space increases with the volume, as the graph shows. However, the sound-absorbing properties of the walls, ceiling, floor, clothing of the audience, and other surfaces, have the effect of reducing the reverberation time because the sound dies away more quickly each time it strikes an absorbent surface. Thus a hall's reverberation time can be changed, within limits, by changing suitable surfaces. Note, however, that for the same reason a hall filled with spectators will have a shorter reverberation time than the same hall only partly filled, unless the seats are designed to have similar absorption characteristics to those of an audience.

Reverberation times which are typically suitable are: 1.5 to 2.5 seconds for orchestra, choral and organ music; about 1 second for cinema purposes; and about 0.5 to 1 second for jazz or chamber music (which, of course, is written for performance in what used to be called a chamber — typically a principal room in a large house). Speech requires the lowest practicable reverberation time — preferably not more than about 0.5 to 1 second.

How, then, can a multi-purpose hall meet these changeable requirements? The answer is to equip it with a sound-amplifying system to enable the acoustics to be adjusted to suit each application.

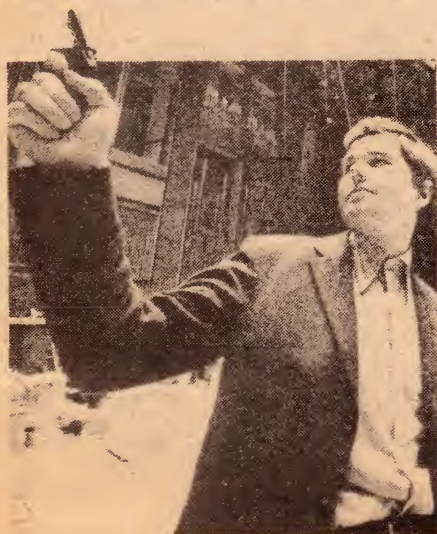If it is a hall with a long reverberation time, suitable for orchestra or choir, it can be equipped for speech with a directional sound-reinforcement system or a stage amplification system, the loudspeakers of which beam the sound of the human voice only to the audience, thereby minimising reverberation. In the case of a large hall, loudspeakers placed farther away



An engineer tests the acoustics of the new Oslo Concert Hall by using a pistol as the sound source.

from the sound source (eg. towards the back of the hall) are supplied with a signal which is delayed so that, for the audience in that part of the auditorium, all the sound arrives at the same time both directly from the person speaking and indirectly from the loudspeakers.

If, however, the hall has a short reverberation time, appropriate to speech, drama, etc., it can be given the characteristics of a long reverberation time, to suit orchestral, choral or similar music. This facility can be provided in various ways. For example, the sound of the orchestra or choir can be picked up by near-by microphones and fed into a reverberation device (there are several possible types), which has a number of outputs, each connected to loudspeakers. The overall effect is to produce a reasonably adequate indirect sound field.


The newly-developed Multi-Channel Reverberation (MCR) system from Philips, however, provides a more advanced solution to this problem and has advantages over the earlier reverberation devices mentioned above. A large number of microphones, distributed throughout the hall (in the ceiling and walls), pick up the indirect sound field, and the signals from these microphones are fed to individual loudspeakers.

The effects of MCR are to enhance the sound-reflection characteristics of the hall. It enables direct control of reverberation time and reverberation level to give the desired sound necessary for the music being played. In addition, an important new feature is that the musicians can be supplied with the same diffuse sound as the audience, which is very helpful to them. It gives them a sense of "ambiance" — each musician no longer feels he is playing in isolation but experiences a certain inspiration from hearing the others.


Without explaining all the possible ramifications of electro-acoustics in all kinds of halls — each hall is unique in its requirements — it is perhaps sufficient to point out that these systems are not restricted to multi-purpose halls. They can be applied to existing or new halls; they can convert a limited-purpose hall into a multi-purpose hall; they can improve the acoustics of a hall which was built with certain purposes in mind but which has fallen short of the ideal — it is hardly possible to cover all variations.

However the complexities and subtleties of sound — particularly the sound of music — are so important artistically, that we must consider another factor.

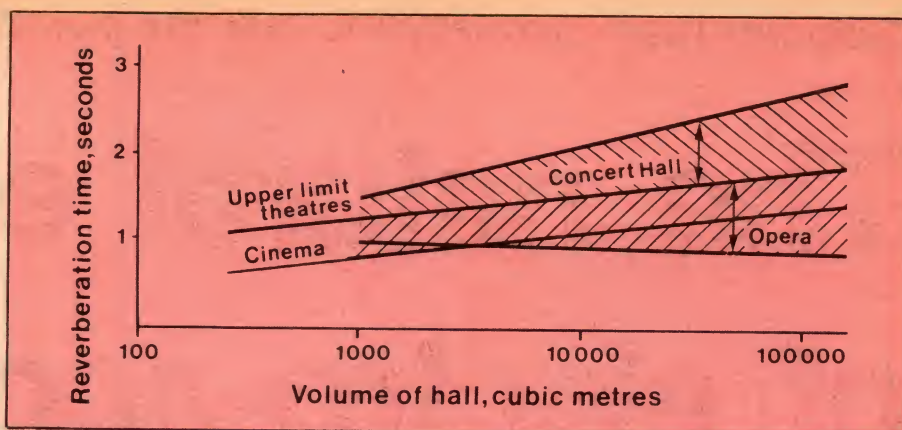What has to be done to ensure that the loudspeakers reproduce the sound of, say, an orchestra faithfully, so that the balance between different instruments, over the full frequency range of the whole orchestra, is maintained exactly in conformity with the



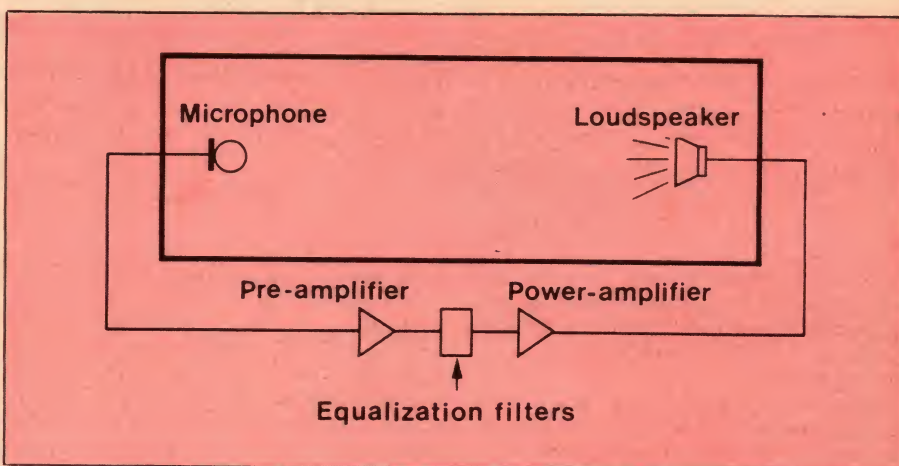Typical reverberation times for theatres and concert halls.



The basic elements of one loop of a sound reinforcement system.

desired balance for which the conductor and the musicians have striven?

Unless steps are taken to ensure this maintenance of the original balance, the particular characteristics of the chosen microphones and loudspeakers, in association with the acoustic environment, have the effect of accentuating certain frequencies at the expense of others.

The method of correcting this effect is known as "equalization", ie ensuring that, as far as possible, the system provides equal amplification throughout the frequency range.

Equalization has to be done in two ways: first, equalizing the loudspeaker-plus-hall-acoustics system; second, equalizing the sound reinforcement system. The latter must be considered as a loop, and includes the acoustic path between the loudspeakers and microphones.


It should be noted that failure to equalize the amplification throughout the frequency range would not only distort the sound of the music; it would also increase the risk of "howl" or "acoustic feedback", and at the same time unnecessarily limit the capacity of the system to amplify the sound.

The accompanying diagram shows the basic elements of one loop of a sound reinforcement system in a hall. It

will be noted that instead of there being simply one amplifier, there are two: the pre-amplifier raises the voltage of the signal from the microphone from its very low level, and the power amplifier both raises the voltage still further and delivers sufficient power to drive all the loudspeakers.

Equalization is achieved by interposing special filters between the two amplifiers. These filters reduce the peaks, ie. at the frequencies where amplification is too much; and lift the dips, ie. at the frequencies where amplification is too little. They give remarkable improvements in sound quality.

Thus the system as a whole maintains the correct balance, and it can be used to its maximum amplifying power without causing howl.

With the reverberation characteristics of the hall variable and under control, with the frequency characteristics of the music or other sound maintained, and with the sound level perfectly suited to the needs of every member of the audience, we have a hall which always sounds natural, whoever is using it. 

Reprinted with acknowledgement to N.V. Philips' Gloeilampenfabrieken "Sound + Image" magazine.

Solar power: cutting the costs

With the price of conventional fossil fuels set to skyrocket, solar power looks like becoming an increasingly important energy source over the next few decades. The main hassle so far has to do with solar cell costs. Researchers at RCA Laboratories in Princeton, New Jersey, have come up with one possible answer to the problem.

Up to now, the cost of tapping electricity directly from the Sun has been very high indeed. At around \$15 a watt, cost is the main reason large solar cell arrays are not delivering tens of kilowatts or megawatts to homes and buildings.

Technological limitations combined with a small, specialised market are the main reasons why solar cell prices have remained so high over the years. The major use of solar cells to date has been in spacecraft, where they must be used regardless of cost. However, they have also been used for low power applications in remote locations on Earth.

That situation may change in the near future, however. With the energy "crunch" firmly in view, there's a growing effort to reduce solar cell costs and bring solar power down to earth. The

industry goal now is to cut the cost to around 50¢ a peak watt by 1986 and to 30¢ by 1990.

At those prices, solar cells would be able to produce electricity at a cost competitive with conventional sources of power.

A number of schemes are now under development to reduce solar cell costs. Such schemes include the development of techniques more suited to mass production, new crystal growing methods, and solar tracking and concentrator mechanisms to improve overall system efficiency.

One promising technique, now under development at RCA Laboratories, involves making solar cells by depositing low-cost amorphous silicon on glass. Conventional solar cells, on the other hand, have to be made from a special high-purity silicon that is

processed at high heat levels and then sliced into wafers (which results in loss of some of the material). The latter method is both time consuming and expensive.

RCA's new solar-cell technology is now covered by a US patent, granted towards the end of last year to Dr David Carlson. Dr Carlson is head of Photovoltaic Device Development in the RCA Energy Systems Research Laboratory (Princeton), and has been researching the properties of amorphous silicon since 1974.

Dr B. Williams, Director of the Laboratory, said that the amorphous silicon covered by Dr Carlson's patent is "the only amorphous material we know of that has been used successfully to make high performance, photovoltaic solar cells."

He added that although future amorphous silicon cells may involve different geometrical arrangements, the devices will basically be extensions of those patented by Dr Carlson rather than new ones. Because of this, RCA considers the patent one of the most important yet granted in the solar energy field.

Amorphous silicon solar cells are low cost because: the material (a sand derivative) is plentiful; the fabrication process involves a low temperature process (glow discharge); extremely thin layers of the material (about 1/20th the thickness of a human hair) can be placed on large area substrates of inexpensive glass or steel sheets; and initial

RCA scientist Dr David Carlson operates glow discharge equipment used in making solar cells from hydrogenated amorphous silicon. RCA believes that amorphous silicon solar cells may produce power at a cost competitive with conventional power sources by the mid-1980s.



tests indicate it is a long lasting, stable material.

Glow discharge systems are well known and have long been used in electronics for depositing thin layers of materials. Conventional fluorescent lights, in effect, employ glow discharges.

To make amorphous silicon, silane gas, consisting of silicon and hydrogen atoms, is processed in a low pressure glow discharge chamber. The hydrogenated amorphous silicon created by the process is spread thinly and evenly over the desired substrate.

Amorphous silicon differs from the crystalline silicon used in many solar cells in that the arrangement of the atoms in amorphous silicon is not as orderly, or periodic, as the atoms in crystalline silicon. Therefore the material is easier to grow and may be deposited on a large variety of inexpensive substrates. Amorphous silicon also differs from crystalline silicon in that the amorphous silicon contains about 20 percent hydrogen.

Conventional solar cells are more efficient than amorphous cells but, as Dr Carlson is quick to point out, are considerably more expensive. And crystal silicon processing requires temperatures of more than 1100°C, compared with 300°C for the amorphous material. Furthermore, crystalline solar cells are roughly 250 times thicker than amorphous cells and, for the most part, are limited by fabrication problems to relatively small areas.

For example, many conventional cells are made of wafers only 7.5cm in diameter. Yet amorphous cells can be fabricated in 30cm square areas, according to Dr Carlson.


The projected cost of RCA's new cells is around \$1 per watt once they are in full production.

Initially, RCA experts think that the amorphous silicon cells could be used for electrification projects in developing nations lacking the extensive electric power distribution networks of America and Europe. Also, Dr Williams stated, many developing nations are in areas that receive a great deal of sunlight and their societies are built around small communities or villages with very modest electricity requirements. Solar cell power supplies seem particularly well suited to this environment.

Later on, as the technology is improved, amorphous solar cells could be employed in more developed nations, particularly in applications using large amounts of DC power.

The US Government has partially funded RCA's solar energy work since 1976, and at present the US Department of Energy is cost-sharing a greatly enlarged research program with RCA Laboratories. The goals of the on-going program are:

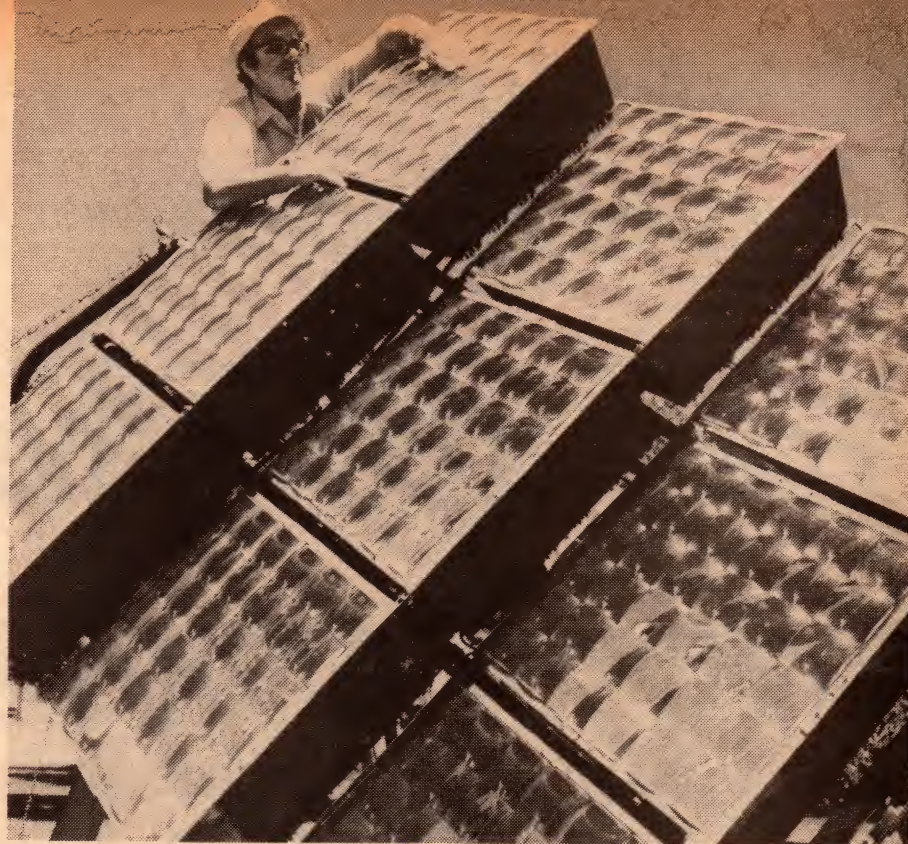- to demonstrate high performance in large area cells;



Researcher John Hughes examines an array of plastic lenses used to focus the Sun's energy onto silicon solar cells. RCA's experimental 300W system continually tracks the Sun, and could significantly reduce solar energy costs.



RCA's Olga Gervasoni tests experimental solar cells by measuring the electricity they produce when they are placed in the beam of a simulated sun — in this case an arc lamp. Her work is part of the research program at RCA Laboratories in Princeton.

- to improve the efficiency of amorphous cells, now at six percent, to 10 percent;
- to confirm initial tests showing that the material is very stable; and
- to achieve a better understanding of the mechanisms involved in amorphous silicon electronic devices.

It will take several years of extensive research to achieve these goals, according to Dr Carlson. But success in this and other solar energy research programs is vital if we are to secure our energy future.

Perhaps it is only a matter of time before the rooftops of suburbia are studded with low-cost solar cell systems.

Piezoelectric transducers based on polymers are now being put to work in many diverse applications, ranging from stereo systems through to automobile crash studies. With these transducers, it is possible to design the measuring instrument to suit the measurement conditions, rather than to try to adapt the conditions to suit the instrument. . . by Madeleine Jacobs.

The world of the piezoelectric polymer

It has been a long hard day at the office and you're tired. You arrive home, kick off your shoes, settle down in your favourite easy chair, and turn on the stereo. Suddenly, it's as if you're sitting in a concert hall, listening to Berlioz' *Symphonie Fantastique*. The music can only be described as exquisite.

The realism of the sound is due to a specially processed polymer material in the stereo speakers that makes it possible to transform electrical energy into acoustical energy with nearly complete accuracy. The unique substance is an example of a class of materials known as piezoelectric (often pronounced pe-a-zo-electric)

polymers. Their use is so new that the "Encyclopedia Britannica" fails to mention them in its section on piezoelectric devices.

And yet, as a class, piezoelectric polymers are being used increasingly, not only in some stereo components but also in applications involving health, safety, national security, nondestructive evaluation, and even printing of currency.

"The most surprising thing about piezoelectric polymers is that they exist," declares Seymour Edelman, a physicist at the National Bureau of Standards and a leading pioneer in the field of piezoelectric polymer applications. "Polymers differ from conventional piezoelectric materials in so many of their properties that it seems strange that they should be comparable in their piezoelectric response.

"For example, conventional piezoelectric materials are typically crystalline or polycrystalline, hard, stiff, brittle, and dense," he continues. "They're difficult to machine into thin layers, they are not readily available in sheets of large area, and they are expensive. On the other hand, polymers are pliant, flexible, tough and light. They are available commercially in layers as thin as six micrometres in 1000 metre rolls over one metre wide. And they are relatively inexpensive."


These properties make polymers uniquely suited for a variety of piezoelectric devices. While the Japanese have been studying the phenomenon in polymers longer than anyone else, NBS is at the vanguard of a handful of laboratories in the United States studying the theory, materials properties, and applications of this strange class of polymers.

Most piezoelectric devices today are based on certain crystals which, when deformed by pressure, generate an electric charge. The phenomenon is due to the electrically polar nature of the crystals. That is, they contain positively and negatively charged ions which separate when the crystals are subjected to stress.


This effect was discovered experimentally in 1880 by the Curie brothers, Pierre and Paul-Jacques. By placing a weight on a crystal, they observed a voltage on the surface of the material. The inverse effect was also found — that is, by applying a voltage to the material, a deformation of the crystal could be produced. The two effects go together in piezoelectric materials. (The latter is the basis for the use of piezoelectric devices in stereo components and other acoustically-based instruments).

Eventually, they found the effect in a number of crystals, including quartz, Rochelle salt, and tourmaline. Although Pierre Curie and his wife Marie later used the piezoelectric effect to study radio-activity, piezoelectricity in general remained a scientific curiosity until World War I, when it was used to produce acoustic waves in seawater to detect the presence of submarines.

Applications of the effect involved ceramics and other brittle crystalline materials. The first indication that still other substances might exhibit the effect came in 1892. A British scientist, Oliver Heaviside, postulated that certain waxes would form permanently polarized dielectrics when allowed to solidify from the molten state in the presence of an electric field. He viewed these as being the electrical analog of magnets. His theory was confirmed in

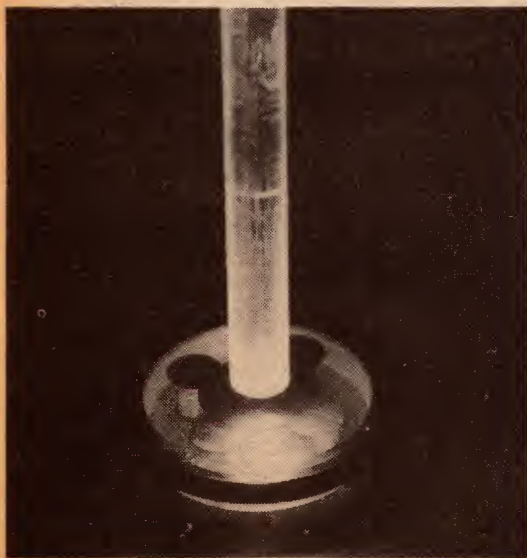


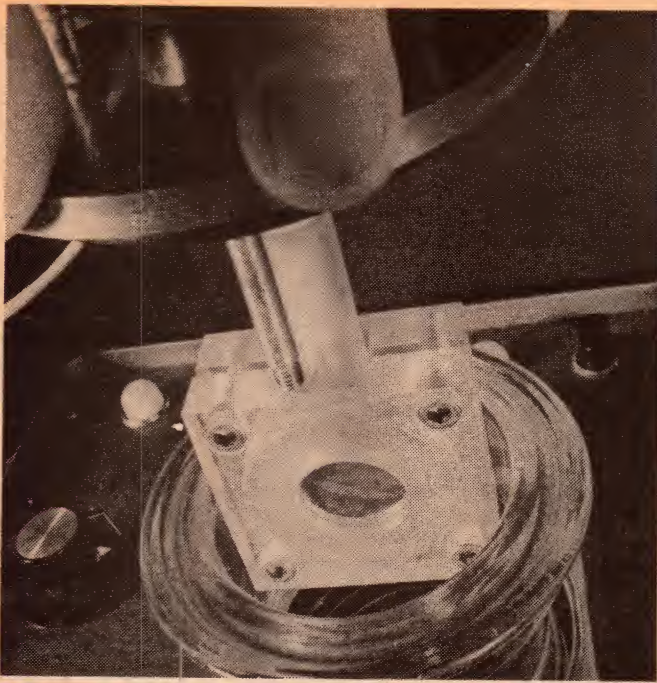Thermal pulse experiments can yield information about piezoelectricity in polymers. Here a light pipe is shown illuminating a polymer sample.



NBS scientists use a plasma or ionised gas, to generate poling fields large enough to induce piezoelectricity. Photo shows a polymer sample being lowered into a glass container where the plasma will be generated.

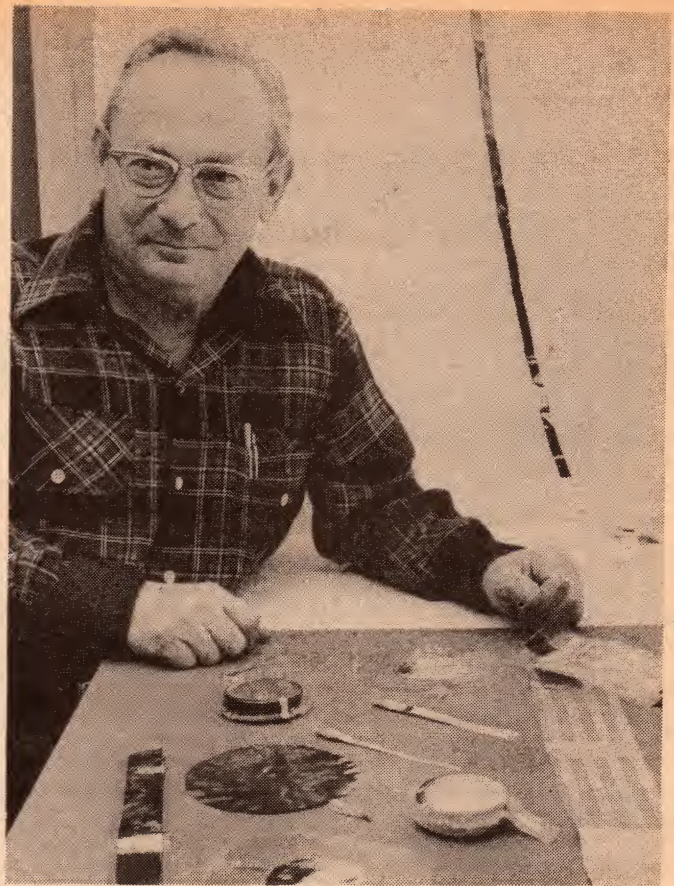NBS physicist Seymour Edelman displays a variety of piezoelectric polymer transducers. The devices can be made in nearly any desired shape or size.



the 1920s, but not much else happened until the early 1940s when researchers in other countries began investigating piezoelectric effects in rubber and other materials.

NBS became involved in the research around 1968, recalls Edelman, who was then chief of the Vibration Section. "One of the major problems we had in calibrating instruments used to measure vibrations was getting rid of low frequency resonances. I had learned that rubber was piezoelectric from Dr Archibald T. McPherson, then associate director of NBS. It occurred to me that if the surface of the instrument were mounted on such a polymer and if we controlled it electrically, we could get rid of all the resonance frequencies that interfered with our measurements.

"We then looked at a number of polymers and tested them for piezoelectricity. At that time, there was only a limited amount of research reported in the literature on piezoelectricity in polymers."

This was the beginning of 10 years of application research, which has led to the development of many new and innovative devices. At NBS, the development of a device begins with inducing the property of piezoelectricity into a film of polyvinylidene fluoride, also known as PVDF. Polymers do not normally exhibit piezoelectric activity to any great extent — it must be induced.

NBS physicist Steve Roth begins with

a film of PVDF, which looks much like a roll of ordinary plastic wrap. A layer of aluminium is evaporated on both sides of the film to form metallic electrodes. At this point, the material looks like a thin piece of plastic wrap coated with aluminium foil. Next, Roth places the film in an oven and raises the temperature to about 80°C. An electric field is concurrently applied, typically on the order of several hundred kilovolts per centimetre of polymer thickness.

While the voltage is maintained, the polymer is allowed to return to room temperature. This procedure is referred to as "poling".

The piezoelectric property of the material is stabilised in the polymer as it cools. PVDF as a piezoelectric material has a good response to changes in pressure over a wide range of frequencies, which makes it extremely useful for dynamic measurements. It also has many advantages over conventional ceramic materials.

For example, a variety of transducers and devices can be made from the finished material in nearly any shape. Transducers using conventional piezoelectric materials usually have metal bases and housings and require threaded holes or specially ground flat surfaces of appreciable area for mounting. Polymer transducers, on the other hand, usually consist only of the active material and a metal lead. The finished film can be attached to the surface to

be measured with rubber cement, cyanoacrylate, epoxy, or other cement. The transducer can be attached to curved, twisted, or pliant surfaces.

In addition, PVDF is not likely to be harmed by the usual conditions under which sensors are used, such as salt water, soaps, common organic solvents, nearby explosions, or other mechanical shocks.

Conventional transducers also tend to have many large amplitude resonances, both because of their internal spring-mass systems and because of the effect of the mass of the instrument on the mounting surface. Polymer transducer response is flat with frequency over wide ranges, typically into the megahertz range, their resonances are highly damped, and their mass is so small that they do not perturb the motions of the mounting surface.

Another important property is the piezoelectric modulus, g , which is the electric field per unit mechanical stress. This value governs the usefulness of a material as a detector and is about six times as large for PVDF as for a typical lead zirconate titanate ceramic.

Yet piezoelectric polymer devices are far from perfect for every use. For example, the value of the d modulus (strain per unit electric field), which measures the usefulness of the material as a generator of motion or as a sound source, is 20 times greater for ceramic devices than for polymer devices. (Use

The world of the piezoelectric polymer . . .

of piezoelectric polymers in stereo components is justified on the basis of their other properties and advantages.)

Another problem is temperature. Piezoelectric polymers are also pyroelectric; that is, they generate an electric charge with a change in temperature as well as with a change in pressure. There is no way to separate the two effects if the temperature and stress are changing together. Fortunately, many measurements are made at a constant or slowly changing temperature.

Many devices have been developed at NBS which take advantage of the remarkable versatility of piezoelectric polymers. The projects have been supported by other government agencies that have come to NBS for help with a variety of different measurement problems.

For the Frankford Arsenal and the Office of Army Research, for instance, NBS developed piezoelectric polymer devices as detonators for explosives. Edelman and a colleague demonstrated that these devices had sufficient electrical output in response to impact so that they could be used in place of ceramic elements in ordnance fuse systems. This application depends on the fact that in the process of poling, a polymer stores about one-and-a-half times as much energy per unit volume as is stored in ceramic devices under similar conditions.

Polymer sheet is also preferable to ceramics for this application because it can be connected to provide a desired electrical output impedance more readily and can be used to line a shell to provide detonation on any angle of in-


cidence. For this research, the NBS scientists received an Army Commendation Award.

The thinness and flexibility of polymer gauges make them feel and act mechanically very much like skin. These properties were valuable when NBS was asked by the National Highway Traffic Safety Administration of the Department of Transportation to develop polymer stress gauges for automobile crash studies.

Two types of polymer gauges were developed. One was used for pressure changes during the impact of a collision between an anthropomorphic dummy and the instrument panel of a motor vehicle during a simulated crash. The other was used for measuring pressure changes in the brains of animal subjects during tests of controlled impact to the head.

The value of polymer devices in these two applications is obvious, Edelman explains. "Since the gauges behave very much like skin, they do not disturb the anthropomorphic behaviour of the dummy. Because they are flexible, they are not likely to be damaged in the crash or to damage parts of the vehicle on impact. The polymer gauge has a density close to that of brain matter, which makes it useful in the second application. If a conventional ceramic gauge were used, inertial effects would produce more signal than the pressure change."

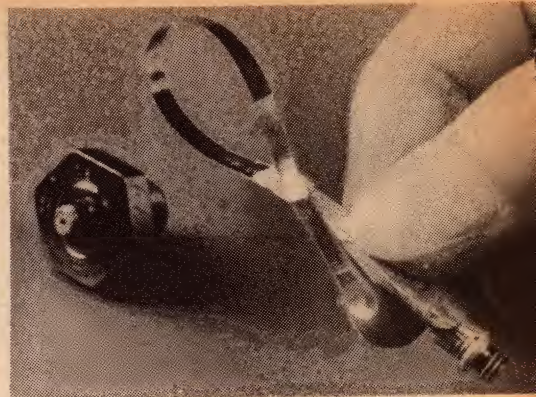The similarity to body tissues means that polymer gauges can be applied easily to the skin like an adhesive bandage to monitor heart sounds and pulse rates of patients during exercise. "Conventional instruments can be used




The advantage of piezoelectric polymer transducers over conventional ceramic devices is illustrated in this photo. The polymer device is not only flexible, but weighs a mere 0.3 milligram (without the metal lead) compared to the ceramic device which weighs around 21 grams.

for these applications, but their size and mass make the patient conscious of their presence and his behaviour is not entirely normal," Edelman notes. "He is much more likely to forget polymer gauges."


Piezoelectric polymers can also be used as strain gauges, Edelman says. "In this application, they have nearly the same sensitivity as semiconductor gauges but they can be used without the need for bias voltage or bridge balancing. They can be used where mechanical shock occurs and on curved surfaces."

One potentially important use of polymer strain gauges is to detect and measure strains accompanying stress waves in the soil. These gauges might be used to detect and follow tunneling operations, to detect vehicle movements, to calculate the effect of

1.

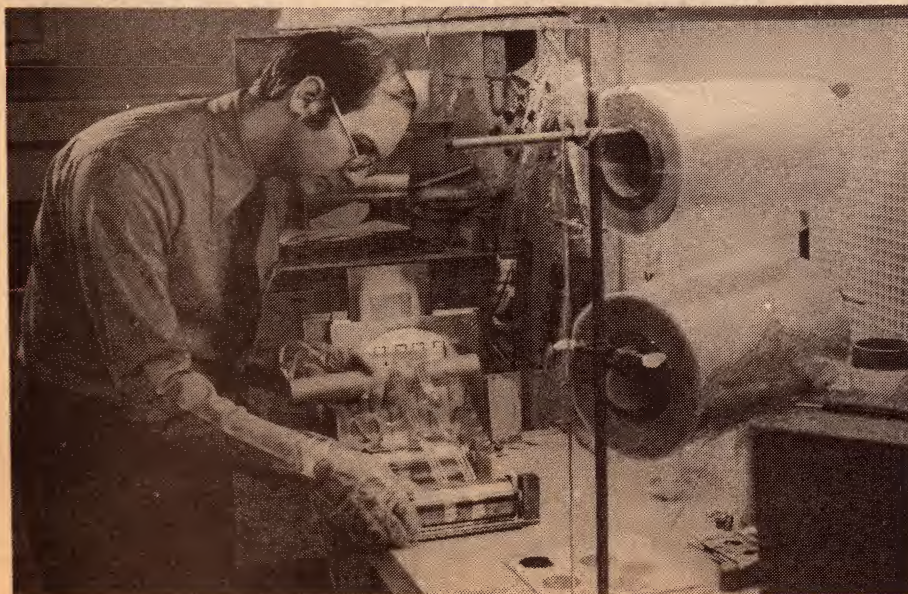

2.

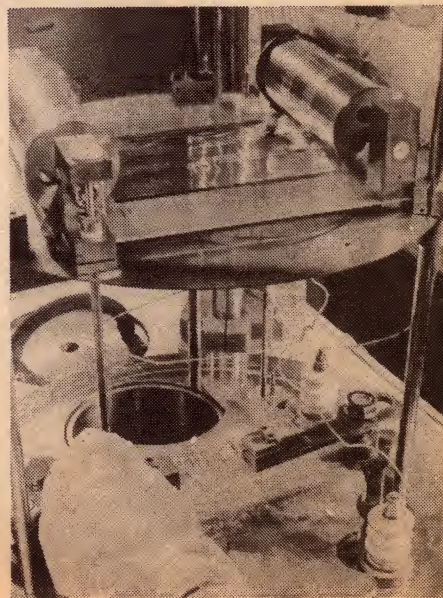

explosions on buried structures, or to detect disturbed ground and buried mines.

Similar gauges supplemented by acoustic emission (sound) sensors attached to bedrock can be used to detect and locate mining operations, progress of a tunnel, sudden movements in earth dams, and incipient avalanches in snow fields.

In another project, NBS built piezoelectric hydrophones for listening to sonar signals under water, an application that was funded by the US Navy. Similar units could be made up as arrays and used for finding fish or for underwater geophysical exploration.

Two recent projects are a further indication of the range of applications for piezoelectric polymers. NBS is working on gauges for the Department of Treasury to be used on the presses that print US currency. The Treasury Department needs a built-in gauge to monitor pressure on the presses that operate at very high speeds. Precise pressure is needed to maintain quality control. Piezoelectric polymer sensors, which can be cut to nearly any shape, could do this very well.

The list of potential applications runs to pages, but whatever the application, the key point, Edelman says, is that with piezoelectric polymers, "it is possible to design the measuring instrument to be suitable for the conditions under which the measurement is made, rather than try to adapt the conditions of the measurement to suit the needs of a conventional instrument designed to have general utility."

Much more needs to be done to understand the behaviour and theory of piezoelectric polymers. But without waiting for theory to catch up to applications, industry is already using the materials in an increasing number of ways. Of the many transducer manufacturers who have come to NBS to learn about this new technology,

Explaining polymer piezoelectricity

Currently, there are two schools of thought to explain the phenomenon of piezoelectricity — the molecular dipole model and the trapped space charge model. These are highly complicated mathematical theories. Below are simplified explanations of the two theories.

Molecular dipole model

This model explains piezoelectric behaviour in two types of polymers — amorphous and semi-crystalline. Polymer molecules are made of polar sub-units called dipoles, which line up in an electric field like magnets in a magnetic field. Usually these dipoles are randomly oriented and cannot produce piezoelectricity.

If the dipoles can be oriented in one direction with an electric field and the orientation can be frozen (by cooling below the glass transition temperature in the case of

amorphous polymers or by producing a polar crystal phase in the case of semi-crystalline polymers), then the polymers will be piezoelectric. That is, the surface charge on a poled film will depend on the net dipole moment divided by the film volume. The volume changes whenever the sample is stressed and induces charges on the film surface. The larger the dipoles and the more complete the alignment, the more active the film will be.

Trapped Charge Theory



This school of thought rejects the explanation that the aligning of dipoles is the basis for the piezoelectric responses of polymers. Instead, real charges in the material are trapped in certain polymer sites and it is these charges that respond to the electric field, according to this idea.

several have developed commercial applications. "Transferring our know-how to industry and other agency labs has been a primary goal of our work," says Martin Broadhurst, chief of the Bulk Properties Section in the Polymers Division at NBS.

Scientists involved in the research believe that someday piezoelectric devices made from polymers will be as commonplace as the plastic wraps found in nearly every household. Says Edelman of the outlook for piezoelectric polymers, "Some day, the applications of piezoelectric polymers will be limited only by the imagination of the user."

Reprinted from Dimensions, Journal of the National Bureau of Standards, Washington, DC.

To make piezoelectric polymers, physicist Steve Roth positions a film of poly vinylidene fluoride in front of a mask to allow metal to be deposited (1). Film is placed in an evaporator to form metallic electrodes (2), then moved to an oven (3) where electrical leads are attached (4). The temperature is raised to 80°C and an electrical field is applied. Finished devices (5) will be used as pressure gauges on printing presses for the US Treasury Department.

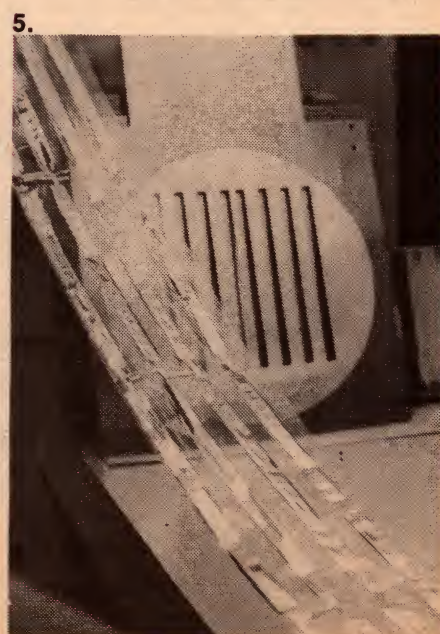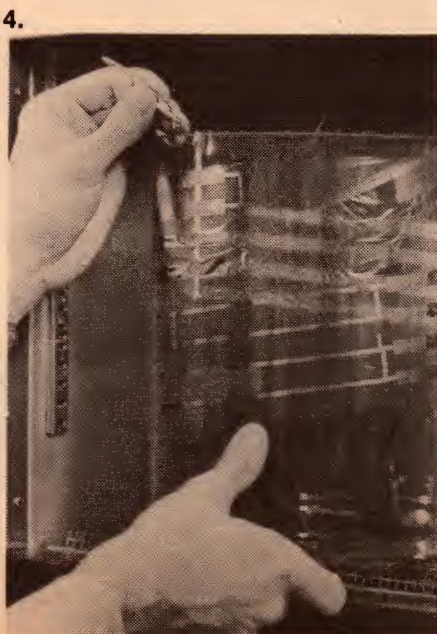



Bits and pieces month, but first: the Boeing satellite power source

Every now and again, I find it necessary to have a "bits and pieces" month, when I clear the file of some of the oddments that tend to collect when the space is occupied by major items. First a denial by Boeing that they were guilty of a major error in the calculations to do with their proposed satellite/solar power station.

You may remember that we carried the original story in our December issue, last. It involved assembling and positioning an array of huge satellites in space in a geostationary orbit above the equator. Bathed in sunlight for 99% of the time, they would convert solar energy into microwave radio energy and beam it to antenna collector arrays on earth. Boeing envisage anything up to 45 such satellites in a long line across the sky, each one of them producing 10,000 megawatts of electricity.

Boeing see the scheme as mind-bending in its magnitude but certainly not "far-fetched". We already have the basic technology, they say, the essential problem being one of scale. And even the cost would not appear to be impossible, considered against the world need for energy, its rapidly rising costs and our dwindling resources.

E.A. readers appear to have taken the story at its face value, but not so R. W.

Johnson of Ben Lomond, California. He saw reference to the proposal in an American publication and wrote a letter to "Electronics" magazine, which we reprinted in our July issue under the title "A Boo-Boo by Boeing?"

Mr Johnson made certain assumptions about the likely height of a geostationary satellite, the frequency at which the energy would be beamed to earth, the beam width, the size and gain of the antenna arrays at both ends and the atmospheric losses en-route. He ended up with a power level at the earth station of 631 watts: "about enough to power a toaster."

From the rest of the letter, it was clear that Mr Johnson regarded the whole idea as Boeing "pie in the sky" and felt that the money could be invested more productively in a chain of nuclear power plants, each delivering a "safe" 1100 megawatts.

We reproduced the letter as a matter

of interest but made the comment that: "it seems unthinkable that Boeing engineers would not have been through a similar exercise". In particular, we suspected his reference to the square law, which assumes that the receiving antenna is intercepting part only of a diverging beam.

The letter has since been answered, again in "Electronics", by Ervin J. Nalos, on behalf of Boeing. He points out that the Boeing scheme is not a sudden or recent inspiration but has been kicked around for about 10 years by several NASA centres. It certainly has not been kicked out!


He specifies a likely frequency of around 2.45 gigahertz with a transmitting antenna array about 1km in diameter. It would comprise 7,220 sub-arrays, using retrodirective steering, to produce a beam width of 0.46 minute of arc. He goes on to say that research by NASA has established an error level of 0.0006-arc-minute, equivalent to a displacement of six metres on the ground. The system compensates automatically for ionospheric diffraction effects.

In short, the whole concept is far more sophisticated than anything envisaged by Mr Johnson:

With such a system, it is possible for the receiving antenna to approximate the area of the beam footprint, thereby virtually eliminating the devastating square law problem. The losses subside largely to those occasioned by the atmosphere, which could be tolerated at the nominated frequency.

With those problems resolved, the discussion seems to boil down to three main questions:

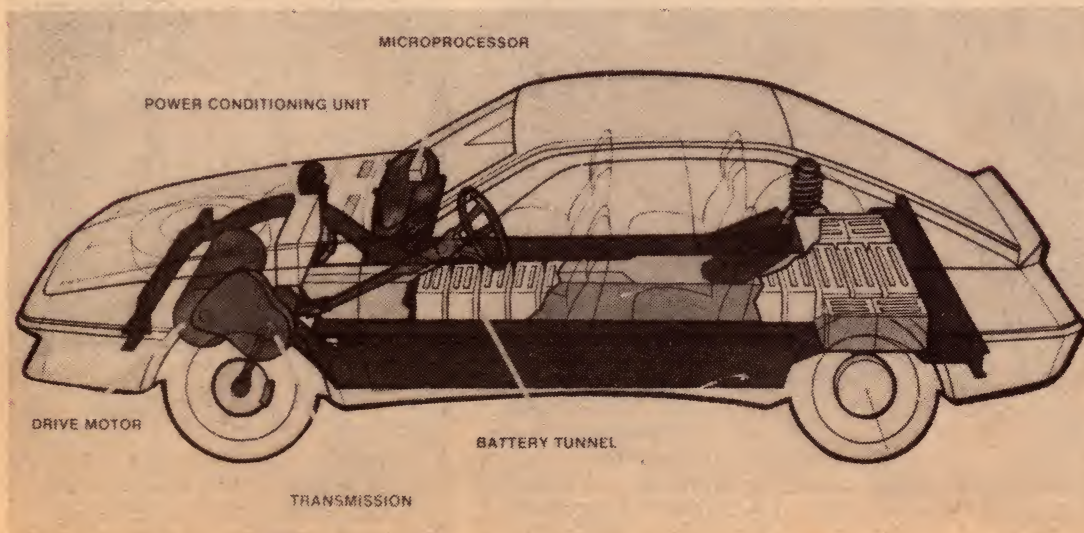- How "safe" is the nuclear alternative favoured by people like Mr Johnson, not only in the handling and operation of nuclear fuels but in the possible heritage of non-disposable wastes and obsolete plants.
- How safe would satellite power stations be in time of war? One would think that the effort to



An artist's sketch of the electric car currently under development in the U.S. Design range is 145 miles at 35mph, or 75 miles of stop-and-go in city traffic with a full passenger load. Available cruise speed will be 55mph. The body shape stresses aerodynamics — the nub of the question is: would you buy it in preference to a '...?

destroy them and the effort to protect them from destruction would make "The Dambusters" episode of World War II look like a scuffle on the carpet.

- For how long can we go on increasing our demands for energy, while disputing alternative means of obtaining it? In every year that so passes, we are burning up non-renewable resources that should more appropriately be reserved as a source of materials and chemicals for the future.

I couldn't help but think along these lines a few months ago, during a visit to the Shetland Islands, where I have a family connection. For as long as anyone can remember, the Shetlanders have relied on their abundant resources of peat to warm their croft-houses and to do their cooking. For all that time, the ritual of digging and stacking the peats has been an essential part of Shetland life.

But, today, most of the old stone croft-houses lie abandoned and empty, while island families live in concrete block homes, with lighting, cooking and heating provided by electricity from a central power station. The peat on the hills is largely forgotten amidst the technological scramble to win oil from the adjacent North Sea, so essential to sustain — modern technology!

Don't misunderstand me. I guess that if I (or we) lived there, I (or we) would gladly settle for a modern house, electric light, electric heating, colour television, hifi, &c — as we do right here in Australia. I mention it because it's such an eloquent microcosm of the impact and demands of modern technology.

We're all a part of it!

ELECTRIC CARS ...

While on this particular theme, the accompanying drawing of a planned new electric car appeared on my table a few days ago. The caption explained that it was being developed for the Near-Term Electric Vehicle Program of the US Department of Energy. The structure of the car would be built by the Chrysler Corporation, while General Electric would provide the separately excited direct current motor, electronic controls and regenerative braking system. Globe-Union would provide the high density lead-acid battery bank supplying the requisite 108 volts.

The 2-year \$5.98 million project is scheduled to climax in about twelve months time with the production of two of the "sub-compact sized, four passenger" test vehicles.

The standard reaction to such an announcement is: "Ho-hum! Yet another electric car." This may be embellished by follow-up remarks like: "When will they develop one that really works?" Or, "If they can send a man to the moon, you'd think they could build a

decent electric car." Or yet again: "Even if they did, the oil companies would kill it!"

While I don't dispute the possibility of some politicking over the years, the real enemies of the electric car are the potential customers: you and I. And I say this on very firmly established customer preferences.

Rarely is our choice of vehicle dictated by basic needs. We all tend to over-specify and over-buy.

We plainly prefer a car large enough to accommodate the passengers we think we might want to carry; a boot to accommodate the luggage for the tour that we might undertake; a range sufficient for that possible long, overnight journey; acceleration that we could use if roads were better; a top speed faster than we care to travel, anyway!

For the privilege, we're prepared to pay extra money — indeed a good deal of extra money!

Why then would we be likely to opt for a vehicle with limited speed, limited range, limited passenger and luggage space, and limited re-fuelling potential? At higher cost and with unproven reliability and resale value?

From the suppliers' viewpoint, what executive, in his right mind, would seek to launch such a vehicle on the market against established designs which would out-perform it in just about any direction?

While we — the public — may profess concern about conservation and the environment, I doubt that many will opt for an electric car until such times that we are enticed, or obliged, to do so. And that includes those of us who may have an initial bias towards electronics!

So much for basic energy and our attitudes to it. Let's get back to more familiar ground, to the subject of audio and hifi. First a brief but plaintive letter from a reader in Wahroonga, NSW, who faces a domestic problem:

DOMESTIC CRISIS?

Dear Sir,

How can I convince my wife that reception via FM is interference and static-free when, every time a car goes by, my "crystal clear stereo FM music" is punctuated by the machine-gun rattle of ignition noise?

What does one do about it?

J. R. (Wahroonga)

First off, J. R. is not unreasonable in expecting crystal-clear, noise-free sound from his stereo FM tuner. The textbooks abound with diagrams showing how the limiter stages slice away noise pulses, while sales brochures support the theme with unalloyed superlatives. However, it doesn't seem to work that way for J.R.

One possible explanation is that he may be on the wrong side of a hill and shielded from the FM signals. A modern FM tuner can typically receive

P.A. — SOUND




For Public Address and Commercial Sound, it will pay you to consider these and other products from NOMIS.

ASTATIC 950
LS/HS
professional card-
oid microphone.
For studio indoor
and outdoor.



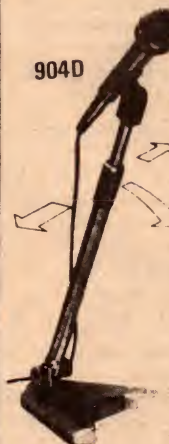NOMIS
PORTABLE P.A.
SYSTEM SC-15E
— 15 watts
RMS. 240V AC or
12V DC. Two
mikes SC-15EW.
Same but for cor-
dless mikes.
36.7MHz (Ap-
proved).



NOMIS
MICROPHONE
FITTINGS 904D.
All chrome
telescopic
horizontal and
lateral adjustments.



SANYO AMPLIFIER PAM — 60/30
(60 and 30W RMS) 6 mixer input
(3LoZ mike). Multi V.C. — line OP.
High quality — there's nothing like it.


"The Sound People"

NOMIS

NOMIS ELECTRONICS PTY LTD,
689 South Rd, Black Forest, SA 5035.
ALL TRADE & DISTRIBUTOR ENQUIRIES WELCOME.



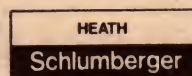Continuing Education Series— the fast, easy, low-cost way to learn electronics!



These three basic programmes provide an excellent overview of contemporary electronics—they'll provide you with the fundamentals you need to follow your interests wherever they may lead you. The programmed learning text is clearly written, with technical material fully explained as it is introduced. Built-in quizzes let you test your knowledge at each step. The records give you a "personal" outline of text material and additional information, and electronic parts are included for use in the experiments. Each course leads logically into the next, and when you complete all three, you'll have a thorough knowledge of basic electronics.

Part 1: DC Electronics— electrical fundamentals, theory and practice—

- | | |
|---------------------------|--------------------------------------|
| 1. <i>Electron Theory</i> | 6. <i>Electrical Measurements</i> |
| 2. <i>Voltage</i> | 7. <i>Network Theorems</i> |
| 3. <i>Resistance</i> | 8. <i>Inductance and Capacitance</i> |
| 4. <i>Ohm's Law</i> | |
| 5. <i>Magnetism</i> | |

Includes all texts, records, 56 parts for 20 experiments. Average completion time, 20 hours.

Programme EE-3101 \$65.00

Part 2: AC Electronics— sine waves, inductive and capacitive reactance, impedance, phase shift, transformers and filters

1. *AC Fundamentals*
2. *AC Measurements*
3. *Capacitive Circuits*
4. *Inductive Circuits*
5. *Transformers*
6. *Tuned Circuits*

Includes all texts, records, 16 parts for 8 experiments. Average completion time, 15 hours.

Programme EE-3102 \$65.00

Part 3: Semiconductor Devices— transistors, zeners, SCR's, FET's, digital and linear IC's, LED's, opto-electronics

- | | |
|--|------------------------------------|
| 1. <i>Fundamentals</i> | 7. <i>FET's</i> |
| 2. <i>Diodes</i> | 8. <i>Thyristors</i> |
| 3. <i>Zener Diodes</i> | 9. <i>IC's</i> |
| 4. <i>Special Diodes</i> | 10. <i>Opto-electronic Devices</i> |
| 5. <i>Bipolar Transistor Operation</i> | |
| 6. <i>Bipolar Characteristics</i> | |

Includes all texts, records and 27 parts for 11 experiments. Average completion time, 30 hours.

Programme EE-3103 \$65.00

Heathkit Experimenter/Trainer

For the Heathkit DC, AC and Semiconductor programs—helps you perform each project quickly and easily. And after you finish the programs, it's ideal for "breadboarding" your own design projects. Has solderless breadboarding sockets, 2-range variable sine and square wave signal source, dual-variable power supplies for positive and negative voltages (both variable over 1.2 to 16 volts, 120 mA, both regulated and short-circuit protected). Built-in 1k and 100k linear potentiometers. Center tapped power transformer secondary provides 30 V rms, 50 Hz for line experiments.

Kit ET-3100 \$114.00

NOW AVAILABLE! ELECTRONIC CIRCUITS

Programme EE-3104

\$81.00

Heathkit Digital Design Experimenter/ Trainer

Use it to perform all the experiments in the Heathkit Digital Techniques Programme, also to develop projects, build and test prototypes, verify circuit operation, check digital IC's. Has solderless breadboard sockets, four binary data switches, 2 "no-bounce" switches to pulse logic circuits, 3-frequency pulse clock generator, 4 LED's for visual indication of logic states. Three regulated power supplies: +12V, 100 mA current limited; -12V, 100 mA current limited; +5V, 500 mA, overload protected. Accommodates up to eight, 14 or 16-pin dual-in-line IC's, also 24, 28 and 40-pin DIP's.

Kit ET-3200 \$132.55

Digital Techniques Program—For the advanced experimenter, technician, hobbyist or engineer.

Learn digital fundamentals, circuit design, TTL, ECL, CMOS, PMOS, NMOS integrated circuits; SSI, MSI and LSI; ROM's, PLA's; microprocessor theory

1. *Introduction: techniques and uses, binary numbers, digital codes.*
2. *Semiconductor Devices for Digital Circuits.*
3. *Digital Logic Circuits: AND gates, OR gates, NAND / NOR logic, etc.*
4. *Digital Integrated Circuits: TTL, ECL, CMOS, nMOS, pMOS; how to choose.*
5. *Boolean Algebra.*
6. *Flip-Flops and Registers: latches, D & JK flip-flops, storage registers, applications.*
7. *Sequential Logic Circuits: binary, BCD, modulo N, up / down counters, dividers, shift registers.*
8. *Combinational Logic Circuits: encoders, decoders, exclusive OR, comparators, multiplexers, ROM's, PLA's.*
9. *Digital Design: combinational and sequential circuits, procedures.*

10. Digital Applications: counters, computers, microprocessors.

Update your knowledge of electronics with this program in digital fundamentals. Provides a solid background with particular emphasis on circuit design. Covers the latest integrated circuits; ROM's and PLA's; even microprocessors. Helps you learn to design digital circuits for virtually any application.

The program assumes a prior knowledge of electronics fundamentals, either completion of the Heathkit basic electronics programs or equivalent knowledge. It can be successfully completed by technically-oriented people with a math or science background.

The program includes all texts, records and 44 parts for 24 experiments. Av. completion time: 40 hours.

Programme EE-3201 \$81.00

ORDER BY COUPON NOW OR COME TO OUR SHOWROOM

Please rush me the programme of my choice. My cheque for \$ _____ is enclosed plus \$2.50 for package & post.

Name

Address

.....P/Code.....

Send to: W. F. Heathkit Centre,
220 Park St., South Melb. 3205. Phone: 699-4999

- ☐ Programme EE-3101
☐ Programme EE-3102
☐ Programme EE-3103
☐ Kit ET-3100
☐ Kit ET-3200
☐ Programme EE-3201
☐ Programme EE-3104

FORUM — Continued

and resolve a signal as low as 2uV in mono mode, and a somewhat larger figure in stereo mode. However, such signals would not be noise-free. For 50dB of quieting in stereo mode, a signal level of around 40uV may be required, while a still larger figure may be necessary to ensure complete rejection of external impulse noise.

A further consideration is the nature and position of the antenna which feeds the tuner. Ideally, it should be horizontally polarised (as for TV); it should have adequate pickup over the FM range (88-108MHz), be mounted high up out-of-doors and be orientated towards the transmitters. J. R. would have to be in an atrocious situation in Wahroonga for such an antenna not to pick up an adequate signal.

But does he have such an antenna, or is he relying on a stray piece of wire or an improvised "split" from the TV antenna? If, for any such reason, he is starving his tuner for signal, he may still pick up the stations in normal stereo — but with less than the normal ability to discriminate against impulse noise.

The other point which comes to mind is the behaviour of the FM tuner itself. There may be some fault in its design, or operation or adjustment, which is letting the noise pulses through, signal notwithstanding. Perhaps he should have it checked over by the suppliers with the specific problem in view, or else borrow another tuner for comparison.

A significant omission from the letter is any mention of a similar problem with TV sound. That, too, uses an FM system and, in the case of the ABC station at least, comes from the same tower. If the television sound is free from ignition interference, it would indicate that J. R. should have a closer look at his FM antenna, or his tuner, or both.

LINEAR PHASE?

Still on an audio/hifi theme, the accompanying letter from R. C. expresses his reservations about the current fad for linear phase loudspeakers. Without consciously trying to sit astride the fence, I'd say that he is, at the one time, both right and wrong.

He is right to the extent that virtually all available program material has been through processes which, to say the least, would modify the phase relationships between sound components of different frequency. It is arguable, of course, whether this in itself detracts from the listening pleasure, because a significant proportion of such material is still very impressive. If the quality has been damaged by phase mutation, it is difficult to say in what way.

But, impressive or not, R.C. is simply

Dear Sir,

I cannot get excited about those phase linear loudspeakers. Until we have phase linear tape recorders and, just as important, phase linear tone controls then why — except for gimmickry — worry about phase linear loudspeakers?

I agree that, with pure tones, phase shifts can be heard. But music doesn't consist of single tones, or even of just first and second and other direct harmonics.

By the time Mr Dolby's "A", a couple of tape transfers, Mr Dolby's "B" and a cassette deck intervene, those beautiful square waves referred to in the tests (E.A. for April) would look pretty sick.

Perhaps, when everything else is digital, except the human ear of course, we can come back to phase linear!

R. C. (Ewey Bay, NSW)

saying that if the vast majority of available program material has been processed without critical attention to phase, there is no point in attaching so much emphasis to it at the loudspeaker.

That argument is hard to shoot down. All other things being equal I, personally, would not advise anyone to discard (and lose money on) an existing high quality loudspeaker system, merely to replace it with a linear phase equivalent

— unless the latter had advantages in other respects: better frequency response, lower distortion, freedom from intermodulation, &c.

To that extent I'm on side with R.C. But one can look at it in another way:

It is reasonable to attach some significance to the square wave tests described in the April issue and, on the strength of those tests, to opt for a deliberate rather than a random phase relationship between the driver cones. Such a choice could hardly be wrong but there's a chance that, in the longer term, it could turn out to be right.

On this basis the engineering decision to proceed with the phase linear concept has a certain logic.

Whether the difference will be apparent with currently available program material, or whether the engineering decision can live up to the weight of promotional ballyhoo, is quite another matter. But, fairly obviously, it would be too much to expect copywriters not to enlarge upon an idea which even they can understand!

I can only repeat the sentiments which I have expressed earlier on this subject: I am quite happy to accept the linear phase concept as a possible bonus in a loudspeaker system which has been carefully designed in all other respects. I would be biased against a system, built to a price, which traded driver quality for a fancy linear phase enclosure profile.

Mr Blob says



"COME SEE ME AND GET YOUR FREE POT"

Come to the blob stand at the cetia exhibition in the Melbourne Exhibition buildings in October and see me and my fabulous range of blob boards and decks. Get a free pot of your choice with my compliments. See how easy it is to solder components onto blob boards with a scope iron.

Blob boards are multi-layered roller tinned circuit boards and give you the modern low cost easy way to build circuits on which each track is identified by a letter or number system. Simply tin the end of the component, butt the component lead against the rolled tinned track, apply a blob of solder, and the component is blobbed into place. Soldering is much easier, all the circuitry is on one side of the board and so they can be mounted flush to a case, and they can be re-used, simply apply a soldering iron to the blob and remove the component.

If you would like to come to the exhibition, write to Mr BLOB, enclosing a stamped self addressed envelope, for complimentary invitations.

BLOB BOARD ASSOCIATES

P.O. BOX 23, SURREY HILLS, VIC. 3127, OR RING (03) 89 1019.

Andrew Darbyshire: apprentice at station 3DB

Because of the difficult economic conditions that have prevailed over the last few years, many firms have ceased to employ apprentices. However, an apprentice can be an important and valuable staff member, particularly in radio and television broadcasting stations. One such success story is Andrew Darbyshire, a radio apprentice with radio station 3DB in Melbourne.

by GRAEME SCOTT*


Andrew started his apprenticeship at 3DB in mid-1976, beating competition from 276 other applicants for the job! He commenced the full-time technician course at RMIT and in 1977 converted to the one day per week apprenticeship course. In 1978 he chose, in conjunction with 3DB's management, to do the fifth elective stream offered to electronics/radio apprentices. This is the communications stream which concentrates on transmitters, aerials, receivers and test equipment.

The work experience 3DB has offered Andrew includes studio control, transmitter tuning and repair, tape recorder and turntable maintenance, limiter adjustment, program-line equipment alignment, outside broadcasts, and construction and installation

of studio equipment. He has also helped repair damage to the aerial system and transmitter caused by a number of lightning strikes, a job which involved Andrew climbing the tower to inspect and repair the loading coil.

Andrew believes the apprenticeship course is the best way to get his training as it offers a co-ordinated program of work experience and related schooling. He said that heavy emphasis has to be placed on digital techniques as they are being encountered in both studio equipment and transmitters nowadays. However, power valves are still used in transmitters and so must still be covered in the school course.


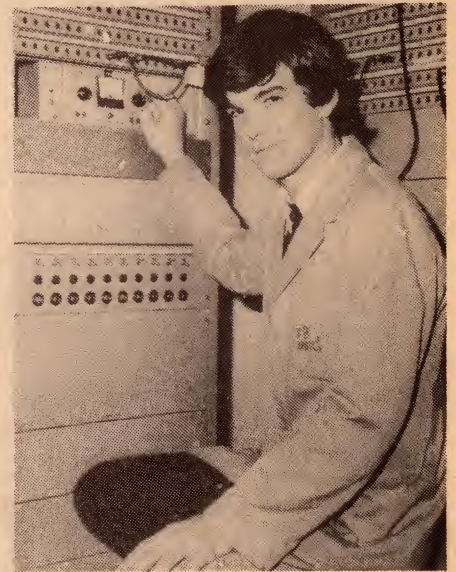
Andrew's supervisor, Murray Cauf, the station engineer at 3DB, is giving him every encouragement and assists



with any difficult theory problems.

Andrew intends to continue his education past the mandatory apprenticeship schooling, and hopes in the future to become a station engineer. ☺

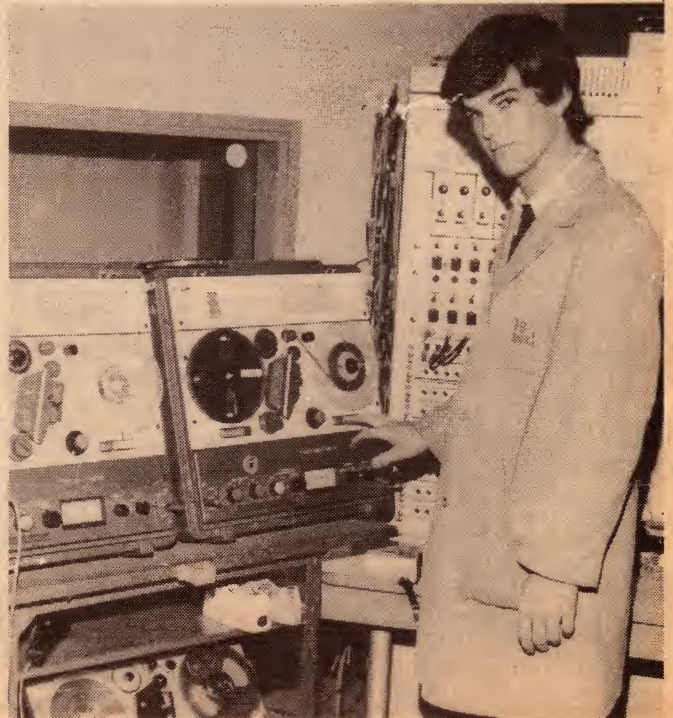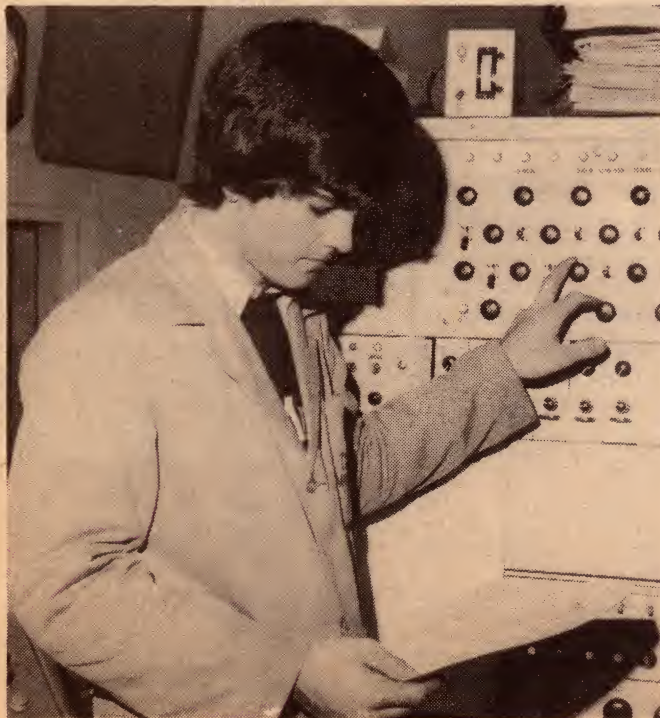*Training adviser and liaison officer, Industrial Training Commission, Victoria.




What do you hear from Foster and Fostex?

Simply a better sound.

The Plessey Foster-Fostex range of hi fi speakers. If you've ever heard from them you'll know you've listened to the results of superb craftsmanship in the science of sound. Top performance can be yours through Plessey with the Foster-Fostex range of speakers.

Here they are, and we'd like to hear from you if you'd care to have the catalogue of their impressive technical features. Please write Plessey Australia, Components Division, PO Box 2, Villawood NSW 2163 or phone 720133.

PLESSEY

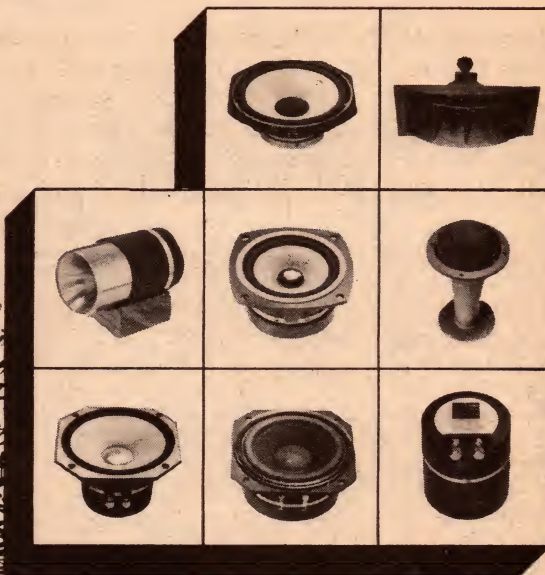

HOLT AD108

MORE GOOD NEWS FROM N.L.S.

LM300 Full Three Digits



LM300 D.M.M.


Features: LM300-3 DIGITS, LM350-3½ digits, portable batt operated, large L.C.D. display, auto polarity, decimal and overload indication, no zero adjustment, no full scale OHMS adjustment, up to 15 hours operation on AA size alkaline batteries.

Ranges: D.C. volts, A.C. volts, OHMS and AMPs.

Options: rechargeable Nicd batts & charger, E.H.T. probe, handle/tilt, stand, panel mount flange and leather case.

Price: LM300 \$109.00* LM350 \$121.00*

Dual Trace Miniscope

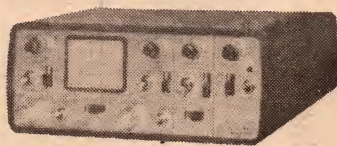

M.S.-215 Miniscope

Features: Dual trace-2-channel; separate, chopped, or alternate modes, 15 mhz bandwidth, ext. and int. trigger, time base — 0.1 U/SEC to 0.5 sec/div-21 settings completely portable batt or line operation, auto or line sync modes, less than 15 watts power consumption, .01 to 50 volts/div-12 settings, weighs only 3lbs with batts.

Size: 2.9" high, 6.4" wide, 8.0" deep.

Options: Carry case, x10 probe.

Note: Single trace scope also available with same specs.

Price: Single trace \$325.00* Dual trace \$449.00*

LCD or LED Panel Meters



R.M. series D.P.M.

Features: Mos/LSI construction, fits DIN or NEMA cutouts, large 0.6" LCD or 0.5" LED DISPLAY, No zero adjustment, plug-in range change capability, programmable decimal point, o/load indication, auto polarity, i/p voltage protection, mating edge connection or terminal block.

Ranges: 0.2V, 2V, 20V, 200V or 1000V. Available in D.C. reading A.C. powered or A.C. reading D.C. or A.C. powered.

Size: 1.645" high, 4.072" deep, 3.580" wide.

Price: From \$47.00*

For further information, contact **Non-Linear Systems** 61 Lothian Street, North Melbourne, Vic. 3051. Phone 329-9951 or your nearest distributor.

Radio Parts Group Pty Ltd,
562 Spencer Street,
West Melbourne, 3003.
Ph. 329-7888

L. E. Boughen & Co.
Cnr Milton & Baroona Rds,
Queensland, 4064.
Ph. 36-1277

Browntronic Pty Ltd,
174 Parramatta Rd,
Camperdown,
Ph. 519-5855

Radio Despatch Service,
869 George Street,
Sydney
Ph. 211-0191.

Protronics Pty Ltd
174-180 Wright Street,
Adelaide.
Ph. 212-3111.

ALL AUDIO SHACK STORES

*Plus 15% sales tax if applicable.

A trip through 'Silicon Valley'

During his recent trip to the west coast of the USA, Editor Jim Rowe was able to visit most of the major semiconductor manufacturing firms — including a number in California's "silicon valley". Here he reports on the main things he learned concerning current production techniques, research trends and future prospects.

Although many of the big US semiconductor manufacturers have fabrication plants in a variety of states, as well as assembly facilities in other countries, most of them have plants in the "silicon valley" area of California. This is the traditional birthplace of silicon planar technology, and is still the nominal hub of the semiconductor revolution.

Actually the term "silicon valley" mainly came into use because of the number of semiconductor plants congregated within a relatively small area, in the Palo Alto — Mountain View — Sunnyvale — Santa Clara district about 60km south of San Francisco. It is true, though, that the area forms part of a large valley which encloses the southern end of San Francisco bay.

During my trip I was able to stay in the area for almost a week, based at a

hotel in Palo Alto just a few kilometres down the historic El Camino Real highway from Stanford University. In the time available I was able to visit most of the larger semiconductor plants sited there.

Only two of the major semiconductor manufacturers do not have plants in the silicon valley area — Motorola and Texas Instruments. Luckily I was able to spend a day in Phoenix, Arizona, later in the trip, looking over a couple of the Motorola plants there. So, all in all, I was able to see quite a representative selection of current US semiconductor factories.

Before talking about specific companies, perhaps I should make a few general comments.

When I visited each firm I made a point of asking its executives to comment on the growing competition from

Japan, and their attitude to it. This seemed particularly relevant in view of some of the statements made recently by US industry spokesmen.


In almost every case the answer I got was that, although the problem has been somewhat exaggerated, the US industry is concerned because it sees itself disadvantaged in two main ways. One is the import tariff disparity between the two countries: imports into Japan attract 12% tariff, twice that into the USA.

This makes it significantly harder for the US industry to compete — not so much for the domestic Japanese market, but for the much larger export market. Japan is now a major supplier — if not the largest — of the world's electronic equipment, and US semiconductor makers believe they must have reasonable access to this market.


This problem could conceivably be solved by negotiation between the US and Japanese governments, with a view to equalising the tariffs, and the industry is currently urging their government to seek such an agreement. But



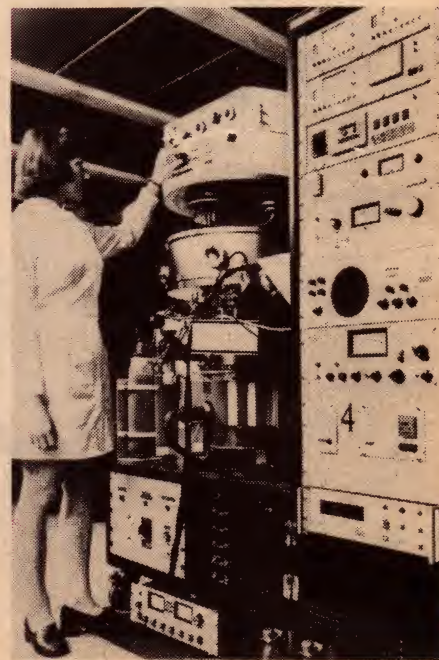A fairly typical sight in "silicon valley". This shot shows the Signetics Corporation administration building in Sunnyvale.



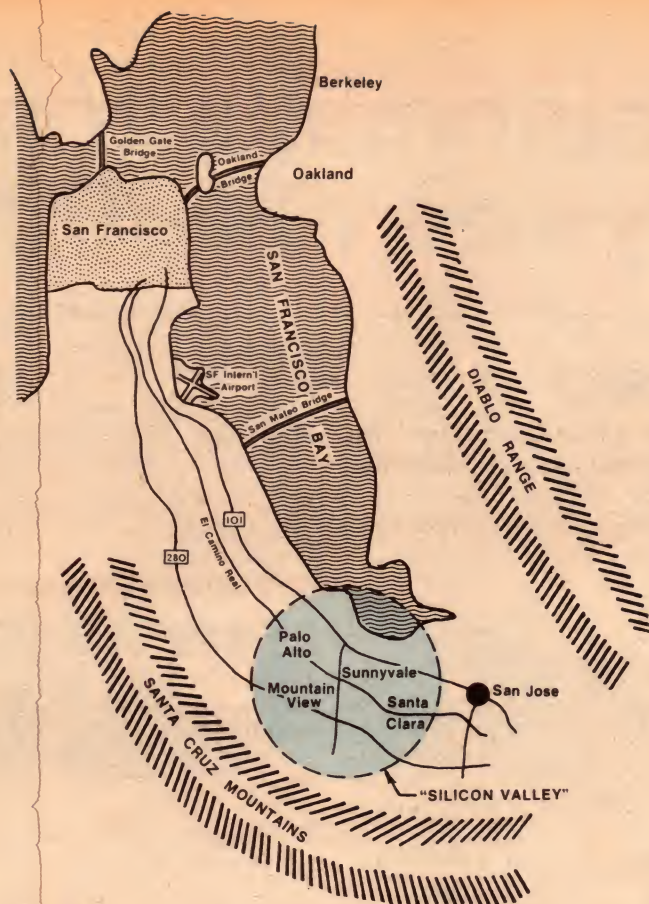Many IC wafer fabrication steps are now computer controlled. (Courtesy Signetics.)



just what could be done if such negotiations fail is hard to say — the US industry could hardly ask for the US tariff to be doubled, as this would conflict with their free enterprise and trade policy!

The other main problem, as the US industry sees it, is that the Japanese

semiconductor industry is being coordinated by their government to minimise R & D duplication and to raise business efficiency by segregating market areas. This effectively makes the total Japanese semiconductor industry into a single monopolistic competitor, of formidable size.

Needless to say the US firms see this as leading to a "united they stand, divided we fall" situation. But the way to prevent this is not at all clear.

There's no way of preventing the Japanese from uniting, yet the idea of having the US Government coordinate their own industry conflicts strongly with the concept of free enterprise. And, of course, it must be conceded that the free enterprise system does generate a tremendous amount of technological and marketing initiative, despite the negative aspects of competition and duplication.

One interesting way in which this initiative makes itself apparent is in working conditions. What impressed me about all of the semiconductor manufacturing plants I visited was the working environment, which seems particularly pleasant.

Each plant is generally set in spacious landscaped grounds, with many attractive trees and shrubs (incidentally many of the trees in California are eucalypts, originally imported from Australia). Many have well-appointed employee rest areas, and most have a bright canteen-restaurant offering excellent food at subsidised prices.


At one such canteen there is an outdoor eating area, with redwood tables and benches set on an attractive brick-paved patio beside a charming landscaped lily pond.

Virtually all of the plants provide a large car park for employees, and even these are usually dressed up with shrubs and gardens, to improve the overall outlook.

What makes all this particularly significant is that there are virtually no trade unions operating in these plants.



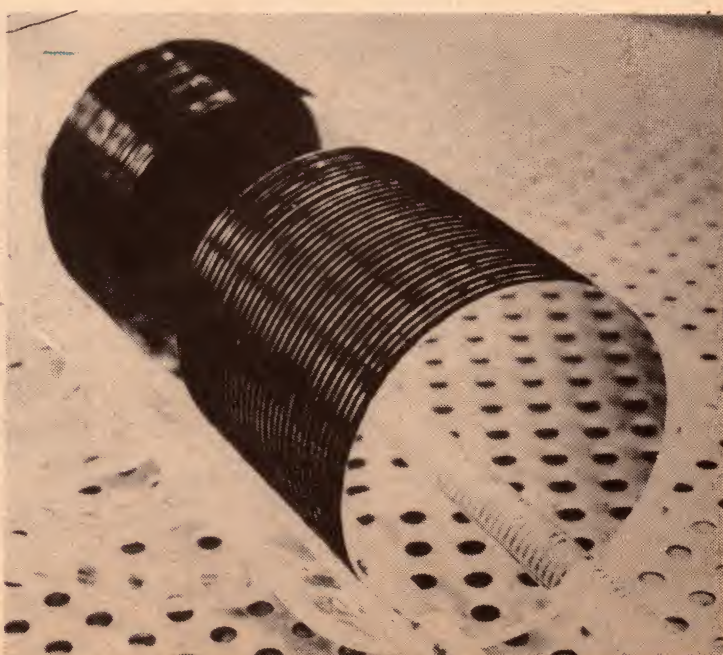Now well established, ion implantation chambers are also largely computer controlled. (Courtesy Signetics.)



Many of the semiconductor makers are now processing 100mm-diameter wafers, with 150mm wafers already envisaged. (Signetics.)

Now—one automatic iron replaces any size 10w–60w.

SCOPE TC 60

- Variable Wattage
- Variable screw on tips
- Variable Temperature 200°–400°
- 240V Mains Operated

Automatic Wattage Selection

Let the actual wattage required for the job be decided by the iron's simple mechanical sensing and control system.

Automatic Temperature Control

Dial any intermediate temperature 200–400°C without changing the tip; holds $\pm 2\%$ of any selected temperature.

You Decide Tip Size

Without the need to buy up to three irons to cover tip sizes normally used, you can screw on any tip shape and weight combination from 0.8mm to 6.4mm.

Cooler Finger Grip

Cooling fins keep your finger tips comfortable — handle shape aids good balance and feel.

Have you experienced the frustration of starting to use your 15 watt iron only to realize the tip is going cold before the solder flows — alternatives?

(a) Wait 5–10 minutes to heat up your 30 watt (even though the tip on it is really too big). (b) Be a supreme optimist and hope your 15 watt will eventually heat up the joint before you cook the component and lift the track. (c) Switch on your SCOPE TC60 and while waiting the 45 seconds to heat — screw on the tip size you really want.

The SCOPE TC60 will decide the wattage required for each joint.


Some other SCOPE TC60 features —

- **Component Protection** is aided by earthed tip and barrel. Critical components and operator can then be earthed to common point.
 - **Simplicity** of temperature control system suggests less maintenance. An expanding metal probe detects temperature variations inside each tip and operates a mini micro switch in the handle.
 - **Temperature Key** is inserted into handle. 40°C variations per quarter turn. Key is removable to discourage unwanted alteration to temperature setting.
 - **Neon** indicates when power is being applied to elements — monitors control system.
- 50V, 24V Versions are available with 50W element.

SOLDERING—DESOLDERING STATION



Long life tips for Scope TC60 iron.

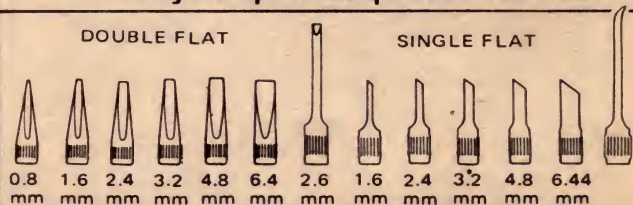

Iron plated screw-on pre tinned. *This tip is fitted as standard.

SCOPE TC60

The iron you completely adjust to your job.

FOR YOUR NEAREST STOCKIST RING:

MELBOURNE VIC.
(03) 338 1566
SYDNEY N.S.W.
(02) 818 1166
ADELAIDE S.A.
(08) 212 3111

BRISBANE QLD.
(07) 221 1933
TOWNSVILLE QLD.
(077) 71 3448
ROCKHAMPTON QLD.
(079) 27 3370

HOBART TAS.
(002) 34 2811
LAUNCESTON TAS.
(003) 31 5545
PERTH W.A.
(09) 381 4155

AUCKLAND N.Z.
54 6029
WELLINGTON N.Z.
85 9578

A trip through "Silicon Valley"

All of the amenities have been provided by the firms in response to competitive pressures. As one plant worker replied when I commented on this, "Well, the company knows that if they don't provide good amenities, we are likely to quit and get a job down the road!"

On the technological side, as one would expect, the competitive pressures are pushing all of the companies ever onward into LSI (large-scale integration) and parallel technologies like magnetic bubbles.

Most of the companies seem to be getting into bubble technology, even though it requires rather different processing from conventional semiconductor devices. Perhaps more of them are committed to CCD (charge-coupled devices), although the consensus of opinion seems to be that standard N-channel MOS technology is still capable of considerable development.

Broadly speaking, most companies seem confident that product developments will continue to take place at the current rate. For example memory devices are expected to continue doubling in capacity every three years or so.

Needless to say, maintaining this rate of production development involves heavy investment in both R & D and fabrication plant. Most of the US semiconductor companies plough between 10% and 12% of their profits back into R & D, while I was told that production costs tend to increase by a factor of 10 times for each doubling of memory device capacity (for example).

In the area of fabrication, most companies are currently using 75mm diameter silicon wafers, although a number are in the process of changing to 100mm wafers. The next likely shift is to 150mm wafers, but this is probably about two years away.

Some firms are still using contact printing for wafer masking, but most seem to have either changed or are in the process of changing over to optical projection printing. Some have started to work with electron beam masking, but this still seems to be experimental as yet.

An exotic new technique only a few years ago, ion implantation is now a standard fabrication procedure. Although still a costly and impressive machine, ion implanters are now "just another piece of fabrication plant", found in many facilities along with diffusion furnaces, epitaxy reactors and metalisation chambers.

Incidentally as you might expect computers are now used not only for product testing and sorting, but to control many of the wafer fabrication processes as well. In fact most of the

major fabrication steps are now fully automated, removing variables due to the human element.

Turning now to specific companies, the first firm I visited was the Intel Corporation, in Santa Clara. This is the company which was founded only 10 years ago by semiconductor pioneers Dr Gordon Moore and Dr Robert Noyce, the acknowledged inventor of the microprocessor. It specialises in high-technology LSI products like memory chips and microprocessors, and tends to lead the field with new developments.

At Intel I was shown around by Mr Ward Gebhardt, their director of international market development.

Among the interesting things I learned from talking with Ward Gebhardt



As with fabrication, testing of both wafers and final devices is now almost completely computerised. (Signetics.)

was the news that Intel are shortly releasing a 16-bit microprocessor, the 8086. It will have a more powerful instruction set than 8-bit processors, together with a significantly enhanced addressing capability.

Intel are also working on magnetic bubble memories. As was announced in the US technical press a couple of months ago, they have entered into an agreement with IBM, to exchange their own single-chip microcomputer technology for IBM's bubble memory know-how.

One of the areas where Intel has been leading the field is in EPROMs of course. They have recently announced a new family of single-5V-supply

EPROMs which includes a 32k bit device, and have for some time been making a single-chip microcomputer featuring an EPROM on the same chip as the processor and RAM memory.

As EPROMs have the reputation of being tricky things to make, particularly when combined with other types of element on the same chip, I asked Ward Gebhardt if Intel had struck any problems. He smiled broadly and said "No more than we expected!" Fairly obviously they solved whatever problems they did encounter, and are now getting good yields.

The next firm I visited was Fairchild Semiconductor, with plants in both Santa Clara and Mountain View. Fairchild is basically the oldest of the semiconductor firms in silicon valley, having started there at the beginning of the silicon transistor era. They still hold the key patents on planar technology, used in virtually all modern transistors and integrated circuits.

Because Fairchild has been in the business so long, almost everyone working in the silicon valley area seems to have worked there at one time or another. Many engineers have gained their basic training there, and many of the other firms have been started by ex-Fairchild employees wanting to "go it alone". As a result the firm is often described jokingly as the "university of Fairchild".

Fairchild has a high degree of "vertical integration", being involved directly in just about every phase of product manufacture and application. On the manufacturing side they start right from scratch, growing their own silicon crystals and refining them before performing all of the normal fabrication processes.

And after the semiconductor devices are made, they also use them in a variety of proprietary product lines. These include digital watches, clocks and video games.

During my visit to Fairchild I met Mr Bill Wirth, international operations manager for their video products division. Bill Wirth gave me a very interesting demonstration of the Fairchild "Channel F" microprocessor-based video game, with its range of plug-in "Videocart" game cartridges.

The basic game itself contains 3 of the Fairchild F8 microprocessors, together with 4 ROM program storage chips. Each of the various plug-in games cartridges contains a PC board with additional F8 and PSU chips, giving a very flexible system. The two hand controls each have 8 directions of movement. All in all, a most impressive game indeed.

In fact, it is so far ahead of the familiar "ping-pong" type video games that Fairchild have been presented with quite a marketing challenge. As Bill Wirth explained, it hasn't been easy to convey the game's full potential to an electronically unsophisticated public.

A trip through "Silicon Valley"

Despite this they are now starting to sell really well, and you can see them in many US department stores.

The third company I was able to visit was National Semiconductor Corporation, with a number of plants in Santa Clara. Like Intel, National was formed in the 1960's by ex-Fairchild people, and is currently headed by former Fairchild executive Charles Sporck.

National is a broad-based company, however, and makes a wide range of semiconductor devices. It also has a high degree of vertical integration, making memory systems and industrial mini and micro computers as well as consumer products like digital watches and calculators.

I was shown around National by Mr Jack Query, their marketing coordinator for the far East region. Jack had organised a very interesting tour, and I was able to meet many of the National engineers and executives as well as see a variety of product fabrication lines and other facilities.

I was able to see fabrication lines of both the "batch" and "continuous" type, and the comparisons were interesting. With the batch type of line less equipment is required, as the same equipment may be used for a number of different stages in the fabrication sequence. In contrast the continuous type of line requires more equipment, as the wafers pass through each station only once.

The continuous type of line has the potential for greater throughput, but requires a somewhat greater capital investment. It also tends to be more vulnerable to stoppages due to equipment breakdown.

Talking with National engineers I learned that they will shortly be coming out with a new single-board microcomputer system for industrial applications. Based on SC/MP, it will have 4k bytes of RAM, National's NIBL (extended Tiny Basic) interpreter in a single Max-ROM, parallel I/O and a programmer for 8k/16k PROMs, all on the single PCB.

Looking further into the crystal ball, I was told that they expect to release a 1k byte static RAM chip within about 12 months. Shortly after that we should see 32k bit EPROMs, with 64k EPROMs only about 3 years off at the most.

Incidentally one of the people I met at National was Ms Georgia Marszalek, director of their microprocessor user's group. We had a very friendly talk, and compared notes on the problems of publishing a technical magazine. Georgia told me that her "Compute" newsletter now has a circulation of about 12,000 worldwide, with about 500 coming to Australia.

The final semiconductor company I

was able to visit in the silicon valley area was the Signetics Corporation, in Sunnyvale. As most readers will be aware, Signetics became part of the worldwide Philips organisation in 1975. Before that it was a subsidiary of Corning Glass.

Signetics started in 1961 as a supplier of a broad range of fairly standard devices. Later it came out with quite a few pioneering products of its own, including such things as phase-locked loop chips and the classic 555 timer IC.

My host at Signetics was senior sales engineer Mr Herb Jesse, who again had organised a very interesting day of plant tours and meetings with

dustrial and hobbyist users with 2650-based systems.

One of the many interesting things I saw at Signetics was a demonstration of a new video game chip set, currently under development. One of the games provided by the set was a fascinating "boxing" game, in which two humanoid figures appear on the colour TV screen. By manipulating the game's hand controls you can make them slug one another, knock one another out and so on.

The game is complete with sound effects, so that each figure makes the appropriate noises when hit. The game also monitors the expended "energy" used by the two figures, and this together with a random factor is used to determine whether a boxer recovers from a knockdown or stays down for



Outside one of the Motorola plants in Phoenix, Arizona. Note the large cactus on the right, with palm trees behind it.

engineers and executives. I met the people behind the 2650 microprocessor, and saw a new 2650-based microprocessor tutor unit which they will be releasing shortly.

One of the things that the Signetics people were keen to stress was that although the 2650 microprocessor may have been a little late to enter the market, they are definitely committed to it and its fast-growing family of interfacing chips. They certainly don't see it as an "also-ran", in danger of being eclipsed by the older and more established microprocessors.

One of the new chips coming out shortly as part of the 2650 family is a 2k-byte ROM with an improved version of the Signetics "PIBUG" debug/monitor, together with a new line assembler known as "PIPLA". This should be of great interest to both in-

the count. It sure is a far cry from the familiar "ping-pong" type of simple video game!

About a week after leaving the silicon valley area, I was able to spend a day in Phoenix, Arizona, looking over some of the plants of Motorola Semiconductor. As most readers will be aware, this firm is a subsidiary of Motorola, Inc — one of the largest US electronics companies.

I was shown around the Phoenix plants by my old friend Jim Wiggins, who ran Motorola's Sydney office for some years. It was good to meet him again, and to hear how successfully he has settled in sunny Arizona.

Another familiar face at Motorola belonged to Mr Bob Hammond, marketing manager for solar operations, whom I met about a year ago when he visited Australia to

promote the new Motorola silicon solar panel. He was able to tell me that since then the solar panels have been selling extremely well — so well, in fact, that they can't make them fast enough!

Speaking of solar energy, Bob was able to tell me of two interesting new developments. One is that Motorola has developed a high efficiency concentrator-type solar cell, with integral mirror system and heatsinks. A prototype array of these cells is likely to be set up at Pheonix airport, as described in a featured story in last month's issue.

The other development is that Motorola has made considerable progress with ribbon fabrication technology, believed to hold the key to low cost solar electricity.


Whereas other firms have been

reason why they are as yet more expensive than LEDs. The LCD displays are used in Motorola's watch modules, which are sold to many watch manufacturers.

Needless to say, Motorola is very active in the microprocessor area.

Their 6800 is still going strongly, with a growing family of peripheral chips and additional processors. An interesting new addition to the family is the MC14500B, a single-bit processor designed specifically for decision-orientated controller applications.

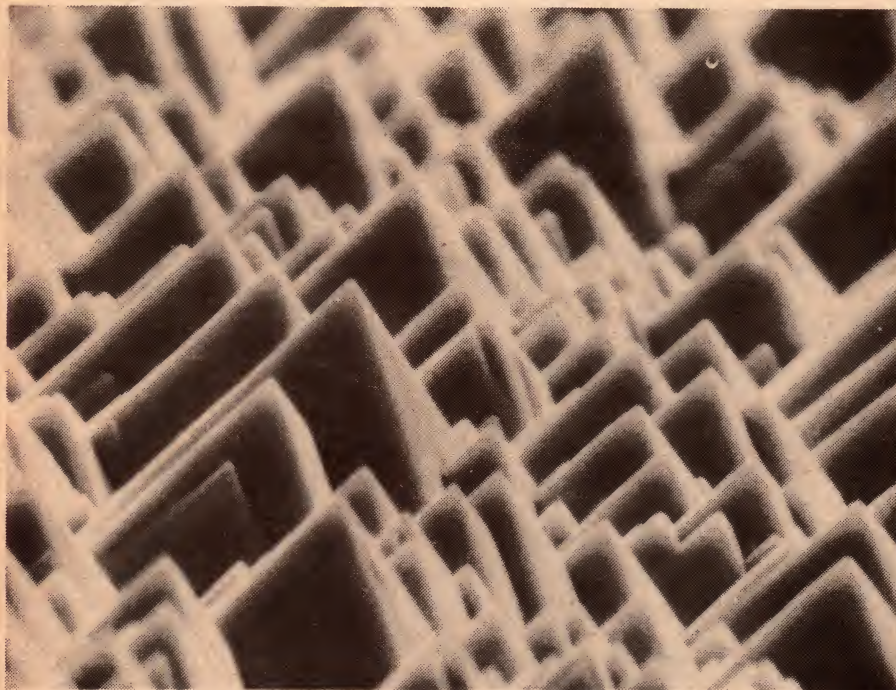The MC14500B is described as an "industrial control unit" or ICU. It has an instruction set with only 16 instructions, and is designed to be used by engineers without any previous knowledge of microprocessors. Motorola sees it as filling an important application area,



A microscopic view of one of Motorola's silicon cell wafers. The texture-etched pyramids give an exceptional 99 per cent energy absorption rate.

working on die-pulling methods of making a continuous silicon ribbon, Motorola has developed a method of depositing a polycrystalline layer on a continuous band of special substrate material. The two are then separated, and the resulting thin silicon ribbon is zone melted by a high-power laser beam to recrystallise it into single crystal form.

In one of their development labs I saw 50mm-wide ribbons about 200mm long made in this way, with a 500 watt carbon dioxide laser being used for the zone melting. The results certainly look promising, although my impression is that it could well be 2 or 3 years before we see the resulting low-cost solar cells.

In another Motorola plant I saw liquid-crystal displays for watches being made. These involve quite a deal of skilled labour at present, possibly one

doing control jobs which are really too simple for even 4-bit conventional microprocessors.

Well, I hope the foregoing has given you a good idea of the main things I learned on a quick tour of most of the major US semiconductor firms. Perhaps it has also given you some idea of the sort of developments we can expect from these firms in the next couple of years. Judging by what I saw, we should see some exciting new products.

Finally, a note of thanks. This sort of tour would not have been possible without the generous cooperation of many people in the firms concerned, and I am most grateful to all the people concerned. This includes not only those in the US facilities I visited, but also those in Australia who arranged the various visits.

TRIO TEST INSTRUMENTS

CO1303D 5MHz Single Trace Oscilloscope

- A high vertical sensitivity of 10 mV/div and a wide bandwidth of DC to 5 MHz make the CO-1303D a versatile all-purpose instrument
- Its vertical and horizontal DC amplifiers permit observation in a variety of applications particularly at very low sweep rates below 1 Hz
- A direct-coupled vertical deflection allows observation of waveforms up to 450 MHz
- External synchronization assures you of a more stable waveform observation

VT108 Volt-Ohm Meter

- Measures DC voltages 0 to 1500V, AC voltages 0.1 to 1500V r.m.s., and resistances 0.1Ω to 1000 MΩ
- All solid state circuitry including P.E.T.s, makes the instrument compact and lightweight. Handy enough to be brought to any location where electrical measurements are made. Unique appearance with controls arranged for maximum ease
- Only four "C" size batteries assure one month, or longer, service
- A measured value can be stored for a moment for later reading
- The bandwidth is as wide as 15 Hz to 5 MHz

Available from leading Electronic Stores

PARAMETERS LTD


Sydney: 439 3288 Melbourne: 90 7444

SG402 R.F. Signal Generator

- Covers frequencies from 100 kHz to 30 MHz in six ranges as a versatile wide band signal generator
- The output voltage, 0.1V rms min., is continuously variable with an incremental attenuator switch and fine control
- Either internal or external modulation may be switch selected
- Compact, lightweight construction and unique control arrangement make the instrument easy to use
- All solid state circuitry assures stable operation

AG202A CR Oscillator

- A single-scale dial directly reads oscillator frequency ranging from 20 Hz to 200 kHz on four bands
- Output voltage of 10V rms at maximum can be attenuated to -20 dB and -40 dB with a front panel attenuator. It also can be continuously varied with a fine control
- Compact and lightweight. The scale is easy to read with a smooth dial knob
- An external sync. input connector allows output frequency to synchronize with more accurate external signal
- A front panel switch selects either low distortion sine wave or sharp rising square

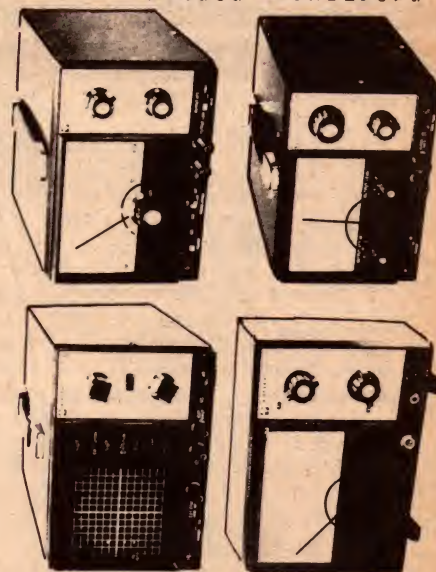

INCREDIBLE BARGAIN LEDS

7 segment readouts:

brand new, prime spec — as used by Electronics Australia.

LT303 common cathode — exact equiv. to Texas TIL313 and H/P 5082-7740.

BUY NOW AND SAVE:

\$1.30 each
10+

Cat Z-4103

(OR \$1.50 IN SINGLE QUANTITIES)

LED INDICATORS AT BARGAIN PRICES, TOO!

Prime spec devices, hundreds of uses. Be quick for these!

Small red — Cat Z-4010

Large red — Cat Z-4030

20¢ each
10+
or 22c each



STILL SUFFERING?

There's plenty of cold weather left yet — and that first cold shock of the morning can well ruin your whole day!

Why put up with that icy shock? A Dick Smith Warmed Toilet Seat will start your day (and end it) delightfully warm. It costs peanuts to run and plugs into any p/point.

\$32⁵⁰

Cat X-2000



SHEER LUXURY!

DICK SMITH'S 1978 CATALOGUE *FREE*

Contains a mind-boggling selection of products for electronics enthusiasts, car buffs, home handymen and hi-fi fiends!

• HUGE 8 PAGE DATA SECTION •

As published in April 1978 Electronics Australia

Get you FREE copy: Send in the coupon TODAY!

Name

Address

State P'code

WOT'S NEW?

Handy size plastic project case


ESPECIALLY SUITABLE FOR DIGITAL READOUTS — CLOCKS, TACHOS, METERS, ETC.

Yes! A compact plastic case ideal for all of those digital readout projects. Front of case is red perspex backed by a false front to support readouts. There is also room for a couple of pots or switches. The rear panel comes out too, revealing PCB supports to make simple PCB mounting. A truly versatile little case which comes complete with mounting bracket as shown.



INCREDIBLE VALUE! \$3⁶⁰

(10+ \$3.00 each) Cat H-3194

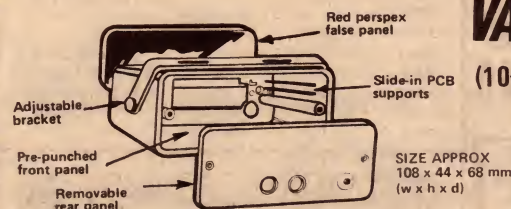

SIZE APPROX 108 x 44 x 68 mm (w x h x d)

COMMERCIAL ENQUIRIES WELCOME!

Interested in buying this case for commercial use? Or other items on this page or in our catalogue? Generous quantity discounts are available to commercial users and resellers: ring Gary Johnston (02-439-5311) for details and terms.

WATCH THIS SPACE

AND FIND OUT WHAT YOU MISSED!

Each month, all of our stores feature an outstanding special which is actually BELOW COST! All you have to do is pop into your nearest store to find out what it is. N.B. — Specials are STRICTLY 'while in-store stocks last'. Don't miss out!

LAST MONTH:

A TE22D AUDIO SIGNAL GENERATOR FOR \$49.70 NORMALLY \$95.00

SAVING \$45³⁰


WHAT'S THIS MONTH'S SPECIAL? CALL IN AND FIND OUT YOURSELF!

SPECIAL!

AM-FM TUNER

Top value: '000s in use all over Australia. Brilliant AM and FM/Stereo FM reception, and we've knocked a massive \$8.00 from the price. Buy now and save while stocks last. Note: not a kit — ready to go. All you do is connect to power & amplifier! Cat F-4615.

29⁵⁰
SAVE \$8⁰⁰

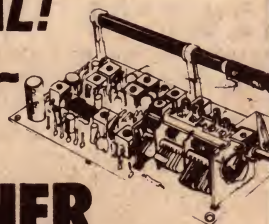

FIBREGLASS PCB from \$1⁰⁰ per sq ft!


IDEAL FOR ALL PROJECTS — Easily cut into smaller pieces. SIZE 13" x 14" (1.26 sq ft)

NORMAL PRICE OVER \$6.00 each!

SPECIAL \$1.50
10 or more \$1.26

BUY A YEAR'S SUPPLY NOW — AND SAVE A FORTUNE!

GET WITH A FEW FRIENDS: BUY IN BULK

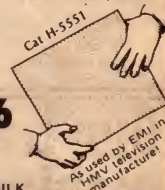

As used by EMI in hi-fi television manufacture!


TEST CLIPS for meters, etc

For hands-free measuring. Two styles, both with spring action and hooked end. Wires insert easily — positive connection.

Small: Cat W-4580 .. 75c (or 50c each for 10 or more)

Large: Cat W-4589 .. \$2.20

from 50¢

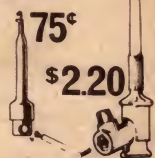

NEW! PCB DIL SWITCHES

4 or 10 SPST rocker switches mounted in a DIL package — ideal for PCB mounting. Use for pre-programming, for changing circuit constants on boards, etc.



from \$1.70

4-way: Cat S-1604 .. \$1.85 (or \$1.70 for 10 or more)

10-way: Cat S-1610 .. \$2.95 (or \$2.65 for 10 or more)



NEW!

DIGITAL WATCH KIT

It's cheap enough to be a toy for the kids (Christmas is close!) but it's far from a toy — it's a full function digital electronic watch kit. Kit? All you do is put a couple of modules in place and snap the back shut! But this electronic master-piece (which sold for around \$50 only 12 months or so ago) shows date, day & seconds as well as hours & minutes. Real value!

Cat. K-3455

\$12⁵⁰

includes strap, batt.

SPARE BATTERIES
Pack of 2 ultra-high reliability silver oxide batteries.
Cat S-3295 \$1.95

HARD BOILED EGGS

Forgive the pun! But our egg insulators are certainly hard. High quality, high insulation, in two styles for all loads.

Small egg: Cat D-5300 80c each (or 50c each for 10 or more)

Large egg: Cat D-5302 \$1.20 ea. (or 99c each for 10 or more)



Build a 200 Meg DFM.

It's one of the handiest pieces of test gear to have in the workshop, the shack, the laboratory — a digital frequency meter.



40MHz: Cat K-3436

\$99⁵⁰

200MHz Version: Add a 95H90 IC (Cat Z-5360)
Now reduced to only \$12.50 (save \$4.00!)

Now you can build your own 200MHz DFM for just over \$100. In fact, if you only need 40MHz, (and many people don't need more) the kit is less than \$100. And if you want to increase it to 200MHz in the future, that's easy — just add a 95H90 pre-scaler IC.

This is the all-new Electronics Australia design (August/September issues) and features exclusive Dick Smith front panel. You'll find it hard to beat our kit — it comes with explicit instructions and a 'Sorry Dick it Doesn't Work' coupon.


CUSTOMERS PLEASE NOTE:

Our ads are often so successful that the stores run out of advertised lines within a few days. Or, in some cases, a last minute hitch may develop: a wharf strike may hold up goods, a parcel may go astray, a flu epidemic may hit our warehouse... What we're trying to say is that SOMETIMES the lines shown on these pages may not be available in the stores when you go in. Please don't blame the shop staff: they're as helpless as we are! So if you're about to drive across town or across the state to pick up a certain line, play it safe: PLEASE PHONE THE STORE FIRST — they'll be able to tell you if what you want is in stock!

Our transformers solve your voltage problems...

Need 'strange' voltage combinations for that special project? Don't despair:

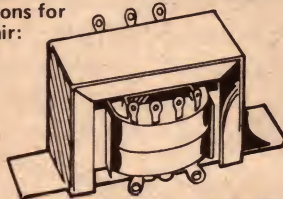You probably thought our multi-tap transformers just gave the voltages shown on them. Wrong! Our transformers give a huge number of combinations of voltages. It's just a matter of picking the taps you need. So even if your voltage requirements are 'strange', you can probably get them from a Dick Smith multi-tap transformer.



M-2155 nominally 15V @ 1A with taps at 6.3V, 7.5V, 8.5V, 9.5V, 12.6V, 15V.
Gives the following combinations: 1.0V, 1.2V, 2.0V, 2.2V, 2.4V, 3.1V, 3.2V, 3.5V, 4.1V, 5.1V, 5.5V, 6.3V, 7.5V, 8.5V, 8.7V, 9.5V, 12.6V and 15V, plus 2.0V CT, 12.6V CT, 15.0V CT. A TOTAL OF 21 COMBINATIONS!

M-6672 nominally 30V @ 1A with taps at 15V, 17.5V, 20V, 24V, 27.5V, 30V.
Gives the following combinations: 2.5V, 3.5V, 4.0V, 5.0V, 6.0V, 6.5V, 7.5V, 9.0V, 10.0V, 12.5V, 15.0V, 17.5V, 20.0V, 24.0V, 27.5V, 30.0V, plus 5V CT, 30V CT. A TOTAL OF 18 COMBINATIONS!

M-6978 nominally 15V @ 2A with taps at 6.3V, 7.5V, 9V, 10.5V, 12.6V, 15V.
Gives the following combinations: 1.2V, 1.5V, 2.1V, 2.4V, 2.5V, 2.7V, 3.0V, 3.6V, 4.0V, 4.2V, 4.5V, 5.1V, 6.3V, 7.5V, 8.7V, 9.0V, 10.5V, 12.6V, 15V, plus 3V CT, 12.6V CT, 15V CT. A TOTAL OF 22 COMBINATIONS!

\$5⁵⁰

\$6⁷⁵

\$16⁰⁰

PARTS FOR NEW KITS

UNIVERSAL MOVIE MIXER (See September E.A.)
Complete kit, including instructions Cat K-3492 .. \$49.50

SEPARATE PARTS:
PC Board (only) Cat H-8354 .. \$2.95
50k A curve 45mm slider pot Cat R-1980 .. 85c
Knobs to suit slider pot Cat H-3774 .. 30c

FET INPUT AC-DC VOLTMETER (See September E.A.)
Not produced as a special kit — all parts available ex stock:
PC Board only Cat H-8353 .. \$2.75
1mA MRA 65B Panel Meter Cat Q-2060 .. \$14.50
Fabricate your own meter scale using the Scotchcal process:
8005 black Scotchcal photo-sensitive aluminium .. Cat H-5694 .. \$6.00
CA-3140 FET op-amp Cat Z-5417 .. \$2.50

DIGITAL DIAL (See September E.T.I.)
Not produced as a special kit — most parts available ex stock.
PC Boards:
ETI 550 Cat H-8619 .. \$2.20
ETI 591 A/B (suit special Dick Smith LT-303 7 segment displays) .. Cat H-8617 .. \$4.00
ETI 591 C (suits yellow H/P 5082-7663 displays) .. Cat H-8618 .. \$1.80
ICM 7217 A up-down counter IC Cat Z-5416 .. \$16.00
5082-7663 yellow 10.9mm 7 segment display .. Cat Z-4160 .. \$4.50
LT-303 red 7.6mm 7 segment display Cat Z-4103 .. \$1.50

LIGHT SHOW CONTROLLER
Not produced in kit form — most components normal stock.

UPGRADED 40/200MHz FREQ. COUNTER (See August E.A.)
Same style as previous kit, but new circuitry means it is easier to build, set up and is more sensitive. Basic counter is 40MHz — by adding a single 95H90 IC the range is extended to 200MHz.
Complete kit for 40MHz, inc. instructions, Cat K-3437 .. \$99.50
95H90 IC to extend range to 200MHz Cat Z-5360 .. \$12.50

SEPARATE PARTS:
PC Boards (set of two top quality boards) Cat H-8346 .. \$8.50
MC-10161 IC (triple differential amplifier) Cat Z-5415 .. \$1.95
MM-5369M IC (oscillator — divider) Cat Z-5781 .. \$3.50
74C926 IC (4 digit counter) Cat Z-5416 .. \$12.00
3.579545MHz crystal (new low price) Cat K-6031 .. \$3.00
LT-303 7 segment display Cat Z-4103 .. \$1.50
All other components are normal stock lines at all of our stores.

PHOTO TACHOMETER (See August E.A.)
Although we do not produce a full kit for this project, all parts are normal stock lines at all of our stores.
PCB (only) Cat H-8352 .. \$1.80
FPT100 phototransistor Cat Z-1950 .. \$2.00

UTILITY TIMER (See August E.A.)
Again, not produced as a special kit — all parts are normal stock lines.
PCB (only) Cat H-8345 .. \$3.50
6V Buzzer Cat L-7003 .. \$1.75
Zippy box case Cat H-2753 .. \$1.95

NEW TO GAME TV GAME KIT (See July E.A.)
Complete kit, including instructions Cat K-3491 .. \$49.50

SEPARATE PARTS:
PCB (only) Cat H-8344 .. \$3.95
Fully built RF modulator Cat K-6040 .. \$3.00
Fully built audio modulator Cat K-6042 .. \$4.50
AY-3-8600 IC Cat Z-6852 .. \$15.00

TRANSISTOR TESTER (See July E.A.)
Complete kit, including instructions Cat K-3052 .. \$17.90

SEPARATE PARTS:
PCB (only) Cat H-8350 .. \$1.95
1mA panel meter Cat Q-2010 .. \$7.90

UP/DOWN PRESETTABLE COUNTER (See E.T.I. July)
Not a full kit. Special parts:
ICM 7212A IC counter Cat Z-5416 .. \$16.00
Special PC boards to suit the Dick Smith Z-4103 7 segment displays:
PC boards A & B Cat H-8617 .. \$4.95
7 segment displays Cat Z-4103 .. \$1.50

STUNT MOTORCYCLE TV GAME (See E.T.I. June)
Full kit, including instructions Cat K-3474 .. \$29.50

SEPARATE PARTS:
PCB (only) Cat H-8615 .. \$3.85
Fully built RF modulator Cat K-6040 .. \$3.00
AY-3-8760 IC Cat Z-6854 .. \$19.50
3.58MHz crystal (new low price) Cat K-6031 .. \$3.00

DICK SMITH ELECTRONICS



SYDNEY 125 York Street, SYDNEY. Ph. 29 1126
147 Hume Hwy, CHULLORA. Ph. 642 8922
162 Pacific Hwy, GORE HILL. Ph. 439 5311
30 Grose Street, PARRAMATTA. Ph. 683 1133

MELBOURNE 399 Lonsdale Street, MELBOURNE. Ph. 67 9834
656 Bridge Road, RICHMOND. Ph. 42 1614
BRISBANE 166 Logan Road, BURANDA. Ph. 391 6233
ADELAIDE 203 Wright Street, ADELAIDE. Ph. 212 1962

MAIL ORDERS P.O. Box 747, Crows Nest, N.S.W. 2065 Post and packing extra. Dealers across Australia.

MAJOR DICK SMITH DEALERS:

Overland Communications 11 53 Wollongong St, Fyshwick ACT Ph 80 42 17
Trilogy Elect. Supplies 52 Princes Hwy, Wollongong NSW Ph 83 1213
Sound Components 78 Brisbane St, Tamworth NSW Ph 66 1363
Hitel Hi Fi 145 Queen St, St Marys NSW Ph 623 4442
Don House Electronics 2 Merriwa St, Gordon NSW Ph 498 1398
DGE Sales 44 Brown Rd Newcastle NSW Ph 69 1222
M&W Electronics 48 McNamara St, Orange NSW Ph 62 6491
Double Diamond 18 Russel St, Goulburn NSW Ph 21 5440
Greg McCartney 99 Fitzmaurice St, Wagga NSW Ph 21 3044
Rivercom 9 Copeland St, Wagga NSW Ph 21 2125
Brian Bambach Elect. 68 William St, Gosford, NSW Ph 24 7246

GCG Communications
The Elect. Hobby
Premier Sound
Summer Electronics
Aero Electronics
Tasmanian Hi Fi
Devon Electronics
A E Cooling
Hutchesson's Commun.
Altronics
BP Electronics

385 Mulgrave Rd, Cairns QLD Ph 54 1035
1168 Gold Coast Hwy, Palm Beach QLD Ph 34 1248
239 Musgrave St, Rockhampton QLD Ph 27 4004
97 Mitchell St, Bendigo, VIC Ph 43 1977
123A Bathurst St, Hobart TAS Ph 34 8232
87A Brisbane St, Launceston, TAS Ph 31 5815
45 Ashburner St, Devonport TAS Ph 24 4216
Town Centre, Peoples St Bldg, Elizabeth SA Ph 255 9196
5 Elizabeth St, Mt Gambier, SA Ph 25 6404
105 Stirling St, Perth WA Ph 328 1599
11 Duke St, Albany WA Ph 41 2681

SHOPS OPEN 9AM to 5 30PM
(Saturday 9AM to 12 noon)
BRISBANE 12 Hume Avenue

ANY TERMS OF CREDIT ARE TO
APPROVED APPLICANTS ONLY

Many lines available from the
Dick Smith Electronics Centres at

GRACE BROS

Bradway - Bondi - Cheltenham - Liverpool
Mandla - Mt Druitt - Parramatta - Roselands
and Warragul Mall



IT'S NOT WHAT IT DOES, BUT WHAT IT UNDOES.

It's no wonder your records are flat. Before they're pressed, about half of the music's dynamic range has been squeezed out.

The vice is the recording process. Live music's dynamic range can be more than 100dB, but the studio recorders have only 58dB of useable dynamic range capacity. So the engineer has to compress the signal, making the loud sounds quieter and quiet ones louder. And that's where the live gets squeezed out of it. Your con-

ventional discs offer less than 50dB of dynamic range.

You can undo much of the damage. Just add a dbx 3BX Dynamic Range Expander to your system, and you'll restore most of the missing dynamic range in your records, tapes and FM broadcasts. The 3BX unsqueezes all kinds of music, making everything sound

richer, clearer and fuller than you've ever heard. And with dramatically less noise as well.

The 3BX works equally well with bud-

get-priced equipment and state-of-the-art systems. You won't need an audio engineer's ears to hear the remarkable improvement in the quality of your recorded music.

But we suggest you hear it for yourself. Take your favorite record or tape to your dbx dealer and ask for a demonstration. Once you hear the 3BX in action, you'll wonder how you ever listened to music without it.

dbx

SUPERSCOPE
(Australasia) Pty Ltd
P.O. Box 604
Brookvale, NSW 2100.
Tel. 939 1900

3BX three band dynamic range expander





Hi Fi News

THE CHICAGO CES: FROM THE WAY AHEAD TO THE WAY OUT!

With electronic exhibitions much in the news of late, our U.S. correspondent George Tillett reports on the most recent Chicago Consumer Electronics Show. He draws attention to some of the items that you may well be aspiring to own during the next couple of years!

The Chicago Consumer Electronics Show keeps on growing and, this year, there were no less than 821 exhibitors spread over some 500,000 feet at the huge McCormick Center and the adjoining McCormick Inn.

For the past two or three years, makers of audio equipment have been pressuring for a separate audio show where they would not have to compete with video games, TV, CB radios, calculators and other such products. So about 80 exhibitors were segregated at the Pick-Congress hotel under the designation "Esoteric High-Fidelity". Another 70 had demonstration rooms at the afore-mentioned McCormick Inn, so it would seem that the CES organizers had listened to the audio critics.

By a strange coincidence, the Institute of High Fidelity (IHF) put on an Audio Show only three weeks before, at Atlanta in the Deep South. Several manufacturers patronised both events (about 200 were at Atlanta) but many found the two shows to be too close together so it is more than likely that next year's IHF affair will be held at a different time.

Space will not permit more than a brief description of a few of the new products seen at both shows. Indeed, many may have found their way to Australia by now, for inclusion in your own recent shows.

First a few words about TV: large-screen projection models are beginning to be more popular and there are now several models to choose from. GE introduced a rear-projection model using an acrylic fresnel lens with a 45 inch (measured diagonally) screen. A special two-gun 13-inch tube was developed and the system uses a three-element plastic lens and two mirrors. EHT supply is 32kV and among the features are remote control electronic tuning and

two loudspeakers. Price is in the region of \$2800.

Another model in the same price bracket is the new Sharp two-piece system which boasts a 72 inch screen. It uses three projection tubes and it has a built-in cross line pattern generator, an ultra-sonic remote control unit and electronic channel selector.

Two-piece models are made by Advent and Sony — the latter company now also marketing two single unit models.

The increased interest in large-screen TV has prompted a number of enterprising firms to market relatively inexpensive models using ordinary 19-inch sets with a lens and screen. Some have separate screens, while others use a rear projection system, but few offer a really bright picture.

The most interesting news in the tape world is the imminent introduction of metal, or metal film tapes which use iron particles instead of oxides. Efficiency can be as much as 10dB higher, with better signal to noise ratio, wider




Forerunner of what may turn out to be a whole new generation of recording tape, this Scotch brand "Metafine" uses particles of metallic iron, as distinct from iron or other oxides. It offers improved performance but requires the use of much higher bias and erase currents.

frequency response and less high frequency saturation.

Several manufacturers like BASF, Fuji and Scotch (3M) are concerned with the development of these new high-coercivity tapes and it is to be hoped that standards will soon be set.

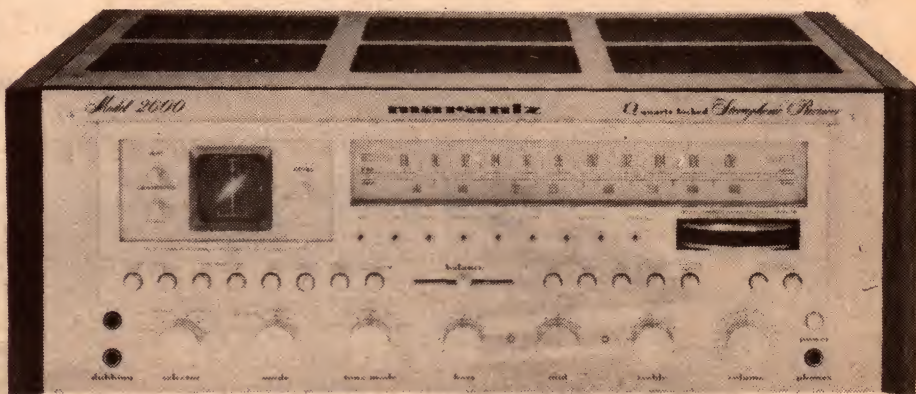Their main use initially will be in cassette decks but tape heads first have to be redesigned and bias current doubled. Equalization might have to be changed as well, although the 3M company has made metal tape which they call "Metafine" in a 70uS format. This was being demonstrated on a special Tandberg two-head cassette deck and a direct-disc record was being used as a comparison.



Most powerful receiver on display at the Chicago CES was this Marantz 2600, offering 400W per channel, from a direct coupled power amplifier. The FM tuner front end boasts dual-gate FETs with a 5-gang tuning, while the signal is displayed on a 3-inch oscilloscope, seen at the top left corner of the panel.

Introducing the new range of EMI Cassettes.



These new cassettes from EMI are designed to meet and exceed the exacting specifications in all performance areas, with special attention given to ensure smooth and trouble-free mechanical operation.


The new EMI Cassettes produce excellent results over the whole range of available equipment. All are available in 60, 90 and 120 minute playing time.

Whatever your equipment, whether they are recording speech or music, the EMI Cassette range will precisely match your needs.

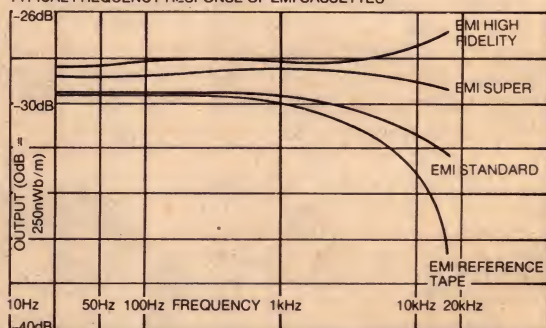1. Measured using the EMI recommended 2.5dB overbias at 6.3kHz, derived from the reference batch C521V (the value of bias internationally used by the majority of domestic recorder manufacturers).
Tape speed 4.76cm/s (1 7/8 in/s)
Track width 0.6 mm
Record head gap length 2µm
Replay head gap length 2µm
Replay amplifier characteristics: 120µsec and 3180µsec
(In accordance with IEC Publication 94 Edition 3, BS1568 Part 1 and DIN 45513)
2. The Frequency Response is obtained when the record amplifier characteristic has been adjusted to give a flat frequency response (25Hz – 15kHz) from the reference tape batch C521V of –30dB (Ref. 1*).

*Ref 1. Relative to an RMS Flux of 250mWb/m Tape Width (25mMx/mm) at a frequency of 315Hz (in accordance with IEC Publication 94 Part 2).

TYPICAL FREQUENCY RESPONSE OF EMI CASSETTES



**RANK
AUSTRALIA**
PROFESSIONAL SERVICES GROUP

12 Barcoo Street, East Roseville, Sydney 2069. Telephone: 406 5666
60 Rosebank Avenue, Clayton South 3169. Telephone: 543 4122
50-52 Vulture Street, West End, Brisbane 4101. Telephone: 44 2851
101-105 Mooring Avenue, Camden Park 5038. Telephone: 294 6555
430 Newcastle Street, Perth 6000. Telephone: 328 3933
120 Parry Street, Newcastle 2309. Telephone: 26 2466

Nakamichi were also demonstrating metal tapes and they were using a modified Model 1000 studio cassette machine; the results were being compared with a tape played on a Revox open-reel recorder.

In addition to showing the capabilities of the new tapes, the Nakamichi demonstration was concerned with noise reduction systems. A 3-position on the deck switched in a Dolby or Telcon (Telefunken) system which gives 20dB noise reduction against Dolby's 10dB. Who knows? This could start another trend!

Most of us have assumed that the Philips cassette license precluded the manufacture of decks with 3.75ips speeds. Either we were misinformed or the situation has changed because B.I.C.-Avenet introduced three decks with both 1.87 and 3.75ips speeds. The top model has a monitor head and the frequency response at the higher speed is claimed to be 22kHz, within +3dB. Playing time is, of course, cut in half but, if the idea becomes popular, perhaps tape manufacturers will take another look at the C.120 cassette.

Several new tuners and receivers were to be seen-in all price ranges and a number of the more expensive models used frequency synthesis. Sherwood's Micro CPU 100 is one of the few tuners that can display the station's call letters in addition to the frequency read-out and it has automatic scanning with preset station selection as well.

The new Dynaco tuner has no fewer than six tuned stages in the "front end" and, as soon as the hand is released from the tuning knob, the read-out frequency display becomes a clock!



Nakamichi's new Model 730 receiver is a most sophisticated unit with some unusual features. For example, the "front end" uses a motor-driven 4-gang capacitor which is controlled by touch sensors and there is a choice of four preset stations. Mode and functions are also controlled by touch sensors and these include the motor-driven volume control. Because of the use of logic circuitry, the design is well suited for a remote control and a pulse operated system with infra-red is used.

Prize for the receiver with the highest power goes (at present) to the Marantz 2600 which can put out 400 watts per channel! Like its smaller(!) 270 watt brother, the 2500, this super-receiver

Modulated plasma tweeter

The Hill Plasmatronic loudspeaker system which uses a modulated plasma "corona" to generate and radiate frequencies above about 700Hz. There is no cone, no mass, no beaming but the leaflet warns: "To achieve uncompromising quality, it is necessary to bleed a small amount of helium into the plasma. About every 300 listening hours a helium supplier will need to come to your home and exchange the tanks".

NEW CONCEPTS FROM THRESHOLD

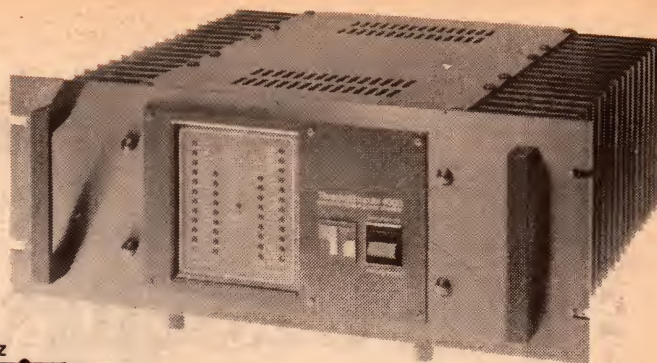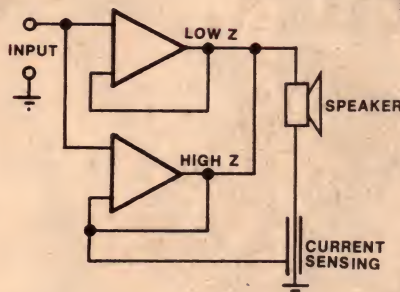

Pictured above is a new high-power amplifier from "Threshold" (see text) which employs class A but uses bias tracking to conserve idling current. In another design (see diagram) they use a conventional high power low impedance amplifier to drive the speaker and a separate precision amplifier to sense and cancel any distortion.

uses a small fan with tunnel heat sinks which certainly keeps the weight down. Even so, you need a strong shelf and a well-lined pocket book as the price is well over \$1500!

Turning now to amplifiers, a California based company called Threshold were demonstrating an all-cascode Class A model which has a one-kilowatt power transformer. A unique biasing circuit tracks the bias under all conditions so that constant Class A operation is maintained. It is claimed that this innovation keeps the idling current down by 75 per cent.

But the most interesting amplifier here was a "feed-forward" model

which used a separate amplifier to null the distortion. The amplifier was the Stasis 1 and Threshold say that "its near perfect operating parameters are achieved through the fact that the only work required of it (the error-nulling stasis amp) is to null out the small inaccuracies appearing in the output of a powerful active current source." This technique is not new, but this design is superior to others because the error nulling amplifier section is connected directly to the load. Power output is rated at 300 watts per channel at a distortion of less than 0.002 per cent.

Among the new preamps was the Crown DL-2 which is called a stereo Controller. It really consists of three units: a small head amplifier, a control unit and a power supply. The head amplifier is designed to mount as close to the phono cartridge as possible and it is fitted with RF suppressors. The control unit has eight dual switched inputs, digital touch-buttons for gain and balance, and high and low filters, with each having 4 selectable positions. There is a separate headphone amplifier, precision loudness compensation, two digital displays and much more. Switching is accomplished by reed relays and the level is adjusted by varying the actual gain. Provision is made for full remote control and computer connections are at the rear. Truly the Rolls-Royce of preamps!

Well, as you might expect, there were all kinds of loudspeakers to be seen and heard at both shows, ranging from tiny shoebox midgets to huge systems like the Infinity Quantum Reference Standard which stands 76 inches high by 48 wide. It uses a 15-inch twin-voice coil woofer with two vertical arrays of flat induction type midrange and treble units. Another seven treble units (called EMITS, or Electro-Magnetic Induction Transducers) are mounted at the rear and two separate stereo amplifiers are required for each





Music gets you up. Our new AD cassette will take you higher.

Music should be white hot, clear through to its soul, like live music. If your music at home doesn't cook like the real thing, check your cassette — the high frequency sounds, where lead guitars, synthesizers and the like really live, and probably getting lost or distorted. ■ Our new AD is designed to deliver those critical highs. The lows, mid-range and highs open up, your music breathes all the way through. ■ AD performs its magic in any cassette recorder, at home, in the car or portable, with or without a 'Normal' bias/EQ setting. AD's ultra-reliable super precision cassette comes in 45, 60, 90 and 120 minute lengths.



TDK AD

The machine for
your machine.

Convoy International Pty. Ltd.
4 Dowling Street, Woolloomooloo, N.S.W. 2011. Tel. (02) 358 2088

pair. Price is about \$6000.

ESS were demonstrating their Transar system — the one with the five diaphragm bass driver, and a French company, Acoustique 3A, were attracting a lot of attention with their coffee table Triphonic systems. The coffee table contains two 12-inch bass drivers, a control unit, amplifiers, crossover, a turntable and a tuner. Frequencies above 100Hz are red to a pair of satellite speakers which can be hung on the wall or placed on a bookshelf. Some tables have space for a telephone and all are fitted with an electret microphone for checking the overall frequency response.

Last year, Koss introduced three systems based on the work in Australia by Thiele and Small, two being conventional reflex types while the third uses a passive radiator with a removable brass weight so the response could have a "bump" at 60Hz if so desired. This year, the range was augmented by a bookshelf model using an 8-inch woofer with an 8-inch passive radiator. At 3kHz, signals are taken to a 1-inch dome which has a short horn.


Quite a number of "linear phase" systems were to be seen and the B&W company, one of the first to take up this concept, were giving a remarkably effective "live versus recorded" demonstration with the aid of a musician who played a saxophone and clarinet. Although I was sitting near the front of the room, I found it quite difficult to tell when the sound was coming from the loudspeakers — a tribute to the synchronization of the performer.

Bozak, Martin and Dynaco all introduced "linear phase" systems and people are becoming accustomed to the "staircase" appearance.

One of the best Japanese loudspeaker makers is Mitsubishi, whose studio monitors are used by the NHK broadcasting authorities. They were showing some new designs including a studio model that weighed over 300lbs! Cones or diaphragms are made of perforated aluminium covered with a semi-viscous plastic to get rigidity with good damping. Mitsubishi call this material a "honeycomb" and it is used in midrange units as well as woofers.

One of the most interesting loudspeakers was the Barcus-Berry glass plate tweeter. It consists of a sheet of glass measuring about five by seven inches mounted at the front of a small box. A driving unit — probably a piezo-electric device — is coupled to the rear and a 2kHz crossover is in the said box. Nothing exceptional about that but the curious thing is this: radiation is not directional but is almost omnidirectional! White noise disclosed a

A different approach to hifi by AIWA

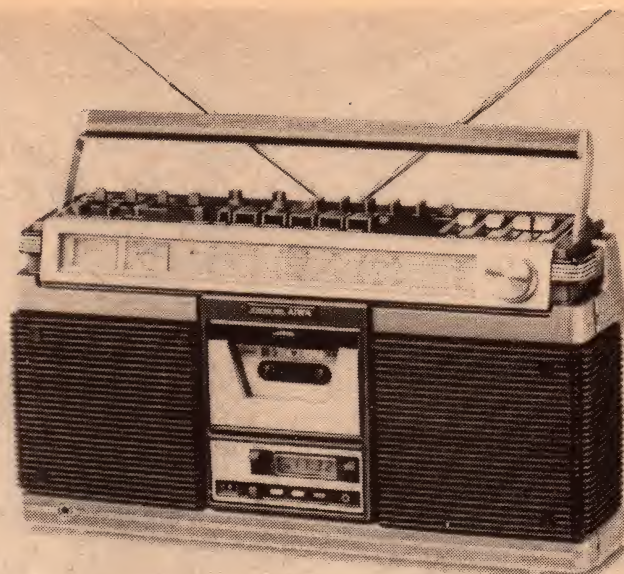

While being more active than ever in the top end of the hifi market, AIWA are also catering for the buyer who is looking for equipment which combines good performance with greater portability and less bulk.

At the heart of the new equipment is a line of portable radio cassette recorders, such as the TPR-980 (illustrated) which is a versatile self-contained unit, yet capable of being interfaced with external hifi components.

As a self-contained unit, it can operate from internal batteries, car battery and AC power mains. It provides for AM, FM and short-wave coverage, while the stereo cassette recorder has specifications which bear comparison with domestic decks.

However, the TPR-980, like other units in the range, has provision for a stereo pair of microphones, headphones, extension bass reflex loudspeakers, and a magnetic phono preamplifier which allows it to be used with a quality direct-drive turntable, such as the AIWA AP-2200. When connected to the latter, the cassette mechanism can be set up to start and stop in synchronism with the turntable.

For greater acoustic output, a compact, a compact power amplifier can be connected between the TPR-980 and the loudspeakers, while a prefabricated equipment rack is also available.

For further details: AIWA Australia Pty Ltd, 14 Gertrude St, Arncliffe 2205. Tel. (02) 597-2388.

certain amount of ringing but I am sure this can be damped out.

An even more unusual system was called the Hill Plasmatronic which used a modulated plasma "corona" for fre-



New heavy duty cartridge

A new Goldring phono cartridge has been announced recently, expressly intended for use by radio station (and other) disc jockeys. Designated as type G800-DJ, it has a nude diamond stylus mounted in a steel shank, reinforced to withstand heavy handling and/or backtracking. It is ground to a spherical tip, 0.0006in dia, and operates with a playing weight of 1.5 to 3.5g. A bold arrowhead simplifies placement in a specific groove. For details: Soundring Distributors, Suite 1, 514 Miller St, Cammeray 2062. Tel. (02) 92-1990.

quencies above 700Hz. I quote from the leaflet, "the incandescent, lavender plasma of the Hill speaker system radiates sound in a spherical pattern with no phase problems". And there is no cone break-up to contend with, no mass, no voice coil and no "beaming". But this dream of perfection has a snag and I quote from the leaflet again, "To achieve uncompromising quality, it is necessary to bleed a small amount of helium into the plasma. About every 300 listening hours, a helium supplier will need to come to your home and exchange the tanks".

IN BRIEF

Sharp had a turntable which used a microprocessor for programming. A laser scanner counts the grooves and initiates the operation ... Revox introduced a straight-line tracking arm with turntable ... DBX were demonstrating the "Boom-Box" which synthesizes low frequency subharmonics from signals in the 80 to 150Hz range ... Empire introduced a new record cleaner called the Audio Groome. A thin plastic solution is applied to the record; when it is dry, the whole film is removed, taking the

Wherever there is Entertainment
you will see a part of

Cash-More Sound




SOUND SYSTEMS &
DISCOTHEQUE LIGHTING



ROPELIGHTS
32ft, 4 COLOURS



12", 18", 20", 24"
MIRROR BALLS

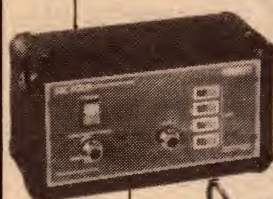


SAC 4
4 x 1000 WATT
SOUND TO LIGHT
CHASER



240V
FUZZ
LITES
RED, YELLOW,
BLUE, GREEN.

SERIES III STEREO

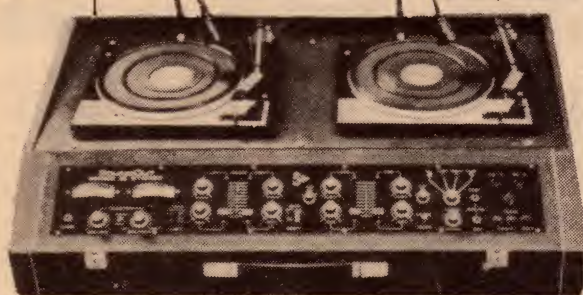

Fabulous Soundout Discotheques — One of the most reliable discos now in use by DJs and Clubs all over Australia and Tasmania. Now with 200 watt inbuilt power amps, stereo or mono, belt drive, T/T, CWE fac., Slave out, tape in, tape out, mic and rexine covered, lock down lid, weight app. 40kg. Fully guaranteed 12 months.



- ☆ PROJECTORS & ACCESSORIES & SPARE PARTS.
- ☆ RAINBOW STROBE CONTROLLERS.
- ☆ STROBES
- ☆ COLOURED LAMPS E.S. 8 COLOURERS.
- ☆ SMOKE BOMBS
- ☆ DRY ICE FOG MACHINES.
- ☆ SPEAKER CABS.
- ☆ MICS ☆ STANDS ☆ N.A.B. CARTRIDGE MACHINES, etc.

**FOR YOUR ENTERTAINMENT NEEDS CONTACT
CASH-MORE SOUND OR VISIT THE
SHOWROOMS AT 149-151 GEORGES RIVER RD,
CROYDON PARK, SYDNEY. TEL. (02) 798-6782,
(02)798-5647.**

FREE BROCHURES — PRICE LIST ON REQUEST

**SALES — SERVICE —
INSTALLATION — HIRE**

HIFI NEWS — Continued

dirt with it.

A hand-held breathalyzer was shown on one stand: it is fitted with 3 LEDs, green, amber and red. Nearby, a salesman was demonstrating battery testers in the form of a figure of W. C. Fields with a red nose! These two companies really ought to get together . . .

AUDAX LOUDSPEAKERS: Bill Webb Stereo of Melbourne have been appointed distributors in Australia of Audax audio products. Initially only the Audax drivers are being imported but future plans call for the marketing of speaker kits, microphones and headphones. Audax speakers are made in France and have become famous over the last couple of years through their use in many of the better quality English speaker systems. Spondor, Rogers, Tangent and Harbeth all employ Audax drivers, and they have also become popular in the UK with do-it-yourself enthusiasts.

Initially the distributors will concentrate on marketing the top quality HD range of drivers. In this range alone there are over 70 units, the largest being a 355mm 100 watt bass driver. At the other end of the scale there are eight different 25mm soft dome tweeters.

Even though speaker manufacturers will account for the bulk of Audax sales, Bill Webb will be happy to discuss the range with interested audio enthusiasts.

For further information on Audax Speakers contact Bill Webb Stereo, 32 Wilson Street, Oakleigh, Vic. Phone: (03) 579 5196.

ORTOFON MANUFACTURING A/S, best known for their moving coil phono cartridges, advise that their production has doubled during the first half of 1978. They are looking for further increases as the result of three new cartridge releases.

One of the three is a new moving coil model, MC-10, intended to meet the rising demand for a moving coil cartridge at a "quality magnetic" price. The MC-10 has an elliptical stylus with an effective tip mass of 0.5mg and a moderate order of compliance (15um/mN) which will allow



Toshiba's new Series 330 audio package may well provide a ready made answer for those confused by the variety of equipment being offered in the hifi shops. The system comprises a fully automatic belt-driven turntable, an AM/FM stereo tuner, a 40W per channel power amplifier, a control unit with dubbing facilities for an extra tape deck and microphone, and a front loading Dolby cassette deck. All these units are mounted in a vertical or horizontal rack, as preferred, and accompanied by a pair of 2-way reflex loudspeakers. For further information: Toshiba (Australia) Pty Ltd, 16 Mars Rd, Lane Cove 2066.

it to mate with most arms. Because of its low impedance and low output, the MC-10 would need to be used, either with a pre-preamplifier or with Ortofon's STM-72 step-up transformer.

The other two cartridges are more conventional magnetic designs using the VMS (variable magnetic shunt) principle. The FF15 X MkII is supplied with a spherical diamond and has a relatively low compliance (0.8um/mN), increased tip mass (0.8mg) and playing weight (5 grams), being intended for use in equipment with high mass tone arms. Nominal output is 1.3mV.

The FF15XE MkII would also appear to be designed for situations requiring a relatively rugged cartridge but it offers higher compliance and an elliptical stylus.

SENNHEISER have recently released their Universal Level Meter model UPM 550, for the measurement of AC voltages from 10Hz to 1MHz. It



provides for 15 overlapping ranges to 300V RMS, the lowest range (0 to 30 microvolts) being adequate to measure the tiny voltages produced by tape heads, microphones, etc.

The utility of the instrument is increased by an in-built CCIR "earcurve" filter, a 1000Hz filter, A-filter and noiseweighting to DIN 45 500. Provision is available to plug in other external filters, as required.

The meter is overload protected and the internal amplifier has "headroom" for peaks up to 10 times the full-scale RMS of the range selected. It can be switched for peak reading mode.

For further information: R. H. Cunningham Pty Ltd, 493-499 Victoria St, West Melbourne 3003, or in other capitals.


NATIONAL PANASONIC (AUSTRALIA) PTY LTD is the name of a new company that has been formed to take over the marketing in Australia of consumer products under the brands of National, Technics and Panasonic. Their postal address for inquiries, orders, accounts, etc, is PO Box 278, Kensington, NSW 2033.

Formation of the new company terminates the long-standing arrangement by which National and Technics products have been marketed in this country by the Haco/Hagemeyer group.

Hagemeyer (Australasia) B.V. have re-located their Sydney head office at Unit C, Centre Court Estate, 25-27 Paul

Soldering printed circuits?

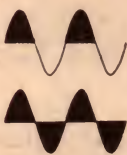The Duotemp soldering tool will idle all day on half-wave AC without overheating.



A touch of the button converts it to full wave, instantly doubling the thermal capacity

- Correct temperature for printed circuits.
- Fast heat-up and heat recovery.
- Power boost for long sequences or heavy joints.

MODEL D30	3mm tip
MODEL D50	5mm tip
MODEL D65	6.5mm tip



DUOTEMP

A new standard in soldering tools — by Adcola.

The Duotemp protects circuits and components at a cost far lower than soldering tools with automatic temperature control.

For electronic feedback temperature control please call for brochure for 'THERMATIC' line voltage, or 'ECT' super sensitive and powerful low voltage soldering systems.

FROM YOUR ELECTRONIC PARTS SUPPLIER

or enquire from

ADCOLA PRODUCTS

Melbourne 848 3777

Brisbane 44 0131

Hobart 34 2233

A781

Sydney 709 5293

Adelaide 42 6655

Launceston 31 2511

Perth 381 5500

St, North Ryde 2113. Telephone (02) 887 1555. New addresses also apply for Melbourne, Adelaide, Perth and Brisbane.

Intag Marketing Corporation Pty Ltd has acquired the entire stock of the Ferris audio division of Kemtron Ltd, as an initial step in a major Intag expansion programme. Mr John J. Manneken, chairman and managing director of Melbourne-based Intag, said the purchase included the Ferris business name and trademark, as well as its service department.

"We will market a range of high-quality new products under the Ferris name," Mr Manneken said. These will include pushbutton radios, exterior cassettes and speaker systems.

Founded in 1972, Intag is an importer and wholesaler of a wide range of

audio electronic products. The company has an office in Sydney, and distributor representatives in Perth, Brisbane, Canberra, Adelaide and Tasmania. Intag is headquartered at 42 Grantham Street, West Brunswick 3055. Telephone: 387 3844.

3M AUSTRALIA PTY LTD has announced the appointment of Mr Rick Downes as Sales Manager, Recording Materials Group, in NSW; also the appointment of Mr Adrian Williams as Sales Manager Recording Materials Group in Victoria.

3M's Recording Materials Group incorporates the Company's Magnetic Audio-Video Division and its Data Recording products Division.

Both men have a broad expertise in these products and are anxious to assist clients.

Sansui G-5000 stereo receiver

The Sansui G-5000 stereo receiver is one of a new series recently released by Sansui Electric Co. Ltd of Japan. It has a rated power output of 45 watts per channel, comprehensive output protection and power amplifier response down to DC.

Compared with former Sansui models, the G-5000 and the other stereo receivers in the Sansui G-line have far less subdued styling. The unit has a lot more brightwork and more colour on the dial scale. The overall styling combines to make the unit seem larger than it really is.

Our black and white photos do not adequately convey this impression. The front panel is bright brushed aluminium, while the dial background is gold. The AM calibrations are blue and those for FM, white. Other colour accents are the beacon and power indicators and the green chamfered edge of the dial glass.

An unusual feature of the styling is the "random knurling" of the control knobs. While perhaps a little less elegant-looking, these are comfortable to grip and probably have less affinity for dirt than straight-knurled knobs.

Overall dimensions of the G-5000 are 464 x 181 x 408mm (W x H x D) including knobs, rubber feet and rear projections. Extra clearance is required at the rear to allow the hinged ferrite rod antenna to be oriented for best

reception. Mass of the unit is 14kg.

The control line-up of the G-5000 is fairly standard. Loudspeaker switching for two pairs of loudspeakers is provided with two push-buttons. Further along the control panel, another pair of buttons provides for defeat of the tone control settings and a sub-sonic filter which has its turnover (-3dB point) at 16Hz.

In the centre of the control panel another pair of buttons provide -20dB muting of the audio program and less usefully, a Loudness characteristic for the Volume control. Then on the right-hand side of the panel are four buttons for FM interstation muting, Mode selector (stereo or mono) and Tape Monitor (for two decks).

Both the Bass and Treble controls have detents which provide 2dB steps in boost or cut at 50Hz and 10kHz. That is useful, because it allows the user to easily apply a fixed amount of boost or cut. But we cannot see the point of the 40 detents on the volume control. It does not have logarithmic calibrations, nor does it have better matching between tracks than ordinary dual


ganged potentiometers used in most other amplifiers and receivers.

On the extreme right-hand of the control panel is a small knob and 6.5m socket which allow connection and mixing of a microphone. It allows you to sing along with the selected program (perish the thought) but cannot be used for recording.

The rear panel of the G-5000 is quite crowded, not because it offers more than the usual number of facilities but because the output transistor heatsinks occupy a major portion of the area.

Over the last few years output transistors have tended to be hidden inside the chassis of receiver and amplifiers. This has been due to a number of factors, one of which is the need to avoid the possible shock hazard of output transistors running at high voltages. Sansui have taken a different approach to this problem in that the output transistors are mounted on a flat extrusion just inside the rear panel. Mounted over this is a large finned casting which makes thermal contact to the aforementioned extrusion via heatsink compound. Not only does this provide a well ventilated heatsink system, but it also gives good access to the output transistors should they have to be replaced.

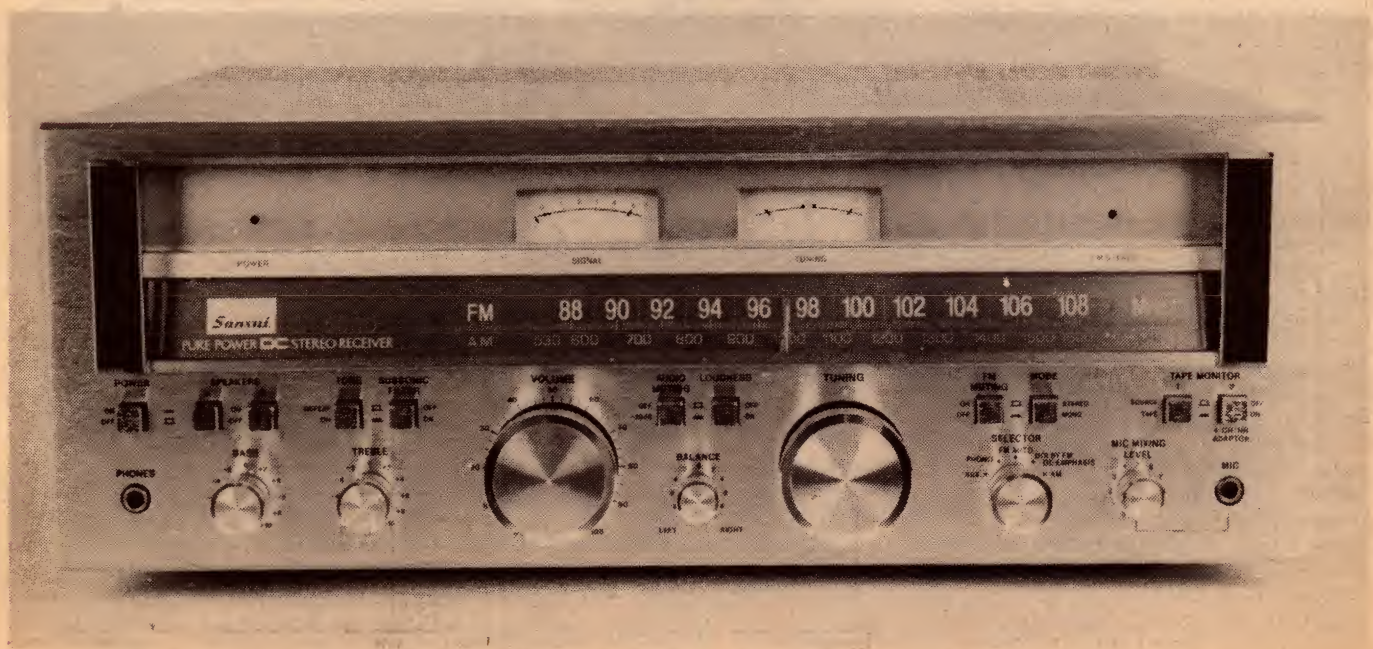Removing the synthetic veneered timber cover reveals a closely packed interior dominated by the large transformer and filter capacitors. At



one end of the chassis is a large PCB for the AM and FM tuners, while an equally large PCB in the centre of the chassis accommodates the complex power supply and output protection circuitry. Almost insignificant by comparison is the vertically mounted stereo power amplifier PCB.

The RIAA preamplifier is sandwiched between the tuner PCB and the bottom panel of the chassis. The rest of the circuitry is scattered along behind the front panel amongst seven small PCB's. Accessibility is not a strong point. Luckily, these behemoths are generally reliable beasts.

A three-core flex with moulded three-pin plug is fitted to the unit, so it conforms to local standards in this regard. However it has two-pin mains sockets for accessories. While some enthusiasts appreciate this feature, other manufacturers have removed them to conform to local standards.

One point we must congratulate Sansui on is the fact they have included a full circuit diagram along with the comprehensive owner's manual.

Like a number of other recently released amplifier and receivers, the Sansui G-5000 has power amplifiers with response down to DC. We have yet to be convinced of the merit of this idea and are of the opinion that it has little or no effect on the accuracy of reproduction. It does require a more complex amplifier and coarse and fine adjustments for offset voltage.


Very comprehensive protection circuitry is included in the G-5000. It monitors the output stages and uses a relay to disconnect the loudspeakers in the event of large dc offset voltage, short-circuits, excessive loading or over-drive. We could not faze it with any likely abuse.

In the G-5000 the AM tuner consists of one integrated circuit followed by a class-B detector. It is the simplest of superhets. By comparison the FM tuner uses 12 transistors and two integrated circuits. The front-end employs a dual-gate MOSFET and the IF stages are discrete transistors. The detector and multiplex decoder functions are provided by IC's.



Performance testing reveals more of the character of the Sansui G-5000. The three graphs summarise the key points. Power output is rated at 45 watts per channel into 8-ohm loads, with both channels driven, for a rated distortion of 0.03 per cent or less over the bandwidth 20Hz to 20kHz.

At the lower frequencies the G-5000 had no problem meeting the specification. We measured 54 watts per channel with both driven into 8-ohm loads, at onset of clipping. With one channel driven, the figure increased to just over 60 watts. With 4-ohm loads the power rises to 80 watts per channel with both driven or 96 watts into one channel.

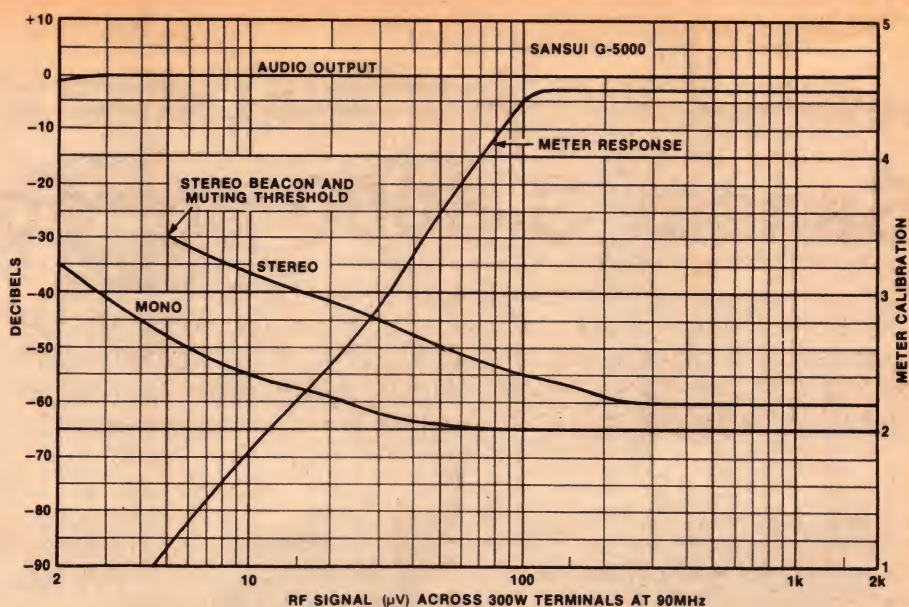With 16-ohm loads, the power output is 33 watts per channel with both



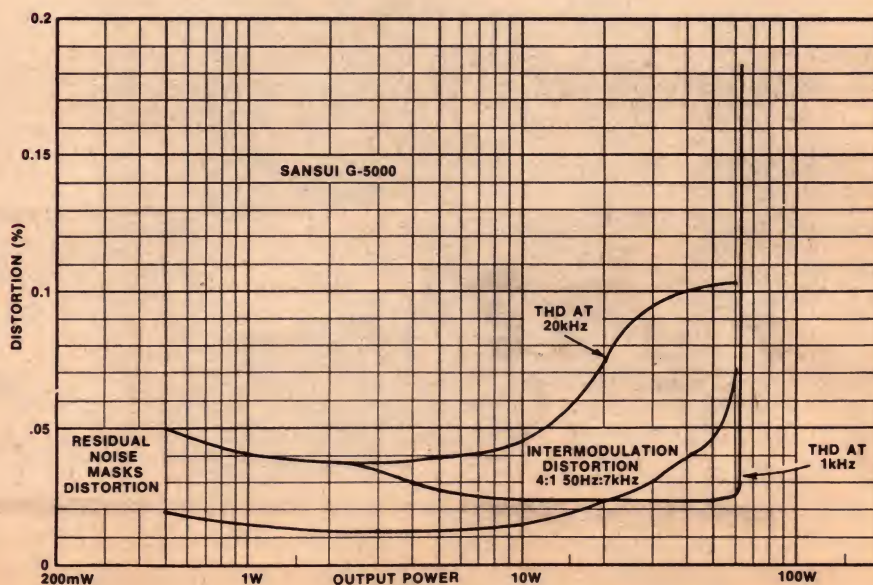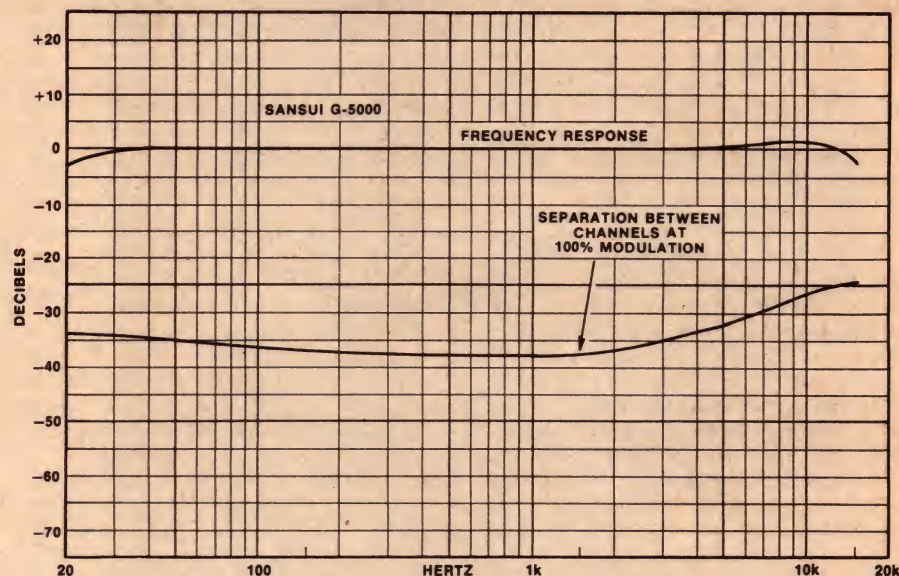This graph shows the Quieting characteristics and meter response of the Sansui G-5000.



"Marantz let me build the speakers I've always wanted to build"

Ed May, Vice President Speaker Engineering for Marantz

Over the past twenty years Ed May has firmly established himself as one of the industry's top experts on speaker systems. Formerly the manager of speaker engineering for JBL, Mr. May has personally been responsible for many of the advances in speaker technology.

As the new director of Marantz Speaker Development we asked him to comment on the new Marantz Speaker line.

"Since joining Marantz I've never been turned down on anything I've wanted to do to improve quality. When it comes to quality, cost is no object."

"Our new Marantz speaker line is one of the top lines in the industry. The reproduction capability of our speakers can equal or out perform speakers that cost two to three times the price."

"We don't follow fads. We stay away from frivolous things that only increase the price tag without increasing performance."

"Our toughest critics are ourselves. Many of the things we measure and test for are seldom encountered in the field."

"My philosophy is to build the speaker so it reproduces all frequencies as smooth, as flat as possible in all angles of radiation. No matter where you sit you hear exactly the same sound."

"I'm very proud of our new Marantz speaker line. It's what I've always wanted to build. My hat is off to Marantz for letting me do it."

marantz®
We sound better.

© 1977 Marantz Co., Inc., 20525 Nordhoff St., Chatsworth, CA 91311.

For Brochures contact — **Marantz Company, PO Box 604, Brookvale, NSW 2100**

Marantz Company is a trading division of Superscope (Australasia) Pty Ltd

SANSUI G-5000 RECEIVER

driven or 36 watts with one channel.

At 20kHz the harmonic distortion was above the rated figure (0.03 per cent), but at powers of 40 watts and below it was 0.1 per cent or less, which is still very good. And the intermodulation distortion measured with 50Hz:7kHz signal in 4:1 ratio is on a par with the best stereo amplifiers.

Distortion is slightly higher for 4-ohm loads (or parallel-connected 8-ohm loadspeakers) and slightly lower for 16-ohm loads. Frequency response at one watt into 8 ohms yielded -1dB points at 10Hz and 40kHz when measured via the auxiliary inputs.

In the interest of providing a better basis for comparisons, we have changed our method of measuring signal-to-noise ratio and separation between channels. From now on (unless otherwise qualified) amplifiers and receivers will have their S/N ratio and separation between channels measured with respect to 10 watts into 8-ohm loads, with undriven inputs loaded with 4.7k and with volume control set for maximum sensitivity. Sensitivity for 10 watts into 8-ohm loads will be stated.

Using the above method, signal-to-noise ratio for the G-5000 is 74dB unweighted for the auxiliary and tape inputs. Separation between channels was 62dB at 10kHz, 72dB at 1kHz and below the residual noise at 100Hz (ie, below 74dB). Sensitivity for the 10W reference power was 70 millivolts RMS.

Phono sensitivity for 10 watts was 1mV at 1kHz. Signal-to-noise ratio with respect to 10 watts and 10mV input at 1kHz is 70dB unweighted with a typical cartridge (Shure M55E) connected. To obtain this latter figure the turntable must be 60cm, or more, away from the receiver, to avoid the substantial hum field of the power transformer.

Phono input overload is 250mV at 1kHz which is far more than adequate. RIAA equalisation is within $+0.2\text{dB}$ from 30Hz to 15kHz.

With power amplifiers having an extended bass response, it is important to have some filter facility for removing unwanted rumble or warp effects when playing discs. Ideally, the way to do this would be to have a steep cut high pass filter (removes low frequencies) with switchable turnover frequencies at say, 20Hz and 60Hz.

While we therefore welcome the inclusion of a subsonic filter in the Sansui G-5000, it really does not have enough attenuation at warp frequencies (only -5dB at 10Hz) to have a worthwhile effect.

Stability testing with capacitances shunting the load tripped the overload protection when performed at high powers. This indicates the protection does a thorough job. No other effects were noted.

Turning now to the tuner section, it


can be seen that the Quieting characteristics are similar to many other fine tuners. Stereo and mono frequency response, with the internal de-emphasis switch set to 50 microseconds, was identical — $+1\text{dB}$ from 30Hz to 14kHz, -3dB at 15kHz. This is very good. Harmonic distortion measured at 100 per cent modulation (75kHz deviation) was 0.2 per cent at 100Hz, 0.14 per cent at 1kHz and 0.3 per cent at 6kHz in mono mode.

In stereo, the respective figures were 0.3 per cent, 0.2 per cent and 0.35 per

cents — mains-radiated interference generated by switch-off of refrigerators, fluorescent lights and so on. This should not be so.

The second was that Sansui have produced an AM tuner which sounds every bit as mellow as a 1955 radiogram. Actually that might be an unfair comparison; quite a few radiograms had respectable wideband AM tuners.

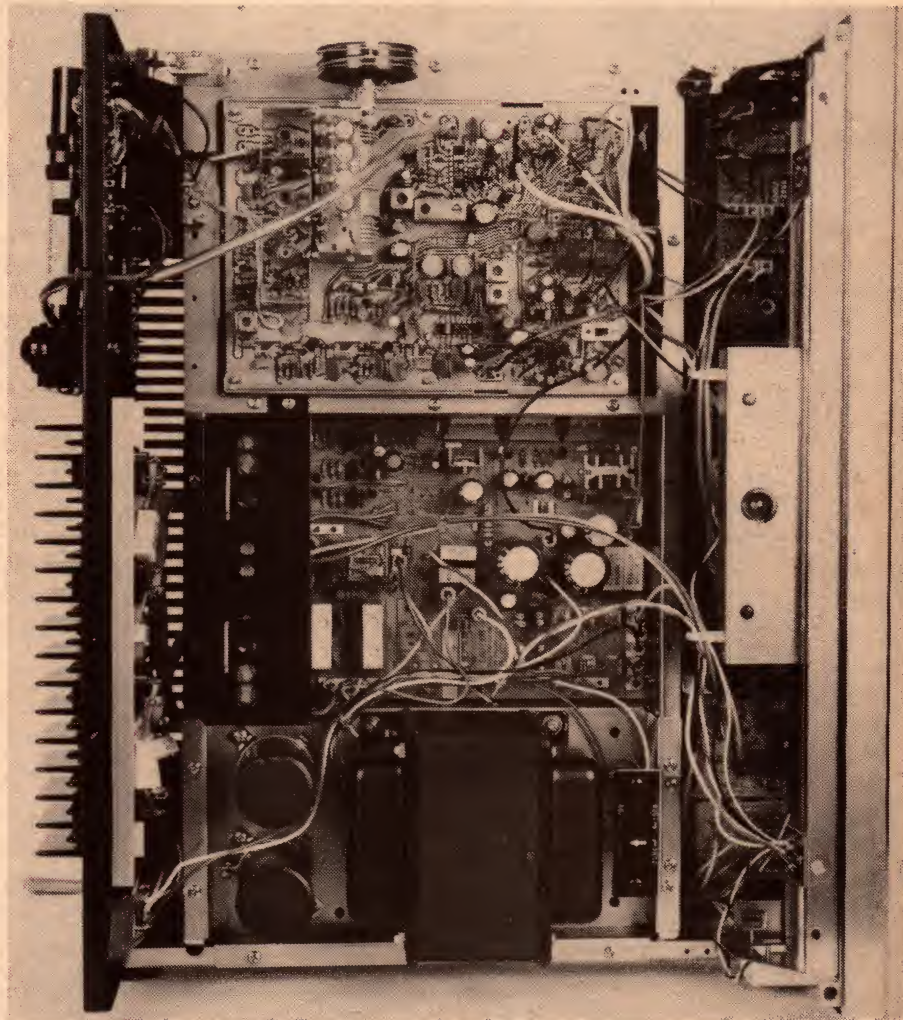While we do not have previous measurements on which to base a comparison, the Sansui did seem to have a particularly narrow AM bandwidth. Sansui claims that selectivity is -35dB at $\pm 10\text{kHz}$, so that gives some idea of the narrowness of the bandwidth.




cent. These figures are in close agreement with the specifications. The same can be said for the graph showing separation between channels.

A period of several weeks' use at home confirmed that the Sansui is a fine performer, with more than adequate power for most situations. It also has good control characteristics, particularly the FM tuning and muting. Several points of irritation did arise though.

The first was that when playing records the unit was unduly sensitive to

While we recognise that most modern receivers have only vestigial AM tuners, we believe the time has come to indicate that it is not good enough in medium and high-priced equipment.

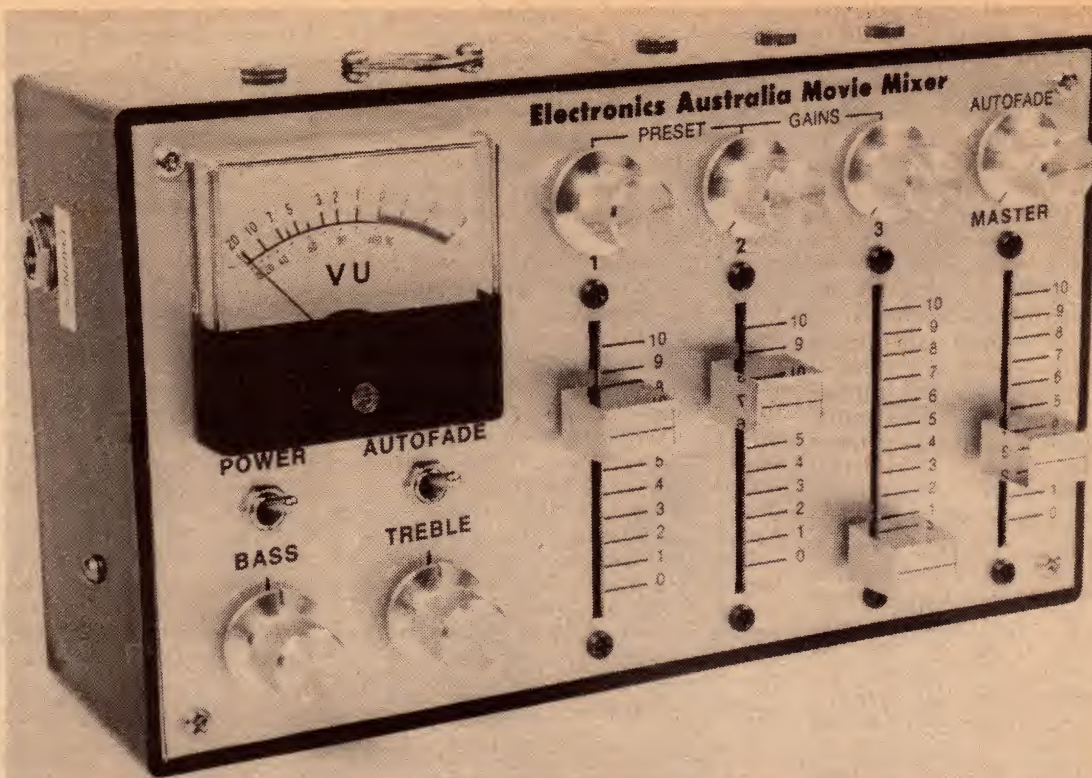Recommended retail price of the Sansui G5000 is \$599.00 including sales tax. Further information can be obtained from high fidelity retailers or from the Australian distributors for Sansui products, Vanfi (Australia) Pty Ltd, 162 Albert Road, South Melbourne, Victoria or 5 Northcliff Street, Milsons Point, NSW. (LDS).



A Mixer for Home Movies

Here is a very flexible three-input audio mixer design with features which should make it of particular interest to home movie and recording enthusiasts. Although very compact it offers bass and treble controls, a level meter, a headphone monitoring output and a handy auto-fading facility. And best of all, you should be able to build it for far less than commercial mixers offering fewer features!

There are now large numbers of home movie enthusiasts making their own sound movies. In fact, since Kodak introduced its Ektasound prestripped super-8mm sound camera film cartridges and direct sound cameras in late 1973, home sound movies have really boomed. You can now buy from a very wide range of sound cameras and projectors from a host of manufacturers, along with a variety of camera cartridges and an ever-increasing range of sound prints made from commercial movies and TV shows.

You can also buy animated-viewer editors with sound reader attachments, home striping units to add a magnetic stripe to your existing silent films, and small sound mixing units.

Why mixing units? Well, most of the currently available sound cameras are fairly limited in terms of input facilities. They generally have only a single microphone input and, because the cameras use automatic recording level circuitry, there isn't even a manual gain control. At most, there may be a two-

position sensitivity switch, to allow the gain to be lowered for shooting in noisy locations.

So if you want to be a little adventurous and use more than one microphone when you're shooting a scene, you really have to use a separate mixer.

For example, few amateurs can rely on having someone to move the microphone during shooting, to ensure optimum sound pickup (i.e., the job of

by JAMIESON ROWE

the professional's "boom operator"). But you can often achieve much the same result by using a number of fixed microphones, and fading from one to another to follow the action. To do this you obviously need a mixer.

It's much the same with projectors. Although most super-8 sound projectors can record as well as play, few are provided with more than quite rudimentary mixing facilities. If you

want to assemble a track with say narration, music and the odd sound effect, you really need an external mixer in order to do the job properly. Some projectors allow you to assemble such a track by means of over-record superimposition or track-jumping using the so-called "balance stripe", but both of these techniques have severe limitations.

A small self-contained mixer can thus be very handy, whether you're working with a sound camera, a projector or both. Unfortunately, the mixers that are made for this purpose by the camera and projector manufacturers seem to be very basic, yet surprisingly expensive. For example one of the few mixers currently available here in Australia is made by a big Japanese firm. It sells for more than \$90 in local camera stores yet offers no level meter, tone controls or other features.

In short, there's a need for a flexible mixer, offering the features most needed by super-8 sound enthusiasts, and at a reasonable price. The build-it-

yourself design presented here is intended to fill this need, and I believe it does so rather well. Yet you should be able to build it for around \$60, considerably less than the simple commercial mixer noted above.

The mixer has three input channels, each of which has an adjustable gain preamplifier so that it can be fed from either a microphone or a variety of other sources such as a record player or tape deck. The preamp gain controls allow each channel to be set up for optimum recording level individually.

For the actual mixing each input channel is also provided with a slider potentiometer, and there is a further "master" slider to set overall recording level. Sliders have been used for these controls in order to allow easy visual indication of channel proportions.

To allow convenient visual monitoring of recording level a small meter is provided, with the appropriate volume unit (VU) scale. Although the meter movement concerned is a low cost imported type and does not have the ballistic characteristic of a true VU meter, we have designed the drive circuit to give it a behaviour which is very similar.

The mixer also has provision for aural monitoring, by means of headphones. For the best results the headphones should be of the medium impedance variety, but the circuit will give satisfactory results with readily available low impedance stereo headphones.

To allow tonal balancing and adjustment, both bass and treble tone controls are provided. These are low distortion active tone controls of the type used in modern hi-fi amplifiers, not simple passive controls. However, the control action has been modified to make them better suited for film recording use. The two turnover frequencies have been brought closer together, to give them greater control within the available recording bandwidth. At the same time the maximum boost and cut range of each has been reduced, partly to compensate for the closer turnover frequencies and partly to allow easier fine adjustment.

A further important feature of the mixer is an "autofade" facility, which may be switched either in or out. When switched in, it uses the signal on input channel 1 to control the mixing levels of any signals on channels 2 and 3, over-riding the sliders for these channels. Thus when a signal appears on channel 1, any signals on the other two channels are rapidly and automatically faded down to a predetermined level; then when the signal on channel 1 ends, the other channels are smoothly and automatically faded back up to their original levels, at a suitable rate.

This facility can be very handy indeed if you have to assemble a sound track in which music and/or sound effects are frequently punctuated by narration or

dialogue. By having the microphone or other source of narration/dialogue on channel 1, and the music and effects on channels 2 and 3, the autofade will automatically fade down the music and effects each time the narration or dialogue has to be inserted.

This lets you use your hands to position the pickup on the record, or to control the tape deck, without any assistance.

The level to which the channel 2 and 3 signals are reduced by the autofade facility can be adjusted over a range, by means of a front-panel control.

The mixer is provided with two outputs, one a low-level output suitable for microphone inputs and the other a high level output suitable for "pickup" or "auxiliary" inputs. As most cameras are only provided with microphone inputs, the low-level output will normally have to be used for camera recording.


The same output can be used for feeding a projector, but if the projector is fitted with a high level input it is generally preferable to use this input fed from the mixer's high level output. The signal to noise level is likely to be better, due to the lower gain required

from the projector amplifier.

The frequency response of the mixer has been deliberately restricted, to give the best results for film recording work. With the tone controls in the "flat" position, for example, the bass response rolls off at about 75-80Hz (-3dB). This is in line with normal professional motion picture practice. It allows the use of higher average recording levels, without the risk of intermodulation from the high amplitude but relatively inaudible and unimportant signal components in the lower bass region. It also reduces the system sensitivity to hum pickup.

Similarly the treble response is deliberately arranged to roll off at about 8kHz (-3dB), again in the "controls flat" position. This is high enough to realise the full attainable recording bandwidth on super-8mm magnetic stripe but, by restricting the signal and noise bandwidth, it gives cleaner recordings by minimising noise modulation and intermodulation effects.

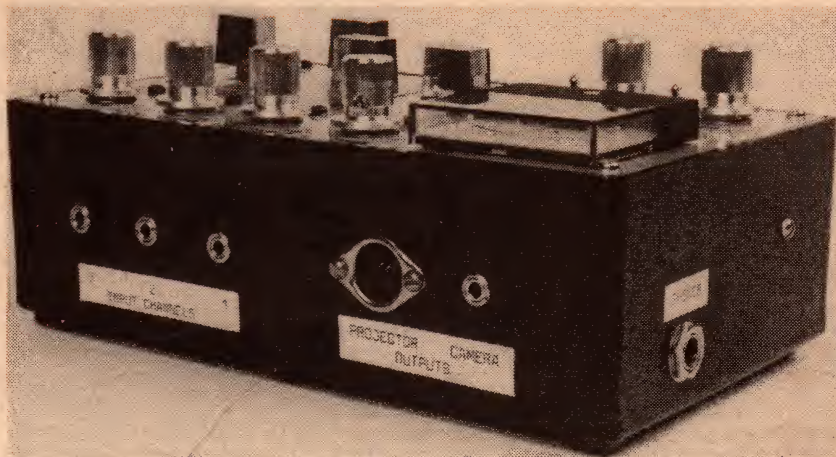Incidentally the response of the mixer and the range of its tone controls can easily be extended to normal "hi-fi" standards, if desired. This means that



HERE IS THE SPECIFICATION:

A 3-input mono mixer, suitable for both home movie sound recording and wide-range recording. Compact and battery operated for full portability. All three input channels are medium impedance with adjustable gain, and may be used with either microphones (dynamic or electret capacitor), or high level sources such as record players or tape decks. Features active bass and treble tone controls, a VU-type level meter, a headphone monitoring jack and a switchable "autofade" facility whereby channel 1 signal can automatically fade channels 2 and 3 to an adjustable low level.

Nominal output level: 0.774V from the high level output, 5mV from the low level output.

Maximum input sensitivity, all channels: 0.7mV or better for nominal output.

Minimum input sensitivity, all channels: approx 100mV for nominal output, with slider at maximum.

Output noise, all sliders at zero: 87dB below nominal output.

Output noise, all preamps at full gain and all sliders at maximum; 60dB below nominal output.

Frequency response, controls flat: 80Hz — 8kHz (-3dB), when used for movie sound recording. Extends to 40Hz — 30kHz (-3dB) when modified for wide-range recording.

Distortion: Less than 1% THD for nominal output at all gain settings and frequencies in the passband.

Tone control range: ± 7 dB at 200Hz, ± 6 dB at 5kHz (see curves) for movie work. May be extended for wide range.

Battery drain: Approx. 9mA at 18V (two 216-type batteries).

MIXER FOR HOME MOVIES

the mixer can easily be adapted for high quality tape recording work — although it may have only limited use in such applications because it is basically only a monophonic mixer. Details on how to extend the response are given later in this article.

As the current drain of the mixer is quite low (around 9mA), it has been designed to operate from batteries. This tends to avoid hum troubles, and also makes the unit compatible with battery-operated cameras.

As you can see from the circuit diagram, the mixer uses conventional discrete silicon transistors. This gives good noise performance and also makes the unit easy to build and low in cost. A total of fifteen transistors are used, all of them readily available low cost types.

The three input channel preamplifiers are all identical, using a well-tried two transistor circuit. The preset gain controls take the form of adjustable feedback resistors, which give improved distortion and signal to noise ratio when the gain is reduced to handle larger input signals.

Following the preamps are the channel slider pots. These are 50k in value, with a 45 mm slider travel (Soanar type VSU45-AH-50k). The pots used have a linear taper rather than "logarithmic", as the linear type are much more readily available. To give them the desirable logarithmic taper, they are shunted by 10k resistors between the slider and the top of the element. The same applies with the master slider.

The signals from the channels 2 and 3 pots are mixed together and fed to emitter follower Q10, while the signal from the channel 1 pot is fed separately to emitter follower Q7. This is done in

order that the channel 1 signal may be used to control the other signals via the autofade circuitry, involving transistors Q8 and Q9.

The autofade works as follows: Q9 is a junction FET, connected between the base of emitter follower Q10 and an AC shunting circuit formed by the 10uF capacitor and the 47k "autofade level" pot. The FET is normally kept cut off, by the reverse bias applied to its gate from the 470k pot at the lower end of the Q10 bias divider. In this cutoff condition Q9 does not affect the signals at the base of Q10.

Channel 1 signals from the emitter of Q7 are fed to transistor Q8, which is connected as a buffer amplifier with a gain of about 10. The amplified signals are then fed to a voltage-doubling rectifier, which produces a proportional DC voltage. When the autofade switch is closed, this DC voltage is fed into Q9's gate circuit, cancelling its standing cutoff bias and driving it into conduction. This causes Q9 to shunt the channel 2/3 signals to ground via the 10uF capacitor and 47k pot, reducing their level accordingly.

If the 47k "autofade level" pot is set to minimum resistance, the channel 2/3 signals are reduced by about 40dB. If it is set to maximum resistance, the reduction is only about 6dB. By varying the control you can set the autofade level anywhere between these limits.

The attack time of the autofade circuit is quite short, lowering the channel 2/3 signals in level within a few milliseconds of an effective signal appearing on channel 1. The decay time is rather longer, taking about 600 milliseconds for the channel 2/3 signals to return to their original levels after the channel 1 signal ceases. This gives a smooth audible fade-up, and also

prevents the autofade circuit from fading-up between individual words.

The outputs from emitter followers Q7 and Q10 are mixed together to form the final composite signal, which is then fed to the master level control slider. Across this control is a .0015uF shunt capacitor, used to limit the mixer's high frequency response as explained earlier.


Following the master level control the signals pass to an amplifier stage using transistors Q11 and Q12. This uses the same basic configuration as the input preamps, but the gain is fixed at about 20 times, compensating for mixing losses and bringing the signals up to their final level.

The signals then pass to the final sections of the circuit, comprising the tone controls, output stage and metering stage. The tone controls are of the Bax-andall feedback type, connected around the output stage in the modified configuration described by P. M. Quilter in the April 1971 issue of *Wireless World*.

Here the capacitor shunting the bass pot has been reduced in value to give a higher turnover frequency, while the end resistors have been increased in value to limit the control range. Similarly the capacitors at each end of the treble pot have been increased in value to lower the turnover frequency, while the end resistors have again been increased to limit the control range.

The output stage uses transistors Q13-14, with Q13 connected as a fairly conventional common-emitter stage directly coupled to Q14 as an emitter-follower. However the load of Q13 is split, with the output signal from Q14 fed back to the split via a 10uF capacitor. This "bootstraps" the lower load resistor, giving it an effective AC value many times its nominal value of 10k, and hence increasing the voltage gain of Q13 quite significantly.

DC base bias for Q13 is derived from

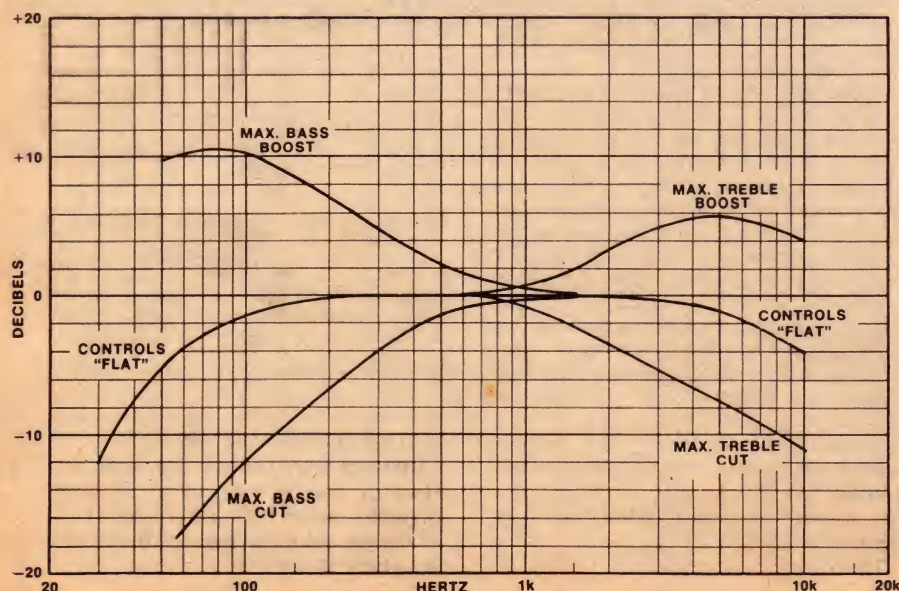

The response curves at left can easily be changed for "hi-fi" recording. The full mixer circuit is shown opposite.

the emitter of Q14, giving a high order of quiescent stabilisation. Also the AC feedback for the tone controls is taken from the emitter of Q14, giving an overall stage gain of unity when the tone controls are in the "flat" position. This high order of negative feedback gives the output stage very low distortion, even when loaded fairly heavily at the output.

The signal at the emitter of Q14 becomes the output signal of the mixer. It is fed to the level meter via buffer transistor Q15, which is connected as a common emitter stage with emitter degeneration to give it a relatively high output impedance. This provides substantially constant-current drive to the meter, making its behaviour ap-

DON'T JUST SIT THERE: BUILD SOMETHING!

IT'S EASY WITH A DICK SMITH KIT — AND THINK OF ALL THE MONEY YOU SAVE AND THE FUN YOU HAVE BY DOING — IT — YOURSELF.

SWITCH ON TO THE DISCO SCENE!

How about turning your next party into a light fantastic? Both these kits are extremely easy to build and like all Dick Smith kits look so good your friends will never believe you built them.

MUSICOLOR Mk III (See September EA 1976)

Build your own lightshow! The Musicolor uses audio output from just about any amplifier to control 3 channels of coloured lights. Doesn't affect the amplifier in any way. You can build this one even if you've never built anything in your life — the 16 page illustrated construction manual makes it so easy!

Cat. K-3140 .. \$59.90

ETI HIGH POWER STROBE

(See August ETI 1971)

Get that fantastic disco 'stop motion' effect. Flash rate can be varied between 1 and 20 flashes per second. Kit includes a 7" photo-



graphic type reflector and perspex safety guard. An extra strobe tube can be added to double the light output. One of our most popular kits.

Cat K-3150 .. \$27.95

AUDIO & AMPLIFIERS

PLAYMASTER 40/40 STEREO AMP.

(E.A. December '76)

Our most popular kit ever. Thousands sold. Easy!

Cat K-3411 .. \$129.50

PLAYMASTER TWIN 25 AMPLIFIER

(E.A. May '76)

Similar to above, but less power. Also a great kit.

Cat K-3410 .. \$105.00

ETI480 100W POWER AMP MODULE

(E.T.I. December '76)

100 watts for \$25.00? Unreal, man! (mono module)

Cat K-3442 .. \$25.00

ETI480 50W POWER AMP MODULE

(E.T.I. December '76)

As above, but 50W. Easily extendable to 100W version.

Cat K-3440 .. \$19.50

ETI480PS POWER SUPPLY MODULE

(E.T.I. December '76)

To run either 1 x 100W or 2 x 50W modules

Cat K-3438 .. \$17.50

100 WATT GUITAR AMPLIFIER

(E.T.I. December '72)

Power for the people. Why waste money elsewhere?

Cat K-3020 .. \$85.00

SPRING REVERBERATOR

(E.A. May '76)

Adds life to your music — amateur or professional!

Cat K-3424 .. \$15.50

ETI 601 MINI ORGAN

(E.T.I. August '76)

YOU can play your favourite tune in style

Cat K-3430 .. \$24.75

LOUDSPEAKER PROTECTOR

(E.A. June '76)

Eliminates turn-on and turn-off surges from most amps.

Cat K-3425 .. \$11.95

LED LEVEL METER

(E.A. June '76)

Bar of light display gives relative power indication.

Cat K-3370 .. \$12.85

GENERAL PURPOSE PRE-AMPLIFIER

(E.T.I. July '76)

Stereo unit, variable gain, suits cartridge, tape, aux, etc.

Cat K-3427 .. \$7.50

COMPUTERS, ETC

2650 MINI COMPUTER (E.A. May '78)

ALL parts, case, front panel, power supply, etc — not a 'part' kit. 4k of memory — a powerful mini system.

Cat. K-3447 .. \$115.00

LOW COST VIDEO DISPLAY UNIT

(E.A. February '78)

Mates with above. Communicate with a computer!

Cat K-3460 .. \$97.50

VIDEO MODULATOR for use with VDU

(E.A. April '78)

Allows above VDU to be used with any TV set.

Cat K-3462 .. \$4.50

ASCII KEYBOARD ENCODER

(E.A. April '78)

Uses our standard keyboard (Cat X-1180)

Cat K-3464 .. \$39.50

CASSETTE INTERFACE

(E.A. April '77)

Use any cassette player to communicate with computer.

Cat K-3465 .. \$24.50

PAPER TAPE READER

Another fascinating aspect of computer technology.

Cat K-3466 .. \$95.00

DIGITAL LOGIC TRAINER

(E.A. July '77)

Want to learn logic? Here's a great way. Teach yourself!

Cat K-3010 .. \$69.00

TEST EQUIPMENT

NEW MODEL TRANSISTOR TESTER

(E.A. July '78)

Checks most transistors and FETs quickly and easily.

Cat K-3052 .. \$17.90

R-L-C BRIDGE

(E.A. March '78)

Ideal project for the beginner. Handy to have around!

Cat K-3468 .. \$34.50

CROSSHATCH/DOT GENERATOR

(E.T.I. August '75)

Keep your TV colour correct with this little beauty.

Cat K-3290 .. \$21.50

AUDIO OSCILLATOR

(E.A. July '78)

Outstanding value for a valuable service aid.

Cat K-3469 .. \$25.00



TV GAMES

10-GAME VIDEO GAME

(E.A. July '78)

Features 4-way bat control, many combinations of bat sizes, ball speeds, angles, etc.

Cat K-3491 .. \$49.50

STUNT MOTORCYCLE GAME KIT

(E.T.I. June '78)

Play 4 different games; motocross, enduro, drag and stunt. Easy to build!

Cat K-3474 .. \$29.50

AMATEUR, CB, ETC.

NOVICE TRANSVERTER

(E.A. April '76)

Use any 27MHz 'CB' on the 80 metre band, 30W out.

Cat K-3134 .. \$89.50

MORSE KEYS

(E.A. April '78)

Perfect Morse code — electronically generated. Inc. paddle.

Cat K-3470 .. \$37.50

VK POWERMATE

(E.A. May '78)

Short form kit — no metalwork, mains wiring etc.

Cat K-3449 .. \$32.00

CB POWER SUPPLY

13.8 volts at 2A continuous (4A peak) complete kit.

Cat K-3448 .. \$29.50

45 WATT VHF AMPLIFIER

F'glass PCB, 13.8V operation. Req. 8 — 12W of drive.

Cat K-3132 .. \$27.50

30 WATT 80 METRE AMPLIFIER

Ideal for the novice. 13.8V. Adaptable to 50W output.

Cat K-3133 .. \$34.95

MISCELLANEOUS

6 DIGIT 240V CLOCK KIT

Hours, minutes & seconds display. Short form w/o case:

Cat K-3364 .. \$19.75

Handsome case to suit: Cat H-3192 .. \$5.00

CAPACITOR DISCHARGE IGNITION

(E.A. July '75)

Save on petrol; end ignition troubles. Pre-wound coil.

Cat K-3280 .. \$25.75

DRILL SPEED CONTROL Mk 2

(E.A. July '76)

Suits 240V 'universal' motors (not electronically switched or controlled types) A must for the home handyman.

Cat K-3080 .. \$11.50

CAR BURGLAR ALARM

(E.T.I. November '74)

A simple kit — which could save your car.

Cat K-3250 .. \$11.50

TV MASTHEAD AMPLIFIER

(E.T.I. August '71)

Can turn an unwatchable mess into a brilliant picture.

Cat K-3230 .. \$29.95

ALL DICK SMITH KITS ARE COMPOSED OF BRAND NEW AND GUARANTEED COMPONENTS.

SEE OUR DOUBLE PAGE AD FOR FULL LIST OF STORES AND DEALERS

DICK SMITH ELECTRONICS



MOVIE MIXER

put stage from being unduly loaded when such low impedance 'phones are connected.

Due to the heavy negative feedback around the output stage, it can deliver more than 800mV RMS (2.2V P-P) with 8-ohm 'phones connected, with low distortion. This should be quite sufficient for most applications. However if you want the mixer to be able to deliver more output before distortion becomes evident, there is a simple remedy: use higher impedance 'phones, or an impedance matching transformer to increase the loading impedance. More about this later.

Before leaving the circuit, here are a few words on extending the frequency response of the mixer for the benefit of those who may want to use it for wide range recording rather than movie work.



To extend the bass response, simply increase the values of the input coupling capacitors for Q7, Q10 and Q11. These capacitors are identified on the circuit, and are easy to find. If you make Q7's input capacitor .047 μ F instead of .022 μ F, and the other two 0.1 μ F instead of .047 μ F, the overall bass response will extend down to about 40Hz (-3dB). This is with the tone controls in the "flat" position.

Extending the treble response is even simpler. All that is necessary is to remove the .0015 μ F capacitor shunting the top of the master gain slider. This extends the treble response of the mixer to about 30kHz (-3dB), again with the tone controls in the "flat" position.

To remove the overlap between the tone controls, making them a little more suitable for wide-range recording, the bass control shunting capacitor should be increased from .022 μ F to .047 μ F. Similarly the two capacitors associated with the treble control should be reduced from .0022 μ F to .0015 μ F. And if you want to give the controls the full normal range provided in a hi-fi amplifier, simply reduce all four end limiting resistors to 10k. These are the two 22k resistors associated with the treble control, and the two 15k resistors associated with the bass control.

As you can see from the photographs, the mixer is built in one of the low cost "zippy" boxes, available from a number of suppliers. The box measures 197 x 113 x 59 mm, and has an impact-resistant plastic body with an aluminium front panel. The box I used came from Dick Smith Electronics, and is listed in their catalog under number H-2752.

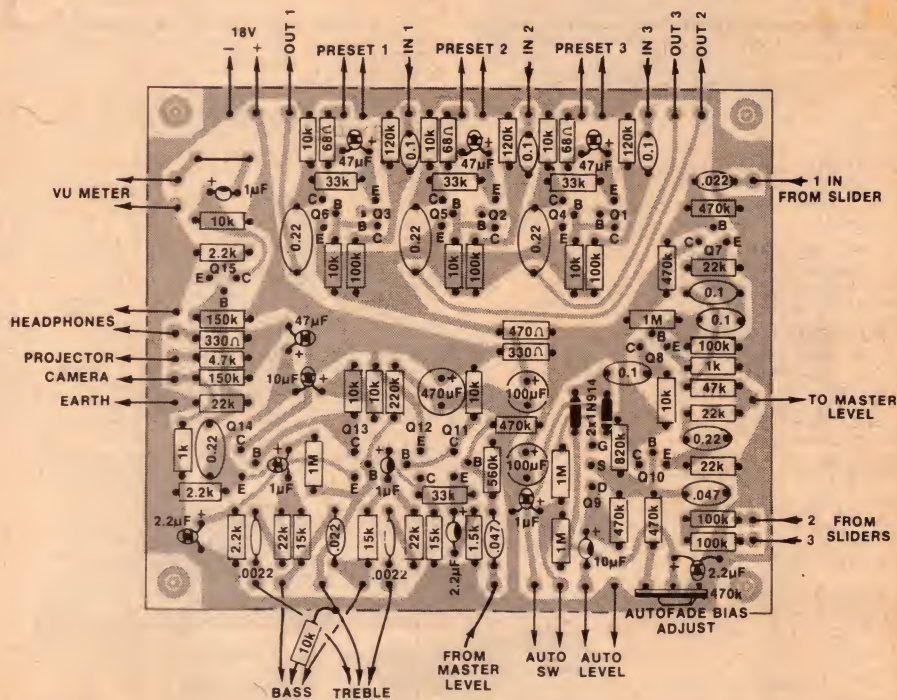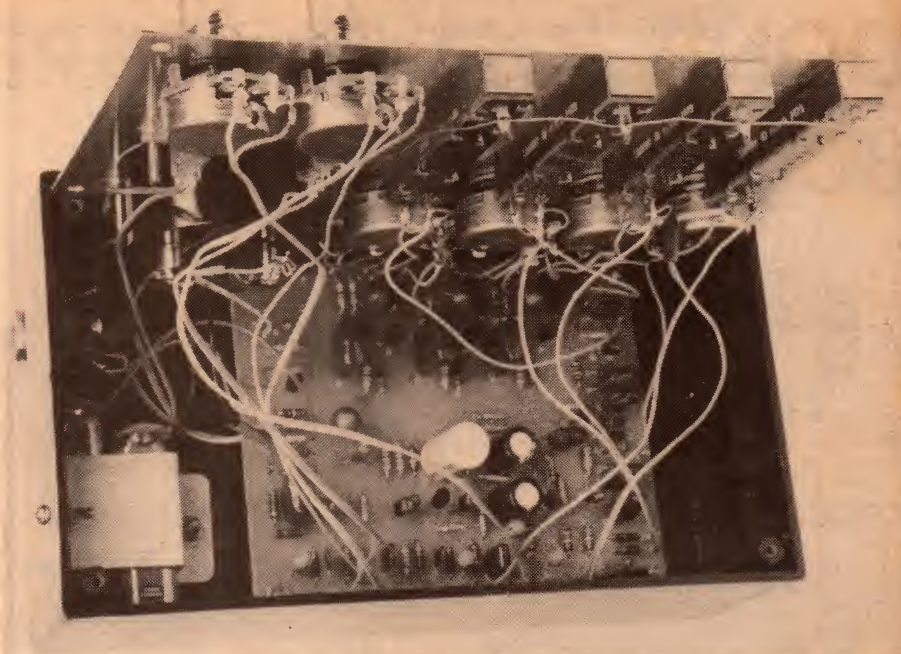There are quite a few controls on the front panel, as you can see, but there is no undue crowding. In the upper left-hand corner of the panel is the level meter, with the switches and tone con-



Above is the wiring diagram for the mixer PCB, with a view of the inside of the complete mixer at the top. Use these in conjunction with the circuit.

controls beneath it. Then in the lower centre of the panel are the three input channel sliders, with their respective preamp gain controls above them. Finally at the right-hand end of the panel is the master level slider, with the autofade level control above it.

There are a couple of small "VU" meter movements available which would be suitable for the mixer, and these can be obtained from a number of suppliers. The meter I have used measures 52 x 49mm on the front, and is identified as "MRA-45" on the lower


part of the scale. It came from Dick Smith Electronics, who have it listed in their catalog under number Q-2050.

Another, slightly smaller meter movement is also available, the model KM-48 from Kyoritsu. This measures 48 x 42mm on the front, and would also be quite suitable. It is stocked by Radio Despatch Service in Sydney, and possibly by other suppliers as well. Like the other meter it has an inbuilt rectifier bridge and VU-meter scale.

The front panel of the prototype was made by hand, using a hand nibbler to

AUDIO TELEX and BOGEN, the best combination of sound products available

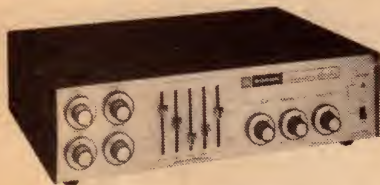DI Series amplifiers have inbuilt balanced, low impedance mic inputs using XLR connectors, constant voltage and low impedance outputs. Outperform the major competition and priced lower. Available in 100, 60 and 35 watts including 100 watt booster.




CT SERIES — AMPLIFIERS

Turner microphones are rugged, reliable and provide excellent quality sound. Wide range of paging, entertainment and industrial types available. Including floor and desk stands and booms.



MT SERIES — BOOSTER AMPLIFIERS

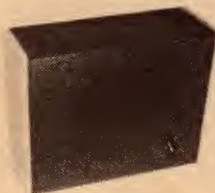Bogen emergency evacuation panels for alerting and issuing directions to the occupants of a building in case of emergency. Systems comply with draft specification. Fire resistant speakers also available.



WALL ENCLOSURES SPEAKERS AND TRANSFORMERS



SOUND COLUMNS



RADIO MICS



DI SERIES

Inbuilt anti feedback equalizer and compression with four mic inputs. When feedback is a problem, the CT series is an excellent choice. (Ideal for churches) available 35, 60 and 100 watts.




SE11 752

TURNER MICROPHONES

Bogen MT series heavy duty booster amplifiers ideally suited for large public address, entertainment and emergency evacuation systems. Available in 125 or 250 watts.



BOGEN EMERGENCY EVACUATION PANEL

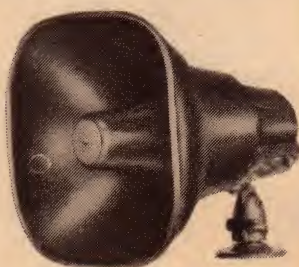

15 & 30 WATT HORNS

FOR FURTHER INFORMATION:

AUDIO TELEX COMMUNICATIONS PTY. LTD.

SYDNEY

54-56 Alfred Street
Milsons Point 2061
Telephone: 929-9848

MELBOURNE

828 Glenferrie Road
Hawthorne 3122
Telephone: 819-2363

ADELAIDE

Werner Industries
28 Gray Street,
Kilkenny 5009
Telephone: 268-2801

BRISBANE

Audio Telex Communications
394 Montague Road
West End 4101
Telephone:

PERTH

Electro Acoustics Pty. Ltd.
11 Frobisher Street
Osborne Park 6017
Telephone: 444-8688

HOBART

Video & Sound Services
141 Murray Street
Hobart 7000
Telephone: 34-1180

MOVIE MIXER

cut out the large hole for the meter barrel. The slots for the slider pots were made by drilling some small holes at the ends, cutting down the slots with a hacksaw blade and then finishing off the slots with jeweller's needle files (quite a job, I can testify!). The panel was then finished off with a self-adhesive label sheet made from 3M "Scotchcal" photosensitive aluminium

PARTS LIST:

- 1 Plastic/metal case, 196 x 113 x 60mm
- 1 PC board, 120 x 100mm, code 78mx9
- 1 VU-type meter, 52 x 49mm or similar
- 2 SPST miniature toggle switches
- 4 3.5mm jack sockets, with contacts
- 1 5-pin DIN socket (180 degree)
- 1 6.5mm stereo phone socket
- 2 9V batteries, 216 type
- 2 Connector leads to suit batteries
- 6 Small knobs as desired
- 4 Knobs to suit slider pots

SEMICONDUCTORS

- 6 BC549 or similar low noise NPN
- 4 BC548 or similar NPN
- 4 BC559 or similar low noise PNP
- 1 2N5459, MPF105 or similar FET
- 2 1N4148 or similar diodes

RESISTORS

- 5% 1/4 watt: 3 x 68 ohm, 2 x 330 ohm, 1 x 470 ohm, 2 x 1k, 1 x 1.5k, 3 x 2.2k, 1 x 4.7k, 16 x 10k, 3 x 15k, 6 x 22k, 4 x 33k, 1 x 47k, 6 x 100k, 3 x 120k, 1 x 150k, 1 x 220k, 5 x 470k, 1 x 560k, 1 x 820k, 4 x 1M
- 3 20k log potentiometers
- 1 50k linear potentiometer
- 4 50k linear slider pots, 45mm travel
- 2 100k linear potentiometers
- 1 470k linear tab pot (vertical PCB type)

CAPACITORS

- Low voltage plastic ("greencap" or similar): 1 x .0015uF, 2 x .002uF, 2 x .022uF, 2 x .047uF, 6 x 0.1uF, 5 x 0.22uF
- 1 1uF 35VW tantalum
- 3 2.2uF 35VW tantalum
- 2 10uF 16VW tantalum
- 4 47uF 16VW tantalum
- 2 100uF 25VW single-ended electro
- 1 470uF 25VW single-ended electro

MISCELLANEOUS

Connecting wire, nuts and bolts, solder lug, scrap of aluminium for battery clamp, solder, etc.

NOTE: Resistor wattage ratings and capacitor voltage ratings are those used for our prototype. Components with higher ratings may generally be used providing they are physically compatible.

THE LOUDSPEAKER THAT LOOKS AT MUSIC THE WAY YOU DO: JBL'S NEW L110.

You're at a concert. The sound surrounds you. There's a guitar. A piano. Some horns.

You hear all of it.

But more than that, you hear each part of it. Each sound. Every sound. All the sound.


Most loudspeakers can't do that. They only meet you half way. Only left and right, all or nothing. JBL's new L110 goes all the way. It looks at music the way you do.

Left. Right. Front. Back.

The L110 has almost perfect stereo imaging—a result of precise, uniform dispersion at every frequency.

Inside the L110, there's a brand new, super-sophisticated crossover network designed specifically to match the new components.

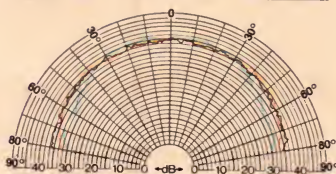There's a new 10" woofer which utilizes a massive 3" voice coil and 7½ lb. magnetic assembly—normally found in 12" woofers.



Frequency Dispersion of the L110

~~~~~ at 400Hz --- at 2kHz ..... at 10kHz

JBL's new L110 loudspeaker is part of the same research and development breakthrough that created our no-tradeoff, top-of-the-line L212 system.

If this graph looks familiar, it should. The L212 produced an almost identical one.

The result is smooth, accurate bass, plus an amazing level of efficiency and power handling capability throughout the entire system. (One more nice: You get more headroom for your amplifier. Less clipping.)

Now look at the L110. The most acoustically transparent grille JBL has ever created is visually transparent, too. You can see right through to the satin black components inside.

If you'd like a lot more technical information on the L110, write us and we'll send you an engineering staff report. Nothing fancy. Except the specifications.

But you really should come listen to the L110. And ask for it by its first name: JBL. You'll be get-

ting the same craftsmanship, the same components, the same sound heard in the very top recording studios in the world.



Over four hundred of the leading recording studios in the world—from Los Angeles to London to Muscle Shoals to Munich to Tokyo to Tennessee—use our sound to make theirs. Shown here is Capitol Records in Hollywood, California.

Distributed by—  
HARMAN AUSTRALIA PTY. LTD., P.O. Box 6, BROOKVALE, N.S.W. 2100.

HA118/78

**JBL**

GET IT ALL.





# Specs with a purpose!

## Sansui's new amplifiers






Sansui's all-new integrated amplifiers have absolutely astounding specifications. Compare them with any others in their class, and Sansui comes out far ahead. But what really makes Sansui's new amplifiers so superior is that all these great specs have a single purpose — outstanding sound quality.

Take response speed, for example. Your amplifier doesn't move, but it does respond. The more rapid its response, the cleaner and the more accurate the sound. That's why the AU-717, for example, features an advanced DC power amplifier design. Sansui's DC amplifier eliminates all capacitors in the signal path and even in NFB loop so amplification is direct without coloration and phase delay. Response is astoundingly rapid — the proof is in the ultra-high (60V/μsec.) slew rate and ultra-rapid rise time (1.4 μsec).


But Sansui didn't strive for such outstanding specs just to be able to print impressive figures. On the contrary, Sansui research showed that to achieve accurate reproduction and reduce signal loss, lightning-fast response was essential.

In addition, special circuits were incorporated to achieve new levels in stamping out TIM (transient inter-modulation distortion), a type

#### SLEW RATE & RISE TIME

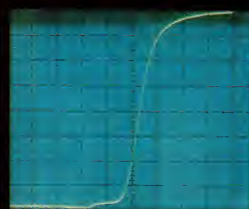

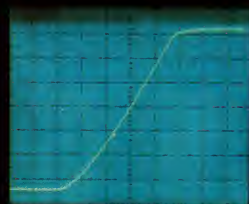AU-717  
Slew Rate:  
60V/μsec.  
Rise Time:  
1.4 μsec.  
V: 10V/div.  
H: 1 μsec./div.



A CONVENTIONAL AMP.  
V: 10V/div.  
H: 1 μsec./div.

of distortion that is now receiving high priority. Still another important benefit of Sansui's DC amplifier is the ultra-wide frequency response from zero (DC) to 200,000 Hz.

The final result is music with a purity and clarity that must be heard to be believed. All the dimensions of

complex musical sounds — the wide dynamic range, the sudden pulsive signals, the nuances of barely perceptible but critical overtones in the ultra-high frequencies — all these are now crystal clear, all are proof of Sansui's new levels in superior sound quality. Impressive power is 85 RMS watts per channel, 20 — 20k Hz, and total harmonic distortion at rated output is 0.015%. That means it can be considered non-existent as far as the human ear is concerned.

Keep in mind that though the AU-717 is special, it's not special for Sansui. Each and every amplifier on the left-hand page embodies the same Sansui commitment to outstanding sound quality. All controls have been carefully thought out and designed for their specific purposes. Sansui has no place for gadgets and gimmicks in its dedication to the ultimate in hi-fi.

The AU-517 and AU-317 also feature the same DC power amplification as the AU-717, and offer 65 and 50 RMS watts respectively. The AU-217 and AU-117 offer 30 and 20 RMS watts respectively, but are not to be under-rated. In fact, they represent exceptional values in low distortion and true hi-fi performance.

Sansui for specs with a purpose — outstanding musical quality.



**Sansui**

**Only hi-fi, everything hi-fi.**

SANSUI ELECTRIC CO., LTD. 14-1 Izumi 2-chome, Suginami-ku, Tokyo 168, Japan

VANFI (AUST.) PTY. LTD. 162, Albert Road, South Melbourne, Victoria 3205, Australia Tel: 699 5473

Suite 5, Uniline House, 5 Northcliff Street, Milson Point, N.S.W. 2061, Australia Tel: 929 0293



# UNIQUE.

## Philips Motional Feedback Speakers.

Every now and then a technical breakthrough is achieved and a unique product emerges to set new standards in its field.

Such is the case with Philips Motional Feedback Speakers.

These electronic masterpieces have been developed after years of exacting research in our European Laboratories and, as a result, we've created a speaker system that comes very close to the ultimate in Hi-Fi reproduction.

Technically speaking, the system incorporates a piezo-electric crystal built into the woofer cone that monitors and converts the acceleration of the cone into an electric signal. The acceleration of the cone is linearly translated back to the original signal driving the loud-speaker. This signal is fed back to a comparator circuit in the amplifier incorporated in the enclosure and compared with the original signal. This enables the loud-speaker to be immediately corrected at the slightest deviation. And, in this way, the acoustic behaviour of the woofer can be completely controlled.

Practically speaking, the results are dramatically simple. A drastic reduction in distortion. Flawless clarity—from the fullest bass notes to the most detailed treble extremes. And a remarkable compactness in enclosure and speaker construction.

Listen to Philips Motional Feedback Speakers. They'll speak for themselves.

**Philips Motional Feedback Speakers.**  
**A step closer to sound perfection.**

### Technical specifications Model 541

|                     |                               |
|---------------------|-------------------------------|
| Volume:             | 8 litres; 4.5 litres acoustic |
| Power of amplifier: | 30 W cont. sine wave power    |
| Frequency response: | 35-20,000 Hz                  |

### Model 544

|                                     |                              |
|-------------------------------------|------------------------------|
| Volume:                             | 15 litres; 9 litres acoustic |
| Total power of amplifiers:          | 60 W cont. sine wave power   |
| Frequency response:                 | 30-20,000 Hz                 |
| Amplifier for woofer:               | 40 W cont. sine wave power   |
| Amplifier for squawker and tweeter: | 20 W cont. sine wave power   |

### Model 567

|                                     |                               |
|-------------------------------------|-------------------------------|
| Volume:                             | 30 litres; 20 litres acoustic |
| Total power of amplifiers:          | 60 Watt cont. sine wave power |
| Frequency response:                 | 27-20,000 Hz                  |
| Amplifier for woofer:               | 40 W cont. sine wave power    |
| Amplifier for squawker and tweeter: | 20 W cont. sine wave power    |

### Model 545

|                            |                                                         |
|----------------------------|---------------------------------------------------------|
| Volume:                    | 70 litres; 50 litres acoustic                           |
| Total power of amplifiers: | 100 W cont. sine wave power                             |
| Frequency response:        | 20-20,000 Hz                                            |
| Low note filters:          | -5 dB at 200 Hz<br>-5 dB at 60 Hz<br>-3 dB at 55-160 Hz |
| Bass Control:              | from +10 dB to -10 dB at 60 Hz                          |
| Treble filter:             | continuously variable,<br>0-20 dB per octave            |
| Amplifier for woofer:      | 50 W cont. sine wave power                              |
| Amplifier for squawker:    | 35 W cont. sine wave power                              |
| Amplifier for tweeter:     | 15 W cont. sine wave power                              |

All specifications are subject to modification without notice.



**PHILIPS**

We want you  
to have the best







Here is the PCB pattern for the mixer, reproduced actual size for those who may care to produce their own board by tracing or photography.

An actual-size reproduction of the front panel artwork is shown on these pages, for those who wish to follow the same course. However I understand that at least one kit supplier is likely to have prepunched and etched panels available for the project, so that you may be able to produce your front panel with rather less work than mine!

Inside the box, just about all of the circuitry is on a small printed circuit board (PCB). The board measures 120 x 100mm, and is coded 78mx9.

Wiring of the PCB should be fairly straightforward using the overlay diagram and the internal photograph as a guide. The main points to watch are that you fit the transistors, diodes, and electrolytic capacitors (including tantalums) with correct orientation.

It is also a good idea to orientate the resistors so that their colour coding bands read consistently "North-South" and "East-West", to make it easier to check later.

I would recommend that you use PC-pins for all of the external connections to the PCB, as this simplifies assembly. You can finish the PCB, mount it into the bottom of the case and then connect it up to the various front-panel controls and connectors.

Note that apart from the front panel controls, the meter, the input and output sockets and the batteries, the only other parts not mounted on the PCB are five 10k resistors and a .0015uF capacitor. One of the resistors connects directly between the rotor (centre) lugs

of the bass and treble pots, while the other four are each connected between the rotor lug and "top" element lug of a slider pot (one per slider!). The capacitor connects from the top of the master gain slider to one of the earthed lugs on the adjacent autofade level pot.

Note also that the metal front panel of the case should be connected to the circuit "earth", to provide some shielding and also to prevent feedback coupling. This can be arranged easily by slipping a solder lug under one of the meter mounting nuts, and connecting the lug to the earth wire used for the sliders and preamp gain pots.

When you are wiring up the various rotary and slider pots on the front panel, check against the circuit so that you wire them for correct action. The small arrows on the circuit indicate clockwise rotation for rotary controls, or upward movement for sliders.

The two 216-type batteries used to power the mixer are clamped in position beneath the tone controls, using a small scrap of aluminium. The two batteries are connected in series, with the resulting +18V lead connected to the PCB positive input via the front-panel power switch. The negative lead connects straight to the PCB negative input.

The wiring for the headphone socket will depend upon whether you wish to use a matching transformer or not. If not, simply wire the stereo headphone jack so that the two wires from the PCB connect to the tip and ring contacts. This will result in the two stereo headphones being connected effectively in series, giving greater volume.

As explained earlier, the mixer will deliver more output at lower distortion if a matching transformer is used to increase the load impedance. Miniature "transistor output" transformers are available very cheaply from a number of suppliers, and most of these are small enough to be fitted inside the mixer case if desired.

Almost any transformer described as a "transistor output" type is likely to be suitable, as long as it is capable of stepping up a few ohms into a few hundred ohms and handling a couple of hundred milliwatts. Among those suitable are those listed in the Dick Smith catalog under numbers M-0226 and M-0216.

If you decide to use a transformer, connect its high impedance primary to the two PCB output pins, and its low impedance secondary to the stereo headphone socket. In this case the tip and ring contacts should be connected together and to one end of the secondary, with the sleeve connecting to the other end of the secondary. It is also a

## AIR IONIZER

See E.A. July 1978

Bion 79 Personal Negative Air Ionizer 240V 0.5W for office and home.

### REDUCE

- Fatigue, migraine headaches in air conditioned offices and rooms
- Pollution from smoke, dust, bacteria, vehicle exhausts, etc.
- Respiratory complaints, colds, flu allergies, etc.
- Tension and anxiety

### INCREASE

- Concentration, alertness
  - Memory and learning
- \$59.00 Plus P&P NSW \$2.00, interstate \$3.00

● Automotice model 78 (12V DC)  
Reduces fatigue on long trips and heavy traffic, attaches to windscreen — \$45.00 Plus P&P \$1.50

WENTWORTH ELECTRONICS

77 Wentworth Ave, Wentworthville, NSW 2145

Ph: (02) 636 4686





## MIXER FOR HOME MOVIES

good idea to connect the sleeve to the mixer PCB earth, to prevent possible feedback effects.

If the leads between the input connectors and the PCB are kept short, it appears to be quite satisfactory to use normal hookup wire rather than shielded cable. Similarly the rest of the mixer interconnections may be made in hookup wire, providing that you don't

make them unduly long. The wiring is not particularly critical, but it is a good idea to keep the input leads well away from the output wiring.

There is only one setting-up adjustment to be made when the mixer is complete. This is the bias adjustment for Q9, the autofade control FET.

To set this control, which is the small preset pot on the PCB, you will need a

source of fairly steady signals. A sinewave tone from an audio oscillator is ideal, but if you don't have access to one of these instruments a recording with some music of reasonably constant volume will do at a pinch.

Feed this signal into either channel 2 or 3, with the autofade switch off, and turn the slider and preset gain pot for the channel concerned, together with the master gain slider, until the level meter is indicating around normal recording level. This will be at the "0dB" or "100%" mark for a tone, or an average of about "60-70%" with occasional peaks into the red area for a musical signal.

It is a good idea to plug in a pair of headphones at this stage, to confirm that the signal is undistorted under these conditions.

Now turn the front-panel autofade level pot to the minimum level position (fully anticlockwise, or minimum resistance), and the PCB autofade bias pot tentatively to the full bias position. This is the position with the rotor at the earthy end, adjacent to the PCB mounting screw alongside.

Make sure that the channel 1 slider pot is pushed right down, to the "0" setting. Next switch on the autofade switch. Nothing should happen at this stage, if everything is in order.


Now slowly turn the PCB autofade bias pot back towards the opposite extreme, listening to the headphones and watching the meter. Stop turning the pot as soon as you detect the incidence of an "edge" of distortion, and/or a drop in the meter reading. Then turn the pot back slightly, until all edginess disappears. This is the correct setting for the pot, and the adjustment is complete.

Should you find that you can turn the pot right to the far end without producing any effect, don't despair. This probably only means that you have a FET with a rather low cutoff voltage. Just leave the pot set to the far extreme (furthest from the PCB mounting screw), and all should be well.

To check that the autofade operates correctly, plug a microphone into the channel 1 input and turn the channel 1 preamp gain pot fully clockwise for a full gain. Then, speaking about 300mm away from the mike, gradually move up the channel 1 slider. As soon as the voice signals reach a certain level the tone or music should drop to a very low level. Then if you stop speaking or lower the channel 1 slider, the tone or music should smoothly fade up to its former level.


If you turn the front-panel autofade level pot to different settings, you should be able to adjust the level to which the tone or music fades when the voice signals are present.

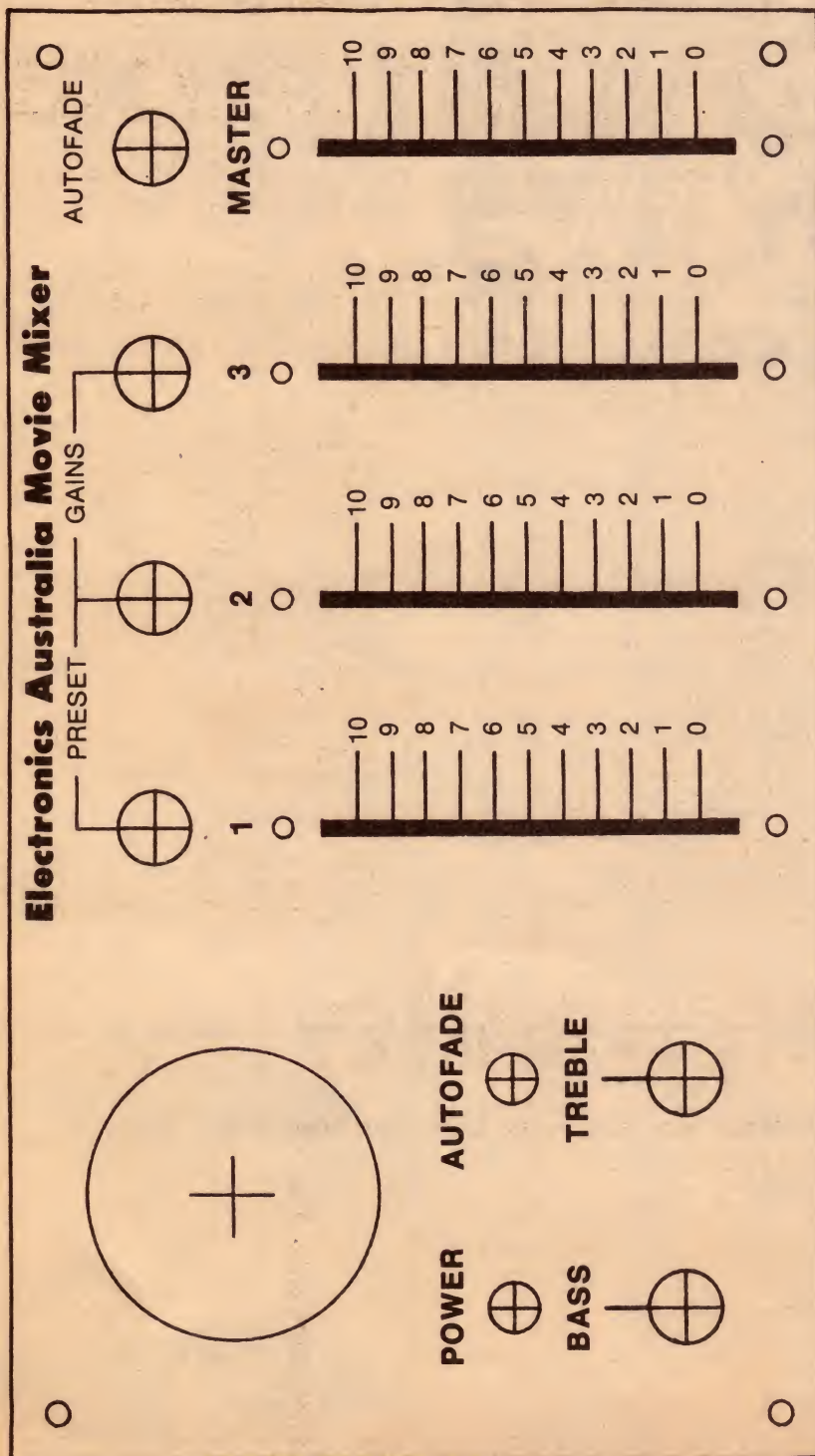All that remains is for me to wish you happy sound movie making, with our new mixer to help you achieve satisfying results on the sound side.



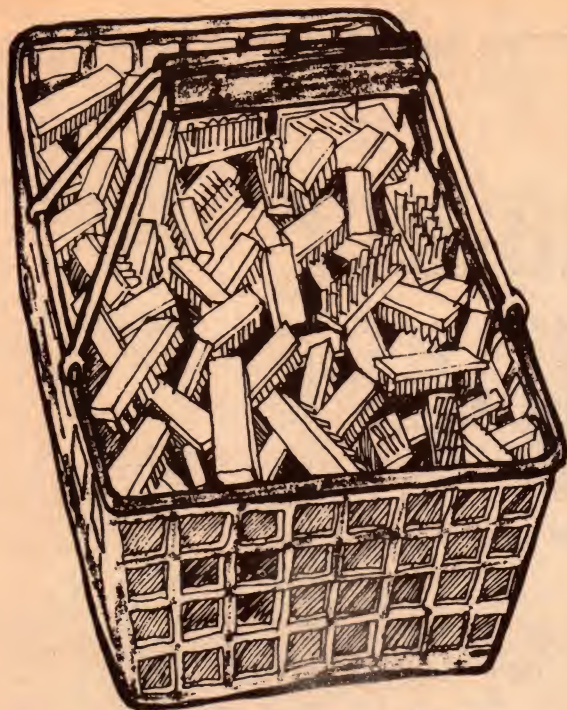Here is the front panel artwork for the mixer, again reproduced actual size.





# Shop at your nearest electronic supermarket

Silicon Valley has a complete range of over 4,000 line items. All products are guaranteed, fully warranted and of current production.

Silicon Valley's mail order division can supply you the products displayed on the Silicon Valley shelves or those supplied to industry by Cema Electronics.

## Silicon Valley Stores

### SYDNEY:

#### Silicon Valley.

Shop 4, PO Arcade, Joyce Street, Pendle Hill.

Tel: (02) 636 6566.

#### Pre-Pak Electronics.

718 Parramatta Road, Croydon.

Tel: (02) 797 6144.

#### Martin De Launay.

Cnr. Druitt and Clarence Streets, Sydney.

Tel: (02) 29 5834.

#### In-Electronics.

84 Ramsey Street, Haberfield.

Tel: (02) 799 3331.

#### Kit-Sets.

657 Pittwater Road, Dee Why.

Tel: (02) 982 7500.

#### Silicon Valley.

23 Chandos Street, St. Leonards.

Tel: (02) 439 2965.

### WOLLONGONG:

#### Martin De Launay.

270 Keira Street, Wollongong.

Tel: (042) 28 6020.

### NEWCASTLE:

#### Martin De Launay.

Cnr. King and Darby Streets, Newcastle.

Tel: (049) 2 4741.

### CANBERRA:

#### Daicom.

29 Colbee Court, Philip.

Tel: (062) 82 3581.

### BRISBANE:

#### Kit-Sets.

293 St. Pauls Terrace, Fortitude Valley.

Tel: (07) 52 8391.

### MELBOURNE:

#### Rod Irving Electronics.

499 High Street, Northcote.

Tel: (03) 489 8131.

#### Stewart Electronics.

240b Huntingdale Road, Huntingdale.

Tel: (03) 543 3910.

#### South West Electronics.

119 Hopkins Street, Footscray.

Tel: (03) 689 3819.

### Ellistronics.

298 Latrobe Street, Melbourne.

Tel: (03) 602 3282.

#### Silicon Valley.

380 Bridge Road, Richmond.

Tel: (03) 429 4780.

### ADELAIDE:

#### Silicon Valley.

170 Sturt Street, Adelaide.

Tel: (08) 51 4080.

#### Ktronics.

Peel Street, Adelaide.

Tel: (08) 212 5505.

### PERTH:

#### Atkins Carlyle.

1-9 Milligan Street, Perth.

Tel: (09) 321 0101.

### NEW ZEALAND:

#### Silicon Valley.

7-9 Kirk Street, Grey Lynn, Auckland.

Tel: 76 1169.

# silicon valley

Return this coupon today, for your free  
Silicon Valley price list:

Name .....

Address .....


.....

..... P/Code. ....

Phone No. ....

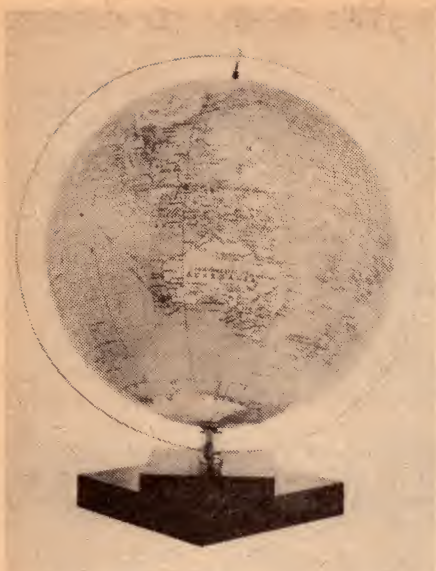Post to Silicon Valley, P.O. Box 898, CROWS NEST, N.S.W. 2065





# How to pick up the amateur satellites

by NEVILLE WILLIAMS

**Perhaps you've collected verification cards from every quarter of the globe and are looking for new worlds to conquer with your high-performance DX receiver. Well then, why not look up, instead of around, and keep an on-air rendezvous with an orbiting satellite?**

To many people, the idea of tuning directly to the signals from a satellite will come as a new thought. If they think about them at all, they envisage satellites as being crammed with highly sophisticated electronic gadgetry, accessible only to earth stations equipped with steerable radar-like antennas and highly specialised receivers.

In the general case, that impression would be substantially accurate but it does ignore two satellites that are currently in orbit, and which cross Australia several times a day; they are known as "OSCAR 7" and "OSCAR 8".

The term OSCAR is an acronym for "Orbiting Satellite Carrying Amateur Radio". The figures indicate that the two currently in orbit — and active in the radio sense — are numbers 7 and 8 in a series.

Both these satellites can be heard at certain times, using a good quality communications receiver and an outdoor antenna — typically a CB base station type or an ordinary wire aerial suitable for short-wave reception.

But more about that in a moment; let's sketch in a little of the background to the two OSCAR satellites.

When the Russians launched the first man-made satellite, back in October, 1957, it emitted beep-beep-beep signals from its radio beacon on 20MHz. Amateurs and hobbyists were able to tune them directly on sensitive shortwave receivers.

Noting the strength of the signals from that original Russian "Sputnik I", amateurs realised that it should one day be feasible to build and launch a

satellite, which would radiate a similar beacon signal on one or more of the amateur bands. Better still, it might even be possible to have an orbiting satellite "repeater", receiving signals from amateur stations on the ground and re-transmitting them from space.

It took just over four years for the dream to become a reality, during which time amateurs had to learn how to build a radio beacon which would perform reliably in space. They also had to convince the US authorities that they should omit a little of the trimming ballast from one of their space shots and substitute an amateur-built satellite beacon instead!

Success crowned their efforts in both directions and the first amateur satellite, OSCAR 1, was launched from the Vandenberg Air Base in December 1961. It carried a simple radio beacon on 144.98MHz, radiating the Morse

message "Hi" — at the one time a greeting and amateur jargon for a laugh. Despite the very modest power level — a mere 100 milliwatts — more than 5000 reception reports were received from 28 countries covering the 15 days in which it remained operative.


OSCAR 2, more or less a repeat of OSCAR 1, was launched in June of the following year and operated for about 20 days. While still carrying only a beacon transmitter, it provided amateurs with further experience in space tracking and reception, ready for the true, orbiting repeaters which were to follow.

OSCAR 3, launched in March 1965, was the world's first non-government free-access communications satellite, receiving signals on 144.1MHz and re-transmitting them on 145.9MHz, at a power level of 1 watt. Also battery-powered, OSCAR 3 failed after 15 days but, in that time, it provided the means for several historic "firsts" in amateur communication and set a pattern for the future.

It was followed by OSCAR 4 and, in January 1970, by OSCAR 5 which, incidentally, was designed and built in Australia.

In fact, OSCAR 5 was the last of the series built by independent groups of enthusiastic amateurs. In the meantime, AMSAT, the Radio Amateur Satellite Corporation Inc. had been founded in Washington DC to coordinate and regularise amateur satellite initiatives. From the outset, AMSAT has enjoyed the support of international amateur groups, financial sponsorship by individuals and companies, and spare-time technical back up from NASA engineers, many of whom are active amateurs.

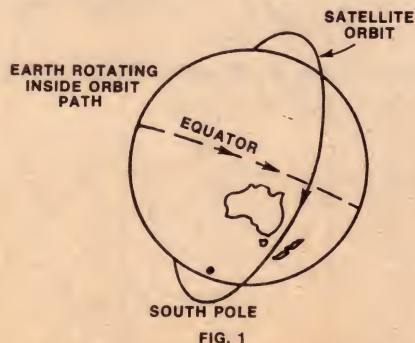OSCAR 6, the first of the new generation AMSAT satellites, was launched in October 1972 and remained serviceable until June 1977.



The orbital track of Oscar 7 and Oscar 8 is nominally over the poles, with the Earth rotating inside the orbit, as shown.



## When you need to listen:

Oscar 6 differed from earlier satellites in that it carried a "transponder" rather than a "repeater" for two-way working. The difference is important: a repeater receives one discrete frequency only and transmits on another discrete frequency. A transponder accepts signals anywhere within a specified band and frequency shifts them for transmission in another specified band. It can handle a number of signals simultaneously within the respective bands and even in different transmission modes, so that a number of amateur stations may communicate through the satellite at the one time.

As we said at the outset, there are currently two AMSAT (amateur) satellites in orbit and active in the radio sense, and these are the ones that you'll want to try for.

OSCAR 7 was launched on November 15, 1974, into a nominal polar orbit at a mean altitude of about 1460km. It completes an orbit each 115 (approx.) minutes.

This is illustrated in Fig. 1 which depicts a satellite orbiting over the Poles, with the Earth rotating inside the "stationary" orbiting path. As shown, the satellite is approaching Australia from the north. Fairly obviously, 12 hours after the situation depicted in Fig. 1, when the Earth will have rotated by one half-turn, the satellite will be approaching Australia from the south.

To carry your thinking a little further, Fig. 2 is, as it were, a "plan" view of the Earth looking down on the North Pole. It is rotating, of course, in an anti-clockwise direction. The Sun is shown at the right, with the "day" and "night" areas on Earth depicted by shading.

The line drawn obliquely across the Earth represents the approximate orbital path of OSCAR 7, with the arrows indicating its direction of travel across the Northern Hemisphere. As mentioned earlier, the orbital track of the satellite is "stationary", in the sense that it always presents the same declination to the Sun, roughly as depicted. It is known as a "Sun synchronous" orbit.

If you look carefully at Fig. 2, you will realise that it must always be morning on most parts of the Earth's surface which are passing under or adjacent to the north-south traverse of OSCAR 7. Similarly, it must be evening when passing under the south-north traverse.

It is not difficult to appreciate that, no matter where on earth a listener may live, he/she can expect to hear signals from OSCAR 7 only when their part of the Earth's surface is adjacent to its orbital track. And that will happen for most listeners during their local morning and evening. It would be quite useless listening at other times, eg, during the afternoons or the small hours after midnight.

In the foregoing paragraphs, we have been careful to suggest that a listener needs only to be adjacent to — not necessarily under — the orbital track to hear signals from OSCAR 7. This is due

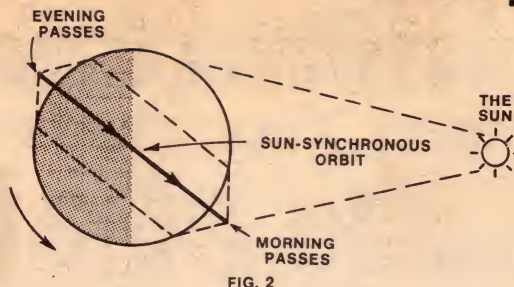


FIG. 2

to the fact that the satellite is at an altitude of 1460km and is therefore visible, in the radio sense, from quite a large area of the Earth's surface.

The area of "visibility" at any instant, or the so-called "footprint" of OSCAR 7, approximates a circle of diameter 7800km. As the circle sweeps across the Earth's surface, it can be envisaged as a track 7800km wide, as shown in Fig. 2. Because of the width of this track, any given spot on earth is likely to lie within the coverage of at least two successive passes during each morning and each evening.

An Australian listener, for example, may hear signals during an orbit that passes somewhere over the Pacific or the Tasman, followed by the next over the continent, and a third over the Indian ocean, making a maximum of three consecutive passes. On other days, one of the passes may be just out of reach over the Pacific or over the Indian Ocean, leaving only two effective passes for that morning or that evening.

Thus the pattern for Australia for OSCAR 7 is two or three passes 115 minutes apart, beginning sometime after 5.00am in the mornings, and two or three passes beginning sometime after 7.00pm in the evening. To be more precise than this involves a certain amount of figuring, which we will get around to explaining later.

The latest AMSAT (amateur) satellite, OSCAR 8, launched on March 5 this

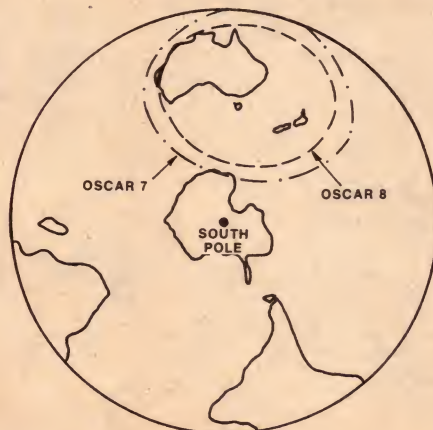


FIG. 3

This diagram shows the extent of the radio coverage or "footprint" of Oscar 7 and Oscar 8 as it would be when they were exactly over Sydney.

Because the Oscar 7 and 8 orbits have a substantially fixed relationship to the Sun, most population centres on Earth pass under the orbital tracks during the morning or evening periods. You won't hear the satellites during the afternoons or the small hours after midnight.

year follows a very similar orbital track to OSCAR 7, but with a mean altitude of 880km and an orbital period of 103 (approx) minutes. For the same reasons as explained in Fig. 2, OSCAR 8 also provides a pattern of morning and evening passes.

Having less altitude, OSCAR 8 is visible (in the radio sense) to a smaller area of the Earth's surface at any one instant — represented by a circle approximately 6500km in diameter.

Fig. 3 will give you some idea of what the coverage of OSCAR 7 and OSCAR 8 would be at the instant when they were positioned exactly over Sydney. The somewhat misshapen "circle" and the unfamiliar outline of Australia is due simply to the fact that they are represented on a great circle projection of the Earth centred on the South Pole. Why we used this projection will become apparent when you see the detailed follow-up article, hopefully in our next issue.

By taking Fig. 2 and Fig. 3 together one can narrow down the earlier statements about availability of the satellites to any given location:

- Access to OSCAR 7 and/or OSCAR 8 is available only during the morning and evening periods, as previously defined, and
- They are available only during specific periods, morning or evening, when the respective "footprints" cover the relevant location.

Expanding upon the last point, it takes a maximum of 22 minutes for the OSCAR 7's footprint to traverse a given point on the Earth's surface, and a lesser time for the fringes of the footprint to pass.


Expressed in more technical terms, the maximum access time to Oscar 7 is 22 minutes for an overhead orbit, and progressively less than 22 minutes for orbits to either side. Therefore access opportunities to OSCAR 7 in Australia are typically limited to two or three periods each morning or evening, with no period longer than 22 minutes.

Maximum access time to OSCAR 8 is shorter, at 18 minutes per pass.

Because the orbits in both cases are slightly out of synchronism with the Earth's own rotation, the passes do not occur at regular times. It is therefore not possible to nominate any fixed time



## Tandy Expands Your Listening Horizons

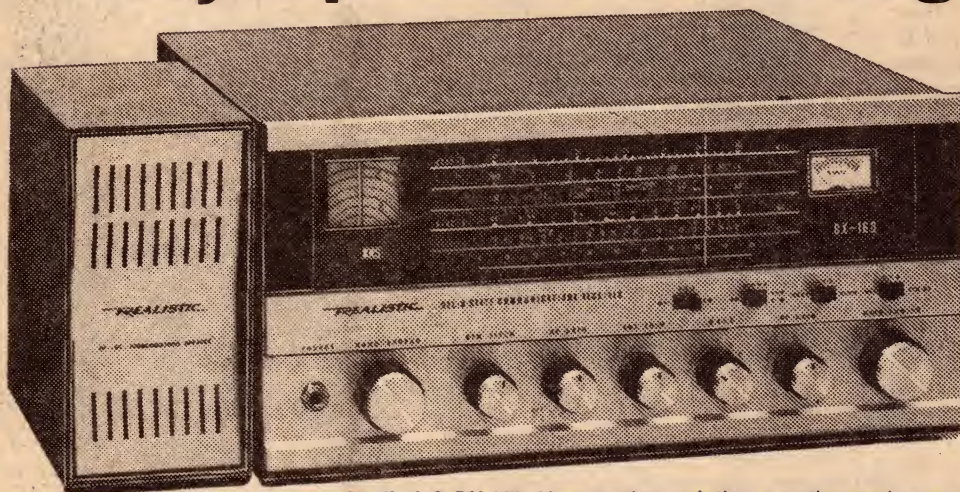

**5-Band Communication Receiver for a World of Listening Enjoyment!**

150-400 kHz Longwave  
535-1600kHz AM Band  
1.5-4.5 MHz Shortwave  
4.5-13 MHz Shortwave  
13-30 MHz Ham and CB

**Covers 5 Action Bands, Including All CB Channels AM and SSB**

**199<sup>95</sup>**

Including matching speaker

**Realistic® DX-160.** Hear marine, aviation, weather and more on longwave. Tune in short-wave programmes and news from major cities around the globe. Get Hams and CB operators, WWV time signals, standard AM. A product detector and variable BFO bring SSB and CW reception, too. Eleven front panel controls, including electrical bandspread tuning and calibrated logging scale. With FET's in all critical stages. Zener stabilisation, noise limiting in IF and audio stages. Illuminated "S" meter. Headphone jack plus instruction manual. For 240 VAC or 12VDC neg. gnd.

20-152




**Patrolman CB-8**

**149<sup>95</sup>**

- Battery Condition/Signal Strength Meter
- Precision Fine-Tuning on All Bands
- Tunes: UHF, VHF-HI, VHF-air, VHF-Low, CB Shortwave, AM/FM

Tunes all CB channels, foreign broadcasts, police, planes, trains—more. Has 10.1cm speaker, squelch on CB/VHF/UHF, dial light, tone control, automatic AC-to-battery switching, FM-AFC, 1/4" headphone jack, telescoping antennas, jack for external SW/CB/FM/VHF antenna. Requires 6 "C" batteries. With AC cord.

12-763

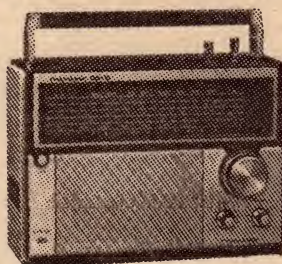

**Patrolman CB-6**

**119<sup>95</sup>**

- Tunes VHF-Low, VHF-HI, UHF, CB, AM, FM
- Automatic AC-to-Battery Switching
- All-Band Fine Tuning • Squelch Control

Hear CB channels, police and fire calls, trains, trucks and aircraft, plus AM/FM. Features big 10.1 cm speaker, 1/4" headphone jack, AFC on FM, dial light button, telescoping UHF and FM/CB/VHF swivel-mount antennas and external antenna jack. AC cord. Requires 4 "C" batteries.

12-761



**Shortwave Listeners' Guide**

Regular price 2.25  
**1<sup>99</sup> SALE**  
Lists stations by country, city, call letters, frequency, power, transmission times. With log.

62-2032




**CB-HAM-SWL Log Book**

**1<sup>75</sup>**

Keeps accurate records of stations heard. 64 pages.

62-2034

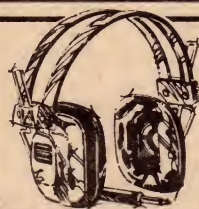

**Monophonic Headphones**

**7<sup>95</sup>**

Soft earcushions and adjustable plastic headband for comfortable listening. Standard 1/4" phone plug. 8 ohms impedance.

279-200



**Base Station Coax Cable Assemblies**

52-ohm polyfoam dielectric cable with PL-259 connectors factory installed on each end. 15.2m RG58/U.

278-971..... 16.95

15.2m RG8/U.

278-970..... 26.95

Low As **16<sup>95</sup>**



**Morse Code Practice Set**

**4<sup>99</sup>**

Buzzer, adjustable spring and contacts, headphone jack. Requires "D" battery.

20-1087



**High Speed, Brass Hand Key**

**4<sup>49</sup>**

Adjustable spring and contacts. Smooth ball-bearing pivots.

20-1084



**PL-259 Plug**

Regular price 2.69  
**1<sup>80</sup> SALE**  
Pkg. of 2 Pkg. of 2

278-205

UHF type connections, screw-on lock.



## THE AMATEUR SATELLITES — Continued

during which access can be assured. If anyone is interested to hear one of the OSCARs, but not so interested as to discover appropriate access times, all they can do is to leave a receiver tuned to one or the other of the satellites' beacon frequency and hope to hear it, during the course of a morning or evening.

It would be nice to say that this "lottery" situation could be avoided by acquiring tables from somewhere which would list the local time and the duration of every single pass for both Oscar satellites, for every day of the year and for a variety of population centres throughout Australasia. However, the difficulty and cost of publishing such lists would make their appearance most unlikely. Anyone requiring the information will have to derive it from less detailed — but available — sources.

Basic predictions are published by AMSAT and reproduced on a month by month basis in magazines such as "Amateur Radio", published by the Wireless Institute of Australia. They are also included in the weekly WIA broadcasts over amateur band stations. The predictions give the time in UTC of the first south-north equator crossing for each day, and the longitude where the crossings will occur.

Working from these data, it is possible to predict the time and the orbital track of passes for that day adjacent to any given location. It can be done by tedious longhand methods or by resort to a suitable computer or programmable calculator. Yet another option, which we will hopefully describe next month, is to make up a circular calculator which will display times and tracks, when fed with the key figures for each day.

### A SIMPLE METHOD

In the meantime, there is a simple approximation method which will indicate access times with about an 85% chance of being right. Suggested by John Dennis of the Dick Smith organisation, it provides a lot better chance of success than by simply relying on luck! This is what you do:

1. Refer to the prediction data for the particular satellite and note the first Equator crossing time for the day; it will

be expressed in UTC. To let you try your hand, we publish the data herewith for the month of September.

2. Add this time to the figures given in the tables below remembering that, when adding minutes, anything over 60 represents 1 hour, which you carry to the hours column. The answer will be in local standard time for the particular city (or state).
3. The calculated time usually gives the first of three possible passes. Listen at intervals of 1 hour 55 minutes for successive OSCAR 7 passes, and at 1 hour 43 minute intervals for OSCAR 8.
4. The times indicate when the respective satellites will be on the same latitude as the cities indicated. Start listening about 10 minutes earlier for the start of each pass.
5. When summer time is in operation, add 1 hour to the calculated times.

As an example, say you needed to work out the first evening pass of OSCAR 7 on September 1 for Sydney. From the prediction tables, you would obtain the figure 0012. Now add 1927 from the foregoing instructions to obtain the figure 1939 in EST, or 7.39pm.

So start listening at 7.29pm, for up to 20 minutes. Try again at 9.24pm and at 11.19pm.

Or suppose you were interested in OSCAR 8 for the same day. The prediction table gives a crossing time of 0011 and the evening pass figure from the table is 1827. Adding 0011 to 1827 gives 1838, or 6.38pm. Again, start listening about 10 minutes earlier, then listen again at 8.11 pm and at 9.54 pm.

Two obvious questions remain to be answered as far as the enthusiast listener is concerned: On what frequency can one expect to hear signals from the satellites and what form do they take?

Amateurs transmitting to OSCAR 7 and OSCAR 8 do so mainly in a frequency segment just below 146MHz and, to a lesser extent in a segment above 432 MHz. On certain days, transmissions from the satellites are confined to these same amateur bands and are therefore accessible only to those who have the appropriate receiving equipment.

#### OSCAR 7

| CITY      | MORNING | EVENING |
|-----------|---------|---------|
| Sydney    | 0522    | 1927    |
| Melbourne | 0523    | 1925    |
| Brisbane  | 0520    | 1929    |
| Adelaide  | 0451    | 1857    |
| Perth     | 0517    | 1922    |

#### OSCAR 8

| CITY      | MORNING | EVENING |
|-----------|---------|---------|
| Sydney    | 0551    | 1827    |
| Melbourne | 0552    | 1826    |
| Brisbane  | 0549    | 1829    |
| Adelaide  | 0521    | 1757    |
| Perth     | 0534    | 1810    |

# ALL RANGE EXTENDED

## LOW PROFILE TRANSFORMERS



#### 20VA CHASSIS OR FRAME MOUNTED

| Type No.  | Series Connections    | Parallel Connections   |
|-----------|-----------------------|------------------------|
| PL12/20VA | 12 volts at 1.67 amps | 6 volts at 3.33 amps   |
| PL15/20VA | 15 volts at 1.33 amps | 7.5 volts at 2.67 amps |
| PL18/20VA | 18 volts at 1.11 amps | 9 volts at 2.22 amps   |
| PL24/20VA | 24 volts at 0.83 amps | 12 volts at 1.67 amps  |
| PL30/20VA | 30 volts at 0.67 amps | 15 volts at 1.33 amps  |
| PL40/20VA | 40 volts at 0.50 amps | 20 volts at 1.00 amps  |

#### 40VA CHASSIS OR FRAME MOUNTING

| Type No.  | Series Connections    | Parallel Connections   |
|-----------|-----------------------|------------------------|
| PL12/40VA | 12 volts at 3.33 amps | 6 volts at 6.67 amps   |
| PL15/40VA | 15 volts at 2.67 amps | 7.5 volts at 5.33 amps |
| PL18/40VA | 18 volts at 2.22 amps | 9 volts at 4.44 amps   |
| PL24/40VA | 24 volts at 1.67 amps | 12 volts at 3.33 amps  |
| PL30/40VA | 30 volts at 1.33 amps | 15 volts at 2.67 amps  |
| PL40/40VA | 40 volts at 1.00 amps | 20 volts at 2.00 amps  |

#### 60VA CHASSIS OR FRAME MOUNTING

| Type No.  | Series Connections    | Parallel Connections          |
|-----------|-----------------------|-------------------------------|
| PL12/60VA | 12 volts at 5.00 amps | single secondary winding only |
| PL15/60VA | 15 volts at 4.00 amps | 6 volts at 6.67 amps          |
| PL18/60VA | 18 volts at 3.33 amps | 9 volts at 5.00 amps          |
| PL24/60VA | 24 volts at 2.5 amps  | 12 volts at 4.00 amps         |
| PL30/60VA | 30 volts at 2.0 amps  | 15 volts at 3.00 amps         |
| PL40/60VA | 40 volts at 1.5 amps  | 20 volts at 3.00 amps         |

Made in Australia and Guaranteed by:

# FERGUSON

FERGUSON TRANSFORMERS PTY. LTD.  
331 HIGH STREET, CHATSWOOD. N.S.W. 2067.



## SATELLITES — Cont

However, on other days, when the satellites are operating in what is referred to as "mode A", they transmit in the "10 metre" amateur band, between frequency limits of about 29.4 and 29.5MHz. These signals are, of course, accessible to anyone with a high quality general-coverage communications receiver.

OSCAR 7 transmits in mode A one day in every 3. In fact the pattern BBA, BBA commenced on Jan. 1, 1978 and, if you want to, you can go through a calendar and mark it accordingly. OSCAR 8 operates on mode A during weekdays. As a further guide, the mode for each day is usually indicated in the same tables which list crossing times. Fairly obviously, there is no point in worrying about a satellite on days when the 29MHz signal is not going to be available anyway.

One other point to watch is that the mode changes at midnight GMT, which corresponds to 10am EAST. Therefore morning passes near Australia which occur before 10am EAST will still be in the mode for the previous day.

You may have noticed that we used the "about" in an earlier reference to frequency. This was quite deliberate because of Doppler effect. As a satellite speeds towards the receiving point, its

signal in the 29MHz band appears to be about 550Hz high. It assumes its nominated frequency when the satellite is overhead (or at the same latitude) and then moves towards 550Hz low as the satellite speeds towards the distant horizon. Therefore, while satellite transmitter frequencies can be nominated, listeners must be prepared to nudge the tuning, as necessary.

The transmissions on the 29MHz band are normally in CW (code) or SSB (single sideband telephony) and the communications receiver must be used in CW and/or SSB mode, preferably upper sideband. Fairly obviously, it must be of a type which is sufficiently stable to cope with 10-metre SSB and calibrated with sufficient accuracy to be set to the required frequencies.

If you are expecting an OSCAR 7 pass, set the receiver to 29.502MHz and listen for bursts of 20wpm code. This will be the on-board beacon signal, which serves to identify the satellite and also to indicate various parameters within which the equipment is working. Having heard the beacon, explore the band 29.4 to 29.5MHz, on the alert for amateur traffic. Expect only brief exchanges, because satellite QSOs are not of the protracted, wordy kind.

For OSCAR 8, the beacon operates on 29.402MHz but traffic is in the same segment as for OSCAR 7: 29.4 to 29.5MHz. Reports indicate that the signal from OSCAR 8 is usually the

## UTC: FIRST S-N EQUATOR CROSSING

| DATE    | OSCAR 7 | OSCAR 8 |
|---------|---------|---------|
| Sept 1  | 0012 B  | 0011 A  |
| Sept 2  | 0106 B  | 0017 J  |
| Sept 3  | 0005 A  | 0022 J  |
| Sept 4  | 0060 B  | 0027 A  |
| Sept 5  | 0154 B  | 0032 A  |
| Sept 6  | 0053 A  | 0037 X  |
| Sept 7  | 0148 B  | 0043 A  |
| Sept 8  | 0047 B  | 0048 A  |
| Sept 9  | 0141 A  | 0053 J  |
| Sept 10 | 0040 B  | 0058 J  |
| Sept 11 | 0135 B  | 0103A   |
| Sept 12 | 0034 A  | 0103 A  |
| Sept 13 | 0128 B  | 0114 X  |
| Sept 14 | 0028 B  | 0119 A  |
| Sept 15 | 0122 A  | 0124 A  |
| Sept 16 | 0021 B  | 0129 J  |
| Sept 17 | 0116 B  | 0135 J  |
| Sept 18 | 0015 A  | 0140 A  |
| Sept 19 | 0109 B  | 0002 A  |
| Sept 20 | 0009 B  | 0007 X  |
| Sept 21 | 0103 A  | 0012 A  |
| Sept 22 | 0002 B  | 0017 A  |
| Sept 23 | 0057 B  | 0023 J  |
| Sept 24 | 0151 A  | 0028 J  |
| Sept 25 | 0050 B  | 0033 A  |
| Sept 26 | 0144 B  | 0038 A  |
| Sept 27 | 0044 A  | 0043 X  |
| Sept 28 | 0138 B  | 0049 A  |
| Sept 29 | 0037 B  | 0054 A  |
| Sept 30 | 0132 A  | 0059 J  |

stronger of the two, presumably because it is at a lower altitude.

Last but not least, there is the matter of receiving antennas. Amateur operators who are keen on satellite communication may well end up with complicated beam arrays, which are both steerable and tiltable, in order to transmit and receive the strongest possible signals. Fortunately, a listener on 29MHz does not need to go to these lengths to add a satellite to his/her list of conquests.

As we mentioned earlier, one can usually do reasonably well with a CB base station antenna, or with an outdoor wire antenna.

However, a contributor to QST magazine has suggested a type of antenna which, he says, works particularly well. Suspend a loop of wire 10.4m long, hopefully about 3m above ground; it can be in a circle, square or triangle, which ever is convenient. Where the ends come together, attach a quarter-wave matching stub (1.7m of 70-ohm coax. cable) and then carry on to the receiver with 52-ohm coax. We haven't tried it, but it's an interesting idea. One other interesting suggestion is worthy of a mention: If you can't cope with the code at 20wpm, record it on an open-reel tape machine and play it back later at reduced speed. However, most enthusiasts will be happy enough merely to identify the signal and to tune to the hasty chatter of amateurs using SSB telephony.



## VIDEO TECHNICS

SHOP 1, BONDI JUNCTION PLAZA, 500 OXFORD ST, BONDI JUNCTION.  
N.S.W. 2022. TEL: 387-2555.  
3RD FLOOR, EQUITABLE LIFE BUILDING, 301 CORONATION DRIVE,  
BRISBANE 4064. PH. 36 1257.

### 3 HOURS VCR VIEWING



3 hours continuous recording/playback. 1-2-3 operation simplicity. Video head and azimuth recording system: key to perfect picture reproduction. The ingenious yet simple "M" loading system, low 35 watts power consumption.

### VIDEO MOVIES

#### FULL LENGTH FEATURES — MANY TITLES AVAILABLE

These movies suitable for all U-matic machines.

Philips and Grundig 1 hour and 2 hour video machines.

Movies available in all classifications from G to R rating.


### VIDEO EQUIPMENT —

Sony, Akai and JVC Colour and BW Portopacks. We have several BW Portopacks traded on colour sets. Also agents for JVC, National, Sony and Nec Umatic equipment. All formats and brands colour and BW recorders, editors, generators and blank video tapes available. New and used equipment. Trade and terms.

Specials. Also transfers from Super 8 film to video tape.
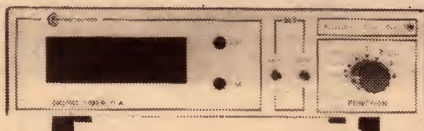
### SPECIAL CLOCK TIMERS

Can be set to switch equipment up to 4 days ahead.



Starting time  
accurate to a second

**\$195 + P.P.**

FRANCHISEES REQUIRED FOR S.A., W.A., VICTORIA AND TASMANIA



# Get started today on your future career.

To get the job you really want let ICS help you get the qualifications you need. Take the first step to change your future and choose a career from the top careers listed below, then mail the coupon. In just a few days you'll receive the ICS career guide on the career of your choice. Inside you'll find all you want to know about that career. The opportunities; the immediate benefits; how the course has helped thousands of students succeed in the career of their choice; and how the ICS method of home study will help you succeed—because you study in your own home, at your own pace.

Mail the coupon now. And start on the way to an exciting new future.

## Civil and Structural Engineering

Civil Engineering  
Surveying and Mapping  
Basic Structural and Concrete Engineering  
Basic Structural Engineering  
Overseer of Works

## Mechanical Engineering

Mechanical Engineering  
Technology  
Works Management  
Hydraulic and Pneumatic Power  
Boiler Inspector  
Boiler Attendant  
Complete Steam

## Electrical Engineering

Basic Electrical Engineering  
Electric Motor Repair and Servicing  
Industrial Electrician  
Electrical Mechanic

## Drafting

Drafting  
Mechanical Drawing and Tool Design  
Electrical and Electronic Drafting  
Structural and Architectural Drafting  
Drafting for Air Conditioning  
Builder's Draftsman and Plan Drawing

## Electronics

Electronics Technician  
Audio, Radio and Hi-Fi Sound Systems Specialist  
Communications  
Broadcasting Specialist  
Electronic Computer Servicing Specialist  
Industrial Electronics Specialist  
Basic Electronics  
Electronic Instrumentation and Control Systems  
Electronic Technology  
Electronics Maintenance  
Radio-Electronic Telemetry  
Electric Motor Repair and Servicing

## Sales and Marketing

Australian Marketing Institute Diploma  
Sales Representative  
Sales Management  
Retail Merchandising  
Modern Marketing Management

## Advertising and Public Relations

Public Relations  
Copywriting  
Advertising Layout and Illustration

## Computer Programming and Data Processing

Computer Programming and Data Processing  
General Computer Programming  
Computer Systems Analysis  
Cobol Programming  
Computer Servicing Specialist  
Institution of Fire Engineers  
Membership  
Graduateship

## Automotive Servicing

Automotive Mechanic  
Institute of Automotive Mechanical Engineers — Member & Associate Member  
Queensland 'A' Grade Motor Mechanic  
Queensland 'B' Grade Motor Mechanic  
Senior Motor Mechanic or 'A' Grade Certificate of Victorian Automobile Chamber of Commerce  
Basic Motor Engineering  
Automatic Transmission Specialist  
Automobile Engine Tune-up  
Automobile Electrician  
Do-It-Yourself Servicing  
Panel Beating and Spray Painting  
Diesel Mechanic  
Air Conditioning for Automobiles

## Writing

All Media Professional Writing  
Professional Writing  
Freelance Journalism  
Short Story Writing  
Script Writing — TV, Radio, Film  
Copywriting

## Art

Commercial Art  
Recreational Art  
Watercolour and Oil Painting  
Cartooning  
Showcard and Sign Production  
Basic Art  
Watercolour Painting  
Oil Painting  
Showcard and Ticket-writing  
Sign Painting and Designing  
Advertising Layout and Illustration

## Hotel/Motel Management

Hotel/Motel Management  
Restaurant and Catering Management  
Financial Management for Hotels and Motels  
Club Management  
Hotel/Motel Owners

## Accountancy

Institute of Chartered Secretaries and Administrators — A.C.I.S. Diploma  
Commercial Education Society of Australia — Diploma in Accountancy  
Practical Accounting  
CES Bookkeeping and Office Practice Certificate  
Costing  
Elementary Bookkeeping


## Building and Architecture

Building Contractor  
Building Sciences  
Building Supervisor  
Architectural Assistant  
Carpentry and Joinery  
Basic Building  
Plumber  
Builder's Draftsman and Plan Drawing  
Carpenter  
Bricklayer

*This list is correct at the time of submission for publication and may vary.*

## ICS

**International Correspondence Schools**  
400 Pacific Hwy, Crows Nest, N.S.W. 2065.  
Tel: 43 2121  
18-20 Collins St. Melbourne, VIC. 3000.  
Tel: 63 7327  
New Zealand: 182 Wakefield St, Wellington.

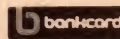 **Your bankcard is welcome at ICS.**

POST THIS COUPON TODAY

**ICS** International Correspondence Schools  
400 Pacific Hwy, Crows Nest NSW 2065. Tel: 43-2121  
18-20 Collins St. Melbourne 3000. Tel: 63-7327  
New Zealand: 182 Wakefield St. Wellington.

Please provide me with Career information on \_\_\_\_\_

Mr Mrs Miss \_\_\_\_\_

Address \_\_\_\_\_

Postcode \_\_\_\_\_

Occupation \_\_\_\_\_ Age \_\_\_\_\_

274 780

## Colour TV Servicing Technician

TV Service Technician  
TV Principles  
TV Engineering  
TV Servicing

## Air Conditioning and Refrigeration

Air Conditioning and Refrigeration Technology  
Drafting for Air Conditioning  
Domestic Appliance and Refrigeration Servicing  
Air Conditioning for Automobiles

## Business Management

Institute of Business Administration Diploma in Management  
Commercial Education Society of Australia — Diploma in Management  
Works Management  
Personnel Management  
Office Management  
Small Business Owners  
Modern Marketing Management  
Modern Management Stores Supervision  
Purchasing and Supply Management  
Club Management

## Secretarial

Pitman's Stenography  
Gregg Stenography  
Clerk-Typist  
Gregg Shorthand with Speed Building  
Gregg Speed Building  
Pitman's Shorthand  
Elementary Bookkeeping  
Typewriting

## Interior Decorating

Interior Decoration Program

## Photography


Photography Program

## Creative Leisure

Dressmaking  
Dressmaking and Pattern Cutting  
Typewriting  
Guitar


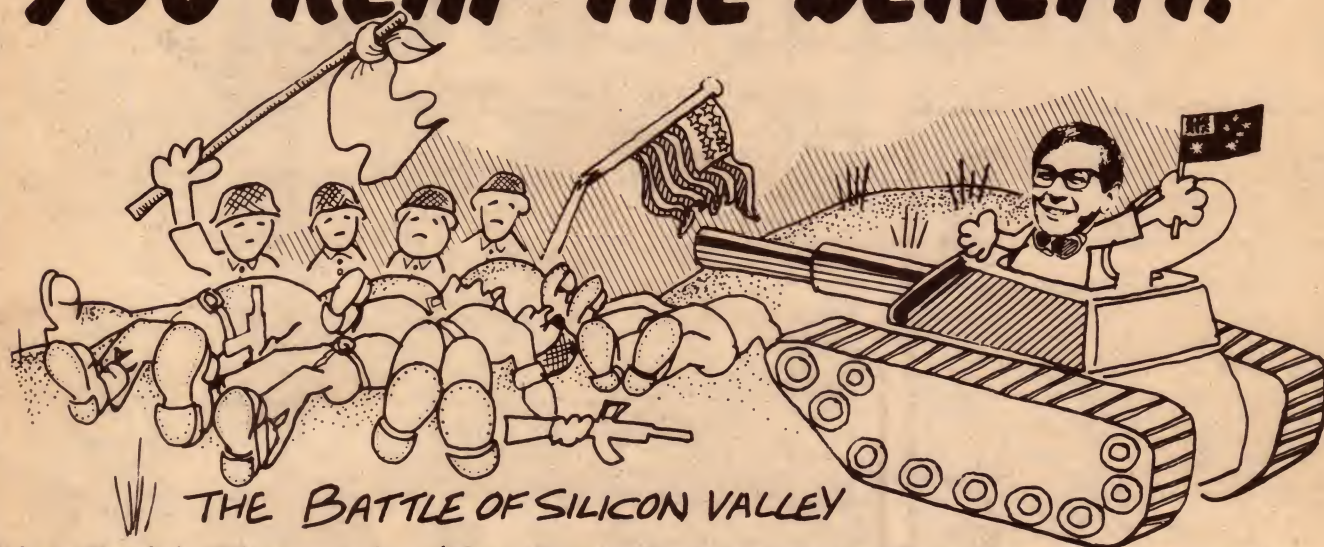
# DICK SMITH ENDS THE SEMICONDUCTOR PRICE WAR ***YOU REAP THE BENEFIT!***



Dick Smith Electronics (the Australian company) will better any price offered on an equivalent quality semiconductor by the U.S. controlled Cema/Silicon Valley Group.

**Yes!** This means that you can purchase your semiconductors from us at the cheapest possible price — and you don't have to buy the 'Uncle Sam' pack system (e.g. 13 diodes in a pack!) — we still sell **just one**.

And you'll be buying from a fully Australian owned company — your one stop electronics shop.

**Look at these items we are ALREADY cheaper on:**

Price comparison based on prices published in July 1978 ETI advertisement.

BC107's & BC108's: 25c each (not 42c each in a pack of three!)  
BC159's: 30c each (theirs are 36c each — still in packs of three)  
MJ2955 & 3055's: \$1.19 each for prime spec MOTOROLA devices (not \$1.19 each for an unknown pedigree)  
2N3055's: 95c each — again prime spec! (theirs \$1.19 each)

NE555's: 40 cents each — only prime spec Fairchild. TRY and beat our price for one-off! (theirs are 62 cents each)  
723's in metal can: \$1.20 each (why pay \$1.49 each?)  
78XX series regulators: \$1.25 each (you guessed it — \$1.33 each)  
79XX series regulators: \$1.75 each (you beat the \$1.83, don't you?)

For us to better any advertised price, simply call in to our stores with the advert showing the price offered by Silicon Valley on equivalent items (or post advert in with your mail order). We guarantee to better any price shown for **single item quantities**. Where a quantity price is shown (e.g. 2, 3 or more to a pack) we guarantee to better the pack price if you are prepared to buy that quantity. Remember this applies to advertised prices and this offer expires on 30th September, 1978.



# COMPARE OUR ONE-OFF PRICES...

## TRANSISTORS

BC107 (silicon NPN, general purpose amplifier, etc) .. Cat Z-1300 .. 25c each  
 BC108 (silicon NPN general purpose amplifier, etc) .. Cat Z-1308 .. 25c each  
 BC109 (Silicon NPN general purpose low noise amp, etc) .. Cat Z-1319 .. 27c each  
 BC157 (Silicon PNP general purpose amp, etc) .. Cat Z-1340 .. 33c each  
 BC158 (silicon PNP general purpose amp, etc) .. Cat Z-1348 .. 33c each  
 BC159 (silicon PNP general purpose amp, etc, low noise) .. Cat Z-1359 .. 30c each  
 BD139 (silicon NPN power transistor 80V, 0.5A) .. Cat Z-1443 .. 95c each  
 BD140 (silicon PNP power transistor, 80V 0.5A) .. Cat Z-1444 .. 95c each  
 2N2646 (unijunction) Cat Z-1786 .. \$1.20 ea.



## NE555

Try and buy better! Yes, our NE555 timer IC's are only 40 cents each in one-off quantity. These are prime spec Fairchild 8 pin DIL. Cat Z-6145

# 40c



## LINEARS

LM301 (General purpose operational amplifier) .. Cat Z-6040 .. \$1.05  
 LM380 (5 watt audio power amplifier module) .. Cat Z-6080 .. \$2.00  
 UA741 (General purpose operational amplifier) .. Cat Z-6382 .. 60c  
 CA3130 (FET input operational amplifier) .. Cat Z-6025 .. \$2.50  
 723 in metal can (3 - 37V IC voltage regulator) .. Cat Z-6360 .. \$1.20  
 723 in DIL pack Cat Z-6362 .. \$1.00



## READOUTS & LEDS

Incredible readout bargain!  
 Brand new, prime spec: as used by Electronics Australia.



LT303 - common cathode (exact equivalent to Texas TIL313 and Hewlett Packard 5082-7740) 1-9: \$1.50 10+: \$1.30

from \$1.30 ea!

LEDS AT BARGAIN PRICES TOO  
 Prime spec, hundreds of uses. Be quick!

Small red - Cat Z-4010  
 Large red - Cat Z-4030




ONLY 22c ea - OR 20c ea 10+
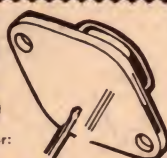
## MJ 2955 MJ 3055

These aren't just ANY transistor: they're prime spec, hard-to-get Motorola TO-3 types. Outstanding value!

MJ2955 (silicon PNP power transistor, 150W 15A) .. Cat Z-1800 .. \$1.15 ea  
 MJ3055 (silicon NPN power transistor, 150W 15A) .. Cat Z-1804 .. \$1.15 ea



## MJE 2955 MJE 3055

MJE2955 (silicon PNP power transistor/driver, 90W) .. Cat Z-2005 .. \$1.50 ea  
 MJE3055 (silicon NPN power transistor/driver, 90W) .. Cat Z-2008 .. \$1.50 ea

PRIME  
SPEC  
FAIRCHILD  
DEVICES



## 2N3055

The famous 2N3055 - probably the most-used power transistor around. Reliable, prime spec Cat Z-2145 .. 95c each!

## DIODES

OA91 (germanium general purpose - great for crystal sets!) Cat Z-3040 .. 25c each  
 1N914 (silicon general purpose signal diode) .. Cat Z-3120 .. 12c each  
 1N4002 (silicon rectifier diode - 1A, 100V) .. Cat Z-3202 .. 15c each  
 1N4004 (silicon rectifier diode - 1A, 400V) .. Cat Z-3204 .. 20c each  
 1N4007 (silicon rectifier diode - 1A, 1000V) .. Cat Z-3207 .. 30c each  
 DS5404 (silicon rectifier diode, high power 200V, 3A) .. Cat Z-3222 .. 45c each  
 1N5408 (silicon rectifier diode, high V & I 1000V, 3A) .. Cat Z-3228 .. 65c each



## REGULATORS

78XX series (3 terminal 1 amp positive voltage regulators)

7805 (5V) Cat Z-6545 .. \$1.25  
 7812 (12V) Cat Z-6552 .. \$1.25  
 7815 (15V) Cat Z-6554 .. \$1.25

79XX series (3 terminal 1 amp negative voltage regulators)

7905 (5V) Cat Z-6555 .. \$1.75  
 7912 (12V) Cat Z-6556 .. \$1.75  
 7915 (15V) Cat Z-6557 .. \$1.75



### PLEASE NOTE:

Where possible, all components supplied will be of the type no. shown here. However, during times of component shortages, substitutions may be necessary.

Where substitutes are supplied, they will be the exact electrical equivalent. In many cases, they will simply be other manufacturer's markings on the same component.

## 4000 SERIES C-MOS



|      |                                        |            |          |
|------|----------------------------------------|------------|----------|
| 4000 | Dual 3 input NOR gate plus inverter    | Cat Z-5600 | 39c each |
| 4001 | Dual 2 input NOR gate                  | Cat Z-5601 | 39c each |
| 4002 | Dual 4 input NOR gate                  | Cat Z-5602 | 39c each |
| 4006 | 18 stage static shift register         | Cat Z-5606 | \$2.00   |
| 4007 | Dual complementary pair plus inverter  | Cat Z-5607 | 39c each |
| 4009 | Hex buffer/converter, inverting        | Cat Z-5609 | 89c each |
| 4011 | Quad 2 input NAND gate                 | Cat Z-5611 | 39c each |
| 4012 | Dual 4 input NAND gate                 | Cat Z-5612 | 39c each |
| 4013 | Dual D type flip-flop with reset       | Cat Z-5613 | \$1.00   |
| 4014 | 8 stage static shift register          | Cat Z-5614 | \$1.75   |
| 4016 | Quad bi-lateral switch                 | Cat Z-5616 | \$1.00   |
| 4017 | Decade counter/divider                 | Cat Z-5617 | \$1.75   |
| 4018 | Presettable divide by 'N' counter      | Cat Z-5618 | \$1.75   |
| 4021 | 8 stage static shift register          | Cat Z-5621 | \$1.75   |
| 4022 | Divide by 8 counter with 8 decoder o/p | Cat Z-5622 | \$1.65   |
| 4023 | Triple 3 input NAND gate               | Cat Z-5623 | 39c each |
| 4024 | 7 stage ripple counter                 | Cat Z-5624 | \$1.35   |
| 4025 | Triple 3 input NOR gate                | Cat Z-5625 | 39c each |
| 4027 | Dual JK flip-flop with reset           | Cat Z-5627 | \$1.00   |
| 4028 | BCD to decimal decoder                 | Cat Z-5628 | \$1.50   |
| 4029 | Presettable up/down 4 stage counter    | Cat Z-5629 | \$1.35   |
| 4030 | Quad exclusive OR gate                 | Cat Z-5630 | 70c each |
| 4049 | Hex buffer/converter, inverting        | Cat Z-5649 | \$1.00   |
| 4050 | Hex buffer/converter, non inverting    | Cat Z-5650 | \$1.00   |
| 4051 | 8 channel multiplexer/demultiplexer    | Cat Z-5651 | \$1.35   |
| 4068 | 8 input NAND gate                      | Cat Z-5668 | 39c each |
| 4071 | Quad 2 input OR gate                   | Cat Z-5671 | 39c each |
| 4081 | Quad 2 input AND gate                  | Cat Z-5681 | 39c each |
| 4416 | Double pole double throw switch        | Cat Z-5710 | 80c each |
| 4426 | Decade counter/7 seg. dec/ driver      | Cat Z-5715 | \$2.50   |
| 4449 | Economy Hex inverter                   | Cat Z-5720 | 55c each |
| 4511 | BCD to 7 seg. latch/decoder/driver     | Cat Z-5730 | \$1.75   |
| 4518 | Dual BCD up counter                    | Cat Z-5740 | \$1.95   |
| 4520 | Dual 4 stage binary up counter         | Cat Z-5742 | \$1.95   |
| 4528 | Dual re-triggerable monostable multi.  | Cat Z-5748 | \$2.00   |

## \*\*\*\*\*EXPRESS MAIL ORDER SEMICONDUCTORS\*\*\*\*\*

If your mail order is for over \$30 worth of semiconductors, we will despatch it post and packing FREE! Simply request free P&P when you place your order.

## \*\*\*\*\*OVER TEN YEARS OF RELIABLE MAIL ORDER SERVICE\*\*\*\*\*

# DICK SMITH ELECTRONICS



**SYDNEY** 125 York Street, SYDNEY. Ph. 29 1126  
 147 Hume Hwy, CHULLORA. Ph. 642 8922  
 162 Pacific Hwy, GORE HILL. Ph. 439 5311  
 30 Grose Street, PARRAMATTA. Ph. 683 1133

**MELBOURNE** 399 Lonsdale Street, MELBOURNE. Ph. 67 9834  
 656 Bridge Road, RICHMOND. Ph. 42 1614  
**BRISBANE** 166 Logan Road, BURANDA. Ph. 391 6233  
**ADELAIDE** 203 Wright Street, ADELAIDE. Ph. 212 1962

**MAIL ORDERS** P.O. Box 747, Crows Nest, N.S.W. 2065. Post and packing extra.

Dealers across Australia.

SHOPS OPEN 9AM to 5:30PM  
 (Saturday 9AM - 12 noon)  
 BRISBANE 1 2 Hour earlier

ANY TERMS OFFERED ARE TO  
 APPROVED APPLICANTS ONLY

Many times available from the  
 Dick Smith Electronics Centres at

**GRACE BROS**  
 Broadway - Bondi - Cheltenham - Liverpool  
 Miranda - Mt Druitt - Paramatta - Rydalmere  
 and Warrington Mall





# Upgraded 200MHz digital frequency meter

## 2nd article completes the construction details

In this second article on the Upgraded 200MHz digital frequency meter, we complete the description of construction and give details of setting-up adjustments and calibration. Also included are useful trouble-shooting procedures and some hints on using the new frequency meter.

by LEO SIMPSON

Construction proceeds with installation of the rotary input switch. Cut the switch shaft to a suitable length for the knob to be used and loosen the clicker plate so the switch can be rotated easily. This is done by bending the clicker plate with a screwdriver to reduce the tension on the detents.

Now refer to the wiring diagram on page 44 of last month's issue. Note that one of the shielded cables has its shield terminated to the underside of the PCB. Cut and strip a 50mm length of shielded cable (any of the lighter audio shielded cable will do) and terminate it at the PCB, leaving the other end free.

Fit Richco 10mm supports to the PCB and mount the whole assembly in the chassis. Alternatively, use screws and nuts or spacers to support the PCB assembly 10mm off the chassis. Fit the regulator IC to the chassis. Its three terminals should be perpendicular to the chassis (rather like the dead flies in the flyspray ads). Connection is made via

short tinned copper wires from the regulator terminals to the appropriate PC pins.

Now connect the pair of wires from the transformer secondary to the PCB and you are ready to switch on. Do not complete the remainder of the wiring at this stage. This can be finished after initial checks are made, so check the power supply wiring and then turn the unit on. Check the 5V and 9V supply rails. The 5V rail should be between 4.8 and 5.2V while the 9V rail is less critical — say 8.5 to 9.5V.


While you are at it, you should also check that the 5V supply is actually connected to the supply pin of each of the IC's.

All digits should be alight and all should be zero, except the last on the right which may show "1". The fun begins if you find missing segments or digits. If this occurs you should be able to trace the fault by following the following text.


Faults such as these can be traced with the aid of a multimeter switched to a low resistance range. Switch off the power to the frequency meter and remove the mains plug from the wall socket.

Remember the following points to help localise the fault. First, the three most significant digits are associated with the left-hand 74C926, while the other four are associated with the right-hand 74C926 (looking from above the PCB). Second, within the above two groupings, all segment lines are common.

Table 1 shows the pin connections to the LT-303 LED displays and the corresponding terminals of the 74C926's. This enables the segment and digit drive lines to be checked for continuity. One point which may confuse the issue when these checks are made is that pins 1, 7, 8 and 14 of the LT-303 device are omitted and so are not shown on the leadout diagram.

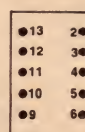

LT-303  
REAR VIEW

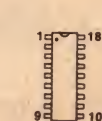

74C926 VIEWED  
FROM ABOVE


TABLE 1

|               | LT-303    | 74C926 |
|---------------|-----------|--------|
| segment A     | pin 13    | pin 15 |
| segment B     | pin 12    | pin 16 |
| segment C     | pin 11    | pin 17 |
| segment D     | pin 6     | pin 1  |
| segment E     | pin 5     | pin 2  |
| segment F     | pin 3     | pin 3  |
| segment G     | pin 4     | pin 4  |
| decimal point | pin 10    | —      |
| cathode       | pins 2, 9 | —      |

TABLE 2

|           | 74C926 |
|-----------|--------|
| 1st digit | pin 7  |
| 2nd digit | pin 8  |
| 3rd digit | pin 9  |
| 4th digit | pin 10 |

Table 2 identifies the lines connecting the bases of the digit driver transistors to the 74C926. Another wrinkle to remember here is that the left-hand

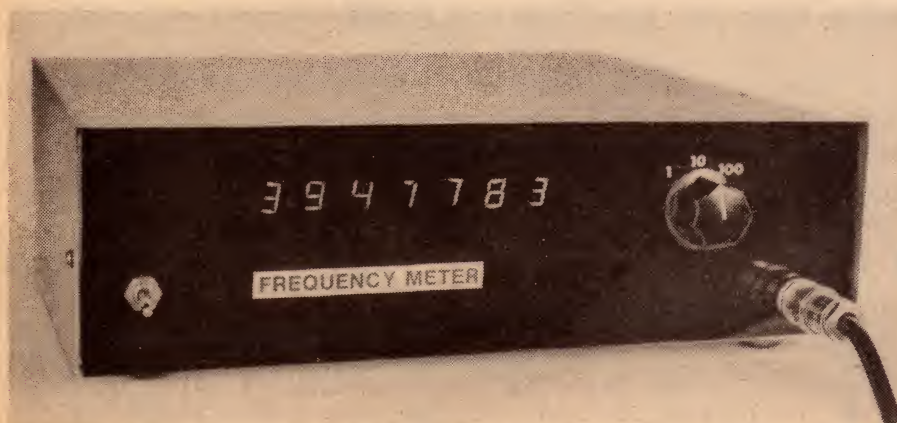

Always use shielded input cables to minimise the pick-up of random noise.



74C926 does not drive its "1st" digit, ie, pin 7 has no connection.

We can provide a few illustrations of how trouble-shooting this part of the circuit might proceed. If, for example, the second most significant digit is extinguished, check continuity between the appropriate transistor base and pin 9 of the left-hand 74C926. These and other continuity checks can be made without removing the PCB from the chassis.

If there is continuity, apply power and short the digit drive transistor between collector and emitter. If the digit lights, try connecting a resistor of a few hundred ohms between base and collector of the transistor. If the display lights up again, the transistor is exonerated and the 74C926 is defunct.

If, on the other hand, the LED display refuses to light with the above tests, try shorting pin 9 of the display to pin 9 of the adjacent display. If it now lights, check continuity in the transistor's collector and emitter circuits. If the display has still not lit, it is probably headed for that great big PCB in the sky!

In comparison with diagnosing missing digits, missing segments are easy to pick. Note that, at this stage, you cannot check the "G" segments since they are not lit when zeros are displayed. If you are really keen to check the "G" segments, short pin 4 to pin 3 of any LT-303 and all the "G" segments of that particular group of three or four digits should light.

Note that when we are suggesting shorting across components, it should only be done briefly to avoid possible damage.

With all LED displays functioning, you can now proceed to the next step. This consists of checking the 10116 input stage. It is possible, that during the foregoing tests, all LED displays were not showing zeros. Some of the least significant digits may have been showing random counts up to several hundred. It should be possible to reduce this count to zero or a very low figure by tweaking the 1k preset pot association with the 10116.

Now put your finger on the input to the 10116. The display should now show a large random count which is updated once every two seconds. That being the case, remove finger and check that display reverts to zero. If no count appears, there is trouble with the 10116 or following 7490A and 7400.

The most likely place for the trouble will be with the 10116 and the level translator, T2. Voltages, around this area can be checked. As noted previously, the 10116 is a triple differential amplifier. It has differential inputs and outputs, all operating at ECL (emitter-coupled logic) levels of between 3.2V and 4.2V (at room temperature).

Pin 11 of the 10116 should be around 3.7V while the collector of T2 should sit at about 0.5V or 2V. If these voltages are not within reasonable limits then

the most likely cause is open-circuit or bridged PCB tracks.


A rough and ready check of the 7400 and 7490A can be made in the following way. Connect the wires associated with S1c (wires 2 and 3). Apply power and put your finger on the 10116 input again. At the same time, switch the range selector between "x1" and "x-10". The resulting random counts should show a ratio of approximately ten.

Now connect the remainder of the cables to the input switch. Fit the lid to the case and apply power, with the range set to "x1"; the readout should be zeros. Now take a low value resistor and use it to connect yourself to the in-

to suggest installing the shields is that with some units it will not be necessary.

The random count is largely a result of the high impedance input circuitry of the FET responding to the hash radiated by the multiplexed displays. You can get some idea of the intensity of this hash signal by positioning a portable radio near the display.

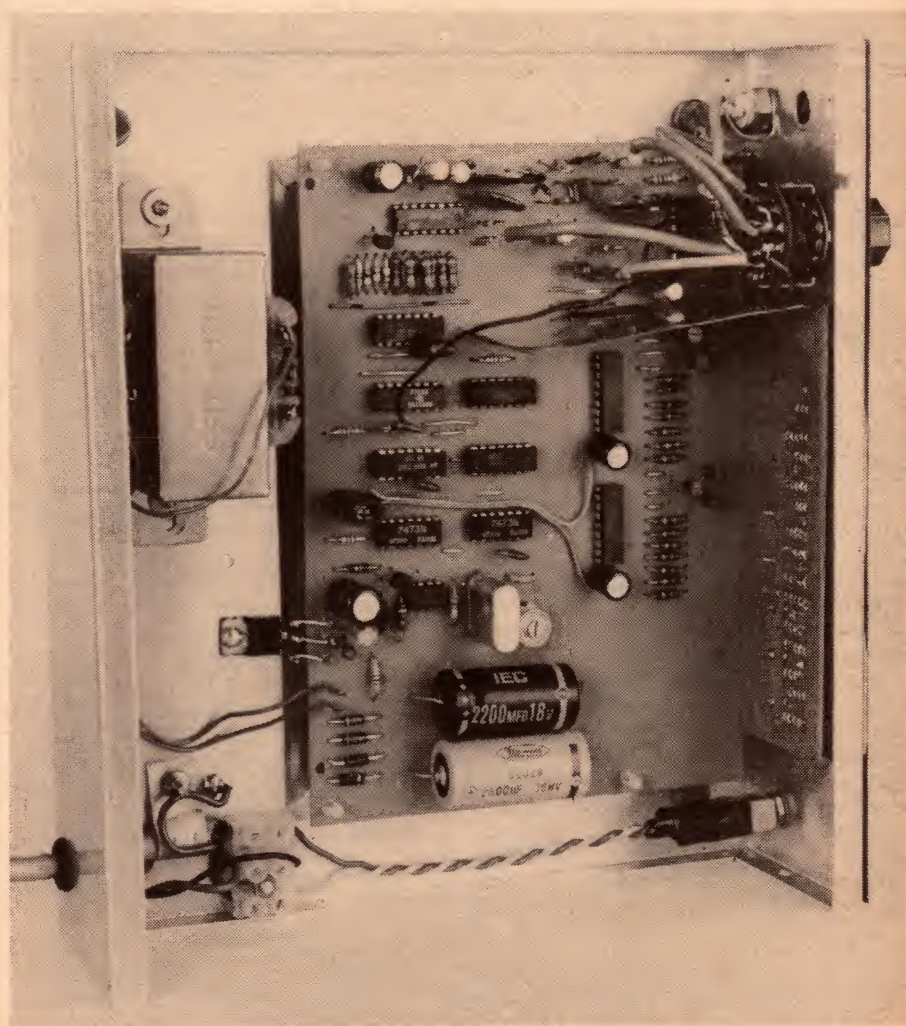We made our shields using tinfoil from tin cans. The shield for the top of the PCB is approximately 90 x 50mm, with a small rectangular cutout from the corner near the top of the front panel. This cutout measures approximately 5 x 15mm and provides clearance to enable the PCB assembly to be removed from the chassis. The



*With PCB standoffs and single-screw fixing of the regulator, the PCB assembly can be quickly removed from the chassis.*

put socket (the "finger" signal again). This should give a large random count on the readout. Removing this noise signal should revert the display to zeros.

If both of the above tests are negative, ie, the display shows a random count with no input signal, then the shields shown in the PCB photos last month must be installed. The reason we have left it till this late stage

shield is soldered to three PC pins on the board, as shown in the wiring diagram and photos.

The top shield can be installed without removing the PCB assembly from the chassis. With it installed, it may cure the hash count problem. If not, remove the PCB assembly and mount the small shield on the underside of the board. The same three PC pins are used for location and solder-



## 200MHz frequency meter

ing. This should cure the problem.

Final test for hash pickup should be with lid fitted and secured with screws, and with no input cable. An open-circuit input cable can pick up substantial signals from the immediate environment. More about this later.

The foregoing tests and procedures are by no means exhaustive and more searching tests can easily be made with the aid of a wide-bandwidth oscilloscope and signal generator. However, it is possible to check the workings of the "housekeeping" circuitry with the aid of a multimeter switched to a range 10V DC or lower. For example, you can check for the existence of 0.5Hz logic pulses on the "reset" and "latch enable" lines to the 74C926's (pins 5 and 13 respectively). Checking for the existence of reset pulses would be necessary if the display continued to increment by a fixed amount every two seconds and did not revert to zero when signal was removed. This would be most likely due to an open circuit in the "reset" line.

It is not possible to tell whether the 95H90 prescaler is working without the aid of a suitable signal source of 10MHz or more. At this stage of completion, switching to the "x100" range will probably produce a random count of the last three digits.


Calibration may now be performed. This consists of setting the timebase accurately and adjusting sensitivity of the 10116 front end and the 95H90 prescaler.

Without calibration, the frequency meter should have a typical accuracy of  $.01\% \pm 1$  count, which will be adequate for many applications. If calibration is to be performed, the frequency meter should be run for 15 minutes or more with the lid on to allow internal operating temperatures to stabilise.

Calibration is performed by tweaking the trimmer capacitor associated with the 5369 oscillator/divider chip. The trimmer provides only a small range of frequency adjustment. Any attempt to provide a larger range is likely to make the oscillator unreliable at the extremes of adjustment.

By far the easiest way to perform calibration is to use a CB transceiver or amateur transceiver for the 28MHz band as the reference source. There is no need to make any connection from the frequency meter to the transceiver. Just connect a short length of wire to the centre-pin of the input socket and dangle it close to the antenna or dummy load for the transceiver.

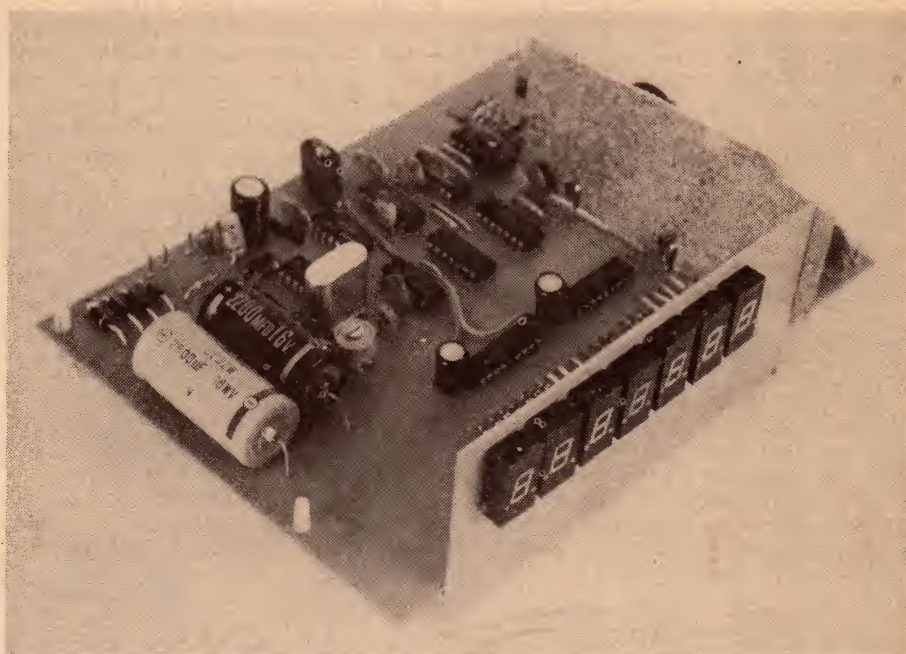The frequency meter must be switched to the "x10" range, otherwise no sensible reading will result. Note that when there is no signal from the transceiver, the short input wire will pick up ambient noise to produce a



*These two views of the PCB assembly show the main tinplate shield mounted. We made provision for decimal point switching on the PC patterns but omitted it in our prototype because it exacerbated hash pick-up.*



random count. This will be swamped out when the transmitter is keyed. The transmitter should be set for AM, not SSB, and there should be no modulation.

This means of calibration assumes that the transmitter frequencies have been accurately set. If there is any doubt on this score, then the validity of the method is dubious.

Another method of calibration is to make comparison measurements with a frequency counter of known accuracy. Yet another method is to use a signal generator and a broadcast or shortwave receiver. Set the generator for zero beat against a station of known fre-

quency (and precision). Then measure the output of the signal generator.

This method, like the others before it, is likely to involve some residual error. In this case the error would be mainly due to the difficulty of obtaining an exact zero beat. A typical error figure for this method could be 50Hz or more, plus the error involved in the transmitter frequency.

However, as long as the accuracy is within about 10 parts per million or so, you are probably achieving as good a result as can be expected from the modest timebase system employed. Higher precision is only available by employing an oven-controlled



timebase oscillator.

Sensitivity adjustment of the 10116 front end is not particularly critical and does not have a marked effect on the sensitivity. The adjustment is a compromise between sensitivity and noise pick-up, and need only be made if it is anticipated that the unit will be used for measuring audio signals of 100mV RMS or less.

If the unit has a high response to noise, ie, both internally generated hash and externally induced noise, the frequency displayed will be higher than actual. The effect will be worse at lower frequencies, as explained in the following paragraphs.


The first two amplifiers in the 10116 increase the input signal by a fixed order of gain which usually means that the second amplifier stage is driven to clipping. For large input signals the output from the second stage amplifier is heavily clipped and almost a square wave — the Schmitt trigger (third amplifier) then produces a clean square wave with short rise and fall times.

Note that the audio oscillator must be connected to the frequency meter via a shielded cable. Using unshielded wires, even short lengths, is sure to lead to errors due to induced noise.

If you have no source of low amplitude audio signals, do not worry about adjustment of the 10116. Just leave the 1k pot centred.

The 95H90 prescaler can be adjusted for optimum sensitivity in the following way. Feed in a VHF signal at 100MHz or higher and adjust the 500 ohm pot until a stable reading is obtained. If the source is a transmitter rather than a signal generator it should be connected via a suitable dummy load and voltage divider feeding no more than 1V RMS into the 50 ohm input.

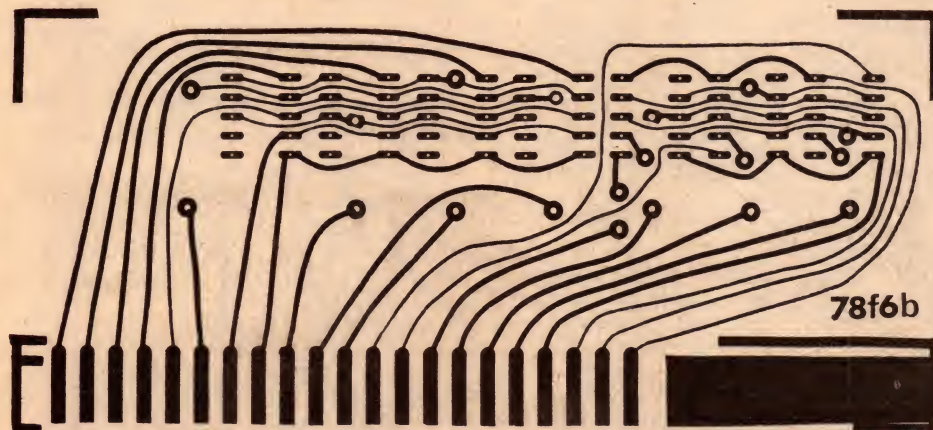With too small a signal to the 95H90, the reading will drop from its correct value and vary randomly — or it may drop to zero. With optimum sensitivity, the 95H90 will be sensitive to random noise when no input is applied. The last three digits will show a reading under these conditions. The 95H90 runs quite



Here is the actual size pattern of the readout PCB, held over from last month.

For small amplitude, low frequency signals, the input waveform may not be clipped at all and the signal takes a relatively long time to make positive-to-negative and negative-to-positive transitions. In one case the Schmitt trigger will make a high-to-low transition at input voltage V1 (say) while in the reverse case it makes a low-to-high transition at input voltage V2. The region between these two threshold voltages is known as the hysteresis of the Schmitt trigger. The longer the input signal is in this hysteresis region the more likely it is that noise spikes superimposed on the signal will produce an erroneous output and therefore a frequency count which is higher than it should be.

The adjustment on the 10116 affects the input bias and thus the hysteresis of the Schmitt trigger. An audio oscillator is needed for the adjustment. Feed in a low amplitude signal at 1kHz or lower. Note the reading and then increase the amplitude to 1V or more. If the reading is slightly reduced then noise is affecting the former reading.

warm to the touch when the optimum adjustment has been made.

To conclude, we have a few comments on the components. The 10116 is made by manufacturers other than Motorola. Signetics, for example, list it as GXB 10116. You may also substitute the very similar 10114 device if the 10116 is unavailable.

The Texas TIL-303 is definitely not an equivalent to the Liton LT-303 LED display. We are informed that the Dialight 745-0019 (distributed by Elcoma) is a suitable substitute.

If you built the previous frequency meter featured in March 1977 it is possible to adapt the readout PCB. The readout PCB cannot be attached to the main PCB, due to the fact that the edge connectors are more widely spaced and in a different order. Note that last point. You will have to attach the old readout PCB to the front panel by means of stand-offs and make connections with short lengths of wire.

An error has been found in the main PCB pattern. Pins 2, 3, 4, 6 and 10 of the 7490A should be earthed.

## printed circuits

- Accurately machine printed etched
- Phenolic & fibreglass-gold tin plated
- EA R & H ET Philips Mullard available
- Specials to your drawing
- POSTAGE small 80c large \$1.10

|         | \$   |                | \$      |          | \$    |
|---------|------|----------------|---------|----------|-------|
| ET638A  | 4.00 | ET248          | 2.30    | ET638B   | 3.00  |
| ET591   | 4.00 | ET810          | 2.80    | ET318    | 7.00  |
| 78TSCT  | 2.50 | 78PT7          | 2.50    | 78VBG7   | 3.50  |
| ET137B  | 2.80 | ET137A         | 3.50    | ET139    | 2.50  |
| ET717   | 3.50 | ET587          | 7.00    | ET640    | 16.50 |
| 78F6B   | 3.50 | 78N            | 2.80    | 78A06    | 2.80  |
| 246     | 4.00 | 489B           | 2.50    | 489A     | 2.80  |
| 78CD4   | 2.60 | 78PS5          | 2.50    | 78C5     | 3.20  |
| 78UP5   | 4.20 | ET140D         | 4.00    | ET140A   | 14.00 |
| ET1140P | 5.50 | ET136          | 2.50    | ET407B   | 7.50  |
| ET487A  | 7.50 | ET588 20       | 10.00   | 78NG4    | 3.00  |
| 78UT4   | 4.00 | 78EK3          | 3.30    | 78T3     | 3.60  |
| 78B2    | 3.00 | 78IA2          | 2.60    | ET450B   | 2.60  |
| ET450A  | 2.80 | ET716          | 1.00    | ET715    | 3.00  |
| ET486   | 3.20 | ET245          | 2.50    | 78C2     | 3.00  |
| 78AF2   | 3.00 | 78S3           | 2.60    | 78CF1    | 2.80  |
| 77CB12  | 2.60 | 77PH12         | 2.60    | 77PM12   | 3.50  |
| ET135   | 3.00 | ET586          | 2.60    | 77MX11   | 2.50  |
| 77SC11  | 3.80 | 77PS11         | 2.50    | 77UP6A   | 3.00  |
| 77MX11  | 2.50 | 77SC11         | 2.50    | 77PS11   | 2.50  |
| ET504   | 2.50 | ET585T/R       | 3.00    | ET635    | 2.80  |
| ET713   | 3.00 | ASC11          | 2.80    | 77UP11   | 6.50  |
| 77T3    | 3.00 | ET603          | 3.00    | ET583    | 2.50  |
| ET134   | 2.60 | 77AL8          | 2.50    | 77T10    | 2.50  |
| 77DVM9  | 2.80 | ET065          | 2.20    | ET071    | 2.20  |
| ET067   | 2.20 | ET063          | 2.50    | ET083    | 2.20  |
| ET072   | 2.50 | ET085          | 2.00    | ET084    | 2.50  |
| ET485   | 2.80 | ET484          | 3.00    | ET581    | 2.50  |
| ET481M  | 2.50 | ET582B         | 2.60    | ET582A   | 3.00  |
| ET547   | 2.50 | ET317          | 2.50    | ET712    | 2.50  |
| 77D7    | 2.50 | 77B7           | 2.80    | 77GL17   | 6.00  |
| 77UP6   | 3.50 | 77TTY7         | 2.80    | 77QB7    | 3.20  |
| ET631/2 | 4.50 | ET481PS        | 3.00    | ET444M   | 2.00  |
| ET444S  | 3.00 | ET316          | 2.50    | ET549A   | 2.50  |
| ET548   | 3.20 | 77TTY6         | 2.50    | HMS276   | 6.00  |
| 77PTV7  | 2.80 | 77PTY6         | 2.50    | ET133    | 2.60  |
| 77E05   | 3.50 | 77PRE5         | 2.50    | 77UP5    | 8.50  |
| ET081   | 2.20 | ET062          | 2.50    | ET546    | 2.50  |
| ET632U  | 4.00 | ET632          | 7.00    | 77TTY4   | 2.50  |
| 77CC4   | 3.00 | 77UP2          | 3.00    | ET132    | 2.50  |
| ET632C  | 8.00 | ET632B         | 6.50    | ET632A   | 6.50  |
| 77UT2   | 3.00 | 77F1B          | 2.50    | 77F1A    | 3.20  |
| ET633FR | 6.00 | 77UT2          | 3.00    | ET633    | 6.00  |
| ET632P  | 2.50 | ET632M         | 7.50    | ET482B   | 2.80  |
| ET482A  | 6.50 | 76CL12         | 2.50    | ET630    | 2.20  |
| 76B4    | 2.60 | ET480PS        | 2.50    | ET480    | 2.80  |
| ET631   | 7.00 | ET630          | 2.20    | ET066    | 2.20  |
| ET064   | 2.00 | ET449          | 2.20    | ET804    | 2.80  |
| ET448A  | 2.20 | ET448          | 2.80    | ET711C   | 2.00  |
| ET711B  | 2.20 | ET068          | 2.00    | ET061    | 2.00  |
| ET044   | 2.00 | ET043          | 2.00    | 76MI9    | 3.50  |
| ET711R  | 2.50 | ET711D         | 6.00    | ET447    | 2.80  |
| ET544   | 2.50 | 76PC9          | 4.40    | 76EX10   | 2.80  |
| ET602   | 6.50 | ET446          | 2.50    | ET533A C | 3.50  |
| ET711A  | 7.50 | ET543B         | 2.50    | ET543A   | 2.50  |
| ET445   | 2.50 | ET241          | 2.80    | ET780B   | 2.50  |
| ET780A  | 3.00 | ET541          | 2.50    | ET444    | 3.00  |
| 76S7    | 2.50 | 76M17          | 2.80    | 76LM5    | 2.50  |
| 76SS6   | 3.00 | 76SW4          | 2.00    | 76R4     | 2.50  |
| 76M5    | 2.50 | 76VG5          | 5.00    | 76E04    | 3.00  |
| 76VG5   | 5.00 | 76M5           | 2.50    | 76R4     | 2.50  |
| ET708   | 2.50 | ET740A         | 4.50    | ET740B   | 3.50  |
| ET514   | 2.50 | ET707A         | 2.50    | ET707B   | 2.50  |
| ET706   | 2.50 | ET130          | 2.50    | 76RT3    | 3.00  |
| 76T2    | 2.50 | 76A03          | 2.50    | 76G3     | 2.50  |
| 76E02   | 5.50 | 75SWILA/Pr4 00 | DMS-RC1 | 4.00     |       |
| 75PC12  | 2.50 | EA78F1         | 2.80    | ET534    | 2.50  |
| ET514   | 2.50 | ET129          | 2.50    | ET28     | 2.50  |
| ET439   | 3.00 | ET420G         | 2.50    | ET123B   | 2.50  |
| ET123A  | 2.50 | ET119          | 2.60    | 75F2     | 2.50  |
| 75L11   | 2.50 | ET438          | 2.50    | 75V12    | 2.50  |
| 75F12   | 2.80 | ET1124         | 2.50    | ET122    | 3.00  |
| 75CL9   | 2.50 | 75PC12         | 2.50    | ET121    | 2.50  |
| ET120   | 2.50 | ET118          | 2.50    | ET117A-B | 2.80  |
| ET704   | 2.50 | ET500          | 2.50    | 75T19    | 2.50  |
| 75R7    | 3.00 | 75C07          | 2.50    | 75FM5    | 2.50  |
| 75TU10  | 3.50 | 75FE5          | 2.50    | 75TU8    | 5.00  |

### ALL SILICON 30/60w PA PORTABLE AMPLIFIER


6 1/2" w x 8 1/2" D x 3 1/4" H 12 — 16V. two inputs 5 & 100mV. 125, 250, 500 ohm output only. No. 763A at \$70 ea. For 240V operation \$33 extra. Freight collect.

COILS and IF's All \$2.50 ea plus post 60c 3/4" w x 3/4" D x 2" H

MAIL cheque or money order (add postage) direct to —

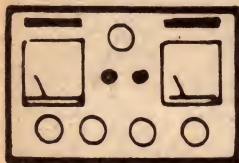**RCS radio pty ltd**  
651 FOREST RD BEXLEY  
NSW 2207 587 3491





# The Serviceman

## *More than an intermittent — a real challenge*

Now and again every serviceman encounters a situation where all the cards appear to be stacked against him. It will demand all his skill, both technical and diplomatic, to ensure that he finishes up with a satisfied customer. It can be a tough challenge, but very rewarding to both ego and reputation if he succeeds.

The story I am about to tell is a classic example; so much so that I would like to think that it, or a story like it, should be compulsory reading for anyone who aspires to be a serviceman. It has all those real life ingredients which one seldom finds discussed in text books or classrooms, but which occur all too frequently in practical service work.

As is usually the case, it started simply enough. The customer walked into the shop and said he was having trouble with his (monochrome) TV set and asked, a little diffidently I felt, whether I thought I could help him. His diffidence made me suspect that this might be a sticky one and, as the story came out, these suspicions were confirmed.

It seemed that he had moved into the district several months ago and, shortly after, the set started playing up. He was quite vague about the nature of the fault, and I didn't press the point at this stage. Suffice it to say that he called in another serviceman and that was when his problems started.

The serviceman established that the fault was intermittent and, on this basis, took it back to the workshop; all of which seemed quite reasonable so far. Subsequently, he returned the set to the owner and assured him that it was now quite OK. In fact, it wasn't very long before the set exhibited exactly the same symptoms as it had before.

So the owner approached the serviceman again, complained that the fault was still in evidence, and requested that he have another look at it. This time the serviceman attempted to correct the fault in the customer's home, but with no more success than before.

This exercise was repeated several more times over the following weeks, and always with the same result; an apparent cure which lasted anything from a few hours to a couple of weeks, but

invariably failed eventually.

At this point the serviceman apparently became fed up with the whole deal and opted out by simply ignoring the customer's request that he have another try to fix the set. Which more or less brought the story up to date, because it was then that the customer sought my help.

Having listened patiently to all this, the first thing I wanted to know was the nature of the fault. The customer went to some trouble to explain what I already knew; that it was intermittent. When he finally came to the crux of the problem he described the picture as "... becoming very grey and smoky." He went on to explain that this varied from being difficult to watch to being virtually unwatchable.

I then asked about his aerial system, and exactly where he lived. It transpired that his location was not a particularly good one, and I was rather shocked when he went on to say that he was using only a pair of "rabbit ears". I don't like rabbit ears at the best of times, regardless of signal strength, and I certainly would not have suggested them for his location. I decided that it just could be that his trouble was nothing more than the variable signal quality which such a setup could produce.

Accordingly, I made an appointment to visit his home the next day and, hopefully, see the trouble for myself. When I was finally ushered into his lounge room I recognised the set as one which Philips produced in the early '70s, being a hybrid type using modular construction.

The customer switched on the set and, when it warmed up, I was surprised to see that it was producing very good quality picture, rabbit ears notwithstanding. There were no serious ghosts and, while there was a little snow, it was not distracting at a normal

viewing distance.

When I commented on the quality of the picture, the owner was not impressed. "Just wait a while", he said, "In a few minutes it will go all smoky, or the screen will go black and we won't get anything."

So we waited. And chatted. And his wife made a pot of tea. And we waited. And talked. And — of course — nothing happened. The set continued to deliver a normal picture. I pulled the back off, had a good look around, prodded and tapped in likely places, but all to no avail.

The customer was somewhat embarrassed by all this. Following the story about the other serviceman's abortive efforts, he felt that it made him look like some kind of crank who only imagined the fault.

I assured him that I had no such illusions, that the situation was quite common, and that it would probably take several attempts to come to grips with the fault. I suggested that he keep me informed and try to contact me when the set was actually faulty, so that I could check it immediately.

A couple of days later he was back in the shop. The set was really bad now; failed nearly every time it was switched on. He was sure that if I came around that afternoon I would be able to see the fault.

I wasn't as optimistic as he was — I've been caught too often — but I kept my fingers crossed and duly turned up at the suggested time. Alas for our hopes; the exercise was a virtual repeat of the first one. All I could do was indulge in some detective type questioning in the hope that I might get a better idea of what was happening, but this was not much help.

The only conclusion I could come to was that the set might be voltage sensitive. If this was so the best chance of it happening was in the early evening during the peak cooking period, so I suggested that I come back at about 6 o'clock and try again.

I was hoping that I would see the fault occur naturally but, having latched onto the voltage sensitive idea, I wasn't above giving nature a helping hand if necessary. Accordingly I fished



out my trusty Variac and took it along.

As before, the set refused to misbehave so, after waiting a reasonable time I connected the Variac and, starting at 240V, gradually wound it down to about 210V. At this point things started to happen. First the picture bloomed, then the screen blacked out completely. By carefully adjusting the brightness control downwards, a weak picture could be produced, but any attempt to lift the brightness would black it out.

These are classic symptoms of EHT failure, normally caused by low emission in either the line output valve, EHT rectifier, or boost diode. More important they were, according to the customer, the same symptoms that he had been observing all these months. I felt quite jubilant at having run the culprit to ground.

I pulled the back off, withdrew the 6CM5 line output valve, replaced it with a new one, and tried again. Unfortunately, this made little difference, so I changed the 1S2 EHT rectifier. This time I struck oil. The set behaved normally at 210V and even at 200V, so I considered the point proved.

In cases like this I make it a point to impress on the customer that they should contact me immediately if the fault shows again. And, just to make sure, I also make a point of dropping in a few weeks later, at a convenient time in my rounds, and enquiring whether the set is still behaving. While normally only a gesture, it is good public relations.

I went through the same routine with this customer, confident that I would hear no more about the problem, then took my leave. It came as something of a shock, therefore, as well as a blow to my ego, when I found a note under the shop door one morning saying that the set was still giving trouble.

It went on to explain that he had left the note because he would be out of town for a few weeks, and that he would contact me when he returned. Which left me with the puzzle hanging over my head for the next couple of weeks; a most frustrating situation. Still, that's all part of the game.

When he did return, he elaborated somewhat on his note. It seemed that the set was now so bad as to be virtually useless and, more to the point, was bad all the time. And while the customer was rather disturbed about this last point, it was the best news I had had so far — if, in fact, it was true.

A little while later, when he ushered me into his lounge room and switched the set on I knew he was right; the set was, as he described it, "... smoky all the time." More correctly, it had all the symptoms of a sick picture tube; low contrast and poor brightness such as occurs when a tube's emission drops.

Which was all very well except for one very important point; I have known picture tubes to have a wide



## "HOW TO TURN ELECTRONIC THEORY INTO PRACTICE AND MAKE IT PAY..."

"If you understand and enjoy radio and electronics and want to extend your knowledge and experience, then we at Stott's can help you.

Stott's have home-study courses for complete beginners in Radio theory and basic Electronics through to the standards needed to maintain and service Colour Television.

Anyone who has these skills at their fingertips can make it pay by turning a fascinating hobby into a lucrative part or full time profession."

*Athol H. Kelly*

Athol H. Kelly B Com. (Hons.) A.A.S.A., F.C.I.S.  
Principal Stott's Technical Correspondence College

**Stotts**  
TECHNICAL CORRESPONDENCE COLLEGE



The name to trust in  
correspondence education.

Melbourne, 159 Flinders Lane, 3000. Tel: 63 6212  
Sydney, 383 George Street, 2000. Tel: 29 2445  
Brisbane, 290 Adelaide Street, 4000. Tel: 31 1627  
Kent Town, 66 King William Street, S.A. 5067. Tel: 42 5798  
Perth, 89 St. Georges Terrace, 6000. Tel: 322 5481  
Hobart, 1st Fl. 29 Argyle Street, 7000. Tel: 34 2399  
Singapore, P.O. Box 3396, Singapore 1.

Please send me free, and without obligation, full details of the following courses.

\_\_\_\_\_, (PLEASE PRINT)

MR MRS MISS \_\_\_\_\_ AGE \_\_\_\_\_

ADDRESS \_\_\_\_\_


\_\_\_\_\_, POSTCODE \_\_\_\_\_

Stott's undertake that no sales counsellor will visit you

ALA/ST547/EA978

The Stott's range of courses in  
Electronics are:

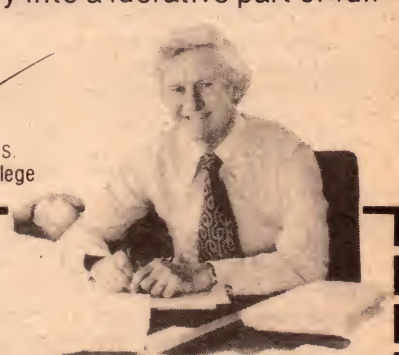Radio for Amateurs  
Introduction to Electronics  
Digital Electronics  
AM Radio Receivers  
Radio/TV Servicing  
Colour Television  
Amateur Radio Operators'  
Certificate  
A full range of Hobby and  
Business courses also  
available.





**TEXAS PROGRAMMABLE CALCULATORS**

FOR QUALITY, VALUE AND POWER.

Ti 59 \$328 \$265 (\$294)

Ti 58 \$147 \$115 (\$127)

Ti 57 \$92 \$75 (\$83)

Ti 55 \$67 \$57 (\$63)

MBA \$90 \$75 (\$83)

The Businessman's Dream!



PC100A with Ti 58

The MBA

**ACCESSORIES FOR Ti 58 and 59**

PREPROGRAMMED MODULES: \$35- \$32 each.

INCLUDING — Marine Navigation • Aviation • Surveying • Applied Stats. • Real Estate and Investment • Leisure Time.

PC100A PRINTER: \$278 \$225 (\$250)

40 BLANK MAGNETIC CARDS — Ti 59 \$15.

**DESK MODELS**

Models from \$100 — \$3000: TEXAS — CANON — SANYO — VICTOR

Business and scientific with display and/or printer and/or programmable.

**FAMOUS TEXAS SR60A**

Business. Research. Personal Computer. Models up to 7920 program steps or up to 990 memories.

Preprogrammed card libraries for — Finance, Electrical Eng. Maths (2), Statistics, Surveying, Payroll.



F11 ONE OF THE GREAT CANOLA RANGE \$420 \$345 (\$380) and ADDING MACHINES TOO!

(WRITE FOR DETAILS AND DISCOUNT PRICES)

**LIQUID CRYSTAL CALCULATORS****NATIONAL SEMICONDUCTOR**

7.5mm thin in billfold wallets.

NS108 Scientific/Statistical (with P-R)

\$59 \$45 (\$51)

NS103 Data Checker — 3 continuous memories

\$52 \$40 (\$48)

NS104 Clock/Calculator (alarm — stopwatch)

\$78 \$60 (\$68)

**SANYO**

super thin with lithium batteries.

CX8179L Beautiful silver executive model

\$38 \$30 (\$34)

CZ8114L Scientific/Statistical (school!)

\$48 \$38 (\$43)

CZ0125L Scientific/Statistical (with P-R)

\$62 \$47 (\$54)

**TEXAS**

Ti 1750 with memory, %, constant

\$23 \$19 (\$21)

NEW! Ti 25 — ASK OUR SPECIAL PRICE

**CANON**

LC QUARTZ Calculator/Clock/Alarm/Stopwatch

\$65 \$52 (\$57)

(Also fluorescent display models — F71 \$75 \$58 (\$65).

F61 \$55 \$43 (\$48), F41 \$24 \$19.50 (\$21.50), F31 \$20 \$16 (\$18))

**PACKING AND POSTING**

Extra \$2 for NSW, elsewhere \$3 per order for certified mail — another \$1.50 for registered.

**SPECIAL** — All LCD calcs. \$1.50Anywhere in Australia.  
(Large items sent by courier)**CANON P10-D**

Display/Printer (plain paper) fits in your hand.

\$142 \$91 (\$100)

**LC QUARTZ**

NS108

**SALES TAX FORMS** must be duly signed and stamped by college, university or school (forms available).**ELECTRONIC CALCULATOR DISCOUNTS**

Phone: (02) 624 8849 (8am till 3pm) P.O. Box 106, Baulkham Hills, N.S.W. 2153

# ELLISTRONICS

**289 LATROBE ST, MELBOURNE. PHONE 03 602 3282**

|                                                            |                      |
|------------------------------------------------------------|----------------------|
| Sinclair D.M. 235 Digital Multimeter                       | \$148.00, p/p \$2.00 |
| Sinclair P.D.M. 35 Digital Multimeter                      | \$ 61.50, p/p \$2.00 |
| Arlec D.M.M. 10 Digital Multimeter incl. ni/cd and charger | \$ 76.50, p/p \$2.00 |
| Kaise S.K. 100 100K/V D.C. 12 amp                          | \$ 47.50, p/p \$2.00 |
| Arlec 200H 20K/V                                           | \$ 12.95, p/p \$2.00 |
| Arlec MF. 15 2K/V                                          | \$ 10.50, p/p \$2.00 |

All prices include Sales Tax where applicable.**PRE-PACKED ELECTRONIC COMPONENTS****BRAND NEW AND USEFUL VALUES**

|                                             |                          |
|---------------------------------------------|--------------------------|
| Qty 100 ½ watt resistors                    | \$1.50 per pack, p/p 60c |
| Qty 100 disc ceramic capacitors             | \$2.00 per pack, p/p 60c |
| Qty 50 electrolytic capacitors              | \$2.50 per pack, p/p 60c |
| Qty 50 polyester capacitors incl. greencaps | \$2.00 per pack, p/p 60c |
| Qty 25 rotary single & dual potentiometers  | \$2.50 per pack, p/p 60c |

Qty 25 slide single &amp; dual potentiometers \$2.50 per pack, p/p 60c

Digitran miniature thumbwheel B.C.D. switch ass- brand new comprises 17 individual switches banked together c/w end plates &amp; spacers \$20.00 ea, p/p \$1.50

Polystyrene capacitors 56pf to .01uf .5c ea

½ watt 5% resistors from .3c ea

Disc ceramic capacitors from 1pf to .05uf .5c ea

" .1uf to .47uf 10c ea

Greencaps .001uf to .0082uf .5c ea

" .01 to .06uf 10c ea

" .1 to .22uf 15c ea

" .47 to .68uf 20c ea

4.7uf 100V polyester capacitors ideal for x-overs \$1.00 ea

Large range of semiconductors, switches, potentiometers, cables, knobs, project boxes, speakers, vero &amp; blob board, phenolic &amp; fibreglass circuit board, soldering irons, B.A.S.F. tapes, audio leads, plugs &amp; sockets, edge connectors, E.A. &amp; E.T.I. project boards, etc., etc.

All at what we believe are Melbourne's lowest prices for the best in electronic components. Trade orders supplies. Also at 297 Little Lonsdale Street, Melbourne 3000.

**MELBOURNE'S ELECTRONIC CENTRE**



## THE SERVICEMAN

variety of intermittent faults but I have never seen one with intermittent low emission. Granted the tube was some six or seven years old, but my reaction when I had first inspected the set was that the tube was in first class condition.

Yet it was now fairly obvious that it had been going through cycles of apparent low emission over a period of several months.

As I removed the back of the set I decided that, if the tube itself was not faulty, the most likely culprit would be the heater supply. Sure enough, a glance into the neck of the tube suggested that the heater was working at well below normal brilliance.

This set has a small printed board sub-assembly on the end of the picture tube. The tube socket is mounted directly on the board which also carries various components associated with the tube elements, and serves as a terminal point for the supply lines to the tube.

I connected the multimeter across the two heater leads where they joined the board and was rather surprised to find a healthy 6.4V. Since this didn't tally with my observation of the heater, I took a closer look at the printed board assembly. The lugs from the tube socket pass through holes in the board and are bent over onto their respective copper tracks and soldered.

Working very gently, I placed the test prods directly on the two filament lugs of the socket. It was a different story here; barely 3V for the poor old heater. Small wonder the tube looked sick.

Closer inspection with a glass revealed a hairline crack in the soldered connection between one of the lugs and the copper pattern. I resoldered this, and all the other socket connections to be on the safe side.

Naturally, the set came good immediately, and it was then simply a matter of tidying up. The customer was quite elated when he realised that I really had found the trouble, but no more than I was.

That was many weeks ago, and a couple of checks with the customer since then have confirmed that, "... it hasn't missed a beat." And so everything ended happily. Even if I didn't make a lot of money out of the exercise I now have a customer who is a walking advertisement for my business.

This story could well end there, having sufficient technical novelty to stand on its own feet. But I feel that there is a lot more to be learned from it than the simple technical fact that caused the trouble.

First, where did the other serviceman go wrong? While it might not be fair to be too critical of his actions, since I have not heard his side of the story, the fact remains that he elected to opt out

when he was not making any progress.

Regardless of his technical competence, it seems that he lacked patience; an essential requirement in tracking down intermittents. And this applies not only to serviceman, but also the customer, and the serviceman must be able to inspire sufficient confidence in his ability to solve the problem to ensure this patience.

This isn't always easy. After all, the customer is experiencing the frustration of trying to use an unreliable set; of having it fail half way through his favourite program or even being denied it altogether. While not always practical, the best approach is to provide a spare set for the customer and keep his on your own bench as long as necessary.

Alternatively, try to take advantage of any holiday break the customer may be planning. In the story just related, a golden opportunity was missed because the customer had left before I realised there was still a problem.

The monetary cost to the customer must also be considered. Charging a full service call fee for each visit, even though no fault is evident and no work is done, is the surest way to destroy the customer's confidence and patience.

But the most important lesson to be learned is how easy it is to be caught, and two aspects of the story illustrate this. First, I was in fact caught by finding a completely different fault which produced similar symptoms and being led to believe that it was the one in question. Only my insistence that the customer call me if the fault returned saved me on that one.

Second, I could have been so easily caught by the behaviour of the picture tube. Had my introduction to the set been at a time when the fault was evident, and had I not known — or had overlooked — the history of intermittent behaviour, I would have almost certainly diagnosed a faulty picture tube. Nor would there have been anything unreasonable about such a diagnosis, considering its age.

Had I done so I would have been faced with the embarrassing situation of involving the customer in a very expensive repair, only to find that the fault was just as much in evidence as ever. It doesn't take many mistakes like that to put a nasty dent in one's reputation.

In short, it is not sufficient to be technically competent, though this is essential. One must also be able to establish a rapport with the customer and gain his confidence, be able to sort out the genuine symptoms from the red herrings the customer will invariably produce, and be astute enough to give them all their due consideration before reaching a conclusion. And dare I add that you sometimes need an element of luck?

If you feel that such a list of requirements is too demanding then I'm afraid service work is not for you. ☺


## KITCRAFT W.A.

557 Wellington Street,  
PERTH. WA 6000  
Ph: 321 3047

### SPECIALISING IN KITS:

|                              |         |
|------------------------------|---------|
| Capacitor Discharge Ignition | \$24.00 |
| 068 Led Dice                 | 6.50    |
| 043 Heads & Tails            | 4.10    |
| 084 Car Burglar Alarm        | 8.50    |
| 065 Siren                    | 8.80    |
| 061 Simple Amplifier         | 6.25    |
| 044 Two Tone Door Bell       | 5.00    |
| 047 Morse Practice Set       | 5.80    |
| 081 Tachometer               | 6.80    |
| Drill Speed Control          | 11.95   |


## ALSO AVAILABLE KENWOOD

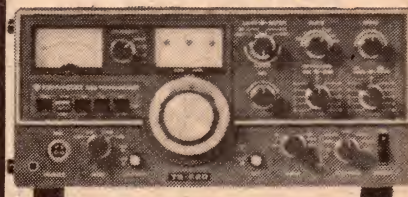

### TS520S 80-10M Transceiver

SSB Transceiver. An excellent example of superb engineering and styling.

Priced at: \$790.00

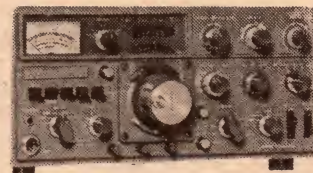


### TS820S

TS820S now has factory installed digital readout. 160 thru to 10M coverage.

Priced at: \$1180.00




## YAESU

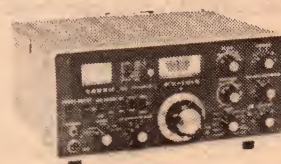

### FT-101-E

The world's number one transceiver. An effective RF Speech Processor is a built-in integral part of this exciting transceiver. Instant operation on 160 thru to 10 meters.

Priced at: \$890.00

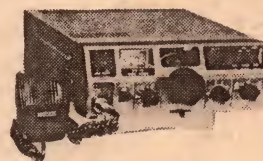

### FT-7

The all-solid state FT-7 mobile transceiver provides high performance on the 80 through 10 metre bands. The FT-7 is designed for operation directly from your car's 12 volt battery.

We have a range of Microprocessors and a complete range of accessories for amateur and ham equipment.



# Circuit & Design Ideas

Conducted by Ian Pogson


Interesting circuit ideas and design notes selected from technical literature, reader contributions and staff jottings. As they have not necessarily been tested in our laboratory, responsibility cannot be accepted. Your contributions are welcome, and will be paid for if used.

## Automatic stepping for Chroma-Chime door chimes

To increase the novelty of the Chroma Chimes as described in April 1978, the option of playing a different tune automatically each time the button is pressed has been added. The suggested modification provides an alternative to the "tune select bridge" formed by S1 and S2. The operation of an additional switch bypasses S1 and S2 and the bridge is now formed by a 1 of 8 and a 1 of 3 bilateral switch in series. These bilateral switches are operated sequentially to count 1 to 24 by the outputs of a binary counter. The counter is stepped one each time the button is pressed.

The logic circuit required for the auto-stepping facility is provided by a printed circuit board assembly about 75mm x 75mm. The board is mounted on the rear dust cover of the Chroma Chimes in the space provided by mounting the chimes on rubber feet. The changeover switch is mounted on the chimes case. Interconnection between S1 and S2 contacts and new PCB is made by wiring directly onto the chimes IC socket pins. The track connecting the S1 and S2 wipers is cut in the middle and both halves wired to the changeover switch.

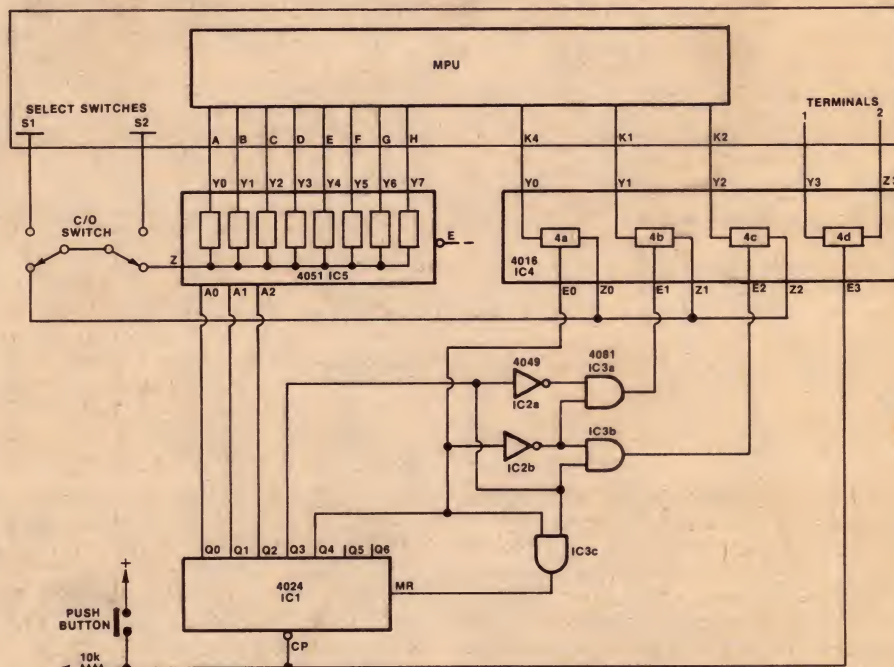The circuit description is as follows: With push button contacts closed, IC4d switch places a loop across chimes terminals 1 and 2, the chimes hunts for the S1, S2 loop and then plays. With push button contacts open, loop removed from terminals 1 and 2, counter IC1



steps one and moves the tune select loop to the next position. The chimes continue to play until the end of the tune. The bilateral switches of IC5 and IC4 are turned on sequentially as the counter steps, IC5 steps for each step of counter while IC4 steps on the 9th, 17th and 25th steps. On the 25th step the output of AND gate IC3c goes high and resets the counter to position 1.

The power supply may be from the same or a separate battery to the chimes because IC4d acts as an interpose relay. Ideally, the circuits would be supplied from a common 15V battery. This is sufficient voltage for the chimes and the maximum specified for the additional ICs.


(By Mr W. N. Paddison, 10/2 Kardella Court, Condell Park, NSW 2200.)

## Pulse generator with variable frequency and mark-space ratio

This circuit is based on a design from the GE Transistor Manual. The frequency ranges from about 60Hz to 1kHz with C1 in circuit and about 600Hz to 10kHz with C2 in circuit. The mark-space ratio is variable over a very wide range. The output is a train of pulses with an amplitude of 9V P-P.

The UJT is used as a conventional relaxation oscillator. A positive voltage swing is produced at the collector of the PN3644 when the UJT emitter voltage is more positive than the BC547 emitter voltage, as determined by the setting of the ratio potentiometer.

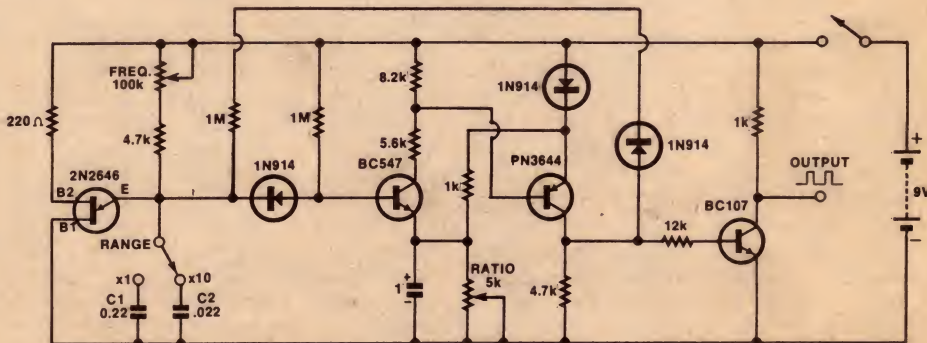The loading of the relaxation oscillator by the transistors is compensated by feeding current from the




PN3644 collector to the emitter of the UJT. This makes the pulse frequency independent of the ratio control setting. The output of the PN3644 is inverted by

the BC107 which operates as a saturated switch.

(By Mr P. Heggie, 2/2a Boonong Avenue, Seaford South, Victoria 3201.)


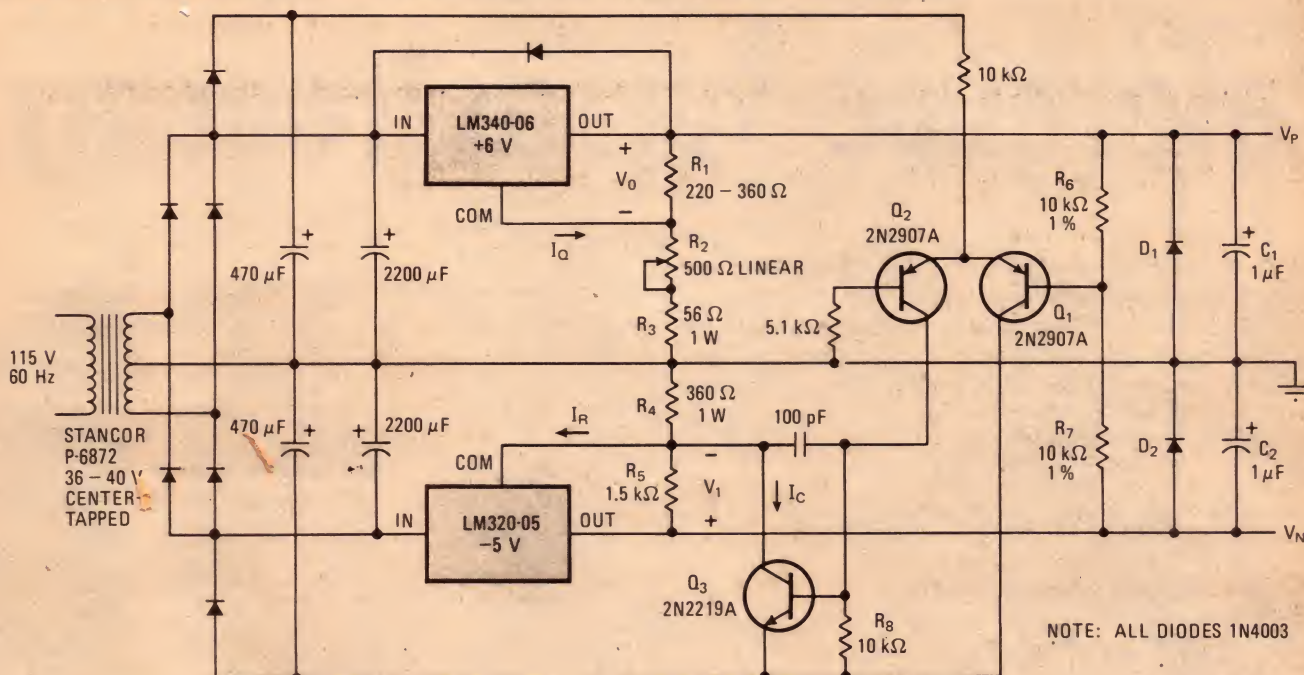
## Fixed-voltage regulator pair forms bipolar power supply



Two fixed-voltage regulators and suitable feedback circuitry can form a bipolar power supply that combines the excellent voltage regulation, trackability, and high current capacity of the three-terminal integrated circuit voltage regulator with the voltage adjustability of more expensive supplies. This unit provides bipolar voltage from 8 to 20V at 1A. The trackability, defined for an adjustable power supply as the voltage difference remaining between the bipolar ports at the desired output voltage, is 1%. Regulation for both line and load is about 100mV.

The diagram shows the regulated supply that employs two popular three-terminal regulators and a three-transistor feedback circuit. Approximately 40V across the centre-tapped transformer secondary is rectified and filtered to generate plus and minus 27V to the input of the respective regulators.

The LM320-05, which is a -5V regulator, and transistors Q1 to Q3 form a slaved configuration. A differential amplifier composed of transistors

Q1 and Q2 monitors the difference in magnitude between  $V_p$  and  $V_n$  through a precision voltage divider R6 and R7 and compares it to a zero reference. Normally, the voltage at this junction is zero, because  $V_p = -V_n$ . Any error voltage is amplified to cause a change in the collector current of Q3, which in turn changes the voltage across R4 and consequently  $V_n$ .

The high output current that can be produced by the supply generates several points where power generation dissipation is great. Components must be selected to ensure that those levels can be adequately handled. The maximum current through Q3 is 78mA. The maximum power consumption is about 500mW. The 2N2219A transistor is used for this application. Both regulators should be mounted on suitable heat sinks. Resistor R3 prevents excessive current through R2 when its value is low.

Heavy common-mode loads may cause difficulty in the operation of the feedback network during start-up unless diodes D1 and D2 are used to

clamp the circuit outputs. C1 and C2 are tantalum capacitors for improved transient response.

(By S. K. Wong, in "Electronics".)

**IN ELECTRONICS**

**QUALITY ELECTRONIC COMPONENTS**

*Serve yourself convenience*

Guaranteed NO junk,  
distressed stock, end of line  
or auction specials

We stock only the best —  
National, Signetics, SSS  
Motorola, IRH,  
Silicon Valley etc

**8<sup>AM</sup> — 8<sup>PM</sup>**  
**6 days**

Haberfield

84 Ramsay Street, Haberfield 2045  
799 3331

North Bexley

North Bexley Shopping Centre  
502 2094 (9am-5pm Mon-Fri, 9-12 Sat)

## Aerial pruning made easy

When erecting dipoles, a bit of pruning is usually necessary to bring the system into resonance at the selected portion of the band. It can be quite a task if the antenna is cut too short.

A method that I use is to cut the antenna slightly short of the calculated length and then solder on an additional length of about 12 gauge copper wire at

each end, making the total length a little longer than the calculated figure. It then comes a simple matter to prune a little at a time until the antenna is precisely where you want it. Usually the added wire is found to be between one and five inches long and it is self supporting.

(By Bill Tucker, W4FXE, in "QST".)



# Adapting the VNG-derived reference for astronomy

Using as a starting point the VNG-Derived Frequency Reference design published in our April 1975 issue, two of our readers have produced a modified reference unit specifically designed for use as a time reference for astronomy. In this article they give brief details of the way they modified the original design for this purpose.

by **DR B. ASHLEY and M. ASHLEY**

When the Derived Frequency Reference from VNG first appeared in April, 1975, it was greeted enthusiastically in our household. For the first time it seemed that it would be possible to determine easily which oscillator circuits were drifting and in which direction. One member of the family, with interests in astronomy, envisaged for himself a source of precision time signals. Further discussion introduced the idea of reference frequencies in addition to the 1.5MHz of the design, and from there it was a small step to decide that it would not be difficult to provide an audible 1Hz pulse to take the place of VNG when the latter faded into inaudibility. Often at the critical astronomical moment!

The instrument which we have produced has the following features: (a) It receives VNG on 4.5MHz or 7.5MHz at the flick of a switch. (b) The receiver has been modified to a double conversion type in which the second IF of 455kHz is fed to a ceramic filter. This greatly improves the selectivity and makes VNG listenable more often than before.

(c) A small audio amplifier and loudspeaker have been added primarily to make listening more convenient (d) VNG-derived reference frequencies, in decades from 1Hz to 1MHz, and also 6MHz, are selectable by switching at DC levels. (e) Simulated VNG pulses, including the five modified tones and the silent interval before each minute, are generated and may be fed to the audio amplifier instead of the real VNG, or used for precision starting and stopping of suitable digital timers.

(f) VNG-derived reference frequencies and simulated VNG tones are synchronised initially with VNG and remain precisely in step so long as the

*A double conversion receiver and the ability to receive VNG on 4.5MHz and 7.5MHz are features of the new unit. Reference frequencies are available in decades from 1Hz to 1MHz, and also at 6MHz.*

crystal is controlled by VNG. The error incurred during periods when control is lost is that due to the 6MHz crystal and its associated oscillator circuit. Although it accumulates, it is negligible unless reception is very poor, and resynchronisation can be regained at any time when the signal returns.

(g) The instrument may be transferred from mains to battery power and vice versa without interrupting reception or accuracy.

Some of the circuit changes and additions used to realise the above will now be described.


Front end overload on very strong signals was countered crudely but effectively by incorporating a switchable resistive "crowbar" from aerial to earth.

Switch selection of either 4.5MHz or 7.5MHz was included as suggested in the article. It has been a valuable feature since there are now few occasions when a usable signal is not available. Coil turns were increased to 19 which allowed both channels to be

peaked by 5-40pF trimmers without having to use large values of additional parallel capacitance.


Selectivity could not be improved significantly by the addition of more IF transformers or stages. The double conversion solution finally used is appealing because it combines excellent performance with simplicity of circuit, and ease of modification of the original circuit.

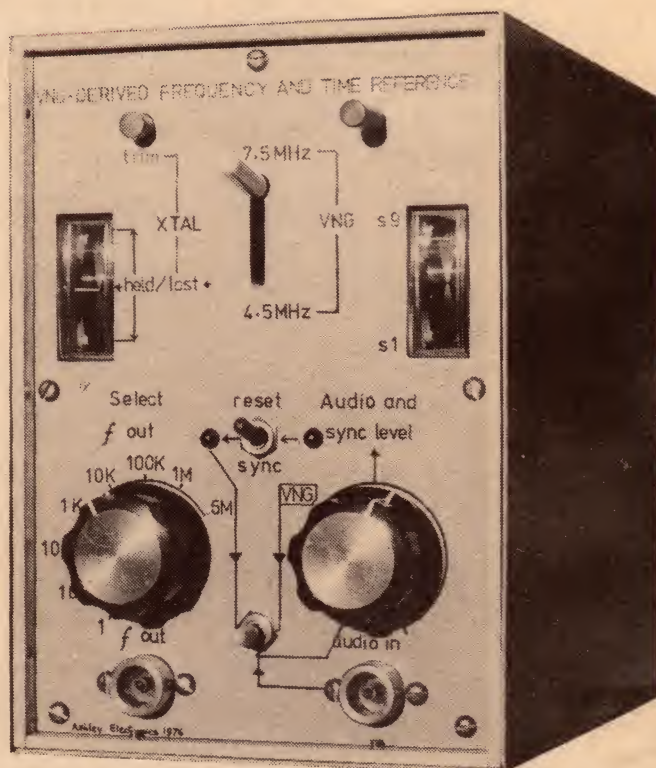It is worth noting that the purpose of the double conversion is to improve the audio reception. Coincidentally, AGC is made more specific for VNG but there is no direct effect on crystal control because this is still derived from the



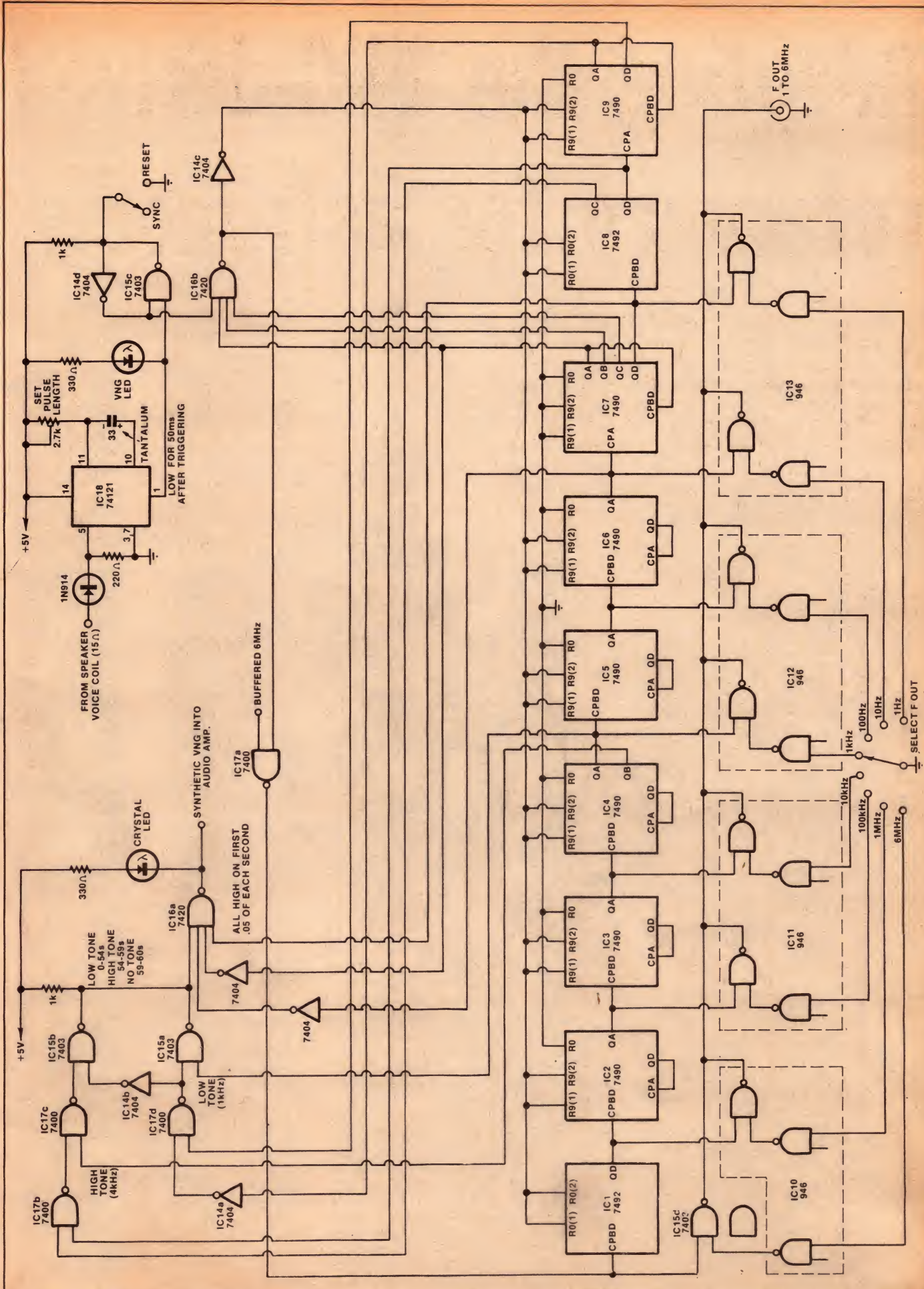*The circuit diagram (facing page) shows most of the relevant parts as referred to in the text. The receiver section has been omitted to save space. It is similar to that originally given in the April, 1975 issue, with the exception of the modifications described.*







## VNG frequency reference

1.5MHz of the first IF. In practice, once locked to VNG the LM1351 circuitry is able to maintain crystal frequency even when VNG is almost inaudible and even when there is powerful adjacent channel interference.

The double conversion stage is placed electrically between TR4 and TR5. It takes its input signal from the emitter of TR4 and feeds its output into the base of TR5. The input 1.5MHz first IF signal is converted to the second IF of 455kHz by means of a self-oscillating mixer, as used in the AM/FM tuner described in September, 1975. The coil is a standard Jabel type 7348 tuned to 1955kHz with the slug, and fine tuned with a concentric trimmer forming part of the tuning capacitance. This has been brought out to the front panel as adjustments are necessary to accommodate oscillator drift.

The new IF is then fed into a 455kHz ceramic filter and the output from this goes to the original audio detector. A small value of coupling capacitance on the ceramic filter gives a bandpass which is adequately narrow.

The increased number of TTL devices and the desire to operate from a car battery led to a higher voltage, higher current transformer being installed and to the use of IC regulators for the +5V and +12V supplies. A diode in series with the battery inlet serves to protect the power supply and regulators from mistakes in battery polarity connection. Although 0.7V is lost across the diode, its inclusion is prudent. Current drain is about 0.53A and the circuit operates happily from the car battery and down to 12V input even though the regulator is not functioning properly.

The 6MHz crystal oscillations can reach the dividers only through a NAND gate. This gate is enabled by a VNG pip as follows. VNG pips are amplified by the audio amplifier and fed not only to the speaker but also to the Schmitt trigger input of a 74121 monostable IC. When pips of sufficient amplitude are available the monostable is triggered and produces an active low pulse with a nominal duration of 60ms. These pulses are made visible by a front panel LED connected to the monostable output. In practice the amplifier volume is increased until the LED is lighting reliably on each VNG pip.

The divider chain is conventional except that two ICs are connected as BCD counters for reasons associated with the simulation of VNG pulses, and that the decade dividers are reset to 9. The 6MHz from the crystal is first divided by 6 by a 7492 IC to yield 1MHz. It is then passed through five divide by 10 stages consisting of 7490s connected as symmetrical dividers, which gives a

10Hz symmetrical square wave. This is then fed into a 7490 connected as a BCD counter. The Qd output of the 7490 is thus a 1Hz asymmetrical square wave, high for 0.25 and low for 0.85.

The method of switching the reference frequencies produced by the divider chain uses the wired-OR configuration described by Waddington in his design for a digital meter in "Wireless World" for March, April and May, 1973. Although it may appear an extravagant use of ICs it avoids having to route square waves at these frequencies to and from switches. We used DTL946s for all except the 6MHz signals. Open collector type 7403s could also be used with a pull-up resistor on the output line, and would give better performance on the higher frequencies.


When making astronomical observations it is often necessary to have a reliable and reasonably accurate source of time signals, to within about .05S. The synthesised VNG incorporated in this instrument can be synchronised to the VNG time signal hours before it is re-

with their leading edges at the beginning of each second. The length of the burst can be increased or decreased by appropriately changing the inputs of the relevant IC. In practice we found that 0.15 bursts were too long and that .05S bursts were just about right.

The .05S pulse output is then used to drive a LED as a visual indication of the time bursts. We mounted this LED close to the LED on the output of the monostable so that very small errors in synchronisation can be detected. Note that the length of the monostable pulses should be slightly longer than that of the VNG pulses, otherwise double triggering will occur, which could be undesirable for some purposes although it will not affect synchronisation.

1Hz pulses are available on the front panel for synchronising digital stopwatches and other devices, to the synthesised time signal.

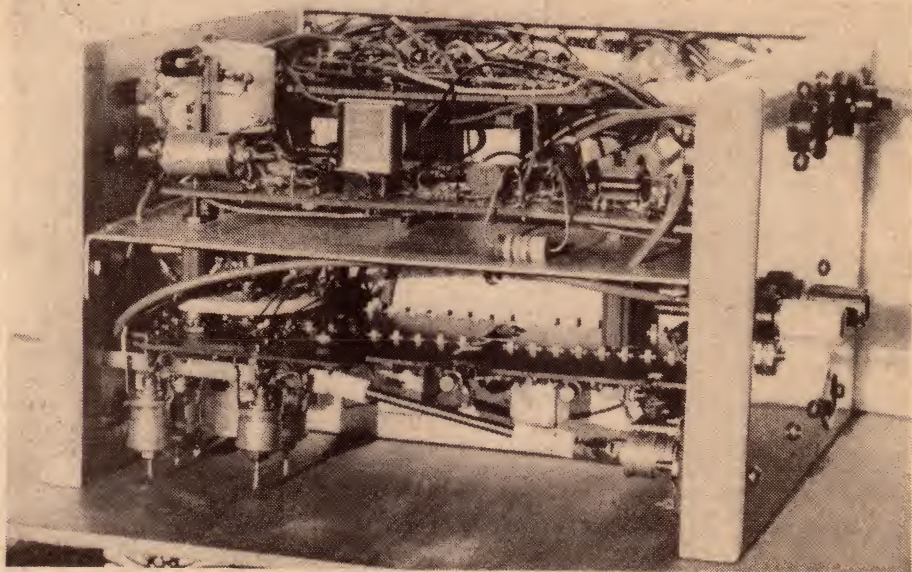Obviously our modifications could again be considerably modified to take advantage of more modern components and to reduce power con-



View inside the completed frequency reference. The unit may be powered from the mains, or by a +12 battery.

quired, thus ensuring a reliable source of time signals during periods when VNG is inaudible. It is also possible to start the synthesised time signal manually so that relative time intervals can be obtained when it is not possible to synchronise the device to VNG. These relative times can then be converted to absolute time by comparing the synthesised signal with VNG at a later time.

The synthesised signal sounds quite similar to that from VNG. It would be possible to make the zero second of each minute longer, or of a different tone from the other pips but it is not easy and the added complication was deemed unnecessary.

The continuous tones present on the output of the open collector NAND gates are converted into .05S pulses

sumption. It would also look a lot better inside if we had used new miniature components instead of some of the bulky and ancient ones and by using a PC board for the dividers.


Editorial note: The article as originally submitted by the authors has been considerably abridged because of space considerations. Also unfortunately, we have had to omit part of the circuit diagram. However, the authors have kindly agreed to furnish further information to interested readers. Requests for a copy of the circuit and possibly a one or two page photocopy of some extra explanatory notes, should be accompanied by a self-addressed envelope and two stamps. They should be addressed to Dr B. Ashley, 25 Melrose Drive, Mawson, ACT 2607.



# REAL POWER LINEUP

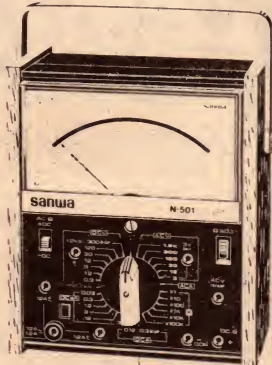
## N-501

2 $\mu$ A suspension movement — 0.05mA/1mV resolution.  
Double protection — fuse & Si diode.  
Constant 1M $\Omega$  input impedance (ACV) — RF-diode rectified current direct to movement.


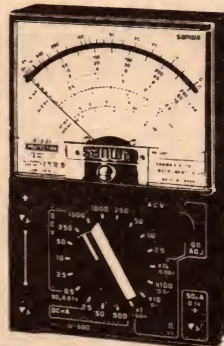
## U-60D

44 $\mu$ A movement — quality performance, diode protected.  
Temperature measurement of -30°C to +150°C with extra scale.



## AX-303TR

44 $\mu$ A meter movement — Si diode protection against pulse input.  
Measures hFE (0-1000) by using the extra connector.



## BX-505

Fast-response, 24 $\mu$ A movement — fuse & diode protected with high resolution factor. (0.4 $\mu$ A/scale division)  
Revised scale marking — intermediate readings readily determined.

## CAM-250D

Clamp meter  
Economical and multi-function. Single motion core arm.  
Compact yet provides 4 ranges on ACA and 2 ranges on ACV.



## PDM-500/C

Performs as low resistance ohmmeter besides insulation tester.  
Measurement, scale calibration and battery check are all operated by pushbutton switches.  
Has constant voltage impressed irrespective of the value of resistance checked.

Sanwa Electric Instrument Co., Ltd. can meet your every marketing requirement for multi-testers with an extensive quality range of more than 20 models. Currently exporting to more than 100 countries, we offer 35 years technical experience as Japan's top manufacturer and innovator in this field.

### (N-501)

•  $\pm$ DCV 0-60m 0-0.3-1.2-3-12-

30 0-120-300-1.2k-30k (w/HV probe) •  $\pm$ DCA 0-2 $\mu$  0-0.03-0.3-1.2-3-12-30m 0-0.12-0.3-1.2-12A • ACV 0-3-12-30-120-300-1.2k  $\pm$ 2.5% Freq. 20Hz to 50kHz • ACA 0-1.2-12  $\Omega$   $\times$ 1- $\times$ 10- $\times$ 100- $\times$ 1k- $\times$ 10k- $\times$ 100k (max. 200M) Batt. 1.5V  $\times$ 1 & 9V  $\times$ 1 • dB-20 to +63  
(AX-303TR)  
•  $\pm$ DCV 0-0.3-3-12-30-120-300-1200 • ACV 0-6-30-120-300-1200 •  $\pm$ DCV 0-60 $\mu$ -3m-

30m-0.3-12  $\Omega$   $\times$ 1- $\times$ 10- $\times$ 1k- $\times$ 10k (max. 20M)  
(U-60D)  
• DCV 0-0.1-0.5-2.5-10-50-250-1k-25k (w/HV probe) • DCA 0-50 $\mu$ -2.5-50-500m • ACV 0-2.5-10-50-250-1k  $\Omega$   $\times$ 1- $\times$ 10- $\times$ 100- $\times$ 1k (max. 5M)  
(BX-505)  
•  $\pm$ DCV 0-0.12-3-12-30-120-300-1200-30k (w/HV probe)  
•  $\pm$ DCA 0-30 $\mu$ -3m-30m-0.3-12 • ACV 0-6-30-120-300-1200

• ACA 0-12  $\Omega$   $\times$ 1- $\times$ 10- $\times$ 1k- $\times$ 10k (max. 20M)  
(CAM-250D)  
• ACA 6-30-60-300 • ACV 300-600 • k $\Omega$  0-50k • Batt. 1.5V  $\times$ 1  
(PDM-500/C)  
• V/ $\Omega$  rated 500V/100M  
• Scale range 0-0.1-100-200M (1st effective scale range underlined) •  $\Omega$  0-100 $\Omega$  • Power source AM or UM-2 $\times$ 3



**WARBURTON FRANKI**

ADELAIDE 356-7333. BRISBANE 52-7255 HOBART 23-1841. MELBOURNE 699-4999.  
PERTH 65-7000. SYDNEY 648-1711. WELLINGTON, N.Z. 69-8272

**sanwa**



**Simple, economical design has 10M input impedance:**

# Sensitive FET-input AC-DC voltmeter

While the average multimeter is adequate for routine measurements, its sensitivity and lack of bandwidth can be a severe limitation in measuring many of today's circuits. The simple instrument presented here is an answer to that problem. It uses one FET-input op amp IC and a handful of other components.

Most electronic hobbyists have access to some sort of multimeter and typically it will have a sensitivity of 20,000 ohms/volt on DC voltage ranges and 10,000 ohms/volt on AC voltage ranges. While this can be adequate for most routine testing, most multimeters are quite inadequate for measuring low AC and DC voltages in high impedance circuits.

For example, if a multimeter has a 1V range and its sensitivity is 20,000 ohms/volt, this means it will load the circuit being measured with 20,000 ohms. In many circuits, a load of this magnitude would prevent circuit operation. To put it another way, the impedance of the circuit being measured would have to be 2000 ohms or less for the act of measurement to have slight effect.

Active voltmeters, such as the one presented here, are designed to overcome this problem of sensitivity. Commonly, an active voltmeter for general purpose use is designed to have an input impedance of 10 megohms. More precisely, it will have an input resistance of 10 megohms shunted by

capacitance of about 10 to 30 picofarads.

The input impedance remains constant, regardless of the range selected and whether AC or DC is being measured.

Our active voltmeter presented here is a FET-input operational amplifier IC voltmeter, but since that is quite a mouthful we shall refer to it as a FET voltmeter. The heart of the circuit is a CA3140 IC which, as might be gathered from the above, is an operational amplifier with FET input stages.

In comparison with common op-amps like the 741, the CA3140 is very similar except that some specifications, such as slewing rate, are enhanced. In fact, the CA3140 is a direct drop-in replacement for the 741 op-amp in most applications.

The greatest dissimilarity between these two devices is with regard to the input currents. Whereas a 741 has a typical input bias current of just under 100 nanoamps at room temperature, the equivalent figure for a CA3140 is 10 pico-amps. In other words, the MOSFET input stages of the CA3140 draw 10,000 times less current than the 741 input stages. So it is much easier to obtain high input impedances with the CA3140.

Referring to the complete circuit, the CA3140 is connected in a configuration which may look similar to a unity-gain voltage-follower, but is really a voltage-to-current converter with a meter movement and associated components in the feedback loop. Fig. 1 shows a simplified version of the circuit.

Before describing the operation of the circuit of Fig. 1, perhaps a brief rundown on operational amplifiers is appropriate. Op amps have two inputs known as the inverting input and the non-inverting input. These are so-named because, when a signal is applied, the output signal is in phase with the non-inverting input and 180 degrees out-of-phase with the inverting input.

The two inputs are, in fact, differential in-

puts and the output is a product of the difference in signal applied to the two inputs, multiplied by the gain. The gain figure is extremely high, a figure of 200,000 being typical. In practical circuits, most of this gain is traded for desired performance characteristics by applying negative feedback.

The circuit of Fig. 1 has balanced positive and negative 9V supply rails, provided by two batteries. The non-inverting input of the CA3140 (pin 3) is biased from the zero volt line (ie, the common connection of the two batteries) via the input voltage divider. Since negligible current flows, pin 3 is very close to OV when no external input signal is applied.

At the same time, the inverting input (pin 2) is biased from the output via the negative feedback network.

Now when connected in this fashion, an op-amp always operates to bring its two inputs close together in potential, ie, zero potential difference. This means that if the non-inverting input is set at OV, the inverting input must also rest at OV. And since negligible input bias current flows from the output to this latter input, then the output must also rest very close to OV.

So, with no signal applied, both inputs and the output of the CA3140 rest very close to OV. This means that no current flows through the meter movement (not enough to shift the pointer off the rest, anyway).

Now imagine that a positive voltage of 300mV is applied to the input of the circuit. This is reduced, via the voltage divider, to approximately 200mV which is applied to the non-inverting input of the CA3140. The CA3140 operates via the feedback mechanism described above to raise the inverting input to the same potential of 200mV.

This means that 200mV is applied across the 200 ohm resistor connected from the inverting input to the OV line. As a result one

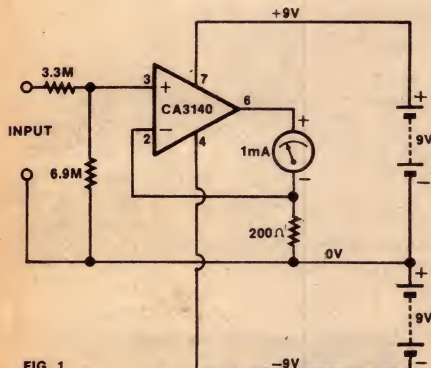


FIG. 1

*This circuit is that of a basic DC voltmeter. The input impedance is determined by the input resistors.*





## by LEO SIMPSON and DAVID EDWARDS

milliamp flows through the resistor and that same current (which is supplied from the output of the op amp) flows through the meter, causing the pointer to deflect full scale.

The circuit can be used to measure AC voltages by a small modification. If an AC voltage of 300mV RMS is applied to the circuit input, the voltage divider will act as before and apply 200mV RMS to the non-inverting input. This means that 200mV RMS is applied across the 200 ohm resistor, and an alternating current of one milliamp RMS flows through the resistor and the meter movement.

Ordinarily a meter movement would not indicate this current, but when connected within a bridge rectifier it will show the current. And even though the input voltage to the op-amp is quite low, the voltage losses and non-linearities of the bridge rectifier tend to be cancelled by virtue of it be-

ing within the feedback loop.

This does not overcome all the problems of reading the value of an AC waveform. AC voltmeters are normally required to indicate the RMS value of a sine wave signal. However, moving coil meter movements respond to the average value of their driving current. The average value of a sine wave voltage (or current) is very close to 90% of its RMS value. Accordingly, for our op-amp circuit to read sine wave signals correctly, the value of the current sink resistor must be reduced by 10 per cent, to 180 ohms. Fig 2. shows how the basic circuit has been modified to read AC signals. The addition of the capacitor at the input of the circuit prevents it from responding to DC signals.

Referring back to the complete circuit diagram, we can now discuss the input voltage divider. This has the desirable feature of providing voltage ranges which increase in 10dB steps, arranged by making the ratio between consecutive ranges is close approximation to the square root of ten, 3.1622... As you can see this has been achieved using preferred value resistors and without the need for parallel combinations. The total divider adds up to just over 10 megohms.

Six voltage ranges are provided, with FSD values of 316mV, 1V, 3.16V, 10V, 31.6V and 100V. The voltage divider is frequency compensated with capacitors shunting each resistor in the divider. The idea behind this is "swamp out" the effects of the input capacitance of the op-amp (typically several picofarads) and the stray capacitance of the input switch and associated wiring.

To this end, the highest value resistor in the divider chain is shunted with a 47pF capacitor. The capacitors shunting consecutive divider resistors increase by the same proportion (3.16) as the ratio between consecutive ranges. The total effective capacitance of the capacitors shunting the

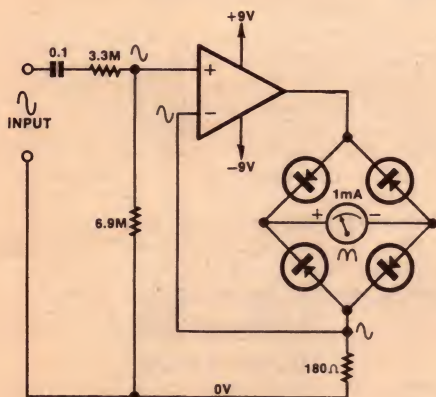


FIG. 2

Compare this circuit with that of Fig. 1, to see how an AC range is added to the basic DC meter.

## PARTS LIST

- 1 plastic case with aluminium lid, 197 x 60 x 112mm
- 1 screen-printed and punched control panel
- 1 meter movement, 1mA FSD, to suit case
- 1 PCB, 78mV8, 87 x 74mm
- 1 2-pole, 6-position rotary switch
- 1 4-pole, 2-position toggle switch
- 1 2-pole, 2-position toggle switch
- 2 Eveready 216 9V batteries plus connectors
- 2 banana jack sockets, one red, one black
- 1 knob

### SEMICONDUCTORS

- 1 CA3140 FET-input op amp
- 4 OA91 or similar germanium diodes

### CAPACITORS

- 2 x 100uF/16VW PC electrolytic
- 1 x 0.1uF/600VW polycarbonate
- 3 x 0.1uF polyester or ceramic
- 1 x .01uF polyester
- 1 x .0047uF polyester or polystyrene
- 1 x .0015uF polyester or polystyrene
- 1 x 470pF polystyrene
- 1 x 150pF polystyrene
- 1 x 47pF polystyrene
- 1 x 68pF polystyrene
- 1 10-40pF ceramic trimmer (Stettner)

### RESISTORS

- (1/4 or 1/2W, 5% tolerance, unless otherwise specified)
- 1 x 4.7M/1W, 1 x 3.3M/1W, 1 x 1.5M, 1 x 470k, 1 x 150k, 1 x 47k, 4 x 22k, 2 x 10k, 1 x 1k, 1 x 220 ohms, 1 x 150 ohms, 2 x 8.2 ohms, 1 x 10k trimpot, 1 x 470 ohms trimpot

### MISCELLANEOUS

- 4 rubber feet
- 12 PC pins
- Aluminium battery bracket, hook-up wire, tinned copper wire (22 B&S or thicker), shielded cable, solder.

*Note: Capacitors and resistors with higher ratings may be used if physically compatible. Where capacitor voltage ratings are not quoted, the rating is unimportant.*

divider string (not including the 3.3M resistor) is 36 picofarads which gives a time-constant for the divider of 248 microseconds.

To nullify the severe high-frequency roll-off effect that this time constant would otherwise have, the 3.3M input resistor is bypassed with a parallel combination of a 68pF capacitor and 10-pF trimmer. This enables the AC performance of the circuit to be optimised for flat response to beyond 100kHz.

A few other aspects of the circuit remain to be discussed. The 10k resistors in series with the two inputs of the op amp, together with protection diodes on the chip itself,




# Central Data

## Get into computing the economical, expandable way
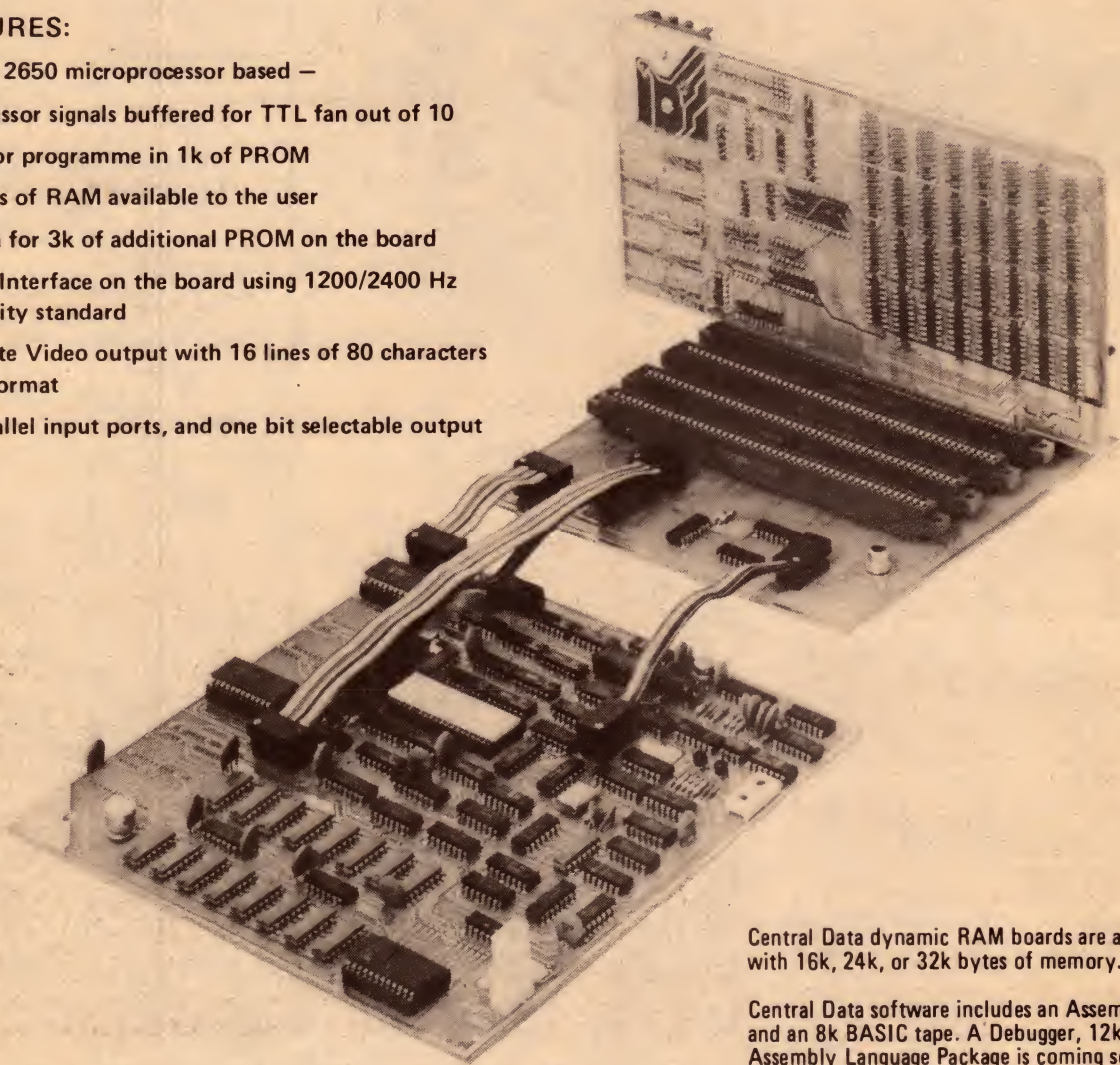
### FEATURES:

- \* Signetics 2650 microprocessor based —
- \* All processor signals buffered for TTL fan out of 10
- \* Supervisor programme in 1k of PROM
- \* 730 bytes of RAM available to the user
- \* Provision for 3k of additional PROM on the board
- \* Cassette Interface on the board using 1200/2400 Hz Kansas City standard
- \* Composite Video output with 16 lines of 80 characters display format
- \* Two parallel input ports, and one bit selectable output port



The Central Data System Board CDYSBDA facilitates the writing of programmes in Hexademical with only the addition of a TV monitor, ASCII Keyboard and power supply.

The System Board can be expanded by connecting the S-100 Board CDS100BDA. This allows you to plug in any S-100 static memory board with an access time of less than 500ns or the Central Data dynamic RAM boards CDXXKBDA.

Central Data dynamic RAM boards are available with 16k, 24k, or 32k bytes of memory.

Central Data software includes an Assembler/Editor and an 8k BASIC tape. A Debugger, 12k BASIC and Assembly Language Package is coming soon.

Other hardware now available and on the way includes Central Data Computer Mainframe with Power Supply, ASCII keyboard with solid-state low-profile keyswitches and +5 volt operation and Floppy Disc controller with one, two or three drives.

For general and specific information:

**TECNICO ELECTRONICS**



Premier Street, Marrickville,  
N.S.W. 2204. Tel. 55 0411.

2 High Street, Northcote,  
Vic. 3070. Tel. 489 9322.







K  
I  
T  
SK  
I  
T  
S**E.T.I. 137 AUDIO OSCILATOR — \$105.04**

(complete kit)

(inc. tax)

**OR INDIVIDUAL COMPONENTS AS REQUIRED**

WHOLESALE AND RETAIL COMPONENT PARTS AND KITSET SPECIALISTS.  
 PROMPT AND EFFICIENT ATTENTION THROUGH OUR MAIL ORDER DEPARTMENT.

**ENQUIRIES WELCOME***ONLY "RECOGNISED BRANDS" AND TOP QUALITY COMPONENTS STOCKED.*

## CHECK OUR ENORMOUS RANGE OF PRINTED CIRCUIT BOARDS FOR E.A. AND E.T.I. PROJECTS

**ET BOARDS:**

001, 003, 004, 005, 005A, 006, 007, 008, 011, 012, 017, 018, 019, 021, 022, 023, 025, 026, 029,  
 034A, 037, 038, 039, 040, 043, 044, 047-048-066, 061, 062, 063, 064, 065, 067, 068, 071, 072,  
 081, 083, 084, 085.

**ETI BOARDS:**

111, 113, 114, 116, 117A, 117B, 118, 119, 120, 121, 122, 123A, 123B, 124, 128, 129, 130, 131,  
 132, 133, 134, 135, 136, 137A, 137B, 139, 140A, 140D, 140P, 218, 240, 245, 246, 248, 305, 309,  
 311, 312, 313, 314, 316, 317, 413, 414A, 414B, 414C, 414D (1), 414D (2), 414E, 416, 417, 419,  
 420B, 420C, 420D, 420E, 420G, 422, 423, 424, 426, 427, 428, 429, 430, 433A, 433B, 438, 439,  
 440, 441, 443, 444S, 444 CON, 444, 445, 446, 447, 448, 448A, 449, 480, 480 PS, 481 PS, 482A,  
 482B, 482 REAR, 484, 485, 486, 487A, 487B, 489A, 489B, 514B, 518, 520A, 520B, 524, 527, 528,  
 529A, 529B, 524, 527, 528, 529A, 529B, 532, 533A, 533B, 533C, 534, 539, 540, 541, 544, 546,  
 547, 548, 549A, 581, 582A, 582B, 583, 585R, 585T, 586, 587, 588, 588C, 591A, 591B, 602, 603,  
 604, 630, 631, 631-2, 632, 632, 632A, 632B, 632C, 632m, 632p, 632U, 633, 635, 637, 638A, 638B,  
 701, 702, 704, 706, 707A, 707B, 708, 710, 711A, 711B, 711C, 711D, 711R, 712, 713, 715, 716,  
 717, 740A, 740B, 780A, 780B, 804, UTILIBOARD, 806, 810.

**E/A BOARDS:**

65/P10, 745/TAA300, 67/A4, 67/P5, 68/T5, 68/A8 MONO, 68/8T, 68/09, 68/M12, 69/P5,  
 69/01, 69/P9, 69/C12, 69/F10, 69/C11, 70/A1, 70/R1, 70/P1, 70/C1, 70/C4, 70/Tx1, 70/BF08,  
 70/K6, 70/P6, 70/G7 70/CD1, 70/A2, 70/Tx2, 70/RD1, 70/PA1, 70/SC1, 71 TU2, 71/R1, 70/F10,  
 71/D3, 71/SA4A, 71/SA4B, 71/SA4C, 71/A8, 71/W7A & B, 71/P8, 71/T12, 71/C12, 72/A6,  
 72/MX6, 72/P3, 72/R2, 72/SA1, 72/T3, 72/PS6, 72/C2, 72/C8, 72/IF6, 72/R9, 72/G7, 72/S10,  
 72/I10, 72/SA9, 72/SA10, 72/S11, 72/I1T, 73/VIA, 73/VIB, 73/T1, 73/3C, 73/D1, 73/S6,  
 73 TU7, 73 TU11, 73 P11, 73/C12, 73/12T, 74/A1, 74/S3, 74/SA5, 74/EM9, 74/C9, 74/08,  
 E8/A, E8/C, E8/D, E8/F, E8/M, E8/S, E8/T, E8/X, E8/10T, E8/SRT, E8/K1, 74 mx 12A, 74 mx  
 12B, 74 mx 12C, 74 mx 12D, 75 Ao1, 75 W3, 75 SD4, 75 FM5, 75 CD7, 75 TU9, 75 FE5, 75 T19, 75  
 TM11, 75 C11, 75, F2, 75/V12, 75/PC12.

76/F1, 76/RT2, 76/T2, 76/E02(G), 76/G3, 76/S3, 76/A03, 76/A3, 76/SA4, 76/VH5, 76/M5,  
 76/CM5, SYNC-A-SLIDE, 76/S7, 76/M17, 76 PC9, 76 E04, 76 M19, 76 B4, 76 R12, 76 CL12, 77  
 TU2, 77 TTY3, 77FIA, 77 FIB, 77 CC4, 77 TT4, 77 PRE5, 77 UP2, 77 UP5, 77 UP6, 77 E05, 77 B7,  
 77/TTY6, 77/TTY7, 77/D7, 77/D7, 77/BFQ7, 77/AL/B, 77/T10, 77/DVM9, 77/DIT7, 77/up11,  
 77/pm12, 77/cb12, 77/th12, 77/up6a, 78/cf1, 78/c2, 78/ek3, 78/d2, vid term board, 78/ia2, 78/t3,  
 78/s3, 78/ut4, 78/c5, 78/cp5, 78/ps5, 78/n6, 78/ao6, 78/tfc7, 78/vbg7.

Complete kits available for E.A. and E.T.I. projects.

Resistors (inc. large industrial types), capacitors, semi conductor devices, switches, meters, valves, metalwork, front panels, plugs,  
 sockets, cable connectors, transformers, speakers, etc. . .

**ALL ELECTRONIC COMPONENTS FOR FRIENDLY SERVICE AND PERSONAL ATTENTION.**  
**ALL ELECTRONIC COMPONENTS — THE FAMILY BUSINESS**

E. D. &amp; E. (SALES) PTY LTD

Now  
Trading  
as**ALL ELECTRONIC COMPONENTS**PHONE  
662-3506

118 LONSDALE STREET, MELBOURNE 3000

PHONE  
662-3506



## FET VOLTMETER

the PCB should be made of fibreglass but in any case, check it on the highest range of your ohm meter. The insulation resistance between two adjacent tracks of the PCB should be several hundred megohms or more.

Assembly can begin with the front panel hardware. The dress panel of the prototype was made from photosensitive aluminium, as was the meter scale. We hope that commercial panels will be available in due course but if not constructors can still make their own using Letraset. We have published the artwork as a guide.




The two nine volt batteries are held with a clamp made from a piece of aluminium approximately 90 x 40mm. It is held in place by the range selector switch. The voltage divider resistors and capacitors are wired directly to the range switch. The rest of the input components are suspended from the positive input terminal and AC/DC switch. The wiring diagram shows the details.

Ideally, the input voltage divider should use close tolerance components. We used a mixture of 1 per cent and 5 per cent resistors and 10 per cent capacitors, but still managed to obtain overall accuracy within  $\pm 2\%$  at full-scale deflection on all ranges.



The meter we used was a one-milliamp movement measuring 100 x 82mm, available from Dick Smith Electronics. It requires a panel cutout 60mm in diameter.

The front panel must be connected to the centre-tap of the battery supply. Use a solder lug secured by one of the meter mounting screws.

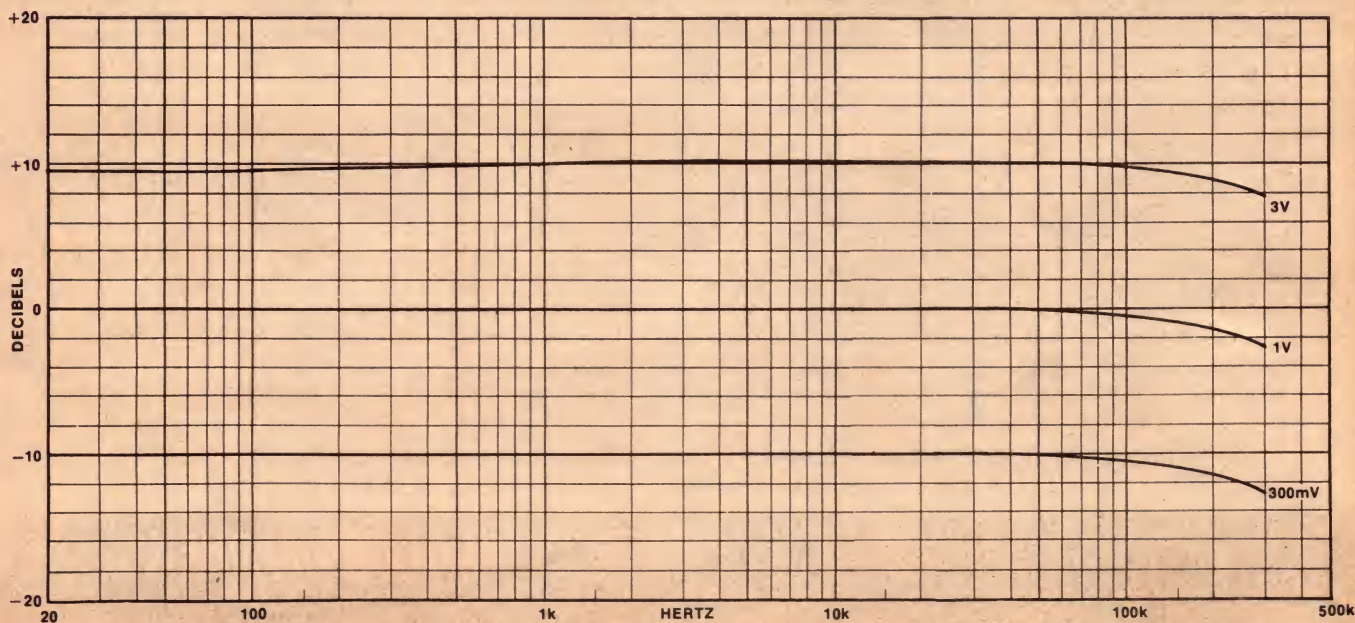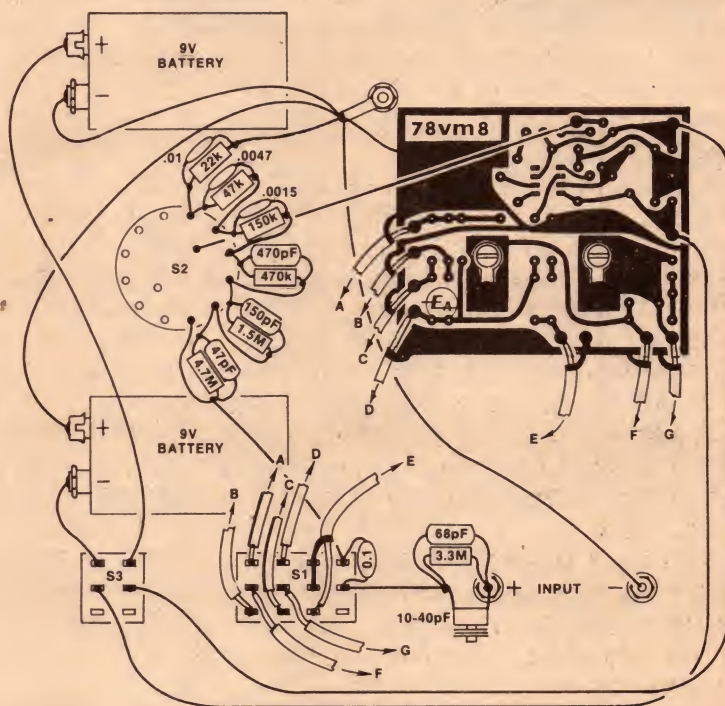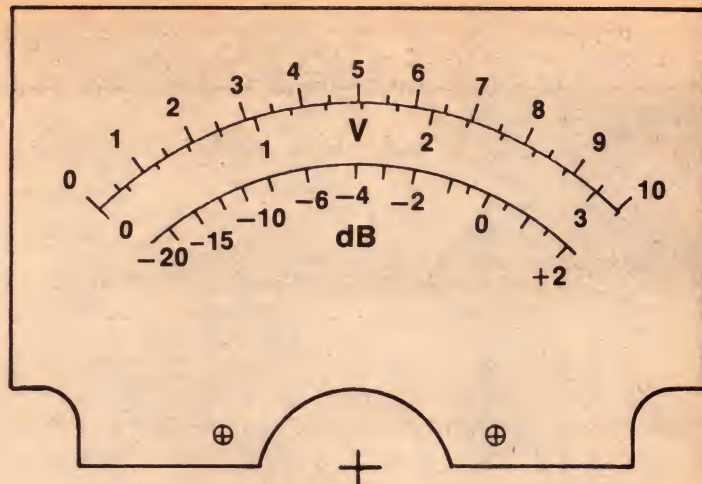At the top is a full size reproduction of the meter scale. Use the wiring diagram at the right to wire the range switch and to complete the remaining wiring. The frequency response curves for the three lowest ranges are shown below.





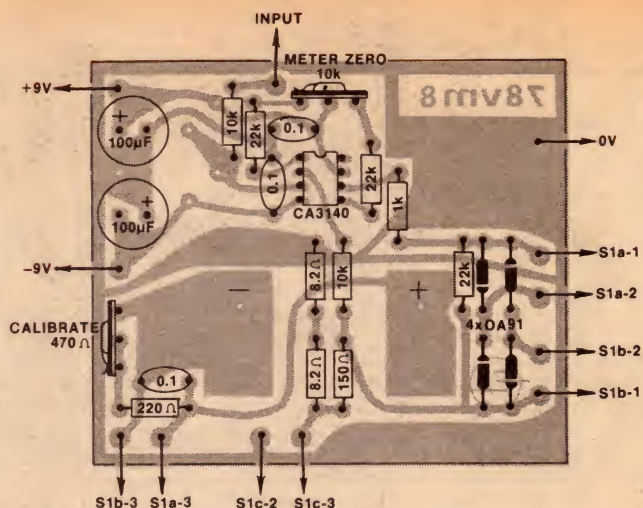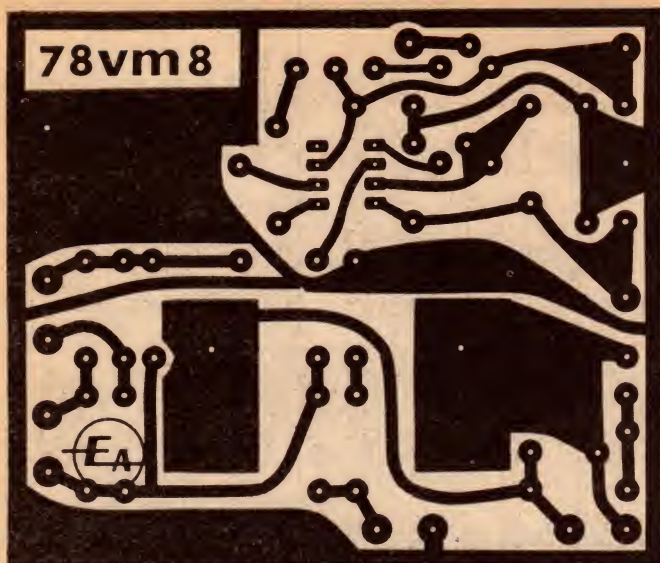

The PCB pattern to the left is actual size. The overlay diagram is reproduced above.

With the front panel wiring virtually complete, the PCB can be assembled.

Depending on the manufacturer, the CA3140 op-amp will be supplied in a TO-5 package with leads either in a circular pattern or formed to fit a dual in-line (Minidip) socket. If yours has the leads in a circular pattern they will have to be bent to fit the PCB. The IC should be pushed down so that it is as close as possible to the PCB. This is to provide clearance between the IC package and the meter housing. For the same reason, several of the capacitors will have to be laid flat.

The front panel artwork is reproduced actual size below, and can be copied or used directly.


The PCB is secured to the meter housing by the terminal screws. Put a solder lug under each screw and solder it to the PCB pattern. Use PCB pins for the interconnections. The shielded cables have their shields terminated at the perimeter of the PCB, with all but one left unconnected at the AC/DC switch to avoid earth loops. The wire connecting the range selector to the PCB is a length of tinned copper wire straightened and bent to suit.

With wiring complete, the unit should be double-checked before it is turned on and calibration performed. Before turning on, check that the meter indicates zero. If not, adjust the meter screw. Now turn on and check that the meter again reads zero. This

check should be done with the AC/DC switch set at DC. Adjust the offset trimpot if necessary.

The meter can be calibrated with a multimeter of known accuracy, if you have access to one. A digital instrument would be ideal. Just connect the two meters in parallel with a suitable voltage source. With the DC ranges calibrated, the AC ranges should also be correct, within the tolerance of the components used in the feedback network.

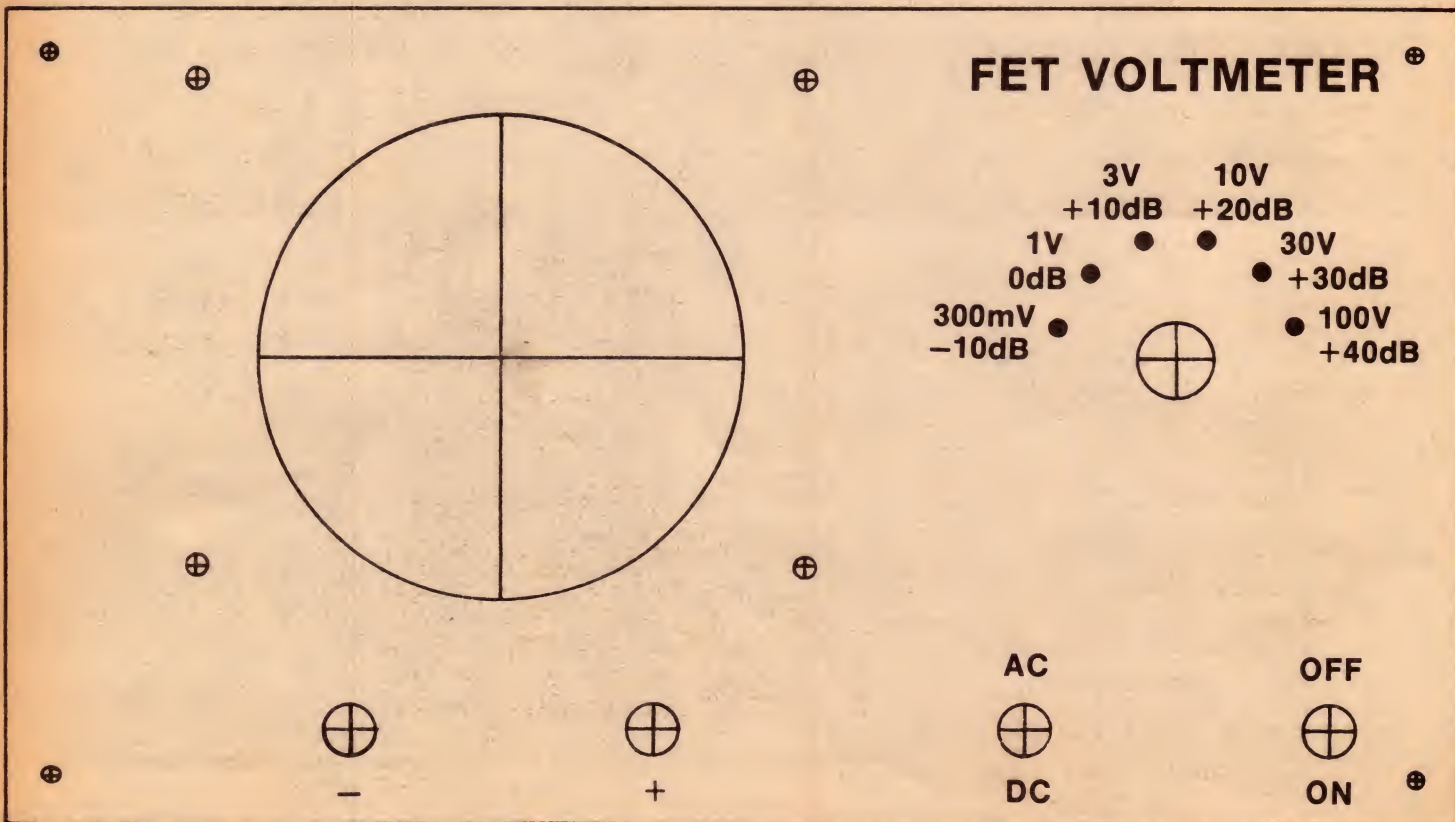The frequency compensation trimmer capacitor can be adjusted with the aid of an audio oscillator with a flat response to 300kHz or so. If such an instrument is not available, adjust the trimmer for about 70 per cent of its capacitance setting.





# How to crack a highly paid job as an electronics technician.



We'll give you excellent training - as good as you'll get anywhere in Australia.

We'll give you free medical, dental and hospital treatment.

We'll provide plenty of good tucker and a comfortable place to stay.

We'll give you substantial leave, and on top of all that, we'll pay you well while you're training.

On your side, you'll give us a period of hard, but interesting and rewarding work. And, when eventually you leave us, you'll find yourself a fully qualified and experienced Electronics Technician. Not a bad thing to be, these days.

So, if electronics is your idea of a great career and you are (at time of entry) approx. 15 to 17 for apprenticeship

and over 17 for an Adult Trainee, join the Navy, Army or Air Force.


Phone us at:

Adelaide 223 2891. Brisbane 226 2626.  
Canberra 822 333 Hobart 34 7077.  
Melbourne 61 3731. Perth 325 6222.  
Sydney 212 1011.

Write to either the Navy, Army or Air Force Electronics Technician Counsellor, GPO Box XYZ in your nearest State Capital City (please

include your date of birth).

**Learn  
Electronics  
with us.**

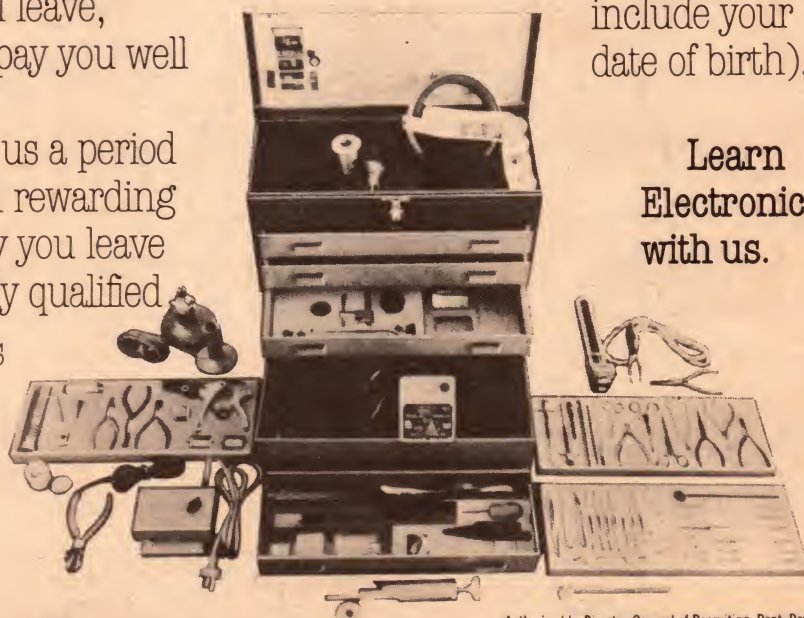

Authorised by Director-General of Recruiting, Dept. Defence.  
TSAP15.FP.48



# Software routines for your ultra-low cost VDU

In this second article describing his ultra-low cost video display for microprocessors using the software-driven DMA technique, the author presents some software routines for its use. These demonstrate the flexibility of software control compared with hardware, and also serve to provide the display with facilities similar to those of a conventional video terminal.

by **DAVID L. CRAIG** 134 Victor Street, Holland Park, Queensland

Owing to space limitations, the PC board patterns and wiring diagram were held over from last month and are shown in this article. Using these diagrams you should be able to produce a PC board for the VDU and also wire it up easily. Note that the board is designed to connect to Motorola CPU boards using the 6800 microprocessor, as explained last month, although it should be capable of being connected to a variety of other CPUs.

Once construction is complete, the VDU can be used immediately, simply by addressing the required display memory location and changing the contents to the ASCII code for the

character to be displayed. This can be done using the "Memory Change" function of the microprocessor system monitor ROM, or by having a user program store data at the location. Where random changes to the display are required, e.g., in video games, this method is probably best.


However, where changes to the data displayed are to be made in some fixed format, it is more efficient to use a program subroutine to control the output of data and to keep track of the address of the next location to be sent data. An important example is the serial output of data to a teletype or a conventional VDU.

To demonstrate the flexibility of us-

ing software to control the output of data to the display, a subroutine which allows the display to simulate the operation of a conventional VDU is presented below. This is useful not only as an example of the flexibility of the VDU, but because many programs a user may acquire are written to output data to a teletype or a conventional VDU (which merely simulates a teletype printer).

Programs written to work with a teletype generally use a subroutine to control the output of characters to the printer. For example, programs written for Motorola 6800 systems using MIKBUG or MINIBUG monitor ROMs generally output a character by loading the A accumulator with the ASCII code for the character, and then jumping or branching to a subroutine called OUTCH in the monitor ROM which actually outputs the character to the teletype.

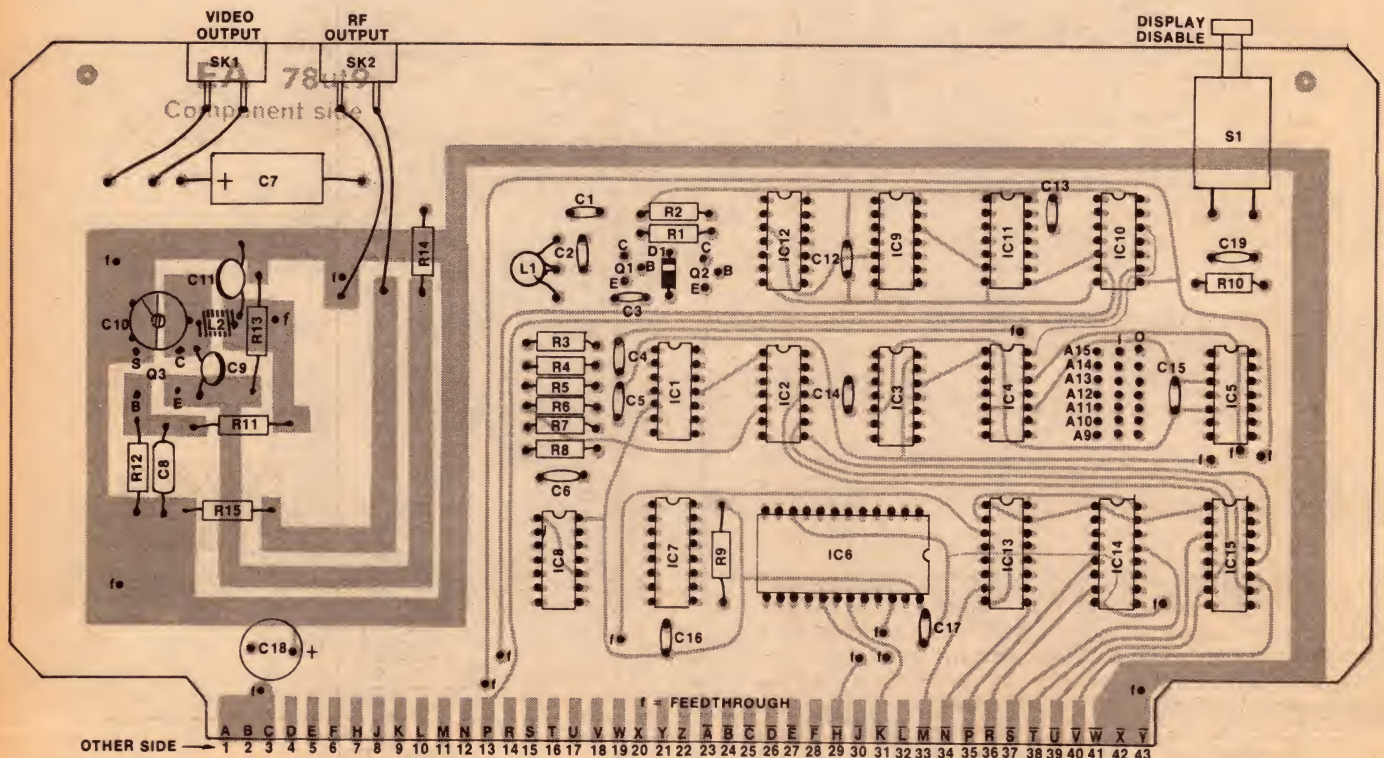The subroutine presented here, called VIDEO P, replaces the MIKBUG or MINIBUG OUTCH routine when this



The wiring diagram for the PCB of the VDU. Use it with the circuit given last month.



# 'VIDEO' SUBROUTINE LISTING

Subroutine to output an ASCII character to the VDU

|      |       |                            |                                                                                                    |
|------|-------|----------------------------|----------------------------------------------------------------------------------------------------|
| 00F2 | TEMP1 | RMB 2                      | Temp.pointer storage                                                                               |
| 00F4 | TEMP2 | RMB 2                      | Temp.pointer storage                                                                               |
| 00F6 | TEMP3 | RMB 2                      | Temp.pointer storage                                                                               |
| 00F8 | --00  | VIDPTR EQU VDSTRT          | Video display pointer                                                                              |
| 00FA | --00  | VDSTRT EQU \$--00          | Display buffer start address                                                                       |
| 00FC | --00  | VIDEND EQU VDSTRT + \$0200 | Display buffer end address +1                                                                      |
| 00FE | --20  | VIDL12 EQU VDSTRT + \$0020 | Start address 2nd display line                                                                     |
|      |       |                            |                                                                                                    |
| 0144 | 36    | VIDEOP PSMB                | Save accumulators                                                                                  |
| 0145 | 37    | PSMB                       |                                                                                                    |
| 0146 | DE FC | LDX VIDEND                 |                                                                                                    |
| 0148 | DF F6 | STX TEMP3                  |                                                                                                    |
| 014A | DE F8 | LDX VIDPTR                 | Load display pointer                                                                               |
| 014C | 8A 80 | ORAA #\$80                 | Normalize left most ASCII bit                                                                      |
| 014E | 85 60 | BITA #\$60                 | Test for control character                                                                         |
| 0150 | 27 21 | BEQ CCHAR                  | Go to control char. routine                                                                        |
| 0152 | 8D 19 | BSR OPCHAR                 | Output character                                                                                   |
|      |       |                            |                                                                                                    |
| 0154 | 9C FC | PAGEND CPX VIDEND          | Test for end of page                                                                               |
| 0156 | 26 0C | BNE CURSOP                 | Output cursor                                                                                      |
| 0158 | DE FA | LDX VDSTRT                 |                                                                                                    |
| 015A | DF F4 | STX TEMP2                  |                                                                                                    |
| 015C | DE FE | LDX VIDL12                 |                                                                                                    |
| 015E | 8D 40 | BSR MCOPY                  | Shift display up 1 line                                                                            |
| 0160 | DE F4 | LDX TEMP2                  | Clear last line and set pointer to start of last line                                              |
| 0162 | 8D 4F | BSR VIDBLK                 |                                                                                                    |
|      |       |                            |                                                                                                    |
| 0164 | DE F8 | CURSOP LDX VIDPTR          | Output ASCII underline as cursor                                                                   |
| 0166 | C6 DF | LDAB #\$DF                 |                                                                                                    |
| 0168 | E7 00 | STAB 0,X                   |                                                                                                    |
|      |       |                            |                                                                                                    |
| 016A | 33    | VIDRET PULB                | Restore accumulators and return                                                                    |
| 016B | 32    | PULA                       |                                                                                                    |
| 016C | 39    | RTS                        |                                                                                                    |
|      |       |                            |                                                                                                    |
| 016D | A7 00 | OPCHAR STAA 0,X            | Store character                                                                                    |
| 016F | 08    | INX                        | Update pointer                                                                                     |
| 0170 | DF F8 | STX VIDPTR                 |                                                                                                    |
| 0172 | 39    | RTS                        |                                                                                                    |
|      |       |                            |                                                                                                    |
| 0173 | 81 8D | CCHAR CMPA #\$8D           | Test for carriage return                                                                           |
| 0175 | 26 0C | BNE NOTCR                  |                                                                                                    |
| 0177 | 86 A0 | LDAA #\$A0                 | ASCII space                                                                                        |
| 0179 | C6 1F | LDAB #\$1F                 | Mask to test for new line                                                                          |
| 017B | 8D F0 | CCHARI BSR OPCHAR          |                                                                                                    |
| 017D | 05 F9 | BITB VIDPTR + 1            | Test for new line                                                                                  |
| 017F | 26 FA | BNE CCHARI                 |                                                                                                    |
| 0181 | 20 D1 | BRA PAGEND                 | Test for end of page                                                                               |
| 0183 | 81 88 | NOTCR CMPA #\$88           | Test for backspace                                                                                 |
| 0185 | 26 00 | BNE NOTBS                  |                                                                                                    |
| 0187 | 9C FA | CPX VDSTRT                 | Ignore BS if pointer is at start of buffer                                                         |
| 0189 | 27 DF | BEQ VIDRET                 |                                                                                                    |
| 018B | 86 A0 | LDAA #\$A0                 | ASCII space                                                                                        |
| 018D | A7 00 | STAA 0,X                   | Store space                                                                                        |
| 018F | 09    | DEX                        | Update pointer                                                                                     |
| 0190 | DF F8 | STX VIDPTR                 |                                                                                                    |
| 0192 | 20 D0 | BRA CURSOP                 | Output cursor                                                                                      |
|      |       |                            |                                                                                                    |
| 0194 | 81 8C | NOTBS CMPA #\$8C           | Test for form feed                                                                                 |
| 0196 | 26 D2 | BNE VIDRET                 | Ignore input                                                                                       |
| 0198 | 86 A0 | LDAA #\$A0                 | ASCII space                                                                                        |
| 019A | DE FA | LDX VDSTRT                 | Clear display and set pointer to start                                                             |
| 019C | 8D 15 | BSR VIDBLK                 | Output cursor                                                                                      |
| 019E | 20 C4 | BRA CURSOP                 |                                                                                                    |
|      |       |                            |                                                                                                    |
| 01A0 | A6 00 | MCOPY LDAA 0,X             | General purpose subroutine for copying a block of data from one set of memory locations to another |
| 01A2 | 08    | INX                        |                                                                                                    |
| 01A3 | DF F2 | STX TEMP1                  |                                                                                                    |
| 01A5 | DE F4 | LDX TEMP2                  |                                                                                                    |
| 01A7 | A7 00 | STAA 0,X                   |                                                                                                    |
| 01A9 | 08    | INX                        |                                                                                                    |
| 01AA | DF F4 | STX TEMP2                  |                                                                                                    |
| 01AC | DE F2 | LDX TEMP1                  |                                                                                                    |
| 01AE | 9C F6 | CPX TEMP3                  |                                                                                                    |
| 01B0 | 26 EE | BNE MCOPY                  |                                                                                                    |
| 01B2 | 39    | RTS                        |                                                                                                    |
|      |       |                            |                                                                                                    |
| 01B3 | DF F8 | VIDBLK STX VIDPTR          |                                                                                                    |
| 01B5 | 86 A0 | LDAA #\$A0                 |                                                                                                    |
|      |       |                            |                                                                                                    |
| 01B7 | A7 00 | MCONST STAA 0,X            | General purpose subroutine for storing a constant in a block of memory                             |
| 01B9 | 08    | INX                        |                                                                                                    |
| 01BA | 9C F6 | CPX TEMP3                  |                                                                                                    |
| 01BC | 26 F9 | BNE MCONST                 |                                                                                                    |
| 01BE | 39    | RTS                        |                                                                                                    |

Here are the author's listings of the VDU service routines, with a flowchart for the main routine.

VDU is used. The ASCII representation for the character to be output is loaded into the A accumulator and the VIDEOP subroutine called to write the character into the display. In this way existing programs written for use with systems with MIKBUG or MINIBUG monitors can be used simply by changing the output subroutine jump address. The routine described below is written for a Motorola 6800, but could readily be rewritten for use with other CPUs.

# 'OPHEX' SUBROUTINE LISTING

Subroutine to output a data byte to the VDU as 2 hex characters followed by 2 spaces

|      |       |                   |                                                                             |
|------|-------|-------------------|-----------------------------------------------------------------------------|
| 011A | 37    | OPHEX PSMB        | Save accumulator B                                                          |
| 011B | 8D 1D | BSR MDIS2         | Separate 2 hex characters                                                   |
| 011D | 8D 0F | BSR HEXASC        | Convert hex to ASCII                                                        |
| 011F | 8D 23 | BSR VIDEOP        | Output MS hex character                                                     |
| 0121 | 17    | TBA               |                                                                             |
| 0122 | 8D 0A | BSR HEXASC        |                                                                             |
| 0124 | 8D 1E | BSR VIDEOP        | Output LS hex character                                                     |
| 0126 | 86 A0 | LDAA #\$A0        | ASCII space                                                                 |
| 0128 | 8D 1A | BSR VIDEOP        | Output 2 spaces                                                             |
| 012A | 8D 18 | BSR VIDEOP        |                                                                             |
| 012C | 33    | PULB              | Restore accumulator B                                                       |
| 012D | 39    | RTS               |                                                                             |
| 012E | 81 0A | HEXASC CMPA #\$0A | Test hex value for number or alpha                                          |
| 0130 | 28 05 | BMI NUMBR         |                                                                             |
| 0132 | 8D 09 | SUBA #\$09        | convert alpha to ASCII                                                      |
| 0134 | 8A C0 | ORAA #\$C0        |                                                                             |
| 0136 | 39    | RTS               |                                                                             |
| 0137 | 8A 8D | NUMBR ORAA #\$8D  | Convert number to ASCII                                                     |
| 0139 | 39    | RTS               |                                                                             |
|      |       |                   |                                                                             |
| 013A | 16    | MDIS2 TAB         | Move low half word of A to B, and high half word of A to low half word of A |
| 013B | C4 0F | ANDB #\$0F        |                                                                             |
| 013D | 84 F0 | ANDA #\$F0        |                                                                             |
| 013F | 44    | LSRA              |                                                                             |
| 0140 | 44    | LSRA              |                                                                             |
| 0141 | 44    | LSRA              |                                                                             |
| 0142 | 44    | LSRA              |                                                                             |
| 0143 | 39    | RTS               |                                                                             |


# 'OPSTRG' AND 'OPXSTG' SUBROUTINE LISTINGS

Subroutine to output string of ASCII data to VDU

|      |        |                   |                              |
|------|--------|-------------------|------------------------------|
| 00F0 | STRING | RMB 2             | Temp. string pointer storage |
| 0100 | DF F0  | OPSTRG STX STRING | Save pointer                 |
| 0102 | A6 00  | LDAA 0,X          | Load data                    |
| 0104 | 8D 3E  | BSR VIDEOP        | Output data in ASCII         |
| 0106 | DE F0  | LDX STRING        | Recover pointer              |
| 0108 | 08     | INX               | Update pointer               |
| 0109 | 5A     | DECB              |                              |
| 010A | 26 F4  | BNE OPSTRG        | All bytes output?            |
| 010C | 39     | RTS               |                              |


Subroutine to output string of data bytes in hex to VDU

|      |       |                   |                    |
|------|-------|-------------------|--------------------|
| 0100 | DF F0 | OPXSTG STX STRING |                    |
| 010F | A6 00 | LDAA 0,X          |                    |
| 0111 | 8D 07 | BSR OPHEX         | Output data in hex |
| 0113 | DE F0 | LDX STRING        |                    |
| 0115 | 08    | INX               |                    |
| 0116 | 5A    | DECB              |                    |
| 0117 | 26 F4 | BNE OPXSTG        |                    |
| 0119 | 39    | RTS               |                    |

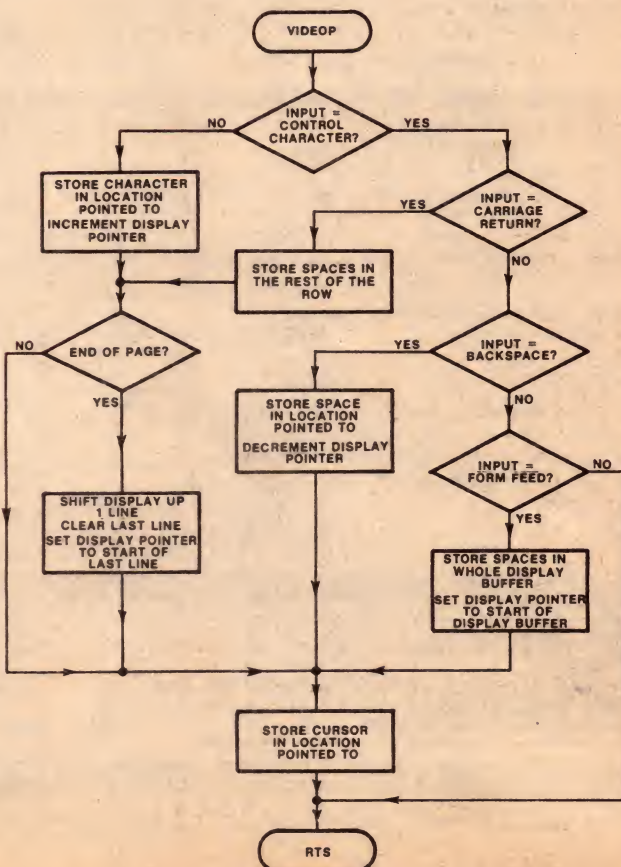



# DG 640 SOFTWARE CONTROLLED VDU

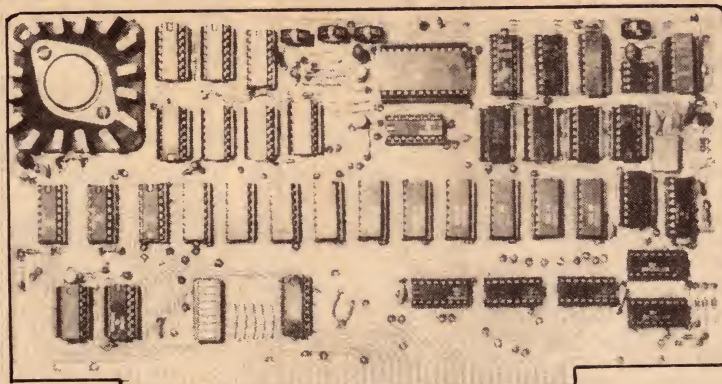

This superb design by David Griffiths and described in *ELECTRONICS TODAY* April, May, and June issues is possibly one of the most useful peripherals you can add to any microprocessor system.

Conforming to the hobby computer standard S100 bus, the DG640 is software controlled to produce

- 16 lines of 64 characters
- Upper and Lower case
- Black on white reversed characters
- Flashing characters
- Chunky graphics
- Direct RAM access

We are pleased to offer our EXCLUSIVE DG640 OWNERS MANUAL which expands the original ETI articles and covers such things as; step-by-step assembly, setting up and troubleshooting procedures typical waveforms, address decoding and software examples for use with 2650, 6800, 8080, Z80 microprocessors.

**ATTENTION 2650 USERS:** Ian Binnie has written a special operating system called "BINBUG" which is specifically designed to operate with the DG640 VDU and emulate "PIPBUG" thus ensuring that all software in the 2650 USERS GROUP is fully compatible and no I/O changes need be made. BINBUG is documented in the DG640 users manual and occupies 1K of RAM. Cassette tapes and a preprogrammed 2708 EPROM are available on request.

We are proud of the quality of the DG640 which uses a top grade plated through fibreglass PCB, reflow solder tinned and hard gold plated edge connectors. All components are prime quality and sockets are provided for all RAMS and the character ROM. The DG640 is not a beginners project but will suit even the most demanding microprocessor enthusiast. Each kit is backed by our famous technical support and warranty service (full details with each kit).

|                                |                                        |                               |                                         |
|--------------------------------|----------------------------------------|-------------------------------|-----------------------------------------|
| DG640 KIT COMPLETE WITH MANUAL | \$140 (tax paid)<br>\$126 (tax exempt) | DG640 PCB with manual         | \$35 (tax paid)<br>\$31.50 (tax exempt) |
| BINBUG CASSETTE FOR 2650       | \$5.00                                 | BINBUG IN PREPROGRAMMED EPROM | \$25.00                                 |

## 2650 SYSTEMS

EA2650 expandable to 4K as described in E.A. May and using the latest 2114 4K RAMS an ideal beginners project. We supply all parts except case and transformer (suitable cases and transformers available separately).

E.A. 2650 with all components and 1K RAM ..... \$89.50

### KT9500 FULLY BUFFERED CPU

This popular kit enables you to expand your 2650 system to a fully buffered system with 2 8 bit bidirectional I/O ports, RS232 interface, TTY interface and on board clock.

..... \$199.00

## NEW E.A. VIDEO DISPLAY TERMINAL

Described in E.A. Feb/April 1978 this is an ideal serial terminal for microprocessor applications. It is not software controlled like the DG640 and is ideal for beginners who need only a serial interface to the computer.

**KIT 1: VDU LOGIC BOARD** complete with all components, plated through PCB, assembly and troubleshooting manual ..... \$99.50

**KIT 2: ENCODER/UART/78UT4** complete kit with all components and instructions but without transformers (see Kit 5 option) ..... \$39.50

**KIT 3: KEYBOARD KB04.** A top quality keyboard kit with our own PCB designed to simplify construction and interface directly with the 78UT4 ENCODER ..... \$59.50

**KIT 4: MODULATOR** connects video signal to TV Aerial inputs ..... \$4.50

**KIT 5: HEAVY DUTY TRANSFORMER** supplies 8V @ 10 Amps + and - 16V at 1 Amp (ideal for later expansion to S100) ..... \$22.00


**KIT 6: METALWORK.** For a really professional finish we now have available limited stocks of a timber sided, marviplate/aluminium extrusion keyboard enclosure. This enclosure has adequate room for all kits and is cut out to fit the keyboard. A microprocessor can also fit in the case resulting in a complete home computer ..... \$49.50



POST & PACKAGING . . . \$2.00 all orders  
CERTIFIED MAIL . . . . . 0.50 extra  
REGISTERED MAIL . . . . . 2.00 extra

POSTAL ADDRESS—P.O. Box 311, Hornsby 2077  
HEAD OFFICE/SHOWROOM—109-111 Hunter St.,  
Hornsby (9.00—5.00, MON. to SAT.)

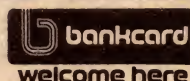PHONE: (02) 476 4758 General Enquiries — (02) 476 3759 (Technical Information)  
PRICES & SPECIFICATIONS SUBJECT TO CHANGE WITHOUT NOTICE





## LOW COST VDU

Each time the subroutine is called, the data in the A accumulator is stored into the next location in the display memory buffer. The subroutine maintains a pointer (VIDPTR), pointing to the next location in which data will be stored. An on-screen cursor displays this location. The cursor consists of an underline character stored in the display buffer where the next character will be written.

As characters are output to the buffer, the pointer is incremented by the subroutine. This results in an automatic carriage return/line feed (CR/LF) at the end of each display line. At the end of the display page, the display is scrolled up 1 line, the last line cleared, and the cursor pointed to the beginning of the last line. The contents of the first line are destroyed. Scrolling occurs each time the last line is filled, so that the previous 15 lines entered are always visible.

Three non-printing control characters are recognized by the subroutine. All others are ignored. Those recognized are Carriage Return (CR), Backspace (BS) and Form Feed (FF). They produce the following results:

- CR (ASCII \$0D) causes a combined CR/LF function, leaving the cursor pointing at the start of the next line.
- BS (ASCII \$08) causes a destructive backspace, leaving the cursor pointing at the previous location.
- FF (ASCII \$0C) clears the display and returns the cursor to the top of the display.


It should be noted that although only 6 bit ASCII codes are used by the VDU hardware to display characters, the full 7 bit ASCII must be output to the VIDEOP subroutine via the A accumulator to allow recognition of the control characters. The eighth bit (left-most) may be either 0 or 1.

Operation of the subroutine should readily be understood by examining the flowchart. A full listing of the subroutine is also given. The subroutine itself requires 123 memory locations and is relocatable, i.e., it can be loaded into any 123 consecutive memory locations without any alteration. The addresses given are simply for reference. In addition, 14 memory locations are required for data. These are fixed at \$00F2 — \$00FF, and are not relocatable unless all references to these locations in the subroutine are changed. The entry and exit conditions for the subroutine are as follows:


- entry — accumulator A contains the 7 bit ASCII code for character to be output
- exit — accumulators A and B unchanged, index register X entry value destroyed.

At right is the actual-size pattern for the component side of the PCB. That for the copper side is shown overleaf.

**EA 78ut9**  
Component side

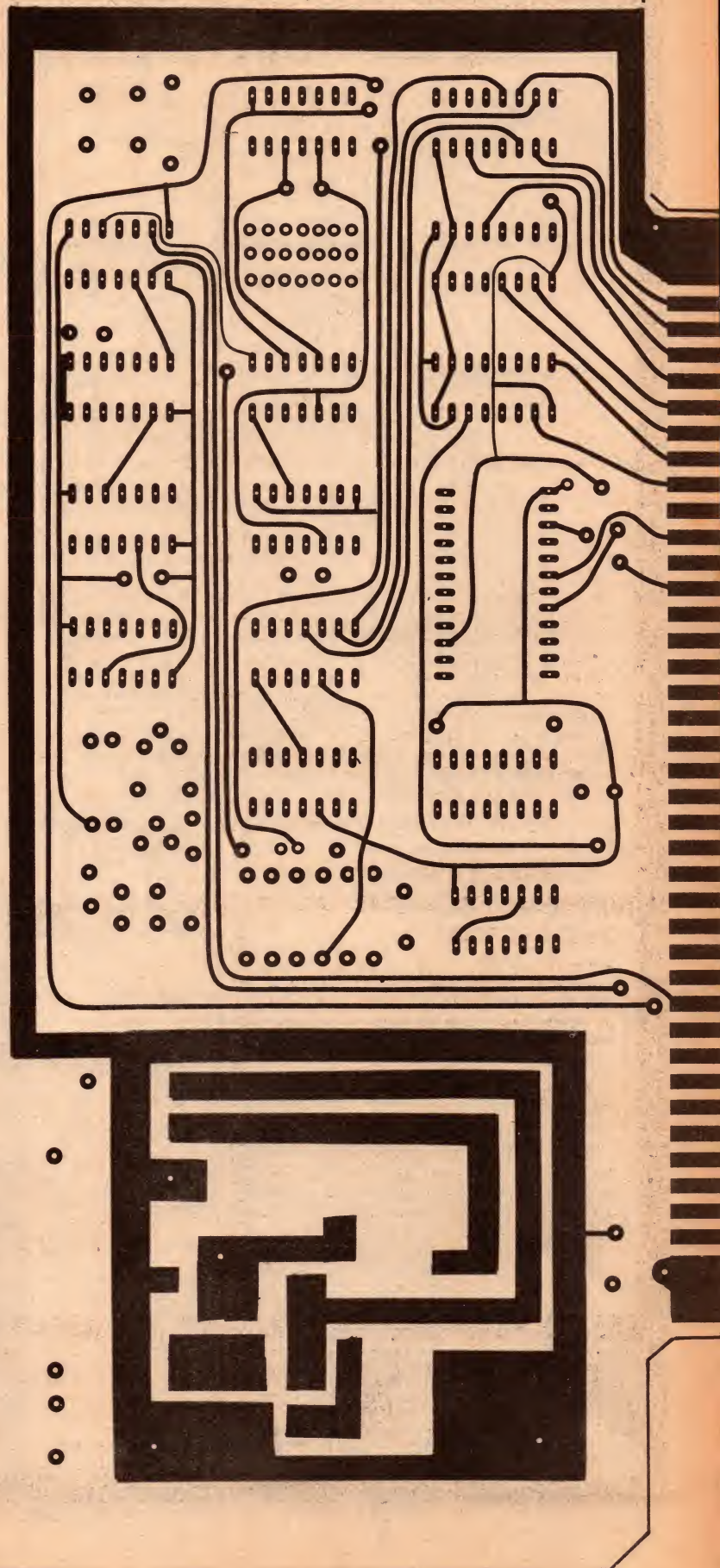



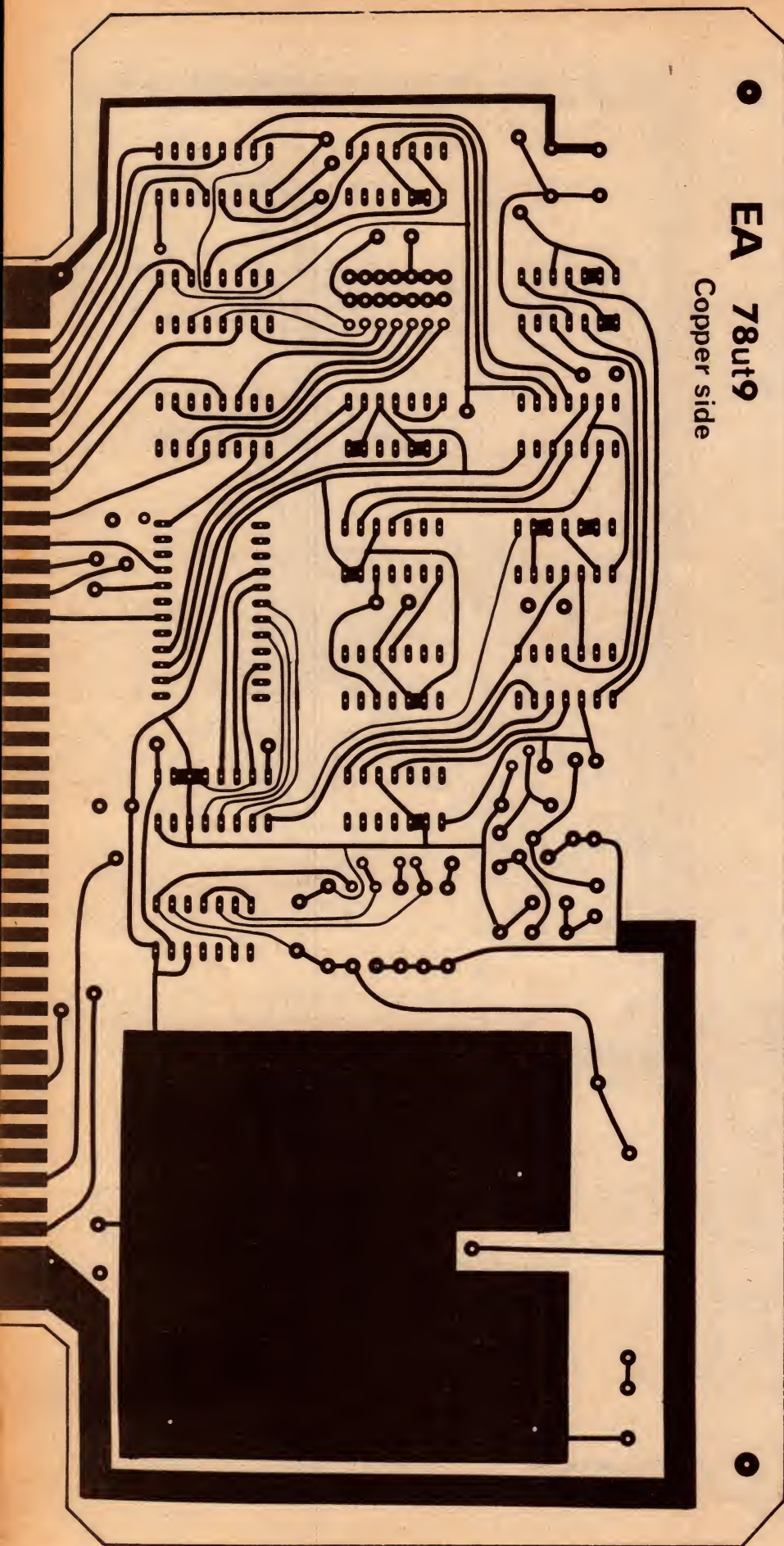

## LOW COST VDU

As will have been seen from the above description, using the VDU with VIDEOP provides a display device with all the facilities of a conventional VDU. If more facilities are required, e.g., if more text editing facilities are required, or additional control characters need to be recognized, it is a fairly simple matter to modify the subroutine to incorporate the changes.

Within the VIDEOP subroutine itself are two general purpose and very useful subroutines called MCOPY and MCONST.

MCOPY can be used to copy a block of data of any length from one area of memory to another. The entry conditions are:

X = FROM start address  
TEMP2 = TO start address  
TEMP3 = FROM end address + 1

The exit conditions are:

A = entry value destroyed  
X = TEMP1 = FROM end address + 1  
TEMP2 = TO end address + 1  
TEMP3 = unchanged

A point to watch with this subroutine is that if the FROM and TO address ranges overlap, the routine can only be used if the TO start address is less than the FROM start address.

MCONST is a subroutine which will store a constant value into a consecutive block of memory locations of any size. The entry conditions are:

A = constant to be stored  
X = start address  
TEMP3 = end address + 1

The exit conditions are:

A = unchanged  
X = end address + 1  
TEMP3 = unchanged

The MCONST and MCOPY subroutines can be used on their own to manipulate data for the display. For example, MCOPY can be used to save a page of display for later use by copying the display buffer to another 512 word block of memory. MCOPY can then be used to reload the display with the same page at a later time. MCONST can be used to clear, or to load the one character into, a number of lines or the whole display.

Also included in the listing are three other useful subroutines which extend the power of the VIDEOP subroutine. These are OPHEX, OPSTRG, and OPXSTG.

These are very simple subroutines which should be easily followed directly from the listing. No flowchart is given. They occupy 68 bytes and can be relocated without change provided they stay in the same position relative to VIDEOP. Two fixed data bytes are also required.

OPHEX is a subroutine to output a



data byte to the VDU as 2 hexadecimal characters followed by 2 spaces. The entry condition is:

A = data byte to be output

and the exit conditions are:

A, X = entry values destroyed

OPSTRG is a subroutine to output to the VDU a string of up to 256 ASCII characters stored in consecutive memory locations. The entry conditions are:

B = No. of characters in string

X = start address of string

and the exit conditions are

A, B, X = entry values destroyed

OPXSTG is a subroutine to output to the VDU a string of data bytes as groups of 2 hex characters separated by 2 spaces. The entry and exit conditions are the same as for OPSTRG.

The ASCII string output routine OPSTRG is useful in outputting messages to an operator in an interactive situation. A number of messages may be stored as part of the program in a compressed form using carriage returns to terminate lines and then output in the required format by specifying the start address and the number of characters and calling OPSTRG.

The hex output routines enable the contents of all 8 bits in memory locations to be displayed at once. (Remember that the ASCII output routines only use 6 of the 8 bits in each byte). This allows the VDU to be used as

a "super front-panel" for the microprocessor. Using OPXSTG the memory contents of any 128 consecutive memory locations can be displayed at once for examination. BCD data coded as 2 digits per byte can also be displayed using these routines.


Finally, here are some further ideas for using the VDU.


Because a conventional VDU can only receive and store characters serially at the rate of 1 character per TV frame, the variety of things that can be displayed is limited. On the other hand, this VDU is much more flexible in what it can display because random access is available for writing to the display memory.

While it is possible to display a list of values as a result of series of calculations, a much more convenient and easily interpreted method is to use a graph. A graphical display can only be obtained using a conventional VDU by completing all the calculations and storing the results in a buffer which is then output to the VDU. With this VDU plotting a graph is very simple. Because random access to the display buffer is available, points can be plotted on the display immediately they are calculated. Any character can be used to represent a graph point, but + or \* would be good choices. Axes can be put on the graph using ! characters for the vertical axis, and — for the horizontal axis. Scales can be added using numeric characters. Obviously resolu-

tion is limited with a 16 x 32 alphanumeric display, but it would be adequate for many purposes.

Video games become feasible with this VDU, because of the random high-speed memory access capability. Simplified versions of the currently popular "ping-pong" style TV games can be produced by setting up static boundaries in the display memory, feeding in bat position information through a PIA and calculating ball position. Bat and ball motion is easily displayed on this type of VDU. On-screen scoring can also be provided. Displays for noughts-and-crosses and many other games can be programmed. Simple video art displays with movement may also be produced.

Pages of display are easily saved on cassette and later reloaded because the VDU shares the CPU memory. The 512 word buffer accessed by the VDU can be dumped directly onto cassette using the PUNCH routine of many system monitor ROMs, and then reloaded directly using the monitor LOAD routine. By organizing the storage on cassette with file gaps between pages, any page can be readily located and reloaded into the display for examination or editing and then saved back on tape. Such a scheme could form the basis of a simple information storage and retrieval system. Depending on the length of file gaps used on the tape, a single C90 cassette would hold 100 or more pages of information. 



# ASP

## MICROCOMPUTERS

### SELECTRIC CONVERSIONS

Convert an IBM Selectric typewriter into a computer output printer. Available as a kit, assembled, or assembled onto a new Selectric. Includes S100 Interface Module, solenoid driver electronics & precision solenoid assembly to fit Selectric. Does not affect use as a typewriter

Australian Distributors for:  
INDUSTRIAL MICRO SYSTEMS  
ESCON PRODUCTS INC.

- DUAL DISK BASED S100 COMPUTERS WITH PRICES STARTING UNDER \$6,000 (32K) (plus Sales Tax)
- SELECTRIC CONVERSIONS - Convert an IBM Selectric typewriter into a computer output printer.
- SOFTWARE PACKAGES - Including Word Processor and Accounting.

DEALER ENQUIRIES INVITED  
(03) 870 9092

FIRST FLOOR MIDWAY ARCADE, 145 WHITEHORSE ROAD, RINGWOOD 3134.

\* SELECTRIC is a Trade Mark of IBM.



# ICS-STC CANNON

ANNOUNCING OUR NEW CANNON STOCKING DISTRIBUTORS.  
NOW AVAILABLE VAST RANGE OF CANNON CONNECTORS  
EG: XLP AUDIO; D SUB. MIN. ETC.

**"WHEREVER YOU ARE THERE IS A  
DISTRIBUTOR TO SERVICE YOUR  
REQUIREMENTS"**

**QLD:** ICS,  
Montague Rd,  
WEST END.  
(07) 44 6667

**Electronic Components,**  
Suite 16, 205 Moggill Rd,  
TARINGA.  
(07) 378 7979

**Fred Hoe & Sons,**  
246 Evans Road,  
SALISBURY NORTH.  
(07) 277 4311

**Total Elect.,**  
316 Adelaide St,  
BRISBANE.  
(07) 229 1633

**NSW:** ICS,  
16 Gertrude St,  
ARNCLIFFE.  
(02) 597 1444

**G. Brown & Co.,**  
174 Parramatta Rd,  
CAMPERDOWN.  
(02) 519 5855

**J. A. Severn,**  
50 Bambara Cres.,  
BEECROFT.  
(02) 869 1058

**Radio Despatch Service,**  
869 George St,  
SYDNEY.  
(02) 211 0191

**Total Elect.,**  
155 Willoughby Rd,  
CROWS NEST.  
(02) 439 6722

**VIC:** ICS,  
248 Wickham Rd,  
MOORABBIN.  
(03) 95 9566

**Browntronic,**  
93 Sackville St,  
COLLINGWOOD.  
(03) 419 3986

**Total Elect.,**  
239 Bay St,  
NORTH BRIGHTON.  
(03) 96 2891

**NEWCASTLE:**  
**Digitronics,**  
186 Parry Street,  
NEWCASTLE WEST.  
(049) 69 2040

**SA:** ICS,  
Suite 8, 147 Ward St,  
NORTH ADELAIDE.  
(08) 267 2393

**International  
Communication System P/L,**  
77 Dale Street,  
PORT ADELAIDE.  
(08) 47 3688

**Ktronics/Ktronics W/Sale**  
206 Wright Street,  
ADELAIDE.  
(08) 212 5505

**WA:** M J Bateman P/L,  
359 Scarborough Beach Rd,  
OSBORNE PARK.  
(09) 444 7788

**Reserve Elect.,**  
140 Loftus St,  
LEEDERVILLE.  
(09) 328 3116

**ACT:**  
**Electronic Components**  
29 Wollongong Street,  
FYSHWICK.  
(062) 80 4654

# CANNON CONNECTS



**Who can meet your  
greatest needs in  
D Subminiatures?**



**Cannon can!**

Six decades on the leading edge of interconnect technology.

**CANNON ITT**



# The down to earth

## CHROMDIOXID.

The day BASF introduced this product, is the day Hi-Fi quality came into cassette technology.

This cassette is the standard for Hi-Fi quality. It delivers an improved dynamic range and crystal clear, high level output. Particularly in the high frequency range, the distortion factor remains remarkably small.



The cassette started life as a controversial item and quite understandably was not taken too seriously.

In the past Hi-Fi quality could only be obtained from reel-to-reel tapes, but now chromium dioxide cassettes from BASF have also reached this Hi-Fi level.

In fact, BASF's chromium dioxide tape set the Hi-Fi standard to which most manufacturers still refer.

Where this improvement has taken place is mostly in the magnetic surfaces used to coat the tape. And, this is where another controversy reared its ugly head; the chrome controversy.

BASF have a straightforward position on chromium dioxide; it's the best.



Now BASF has introduced the new Chromdioxid Super.

By today's high standards of cassette technology, this is the ultimate cassette.


## On the surface of things chromium dioxide is better.

Chromium dioxide is man-made and the individual particles are 'grown' in much the same way as crystals are 'grown'. Ferric oxide on the other hand, has to be ground down to a suitable particle size. Whereas each chromium dioxide particle is a long, thin crystal, a ferric oxide particle is usually made up of a number of shorter crystals that have irregular off-shooting branches.

Through careful quality control during the production of the tape's surface, the uniformity of the chromium dioxide 'needles' (particles) can be merged to provide a better covered, more sensitive surface.

They all fit neatly together because they have no off-shooting branches which cause gaps or 'voids' between the particles. Signals cannot be recorded on these 'voids', therefore the  $\text{CrO}_2$  density of particles delivers higher output especially at high frequencies. You can examine this in the diagram that shows the gain in dynamic range of BASF Chromdioxid Super compared with BASF Chromdioxid and BASF LH.

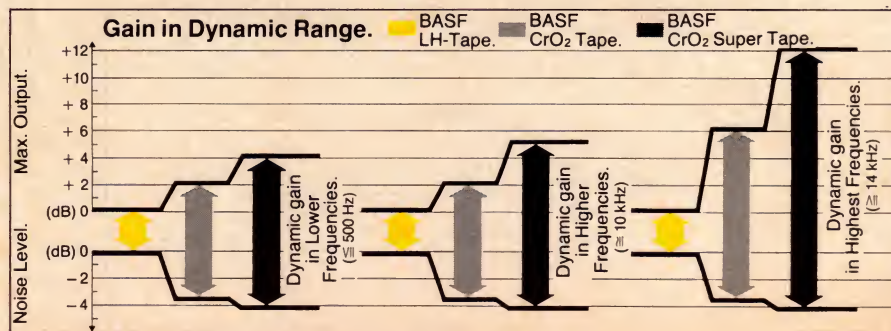Each  $\text{CrO}_2$  particle is one, individual non-porous crystal with one magnetic 'domain'. Because a ferric oxide particle is made up of a number of crystals each capable of holding their own signal, de-magnetization can occur, lowering the tape's recording efficiency.



Tested according to the Bias-setting of the Recorders.



# story on chrome.



## NEW CHROMDIOXID SUPER.

By today's high standards of cassette technology, this is the ultimate cassette.


BASF Chromdioxid Super delivers up to 10dB better high frequency headroom over the leading chrome substitutes in the 11-20kHz range. There is less headwear than with cobalt-doped cassettes. And, at least 2.4 dB lower noise level than competitive products.

## The end of the headwear rumour.

Very simply,  $\text{CrO}_2$  does not wear the tape head any worse, and in many cases a lot better, than ferri-oxide tapes. (See diagram.)
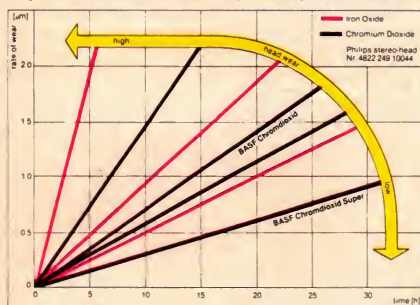
### Head Wear of Cassettes

$\text{CrO}_2$  and other tapes recommended for  $\text{CrO}_2$  bias setting and 70  $\mu\text{s}$  equalization



Du Pont, the giant American chemical company wrote: "Our tests showed  $\text{CrO}_2$  to be fully competitive in headwear characteristics with non oxide tapes, and in many cases superior." The choice of the oxide formula is not a significant factor in headwear. The main cause of contention over this issue results from a confusion between chrome, which is a hard material, and chromium dioxide, which is a different material with completely different properties. The hard chrome is not inserted into the highly sensitive tape surface.

## One tape is as good as the next.

Chromium dioxide is a uniform surface for the tape, which means that the quality and performance is uniform.


One BASF chromdioxid cassette bought one day, will perform as well as another BASF chromdioxid cassette, bought another day. And, the Security Mechanism, SM, which is patented to BASF, ensures the smooth running of the mechanics inside the cassette making sure the tape is transferred smoothly and accurately from one spool onto another.


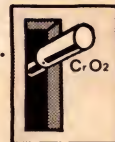
## Switch to BASF Chromdioxid.

One last thought. The value of chrome is clearly recognised by all equipment manufacturers who have all fitted the 'chrome switch' to their best recorders.

So, if you want genuine 'Hi-Fi' performances from your cassette recorder, switch to BASF chrome cassettes.



**BASF Cassettes.**  
**Purest quality across the range.**



# The competition don't like the sound of this at all.

For quite some time, other manufacturers have been trying to produce tape with the qualities of the Maxell UD-XL. At the same time, Maxell have been quietly perfecting an even better series.

The UD-XL I and UD-XL II tapes are designed to attain maximum performance at the ferric and chrome position on your tape deck. Whichever tape position you choose, Maxell can give you a better performance.

## **UD-XL I TAPE, FOR FERRIC (norm.) POSITION (120us)**

UD-XL I offers an excellent sensitivity of 1 dB higher than even UD-XL. MOL performance is also 1 dB higher over the entire audio frequency spectrum. The result is a new standard in ferric tape, with wider dynamic range and less distortion than ever before.

How does the UD-XL I compare then, with ordinary low-noise tapes?

Sensitivity is higher by 2.5 dB, and MOL performance by as much as 6 dB.

Yet, for all this UD-XL I requires no special bias or equalization. Simply set your tape selector as you normally would at the ferric position – but there the comparison ends.

## **UD-XL II TAPE, FOR THE CHROME POSITION (70us)**

UD-XL II tape is such a dramatic improvement on most other tape that can be used in this position, that comparison is really unfair.

For example, if you're familiar with conventional chromium-dioxide tape, you'll know of the associated problems of poor output uniformity – plus low maximum output level and rather high distortion.

UD-XL II tape offers you excellent MOL, sensitivity, and an output improvement of more than 2 dB over the entire frequency range.

Maxell's unique 'Epitaxial' process gives you absolute sensitivity and stability, and no drop-out problems. What's more, the shells are moulded in diamond cut dies, and made to tolerances 5 times greater than the Philips standard. And, like all Maxell tapes, UD-XL II has the 5-second cleaning leader.

In short, if you're recording in the chrome position, you can now achieve all the advantages – with none of the drawbacks.

A prospect we think you'll find very exciting – even if the competition don't.





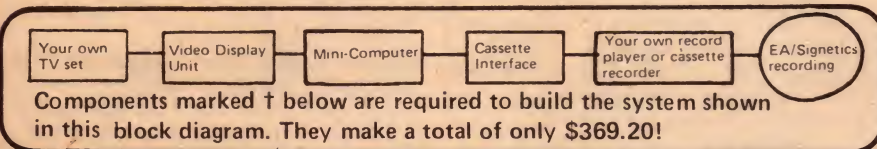
# BUILD YOUR OWN MINI-COMPUTER & SAVE!

A COMPLETE SYSTEM FOR JUST **\$369.20**

Here it is — the first system that enables you to break into the big time without spending big money! You don't have to know about computers to start — just imagine the astounded looks on your friends' faces when you tell them "I built it myself!" When you've built the system you can play games with your computer right away using the special EA/Signetics disc. Then, when you've gained some programming experience, you can use your computer for an incredible variety of tasks. A similar built-up system would cost well over \$800 - think of the money you'll save by building it yourself. It's easy with a Dick Smith kit!



## 2650 MINI-COMPUTER (See E.A. May '78)

Fantastic new 2650 Mini Computer. Complete kit includes all electronic parts, PC board and power supply plus case, Marvplate lid and deluxe brushed aluminium front panel.

Complete kit for above: Cat K-3447.....\$115.00+

### SEPARATE PARTS

PCB (78 up 5) fibreglass: Cat H-8341.....\$5.00

2650 microprocessor chip: Cat Z-9201.....\$28.50

2608/CN0035 pip bug 8k ROM: Cat Z-9309.....\$19.75

2114 ROM chip: Cat Z-9306.....\$14.50

### VIDEO DISPLAY UNIT (See E.A. Feb & May '78)

Incredibly low cost Video Display Unit uses your own TV set as the monitor.

Basic Video Display Kit: Cat K-3460.....\$97.50†

Video Modulator Kit for above: Cat K-3462.....\$4.50†

ASCII Keyboard Encoder kit for above: Cat K-3464.....\$39.50†

### SEPARATE PARTS

UART IC S1883/MM5303N/TMS6011: Cat Z-9204.....\$5.90†

Keyboard Console Metalwork: Cat H-3130.....\$24.50†

Keyboard (fully assembled): Cat X-1180.....\$55.00†

### CASSETTE TAPES

AC/DC cassette recorder ideal for this system.

Cassette recorder Cat A-4092.....\$39.95

Cassette tapes: C60 LN Cat C-3350.....\$1.50

C90 LN Cat C-3352.....\$2.00

Ask at any of our stores for your FREE copy of our new Mini-Computer brochure. Contains full details of our computer kits.

## CASSETTE INTERFACE

Enables your cassette recorder or record player to interface with mini-computers such as the 2650. Kit includes PC board and all components except power transformer. The complete PC board assembly will fit inside your 2650 mini-computer case, the 2650's transformer providing the AC power. We believe this kit to be the best available on the market to suit the 2650 system.

Complete kit (as above) Cat K-3465.....\$24.50+

PCB only (Cat H-8331).....\$3.75

## SOFTWARE RECORDING

This is a 33-1/3rpm recording of useful 2650 system software. Use it on your record player or dub onto a cassette and use it in your cassette interface system. Then you can program the 2650 for new programs and games. It contains 22 programs you can run.

Record Cat B-6300.....\$2.80+

## PAPER TAPE READER KIT

See page 33 of our new catalogue for full details. Ideal for use with the 2650 mini-computer. Kit includes all electronic components, handsome black anodised aluminium case, ribbon interface cable and complete assembly and interface instructions, schematics and software.

Tape Reader Cat K-3466.....\$95.00

# DICK SMITH ELECTRONICS



**SYDNEY** 125 York Street, SYDNEY. Ph. 29-1126  
147 Hume Hwy, CHULLORA. Ph. 642-8922  
162 Pacific Hwy, GORE HILL. Ph. 439-5311  
30 Grose Street, PARRAMATTA. Ph. 683-1133

**MELBOURNE** 399 Lonsdale Street, MELBOURNE. Ph. 67-9834  
656 Bridge Road, RICHMOND. Ph. 42-1614  
**BRISBANE** 166 Logan Road, BURANDA. Ph. 391-6233  
**ADELAIDE** 203 Wright Street, ADELAIDE. Ph. 212-1962

SHOPS OPEN 9AM to 5.30PM  
(Saturday 9AM - 12 noon)  
BRISBANE 1/2 Hour earlier.

ANY TERMS OFFERED ARE TO  
APPROVED APPLICANTS ONLY

Many lines available from the  
Dick Smith Electronics Centres at

**GRACE BROS**

Broadway • Bondi • Chatswood • Liverpool  
Miranda • Mt Druitt • Parramatta • Roselands  
and Warringah Mall




**MAIL ORDERS** P.O. Box 747, Crows Nest, N.S.W. 2065. Post and packing extra.

Dealers across Australia.



# Microcomputer News & Products

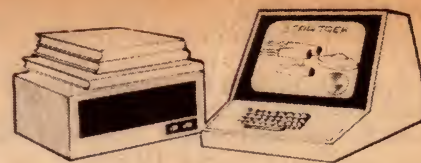

## National ACE

National Semiconductor has released a new software-programmable asynchronous communications element (ACE). The INS8250 device is similar to a UART, but in addition provides programmable baud rate and data format, status reporting and complete modem control.

Easily interfaced to most microprocessors, including the 8080A, SC/MP, PACE, Z-80 and 8085, the ACE device includes an on-chip baud rate divider that accepts any clock input from DC to 3.1 MHz, dividing it by a programmed factor to produce any baud rate from 50 to 56k baud. All normal data communication formats are programmable, and the contents of the control register may be retrieved for inspection.


The INS8250 operates from a single 5V power supply, typically drawing 65mA. It comes in a 40-pin DIL package, and has low-leakage, Tri-state input and output connections.

## 16K RAM card

Pennywise Peripherals has released a new 16K byte static RAM card using the latest 2114 4k-bit memory chips. The PCB measures 247.5 x 152.2mm, and has an edge connector for the Motorola Exorciser bus as used by the popular MEK6800D2 kit. However the control logic is jumper selectable for a variety of other schemes, such as the 8080/85, 2650 or SC/MP. The PCB has plated

through holes and is coated with solder resist.

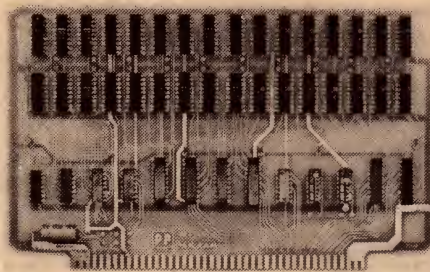The 16K bytes on the card are divided into two 8K blocks, each of which may be switch selected to any of eight positions within the 64K memory space. All bus signals are buffered with Schottky TTL and the bidirectional data bus is driven by Tri-State Schottky TTL



buffers. The card requires only a single +5V supply.

The new memory card is available both as a kit, either with or without 2114s, and as a fully assembled and tested module. Further information from Pennywise Peripherals, 19 Suemar Street, Mulgrave, Victoria 3170.

## Printer options

Italian firm Ing. Guido Gay Misuratori Elettronici has expanded its "Printina" range of alphanumeric printers. Seven basic models are now available, with a wide range of options. New options available include quartz clock and counter, clock with autoprnt, line buffer and hexadecimal

keyboard. All models use noiseless non-impact printing.

One model which may be of particular interest is the Printina CSR, which is in a desk-top cabinet and has a hexadecimal keyboard and display. It is intended as a small and inexpensive terminal for microcomputers, and features paper flowing upward, 24 column line buffer, and bit parallel character serial input.

A comprehensive technical data sheet is available from The Dindima Group Pty Ltd, P.O. Box 113, Balwyn Victoria 3103.

## BASIC for 2650

A BASIC language interpreter is now available for 2650 based systems. Known as TCT Basic, it is distributed by Applied Technology. The body of the interpreter is 4K bytes long, and can be stored in either RAM or ROM. It uses Pipbug routines, and must be located between 0800 (Hex) and 17FF (Hex). RAM scratchpad is required from 0440 (Hex) to 07FF (Hex), while user programs start at 1800 (hex) and extend through available RAM.

The program is available in Pipbug — compatible cassette format, with a 110 baud binary bootstrap loader for faster program loading. A comprehensive user manual, which includes a full listing, is also supplied.

The statements available include LET, GOTO, IF, PRINT, INPUT, FIX, GOSUB, RETURN, FOR, NEXT, DO, UNTIL, REMARK, STOP and PIPBUG. This latter statement allows a return to the Pipbug

**16K  
RAM  
USING  
4K  
STATICS**


- \* Uses popular 2114 4K static RAMS, single 5 volt supply.
- \* Motorola exorciser bus as on MEK6800D2 kit.
- Logic compatible with M6800, 2650, 8080/85, etc.
- \* Both 8K blocks are switch selectable to any 8K area.
- \* Quality PCB with plated through holes.

|                       |               |
|-----------------------|---------------|
| PCB and support chips | Kit \$97.20*  |
| 8K system (450 ns)    | Kit \$257.20* |
| 16K system (450 ns)   | Kit \$410.60* |


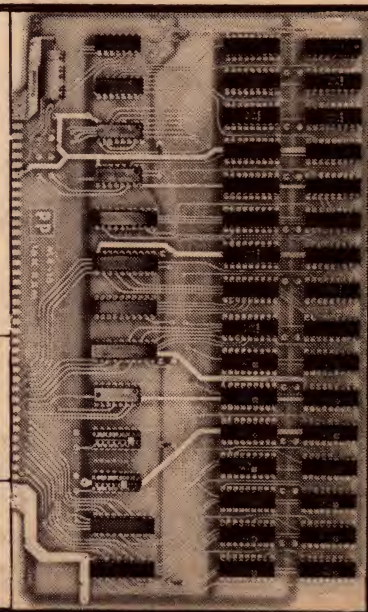
## Pennywise Peripherals

19 Suemar Street, Mulgrave, Vic 3170  
Phone: (03) 546 0308 P&P \$3.00  
Plus \*15% sales tax if applicable.





monitor program.

An unusual feature is the provision of DO UNTIL loops as well as FOR NEXT loops. This allows a loop to be repeated until a specified condition is met. As well as the usual arithmetic operators, (+, -, \* and /), the functions ABS, MOD, INT and FRAC are provided.

In addition, either RND or SIN may be implemented, but only one can be used at a time. Twenty-six numerical variables are provided, and 10,000 string variables. Strings are identified by numbers rather than letters, and so may be referenced by calculations.

Comprehensive error messages are provided, as well as a DUMP command so that programs can be stored on tape. A load command is not required, since the dump format is compatible with normal line input procedure.

We evaluated the interpreter on a 2650 system with 7k of RAM. Loading took about 10 minutes, with another minute or so being required to make the recommended corrections (our tape had a few bugs). Once these were made, operation of the program was completely satisfactory.

Recommended retail price of the TCT Basic package is \$29.50, which includes the cassette tape and manual. Full software backup (notification of errors and further additions) is also provided. Enquiries regarding the package should be directed to Applied Technology Pty Ltd, 109-111 Hunter St, Hornsby 2077.

# MICROCOMPUTER



P.O. Box 380, Darlinghurst NSW 2010



Buy your copy now of the  
"ELECTRONICS Australia"

## LOG BOOK

More than 50 pre-ruled log pages on high quality paper, plus Australian & New Zealand radio and TV stations, FM Data, Frequency Spectrum Chart, Amateur Repeaters, Commonwealth Prefixes, CB Operating Data and more ...

Direct from "Electronics Australia",  
57-59 Regent Street, Sydney

**\$2.95** (post free)

**Sm ELECTRONICS**  
MELBOURNE

**Tax free and assembled, prices on application.**


## S100 EPROM BOARD

S100 sockets \$8.00.

S100 wire wrap board with track pattern for all signals buffered with 81LS95's, \$24.50.

S100 extender board kit with labelled test points for all lines, \$24.50.

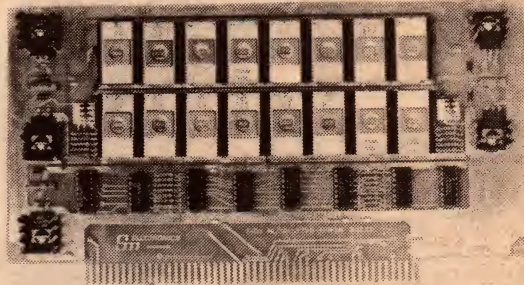S100 mother board — 8 slot with ground plane 7in x 7in, \$24.50.



### UV EPROM ERASER

240 volt, 3in x 4in x 8in. Assembled and tested only.

PRICE \$49.50 + \$1.50 p+p.

S100 16K RAM BOARD

### DIGITAL TACHO

SEE JULY E.T.I.

**\$36.00 + Post free certified mail.**

**Assembled & tested \$48 post free certified mail.**

### 8K/16K 2708 EPROMS

\*switch selection on 8K boundry.

\*S100 bus structure.

\*switch selection of 1-4 wait cycles.

\*low power shottky chips.

\*sockets on all chips.

\*plated through holes.

\*fibreglass board with solder mask.

KIT PRICE \$115.00 + \$1.50c P+P + 2708'S.

**S.M. ELECTRONICS**

10 STAFFORD CRT, DONCASTER EAST 3109  
PO Box 19, DONCASTER, (03) 842 3950.



# Alternative keyboard for Low Cost VDU

We have recently had several inquiries from readers asking how the Southwest Technical Products KBD-5 keyboard with inbuilt ASCII encoder can be used in conjunction with the Low Cost VDU described in our February and April 1978 issues. In this article, we describe the necessary modifications.

by DAVID EDWARDS

The low cost VDU (video display unit) described in our February and April 1978 issues used a keyboard switch assembly which has no ASCII encoder of its own. Accordingly, we provided a suitable encoder circuit as part of the design. However a number of readers have written to ask if it is possible to substitute a different keyboard, the Southwest Technical Products type KBD-5, which is already provided with an encoder IC.

The KBD-5 comes as an assemble-it-yourself kit, consisting of a fibreglass PC board, a bag of switches and keytops, an encoder chip and a few minor electronic parts. It has provision for encoding both upper and lower case

letters, as well as the usual numbers and special characters. It can also be programmed with wire links to provide either a positive or negative "key-pressed" strobe signal.

The encoded outputs from the keyboard are only available in parallel form, so if you wish to construct a serial interface, parallel to serial conversion is required. This is most easily provided by a UART.


The April 1978 issue described a PCB assembly, coded 78up4, which provided a UART, power supply and standard 20mA serial interface, as well as a keyboard encoder chip. In order to use the KBD-5 unit with this it is only necessary to leave out the original

keyboard encoder chip and associated components, and to make two small modifications to the PCB pattern.


Refer to the modified overlay diagram included with this article, and compare it with the original as published on page 53 of the April 1978 issue. As you can see, several components have been deleted, and two small cuts made in the PCB pattern.

Wire the link options of the KBD-5 unit for upper case characters only, and for a negative key-press strobe. Make the eight connections between the two boards using a short length of rainbow cable. The KP signal goes to pin 23 of the UART, while data outputs B1 to B7 connect to pins 26 to 32 respectively.

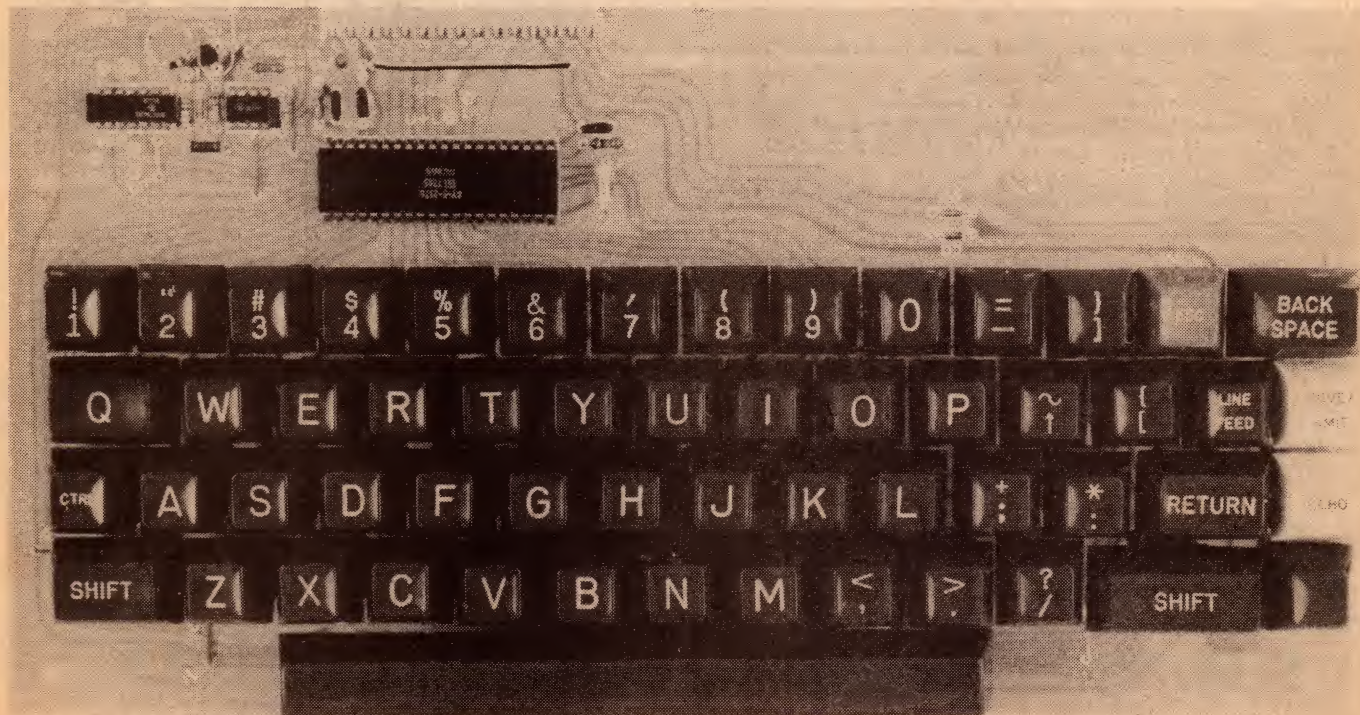*The completed KBD-5 unit is shown below.*





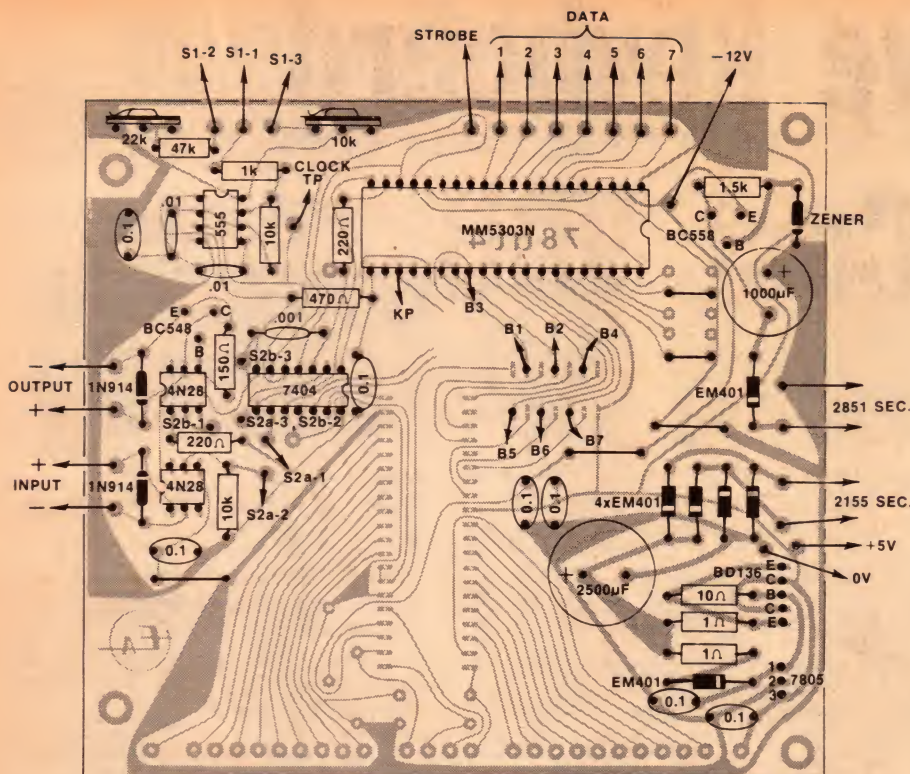

Use this overlay diagram to wire the interface board.

The power requirements for the KBD-5 unit are +5V and -12V, and these can be supplied by the 78up4 board without exceeding the ratings. But we suggest that you check out the operation of the KBD-5 board as detailed in the assembly manual before completing the wiring to the 78up4 board.

We have not provided any mechanical construction and mounting

details, as we felt that these could best be determined by individual constructors. The KBD-5 kit is available from Radio Despatch Service (869 George Street, Sydney), Davred Electronics (104-106 King Street, Newtown, Sydney), Silicon Valley (PO Box 898 Crows Nest, NSW) and Willis Trading (429 Murray Street, Perth, WA).

## TALK TO YOUR COMPUTER

Voice recognition (s-100 BUS SOL, IMS41, Cromenco, etc) with Heuristics Speech Lab Model 50. Includes microphone, handbooks and PC board assembled and tested, 64 word capacity vocabulary, \$314.00.

## VOICE GENERATOR

Computalker speech synthesis for S-100 BUS Computers. Nine acoustic — phonetic parameters. Orders taken, \$415.

## MICRO COMPUTER KIT

SDK'85 with Intel 8085 includes hexadecimal keyboard, \$240.

Also Processor Technology SOL Computers. Tandy TRS 80 users club and software exchange.

Include additional 15% sales tax to all prices or sales tax exemption.

## Introduction to Microcomputers — 8 Evening Lectures \$115

Tandy TRS 80 users club and Software Exchange.

## PITT STREET MICRO COMPUTER SHOP,

375 Pitt Street, Sydney

Tuesday, 12-6 pm

Wednesday, 12-6 pm

Thursday, 12-8 pm

Phone: 235 7229, A.H. 560 6677

PO BOX 105,  
MARRICKVILLE 2204

## COMPUTER & CALCULATORS

PERSONAL COMPUTER/CALCULATOR WITH UP TO 990 MEMORIES OR UP TO 7920 PROGRAMMING STEPS. LARGE DISPLAY THAT CAN ASK YOU QUESTIONS. QUIET THERMAL PRINTER. OVER 250 PROGRAMS ARE AVAILABLE OR WRITE YOUR OWN AND STORE ON MAGNETIC CARDS.

NEW ADVANCED PROGRAMMABLE POCKET CALCULATORS. UP TO 960 PROGRAM STEPS, OR UP TO 100 MEMORIES. AND WHEN INTEGRATED WITH PRE-PROGRAMMED PLUG-IN SOLID STATE SOFTWARE LIBRARIES IT DELIVERS UP TO 5000 STEPS. WHILE BLANK MAGNETIC CARDS LET YOU WRITE AND RECORD CUSTOM PROGRAMS WHICH MAY BE RUN INDIVIDUALLY OR INTEGRATED WITH PROGRAMS IN THE LIBRARY MODULES. PROGRAMS ARE AVAILABLE IN DOZENS OF CATEGORIES: BUSINESS, MATHEMATICS, ASTRONOMY, ENGINEERING, AIR & SEA NAVIGATION, STATISTICS, PHYSICS, CHEMISTRY, ARCHITECTURE, SURVEYING AND MANY MORE. A HIGH SPEED PRINTER IS AVAILABLE THAT PRINTS, LISTS AND TRACES YOUR PROGRAM.

MANY MORE ADVANCED CALCULATORS ARE AVAILABLE INCLUDING A HEXADECIMAL AND OCTAL CALCULATOR/CONVERTER FOR COMPUTER PROGRAMMERS. PRICES START FROM \$30.00 ONWARDS.

## DELTA DISTRIBUTORS

RED BANK COURT  
ST. ALBANS, VIC 3021  
TELEPHONE (03) 366 3742



## SOVEREIGN CITY ELECTRONICS

P.O. Box 623 Ballarat Victoria 3350

### PHILIPS LOCMOS

|            |      |          |      |            |      |            |      |          |      |          |      |
|------------|------|----------|------|------------|------|------------|------|----------|------|----------|------|
| HEF 4000   | .30  | HEF 4015 | 1.24 | HEF 4027   | .57  | HEF 4050   | .50  | HEF 4075 | .32  | HEF 4512 | 1.86 |
| HEF 4001   | .30  | HEF 4016 | .52  | HEF 4028   | .99  | HEF 4051   | 1.24 | HEF 4076 | 1.86 | HEF 4516 | 1.76 |
| HEF 4002   | .30  | HEF 4017 | 1.24 | HEF 4029   | 1.50 | HEF 4052   | 1.24 | HEF 4077 | .39  | HEF 4518 | 1.56 |
| HEF 4003   | .30  | HEF 4018 | 1.28 | HEF 4030   | .52  | HEF 4053   | 1.24 | HEF 4078 | .32  | HEF 4519 | .74  |
| HEF 4004   | 1.28 | HEF 4019 | .73  | HEF 4035   | 1.28 | HEF 4064   | .80  | HEF 4081 | .30  | HEF 4520 | 1.41 |
| HEF 4007UB | .30  | HEF 4020 | 1.41 | HEF 4040   | 1.37 | HEF 4068   | .33  | HEF 4082 | .32  | HEF 4528 | 1.02 |
| HEF 4008   | 1.24 | HEF 4021 | 1.28 | HEF 4041   | .99  | HEF 4069UB | .35  | HEF 4085 | .94  | HEF 4531 | 2.74 |
| HEF 4011   | .30  | HEF 4022 | 1.22 | HEF 4042   | 1.96 | HEF 4070   | .32  | HEF 4086 | .94  | HEF 4539 | 1.12 |
| HEF 4012   | .30  | HEF 4023 | .30  | HEF 4043   | 1.24 | HEF 4071   | .30  | HEF 4093 | .96  | HEF 4555 | 1.02 |
| HEF 4013   | .50  | HEF 4024 | .99  | HEF 4044   | 1.24 | HEF 4072   | .32  | HEF 4510 | 1.34 | HEF 4556 | 1.02 |
| HEF 4014   | 1.28 | HEF 4025 | .30  | HEF 4044AE | 2.92 | HEF 4073   | .32  | HEF 4511 | 1.76 |          |      |

### REGULATORS uA 78C8CU CB Reg. 13.8V 2A 2.45 uA 723 .66 TTL SPECIALS

|      |     |    |      |      |      |    |      |      |      |
|------|-----|----|------|------|------|----|------|------|------|
| 7805 | 5V  | 1A | 1.30 | 7905 | -5V  | 1A | 1.75 | 7400 | .18  |
| 7806 | 6V  | 1A | 1.45 | 7906 | -6V  | 1A | 1.75 | 7408 | .25  |
| 7808 | 8V  | 1A | 1.45 | 7908 | -8V  | 1A | 1.75 | 7410 | .20  |
| 7812 | 12V | 1A | 1.30 | 7912 | -12V | 1A | 1.75 | 7432 | .40  |
| 7815 | 15V | 1A | 1.45 | 7915 | -15V | 1A | 1.75 | 7442 | .75  |
| 7818 | 18V | 1A | 1.45 | 7918 | -18V | 1A | 1.75 | 7447 | 1.15 |
| 7824 | 24V | 1A | 1.45 | 7924 | -24V | 1A | 1.75 | 7474 | .46  |

### OPTO 7 seg. Display 1.6cm 1.40

LED'S Red . . . . 18 LED'S Green . . . . 40 LED'S Yellow . . . . 40

### LINEAR SPECIALS 741 .30 555 .35

(P&P semiconductors only 60¢. Orders including Cable etc. \$2.80)

ARLEC DMM 10  
DIGITAL MULTIMETER \$89.70


SCOPE TC 60  
TEMP. CONTROLLED IRON \$32



# Counting without Controls

Fully automated 80 & 520 MHz performance

New lower prices

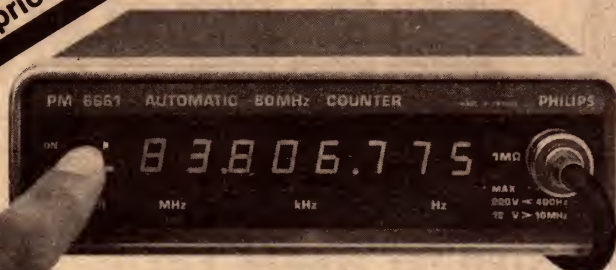

These frequency counters represent the ultimate in easy operation by having no controls, other than the on/off switch. Such simplicity is made possible by the use of advanced LSI circuitry, developed in house, which allows all control functions to be automated. The low power requirements of the Philips LSI LOC MOS circuitry also allows the instruments to be housed in a compact, rugged case without ventilation holes.

Reliability in all operating environments is therefore at the highest possible level.

■ Automatic everything:

- triggering, the input signal is conditioned to give optimum triggering
- noise suppression, to avoid noise and other interference influencing the measurement
- 80 or 520 MHz channel selection (on model PM 6664)
- leading zero suppression

- MHz. kHz. Hz grouped readout
- High 20 mV sensitivity
- High stability timebase
- Lightweight, rugged case
- Bright 8-digit LED display

For more information contact:  
**Philips Scientific & Industrial Equipment**, P.O. Box 119, North Ryde, N.S.W. 2113 or phone Sydney 888 8222 Melbourne 699 0300



Test & Measuring Instruments

**PHILIPS**

HRME-1320031

## DON'T MISS OUT

### 27 DO-IT-YOURSELF PROJECTS FROM ELECTRONICS AUSTRALIA

**ELECTRONICS AUSTRALIA**  
**projects & circuits**  
Number 2



If you like building electronic projects in your spare time, this exciting new book of popular projects is a must. There's a tacho, a dwell meter and a CDI unit for your car; a Doppler burglar alarm; a digital clock; a loudspeaker protector; a variable power supply; plus much more. Order your copy now!

ONLY \$3.00

+ 60c pack & post

Use this handy order form

To: Electronics Australia, PO Box 163, Beaconsfield 2014.

Please send me ..... copies of "PROJECTS & CIRCUITS NO. 2" at \$3.60 each. (Price includes packing and postage.)

NAME .....

ADDRESS .....

..... STATE ..... POSTCODE .....

I enclose a cheque/postal order to the value of \$ .....



## NOVICE AMATEUR: The logical next step for a keen CBER

Over the past twelve months, an increasing number of CB operators have been looking to amateur radio as a means of expanding their new found interest. This article deals in particular with the Novice level examination, by way of which many CBERs have already qualified to operate their own amateur radio station.

by JOHN KOLM\*

The Novice class examination and licence caters for those aspiring to amateur status, who lack the knowledge necessary to qualify for a limited or a full licence. The Novice concept is proving a boon to many CBERs who, having acquired an interest and experience on 27MHz, find that they can study to Novice examination level without undue effort. In fact, many seem thoroughly to enjoy the experience.

Among the successful Novice examination candidates there has also been a number of women — the wives of licenced amateurs — who have rounded out by study what they have picked up from their husband's never-ending technical "nattering".

While a Novice licence provides plenty of immediate opportunity for its holder, it is by no means a limiting document. At any time the licence holder feels that he/she can tackle a higher level examination, they can hopefully upgrade their licence. But that is another story.

The Novice examination and syllabus saga is a long and somewhat involved one. Its present status is the result of the hard work and helpful suggestions of a large number of people, both inside and outside the WIA — the Wireless Institute of Australia.

To the teacher or prospective Novice

reading this article, it is offered as a presentation of the facts as they currently stand. Two areas have been covered; firstly, the Trial Novice Examination Scheme, and secondly, the situation concerning the official Novice examination.

**THE TRIAL NOVICE EXAMINATION** is run by state branches of the Youth Radio Clubs Scheme of Australia (YRCS or YRS). Despite the connotation, anybody is welcome to sit and it is not necessary to be either a youth or a member of a club!

The idea behind the Trial Novice Exam is simple: to enable anyone interested to sit for a realistic Novice licence examination under genuine examination conditions. But what, you say, is the point of that? Surely if you have done the study, passing the exam will be routine.

Perhaps it ought to be but, exams being what they frequently are, sadly, it just isn't so! I believe that most Novice candidates underrate the effect of nerves on their examination performance. You may be letter-perfect while sending Morse to your amateur friend from across the road; but it is a different thing to repeat the performance in front of a stranger who addresses you by your exam number, especially if you cannot stop your hand from quivering like a neurotic jellyfish! Don't laugh, it happens . . .

I am not trying to make the prospective candidate suffer a mild coronary, — or take up knitting as an easier alternative! It is undeniable that people have passed the exam purely by listening to Morse tapes and studying textbooks. However, it is equally true that candidates have failed because of nervousness in a strange environment.

I base this comment on remarks made by candidates, one of whom wrote: "I for one will go on record as stating that there is no way known to man or beast that I would have passed the Novice Morse exam without having attended the trial . . . and that goes for quite a number of other candidates also." (This quote is reprinted by kind permission of CB Action magazine.)



*There has to be a moral somewhere in this scene at the Melbourne Trial Novice Examination, as a relaxed Morse examiner Daurel Coolidge (VK3NCS) chats with an unnamed male candidate.*

\*11 Vista Ave, Kew, 3101. John Kolm is the Victorian Examiner for the Youth Radio Clubs Scheme and a member of the WIA Federal Novice Examination Subcommittee. He compiled the initial Novice Examination question bank (discussed in the article) which is now attended to by the WIA. The Author gratefully acknowledges the assistance of Graeme Scott (WIA Federal Education Coordinator) in preparing the paper.



## The Australian CB SCENE

The Victorian Trial Novice Exam results also provide data for an examiner's report (still being compiled at the time of writing). This will pinpoint general "trouble spots" and should be useful to instructors; hopefully it will appear in "Electronics Australia".

The most recent Trial Novice Exam was held in April in Victoria, New South Wales, and Queensland; there were 171 enrolled candidates in Victoria alone. Trial Novice exams are held roughly a month before Official Novice exams, and the next one is therefore scheduled for late September or early October. There will be plenty of advance publicity.

If you do not live in one of the three abovementioned States and would like the YRCS (or if no YRCS, your WIA Division) to run a trial exam, please get in touch with me. A YRCS/WIA directory is provided below:

ACT: WIA (ACT Division), Box 1173, Canberra City, 2601.

NSW: K. Hargreaves, 52 Marlin Avenue, Floraville, 2280.

Vic.: Supervisor — F H Whitton, 204 Churchill Avenue, Braybrook, 3019  
Exams — J. Kolm, 11 Vista Avenue, Kew, 3101.

Qld.: WIA (Qld Division), GPO Box 638, Brisbane, 4001.

S.A.: G. Preston, 13 McGowan Rd., Para Hills, 5096.

W.A.: WIA (WA Division), GPO Box N1002, Perth, 6001.

Tas.: R. K. Emmett, 111 New World Avenue, Trevallyn, 7250.

The Trial Novice Examination in Victoria is run by the Author. Part of the idea behind the last Trial Exam in April was to try out a theoretical, streamlined, computerised system for speedy processing of examination results. The system appears to have been an unqualified success, and readers may be interested in a brief description of how it was done.

The last Victorian Trial Novice Examination was held at seven examination centres. The main exam. centre was at Melbourne University and was attended by 98 candidates; another 73 candidates were distributed over the other six centres. Five of these remaining centres were "country centres"; the only requirements for anybody wishing to run a "country centre" were that:

- (i) the centre must be 50 or more miles from Melbourne.
- (ii) there must be at least one fully licensed amateur to act as Supervisor and Morse sending examiner.
- (iii) there should be a minimum of, say, ten candidates.

*An aspiring Novice Amateur hard at work during the Morse sending test at the April 1978 Trial Novice exam in Melbourne. In the panel below are six of the 30 multiple choice questions which comprise the Regulations paper. The time allowed was 30 minutes.*



As it turned out, no requests to run a country centre were turned down. The one remaining examination centre was a special one for disabled candidates, run in South Melbourne by courtesy of the Disabled Radio Amateurs' Club.

Each of the six examination supervisors received an instruction pamphlet and was required to make the usual undertakings concerning security. The exam papers were sent by registered mail a few days later. The Morse receiving test was provided on cassette, complete with spoken instructions and pauses; it merely had to be played as it was.

The system ran without a hitch, including the security arrangements. It is worth pointing out that the security factor associated with auxiliary ex-

amination centres is considered to be adequate by the organisers of the Victorian Higher School Certificate Examination; one can, therefore, scarcely be worried about similar arrangements for a Novice exam!

The main examination centre at Melbourne University was attended by an official observer from the Postal and Telecommunications Department, who expressed satisfaction with the way in which the Trial Exam was conducted. One interesting variation was the use of a language laboratory for the Morse receiving test. Each candidate sat in a booth with its own volume control, and the technical facilities ensured first-class audio quality.

Candidates recorded their answers to the multiple-choice theory and

### TRIAL NOVICE EXAM: REGULATIONS

2. The erection of aerial masts by the licensee of an amateur station is usually governed by:
  - A. the Department of Industry
  - B. the Postal and Telecommunications Department
  - C. State and Commonwealth law
  - D. local government and civil aviation requirements
8. A particular amateur station is known to be causing television interference. The District Radio Inspector must be called:
  - A. if the complainant refuses to co-operate in remedying the problem
  - B. when tests are conducted to determine the cause of the interference
  - C. whenever the station is to be used
  - D. whenever the interference becomes evident
13. The frequency on which a ship would normally transmit a distress call by radiotelephony is:
  - A. 500 Hz
  - B. 2182 kHz
  - C. 8364 kHz
  - D. 8600 kHz
15. The friend of an amateur licensee requests him to establish radio contact with another licensee who has the friend's parents at his station, in order to save the cost of an interstate telephone call. Both licensees:
  - A. must refuse to perform the service requested
  - B. may perform the service on frequencies above 52 MHz only
  - C. may perform the service, but only once
  - D. may perform the service provided they refuse payment
18. Which one of the following items does NOT have to be entered in the station log book?
  - A. the date and time of each transmission
  - B. the type of emission used
  - C. the signal report received
  - D. the locality used, if mobile
27. The abbreviation "QSV?" means:
  - A. "Are you ready?"
  - B. "Shall I send a series of V-s?"
  - C. "Do my signals vary?"
  - D. "When will you call me again?"



# MIDLAND CB

## THE 'ROLLS-ROYCE' OF CB

Why is MIDLAND CB the world's number one selling CB?

In one word: **Quality.**

Midland CB radios are crafted in Japan (not Taiwan or Hong Kong) to very rigid specifications and standards, by the world's largest manufacturer of CB. Every stage of manufacture is subject to stringent quality controls on every single set — not just isolated samples as is the case with most other manufacturers. And when the set is completed, every set is thoroughly checked again on every channel in every possible operating mode.

Midland are very proud of their reputation!

That's why they chose Dick Smith Electronics in Australia. Dick is just as proud of Midland — and he backs every set he sells with his now famous 2 year guarantee — exclusive to Dick Smith Electronics.

Sure you may have to pay a little more for Midland than many of those other sets.

Rolls Royces don't come 'cheap', either . . .

## GILT EDGED SECURITY:

**MIDLAND AM 857**

The Midland 857 — simple, reliable, functional. It might be the lowest priced Midland — but it loses nothing in power or performance. Full power transmitter section, with very sensitive receiver to pull in those long range stations. Cat D-1429



**\$119<sup>50</sup>**

**MIDLAND AM 882c**

The Midland 882c: the most widely used AM CB in the world. Tops in range and reliability, even has an antenna warning light just in case something's wrong. Superb set — for the new CBer or for the old hand. Cat D-1436.



**\$129<sup>50</sup>**

**MIDLAND AM 963**

The Midland 963 — the poser's own. You don't have to be a poser to own one of these — but you'll certainly get the admiring looks. Ideal for vans, campers, etc — complete with LED channel readout and SWR/power/strength meter plus full range of controls. Cat D-1437



**\$179<sup>50</sup>**

**MIDLAND AM 886**

The Midland 886: the base station with the future in mind. Beautiful styling — at home in any decor — plus a powerful Midland transceiver inside. Telephone handset for privacy — or switch to inbuilt speaker. SWR/power/strength meter too. Cat D-1438.




**\$199<sup>50</sup>**

Dick Smith personally guarantees that every Midland CB he sells is crafted to the highest standards of quality and workmanship, and has been subjected to stringent performance tests before sale.

If a Midland CB should fail due to manufacturing or component defects (abuse, modification and fair wear & tear specifically excluded) during a period of two years from date of sale, Dick Smith Electronics will, at their option, repair, or replace with a set of similar specifications.

**MIDLAND AM/SSB 892**

The Midland 892 — the SSB set to beat them all. For the absolute top range, clearest signal, the Midland 892 is without peer. Now has exclusive clarifier control on the microphone: great when you're driving around! If you want the best in CB, go Midland. If you want the best in Midland CB, go Midland 892. Cat D-1700



**\$239<sup>50</sup>**

# DICK SMITH ELECTRONICS

**bankcard**  
welcome here

**SYDNEY** 125 York Street, SYDNEY. Ph. 29 1126  
147 Hume Hwy, CHULLORA. Ph. 642-8922  
162 Pacific Hwy, GORE HILL. Ph. 439-5311  
30 Grose Street, PARRAMATTA. Ph. 683 1133

**MELBOURNE** 399 Lonsdale Street, MELBOURNE. Ph. 67 9834  
**BRISBANE** 656 Bridge Road, RICHMOND. Ph. 42 1614  
**ADELAIDE** 166 Logan Road, BURANDA. Ph. 391 6233  
203 Wright Street, ADELAIDE. Ph. 212 1962

SHOPS OPEN 9AM to 5:30PM  
(Saturday 9AM - 12 noon)  
BRISBANE 1 2 Hours earlier

ANY TERMS OFFERED ARE TO  
APPROVED APPLICANTS ONLY

Many lines available from the  
Dick Smith Electronics Centres at

**GRACE BROS**

Bradway - South - Chatswood - Liverpool  
Miranda - Mt Druitt - Parramatta - Roseland  
and Warringah Mall



**MAIL ORDERS** P.O. Box 747, Crows Nest, N.S.W. 2065. Post and packing extra.

Dealers across Australia.



# At last, reliable, convenient CB communication.

## The Philips 40 channel FM 320 UHF. It's what CB radio is coming to.

This ultra-high frequency unit is made here by Philips – Australia's largest manufacturer of two-way radio equipment. With its arrival, CB radio in Australia reaches maturity. Why? Because current CB legislation provides for the allocation of 18 channels for AM/SSB use. Philips FM 320 UHF, with 40 channels, more than doubles this availability.

But that's not all. Because UHF operates on FM, interference such as static, vehicle ignitions, industrial activity and electrical storms will have little effect on reception. Every CBer knows that such interference plays havoc with 27 megahertz equipment, while these rigs provide television interference of their own.




Again, UHF does not generate any television interference as it operates on FM.

In city areas, Philips FM 320 UHF takes the uncertainty out of CB communication. High-rise buildings, bridges and other structures won't affect reception clarity or constancy. In effect, the UHF signal passes through the concrete canyons, instead of bouncing around them.

In conditions of heavy air traffic, Philips FM 320 UHF will capture the strongest signal on a given channel and temporarily silence any other which would otherwise cause interference. On the open road, mobile operators won't be interrupted by foreign "skipping" signals.

The Philips FM 320 UHF features Phase loop synthesiser and 5 watt RF output. A 40 channel L.E.D. readout selector can be push-button operated one channel at a time, or continuously until the desired channel is selected. Built-in remote control change on the microphone allows safe mobile operation. Channel changes are accompanied by an audible "click". Many more exciting features are built-in, like automatic call channel reset.

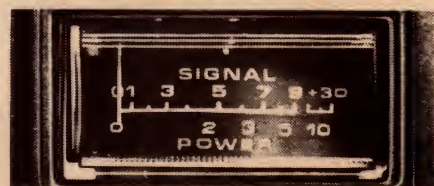

You can choose from a 15 cm quarter-wave tuned high gain type aerial, or perhaps the most universal aerial, the co-axial dipole. Its independence of a ground plane allows positioning almost anywhere on a vehicle.

That's the Philips FM 320 UHF – Australian built and backed by Philips. It turns CB radio into a reliable, convenient communication facility.

**Philips UHF**  
It's what CB radio is coming to.



Philips also offer single-side band and de luxe AM units for 27 MHz CB operation.

To: Philips Consumer Products Division  
Post Office Box No. 308,  
Clayton, Vic., 3168.

I'm interested in the better communication opportunities offered by UHF CB radio. Please send me a brochure on the Philips FM 320 UHF CB.

Name: .....

Address: .....

Postcode: .....

☐ Tick here if also interested in Philips AM or AM/SSB equipment.

**PHILIPS**

We want you  
to have the best



367 2054



## The Australian CB SCENE

regulations papers on a special answer sheet, using an ordinary pencil. These answer sheets were subsequently marked by a microcomputer machine which processes them at a rate of one per second. The entire marking procedure was completed in less than three minutes.

A feature of the machine is that it prints a red bar next to every wrong answer; this seemed to be of value to candidates when their answer sheets were returned.

The final stage was handled by a full-sized computer which, among other things, printed out and addressed a statement of examination results for every candidate. This same computer sent examination slips to every candidate before the examination, and is presently being used to compile relevant statistical data.

The only thing computers didn't do was lick the envelopes! The exam was held on a Saturday; results were ready and in envelopes by Monday evening.

The general feeling among candidates was that they now felt much happier about the actual exam day, by then looming on the horizon.

**NOVICE EXAMS AND ALL THAT:** For quite some time, a number of enthusiastic amateurs have been evolving a provisional Novice Licence Study syllabus under the auspices of the WIA. The availability of a reliable syllabus is essential for the production of examination papers and for the information of teachers and candidates alike. Until recently, no official syllabus existed.

As a result of negotiations between the WIA and the P&T Department Central Office, the Department has issued an official Novice syllabus. The WIA has itself produced a Study Guide, which is written in the form of the syllabus, but much more detailed, and the P&T Department has officially approved it. It is hoped that this will make life easier for students, teachers, and examiners to determine exactly what is required to pass the Novice Licence examination.

The WIA has published an inexpensive handbook containing the official P&T Department syllabus, the WIA Study Guide, and some additional useful information for candidates and teachers. This handbook is currently available for 65c (postage included) from: WIA Federal Executive, PO Box 150, Toorak, Vic. 3142.

The publication of this syllabus delineates the subjects and subject depths of the Novice examination. Its final version has been the result of considerable consultation between the WIA and officials of the P&T Department.

## TRIAL NOVICE EXAM: THEORY

3. An equivalent unit to the "cycle per second" is the:
  - A. Hertz
  - B. Coulomb
  - C. Maxwell
  - D. Marconi
16. The range of audible frequencies is approximately:
  - A. 2 Hz to 20 kHz
  - B. 2 kHz to 20 kHz
  - C. 2 kHz to 200 kHz
  - D. 20 kHz to 200 kHz
17. In a class C amplifier, the term "class C" refers to:
  - A. the frequency range for which it is designed.
  - B. the DC bias used
  - C. the audio quality of the output
  - D. the output power
23. In comparison with a dipole antenna, the impedance of a folded dipole antenna is:
  - A. higher
  - B. lower
  - C. the same
  - D. almost zero
40. The resonant frequency of a coil and a capacitor can best be determined using a:
  - A. cavity resonator
  - B. wavemeter
  - C. cathode ray oscilloscope
  - D. grid dip oscillator
45. An increase in output power of 3 dB represents a numerical power gain of:
  - A. 0.3
  - B. 2
  - C. 10
  - D. 100
49. The wires inside a 3-core mains power cord are coded: brown; blue; green with yellow stripe. These colours correspond, respectively, to:
  - A. active; earth; neutral
  - B. active; neutral; earth
  - C. neutral; active; earth
  - D. neutral; earth; active

Here are 7 out of the 50 multiple choice questions which comprised the Theory paper at the Trial Novice exam in Melbourne during April. Time allowed, 1 hour.

ment. The discussions were held in a spirit of co-operation and the original syllabus underwent various deletions and modifications in the process of reaching mutual agreement on the level of knowledge required of a competent Novice operator.

As a further activity, the author of this article, some months ago, produced a Novice examination question bank. The question bank contained several hundred theory and regulations questions taken from numerous sources, and filed by subject in a card-file system.

This bank was adopted by the WIA, and, at about the same time, a Novice Education Subcommittee was formed. This group held a number of working sessions during which all the questions in the bank were reviewed; some were rejected, others added. The most recent, and also the largest session was held on the 10th and 11th of June in Melbourne and was attended by interstate as well as local participants.


The present WIA/P&T Dept. Novice Examination item bank has become bigger and better than its original parent, and some of its contents have already been forwarded to the P&T Department. Indications are that they have been used in an exam, and there has been a very favourable reaction from teachers and candidates.

I would like to stress that we are only too pleased to receive multiple choice Novice exam questions for possible inclusion in the question bank. If you have exam questions to submit, please send them to the WIA Federal Education Co-ordinator at the WIA address given previously.

The WIA will shortly release a

number of theory and regulations examination questions, which will be published by the Institute and made available at minimum cost. These can be taken by teachers and students as a representative sample.

## THE "ELECTRONICS AUSTRALIA" LOG BOOK

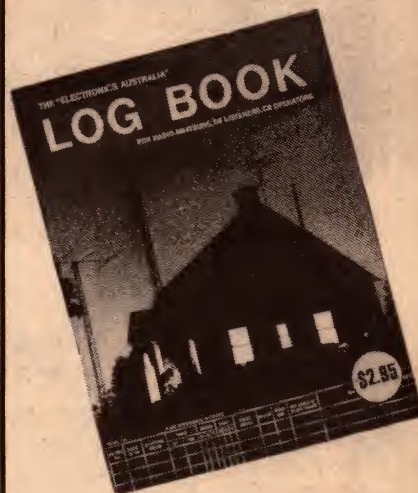

FOR: RADIO AMATEURS  
DX LISTENERS  
CB OPERATORS  
**\$2.95**

From "Electronics Australia", 57-59 Regent St, Sydney.




# MULTIMETER FET METERS & DIGITAL VOLT METERS

CHOOSE FROM MELBOURNE'S LARGEST RANGE

## MULTIMETERS

|                                  |          |
|----------------------------------|----------|
| AVO MODEL 8 MK V                 |          |
| 20K $\Omega$ /V                  | \$287.50 |
| JEMCO US105 50K $\Omega$ /V      | \$51.45  |
| JEMCO US110A 100K $\Omega$ /V    | \$50.30  |
| KA MODEN 360-TR 100K $\Omega$ /V | \$50.87  |
| RAPAR LT-101 1K $\Omega$ /V      | \$12.92  |
| RAPAR SK100 100 K $\Omega$ /V    | \$61.57  |
| RAPAR SK120 20K $\Omega$ /V      | \$33.62  |
| RAPAR SK200 50K $\Omega$ /V      | \$50.00  |
| SANWA CX505 50K $\Omega$ /V      | \$76.75  |
| SANWA 460-ED 100K $\Omega$ /V    | \$81.35  |
| SANWA N501 500K $\Omega$ /V      | \$126.20 |
| SANWA LCD900 50K $\Omega$ /V     | \$214.75 |
| TMK VF4 2K $\Omega$ /V           | \$23.27  |
| TMK TP5SN 20K $\Omega$ /V        | \$27.18  |
| TMK 200 20K $\Omega$ /V          | \$29.91  |
| TMK 500 30K $\Omega$ /V          | \$43.22  |
| TMK 520 50K $\Omega$ /V          | \$48.28  |
| TMK 700 20K $\Omega$ /V          | \$68.00  |
| TMK PL436 20K $\Omega$ /V        | \$26.57  |
| TMK PL50K $\Omega$ /V            | \$34.92  |

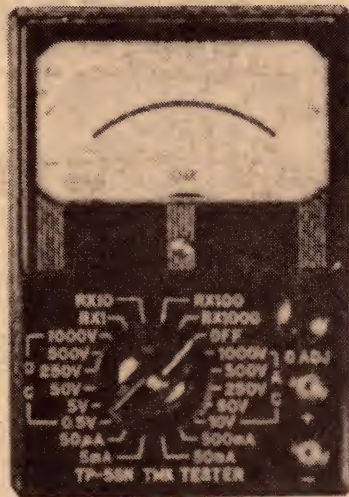

## FET METERS

|                  |          |
|------------------|----------|
| SANWA EM300      | \$82.50  |
| SWE CHECK V.O.M. | \$75.60  |
| TMK 150          | \$64.85  |
| TRIO VT 108      | \$126.20 |

## DIGITAL VOLT METERS

|                    |          |
|--------------------|----------|
| B & K 2800         | \$152.65 |
| DATA PRECISION 175 | \$232.00 |
| NLS LM 3.5A        | \$172.77 |
| NLS LM 40A         | \$213.54 |
| FLUKE 8020A        | \$207.27 |
| TRIO DL703         | \$196.35 |
| SINCLAIR PDM35     | \$70.77  |
| SINCLAIR DM235 ... | \$150.00 |

ALL PRICES INCLUDE  
\$2.00 P & P

Write for comprehensive  
specification leaflets on all  
models. Prices subject to  
change without notice.



Distributed by:



## Radio Parts GROUP

562 SPENCER STREET, WEST MELBOURNE (03) 329-7888  
1103 DANDENONG ROAD, EAST MALVERN (03) 211-8122

PLEASE SEND ME ..... ONLY ..... METER AT ..... EACH.

I AM ENCLOSING CHEQUE ☐ MONEY ORDER ☐ OR PLEASE

DEBIT MY BANKCARD NUMBER .....

SIGNATURE .....

NAME (BLOCK LETTERS) .....

ADDRESS .....

## The Australian CB SCENE

The Examination question bank is being finalised at the time of writing and will shortly be forwarded in its entirety to the P&T Department. The bank will be kept under security and used for setting future Novice examinations, which will consist of questions randomly selected from each subject.

Questions in the bank will periodically be deleted, modified, or increased in number, by a joint WIA/P&T Department Committee.

Learning should be a pleasant experience; being examined should be a fair and tolerable one. In producing fair Novice examination questions, as I believe these to be, there can be no guarantee that every candidate will get the results he wants. However, it will at least help to ensure that each candidate gets the result he genuinely deserves!

The WIA has done its best to set a standard which is neither too low for competence nor too high for examination. It is the belief of the WIA that the present Novice syllabus contains nothing which cannot be learnt with average intelligence and moderate determination, and yet ensures that the gaining of a Novice Amateur Licence is an achievement of which every candidate may justifiably feel proud.

## A handset for mobiles

Designated as HS-6000, this mobile radio handset is manufactured by Primo in Japan.

It is imported into Australia by Paradio Electronics, and sold through distributors such as Radio Despatch Service. It meets specifications laid down by the FCC and by the Radio Branch of the Australian PMG Department.



The HS-6000 is fitted with an 8-ohm headphone and a 500-ohm microphone.

Two switching functions are provided: one in the cradle is actuated when the handset is withdrawn, being used typically to silence a monitor loudspeaker. The other is a normal press-to-talk lever in the centre portion of the handle.

The handset and holder is available in either black or beige.

For further information: Paradio Electronics, P.O. Box 380, Darlinghurst, NSW 2010.



# AMATEUR RADIO

by Pierce Healy, VK2APQ



## Strong amateur reaction to proposed 5A expansion

The federal government's announced policy to expand the use of TV channel 5A has created a strong reaction within the amateur ranks, by reason of likely interference problems. The nature of these problems, and the steps amateurs should take to change the policy are dealt with in these notes.

Announcements that extended use is to be made of television channel 5A (137MHz — 144MHz), for additional (ethnic) TV services, are receiving widespread attention by Australian amateurs. They are concerned at the real possibility of mutual interference between channel 5A and the international amateur band 144MHz — 148MHz, particularly in weaker channel 5A signal areas or within close proximity to an amateur station.

On behalf of Australian amateurs, the matter has been taken up with the Minister of Posts and Telecommunications, Mr A. A. Staley, by the Wireless Institute of Australia federal president, Dr David Wardlaw, VK3ADW.

Letters from the WIA president pointing out the likely problems, resulted, at the request of Mr Staley, in an hour long discussion on the points raised by the WIA. The minister stressed that he regarded the amateur arguments as substantial, though the decision was a cabinet, rather than ministerial, matter.

It was agreed that the WIA would present a fully prepared case to justify its contention that allocation of channel 5A was undesirable because of the inevitable social consequences that would follow from interference to transmissions on this channel.

Many amateurs have taken the matter up with local members of parliament and all amateurs are being urged to do so. A number of varying types of reply are reported to have been received.

In a reply to an objection by Steve Gregory, VK30T, of Hamilton Victoria, his local member of federal parliament, the Prime Minister, Hon. Malcolm Fraser, stated in part; "While it is unlikely that interference will be caused

to amateur radio, I am informed there is a likelihood of occasional interference to the television reception of residents living in close proximity to an amateur radio installation. The Minister has advised me that if this occurs it may be necessary to limit the hours of operation of amateur radio as has been the case in other areas where channels 0 and 5A are being utilised."

Also, it is known that in at least one marginal electorate there are more than sufficient amateurs to unseat the present government member if political decisions, and not technical factors, decide the allocation of ethnic telecasting frequencies. This fact is being actively canvassed among amateurs in that electorate.

In any approach to a member of Federal Parliament (preferably in writing) take care not to "knock" the ethnic TV service concept as such. On the contrary, point out that this service can still be provided, free of interference problems, in the UHF band.

It is also worthwhile questioning the validity of suggestions that using UHF for the additional channels would be more costly than using channel 5A. In either case there will be a substantial basic cost in providing a transmitter, mast, buildings, and other facilities. Against such a cost, the difference between a VHF and UHF transmitter may well be negligible.

The amateur's case should emphasise both the contributions which the amateur has made to society in the past, and the hardship and loss he will suffer if this band is lost or restricted.

The cost of amateur equipment is one example. Modern equipment is expensive; in some cases more expensive than a colour TV set. On top of this is the personal effort of self education

necessary to achieve an amateur licence. Amateurs invest such sums of money, and make such efforts, because the allocation of a band has encouraged them to do so. Are they then not entitled to some guarantee that their interest and investment will be protected?

As well as their personal equipment, Australian amateurs have helped finance several amateur satellites, two of which are currently active, with a third under construction. The benefits of these have ranged well beyond the amateur movement, from pilot schemes for locating downed aircraft, to general education. In the latter case they provide incentive for studying mathematics, geography, the solar system, and foreign languages.

Australian amateurs have also contributed a great deal of time and effort in assisting various youth organisations. These not only provide a healthy environment for young people, but have opened the door to a successful career for many; a career which they may never have been able to embrace otherwise.

If Australian amateurs are deprived of their most active band they will not be the only losers; the community in general will have lost something as well.

Australia is a member of the United Nations specialised agency — the International Telecommunication Union. At WARC 79, what will be Australia's explanation for setting up services within the radio frequency spectrum which are likely to cause interference on international space research frequencies or an internationally recognised amateur service band, including the international amateur satellite projects.

All amateurs are being urged to write, individually, to their local federal member and put a case for the UHF system, based on the points raised above, plus any others that come to mind. Individual letters have far more impact than form letters or petitions.

Act now! It will be too late when cabinet announces its decision.

### IARU REGION III

With the 1979 World Administrative Radio Conference now only months away, a topic of conversation with

Radio clubs and other organisations, as well as individual amateur operators, are cordially invited to submit news and notes of their activities for inclusion in these columns. Photographs will be published when of sufficient general interest, and where space permits. All material should be sent to Pierce Healy at 69 Taylor Street, Bankstown 2200.



# AMATEUR RADIO

overseas stations could well be about the action needed to ensure that amateur requirements are fully appreciated by national administrations, particularly in Region III. Unfortunately, Region III has a very widespread amateur population of many nationalities. In many areas the number of amateurs are insufficient to form a national amateur society. However, they will be affected by decisions made at WARC 79 and should be urged to advise their local administrations of the value of amateur radio within the community.

If the number of call sign prefixes heard from the Pacific area is compared with the following list of amateur societies (Region III, IARU members) the results may be surprising

| Country     | National Society | Prefix  |
|-------------|------------------|---------|
| Australia   | WIA              | VK      |
| Hong Kong   | HARTS            | VS6     |
| India       | ARSI             | VU2     |
| Japan       | JARL             | JA etc. |
| Korea       | KARL             | HM      |
| Malaysia    | MARTS            | 9M2     |
| New Zealand | NZART            | ZL      |
| Pakistan    | PARS             | AP      |
| Papua/N.G.  | PNGARS           | P29     |
| Philippines | PARA             | DU      |
| Singapore   | SARTS            | 9V      |
| Sri Lanka   | RSSL             | 4S      |
| Thailand    | RAST             | HS      |
| USA         | ARRL             | W, K    |

(List acknowledgement to Region III News Feb. 1978)

Remember, amateurs have efficient, modern and flexible communication equipment available today; use it to

## Channel 5A — The Problem

From the amateurs' points of view there appear to be several reasons why use of channel 5A should not be expanded. The most obvious one is that individual TV receivers, particularly those in fringe areas, may suffer interference from nearby amateur transmissions.

A less obvious, but more serious, problem involves any translators associated with channel 5A transmitters. Translators serve areas within the master station service area but which, by reason of shielding in one form or another, receive inferior signals.

The translator takes the signals from the master station and retransmits them into the problem area on any available VHF channel. In many cases the translator takes its signals "off-air" from the master station and it is the possibility of an amateur transmission getting into a translator that is causing concern, because all viewers using the translator would then experience this interference.

At present there appear to be two NSW 5A translators in operation, but some proposals envisage a number of translators operating from a single

5A master station.

In view of such likely problems, amateurs feel that the authorities should consider the alternative approach; that of putting the additional channels in the UHF band. Provision has already been made for such a move, manufacturers are including UHF tuners in most modern sets and, since the move will be made eventually, why not now? Even those sets without UHF tuners could be accommodated by adding a relatively inexpensive converter.

As well as solving this interference problem, expansion into the UHF region would have other advantages. Channel 5A has always been something of a black sheep in the TV allocations. As well as being threatened by interference from the internationally approved amateur band on one side, it can, and has, caused interference to an internationally approved space research channel (136-137MHz) on the other side.

A move into UHF would leave the way open for eventual phasing out of the existing 5A transmitters, with benefit to all concerned.

publicise the amateur's value to the community by expressing your interest and concern for its well being at WARC 79 deliberations.

Let the world know that amateurs are internationally bonded through the International Amateur Radio Union and all amateurs are members of a non-commercial, self educating, self disciplined, non-political, non-sectarian, international communication service. It is

the only such service recognised by the United Nations specialised agency — The International Telecommunication Union.

Above all, help you national society to finance its activities on behalf of the amateur service. You do not necessarily have to be a member. Your help is essential.

### RADIO CLUB NEWS

Time is running out for radio clubs to forward details for inclusion in the December 1978 — Radio Club Directory.

The closing date is 20th October, 1978. Format details the same as last year.

This listing can mean substantial publicity and is a service to those who wish to update to amateur radio.

Do not let your club down — do it now.

**SOUTH WEST ZONE CONVENTION (NSW):** Wagga is the venue for this very popular event, organised by the Wagga Amateur Radio Club on behalf of the South West Amateur Radio Society. Amateurs, their families, and friends are invited to visit Wagga and participate in the activities. A special effort is being made to cater for the whole family.

The dates are Saturday, 30th September and Sunday, 1st October 1978.

For field contestants the Wagga standard will be maintained. Events will be tough and mind-boggling, as the contest committee has had a lot of experience in setting unusual tasks.

## CHIRNSIDE ELECTRONICS

**FRG-700U: a high performance genera. coverage receiver for the discriminating shortwave listener.**

- Digital Frequency Display
- Full MF/HF Coverage ... from 0.25-29.9 MHz, with provision for SSB and AM voice as well as CW reception

**FT-101E 160-10M \$869.**  
Complete AC DC Transceiver with Built in RF processor. The rig comes complete with mic and cables. 250 PEP SSB, 180 Watt CW, and 80 Watt AM plus lots of other features.

**FRG-7 Comm. Receiver.**  
General Coverage Communications Receiver from 5 MHz to 30 MHz. Uses Watley Loop System (drift cancellation circuit). Guarantees excellent stability. **\$348.**

**QTR-24**  
24 hour World Clock. Will tell you the time anywhere in the world at just a glance. **\$33.**

**YP-150 Dummy Load-Power Meter.**  
1.8MHz - 200MHz **\$108.**

**EMOTATOR ROTATORS**

**CHIRNSIDE ELECTRONICS**  
26 EDWARDS RD.  
LILYDALE 3140.  
PHONE (03)726 7353

DEALER ENQUIRIES WELCOME



**all rigs predelivery checked!**



**ICOM**

|                                          |            |
|------------------------------------------|------------|
| IC701 HF digital solid-state transceiver | \$1,380.00 |
| IC701PS matching power supply / speaker  | \$279.00   |
| IC202E 2m ssb portable (new model)       | \$219.00   |
| IC502 6m ssb portable                    | \$219.00   |
| IC402 70cm ssb portable, coming soon!    |            |
| IC225 2m fm mobile transceiver           | \$335.00   |
| RM-3 Remote controller                   | \$169.00   |
| ICSM2 condenser-electret desk mic        | \$56.00    |
| IC245 2m fm digital mobile transceiver   | \$575.00   |
| IC211 digital 2m all mode                | \$785.00   |



**NEW**

399.00

**IC-280 2m fm transceiver**

**REMOVABLE  
COMPUTER  
CONTROLLED  
144-148 MHz  
ICOM**



**KENWOOD**

|                                     |            |
|-------------------------------------|------------|
| TSS20S HF transceiver               | \$789.00   |
| TS820S HF transceiver               | \$1,279.00 |
| SP820 matching speaker with filters | \$66.00    |
| SM220 station monitor               | \$335.00   |
| TL922 Linear Amplifier              | \$1,450.00 |
| AT200 matching antenna tuner        | \$185.00   |
| TV506 6m transverter                | \$236.00   |
| TV502S 2m transverter               | \$290.00   |
| TR3200 70cm fm portable transceiver | \$229.00   |



**KENWOOD TS-820S  
transceiver**

TS-820S features: • Factory installed digital frequency readout • 160 thru 10 meter coverage • Integral IF shift • RF speech processor • VOX • Noise blanker • PLL • Built-in 25 KHz calibrator • CW sidetone & semi-break-in • IF OUT, RTTY, & XVTR • 200 W PEP input

**\$1279.00 Give us a call today**




**KENWOOD TS-520S  
transceiver**

Features: • 160-10 meter coverage • Optional DG-5 digital frequency display • New speech processor w/audio compression amplifier • AC power supply (DC optional) • RF attenuator, front-panel activated • Provisions for sep. receive antenna & phone patch • 200 W PEP input.

**\$789.00 Plenty in stock!**

**rotators**

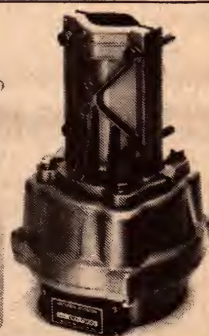

NEW FROM DAIWA, QUALITY ANTENNA ROTATORS COMPLETE WITH 240VAC CONTROL BOX:

|                           |            |          |
|---------------------------|------------|----------|
| Model DR7500S medium duty | <b>NEW</b> | \$189.00 |
| Model DR7600S heavy duty  |            | \$259.00 |

**Trade-ins accepted**

**ANTENNA CHANGE-OVER RELAYS (DAIWA)**

|                                      |         |
|--------------------------------------|---------|
| CX-2L 1.8 thru 170 MHz, 100w pep max | \$48.00 |
| CX-2H 1.8 thru 450 MHz, 200w pep max | \$69.00 |

**COAXIAL SWITCHES (DAIWA)**

|                                           |         |
|-------------------------------------------|---------|
| CS201 2 position, high pwr, up to 500 MHz | \$25.00 |
| CS401 4 position, high pwr, up to 500 MHz | \$59.00 |

**SPEECH COMPRESSORS (DAIWA)**

|                              |          |
|------------------------------|----------|
| RF440 phasing type, 6dB gain | \$135.00 |
| RF550 filter type, 6dB gain  | \$179.00 |

**MORSE KEYS**

|                                   |          |
|-----------------------------------|----------|
| HK702 deluxe key with marble base | \$39.00  |
| HK708 economy key                 | \$21.00  |
| HK706 operator's key              | \$25.00  |
| MK701 manipulator (side swiper)   | \$43.00  |
| EK1032 electronic Keyer           | \$169.00 |
| Palomar IC Keyer                  | \$149.00 |

**MICROPHONES**

|                                       |         |
|---------------------------------------|---------|
| VM-1 noise cancelling, dynamic, low Z | \$9.50  |
| VM-2 Desk mic, dynamic, low Z         | \$29.80 |
| MC-50 Kenwood Desk mic                | \$58.00 |
| MC-35S Kenwood hand ptt mic           | \$20.00 |
| Icom hand ptt, low Z                  | \$14.50 |

**MOBILE SUPPRESSORS**

|                                             |         |
|---------------------------------------------|---------|
| Hansen NB-2 heavy duty type for alternators | \$9.50  |
| Hansen truck 100 amp alternator filter      | \$22.00 |

**TRAP DIPOLES**

|                            |          |
|----------------------------|----------|
| MIDY VN 80-10M, 23.5M long | \$109.00 |
| AL48DXN 40/80M dipole      | \$68.00  |
| AL24DXN 20/40M dipole      | \$65.00  |

**TRAP VERTICALS**

|                                 |          |
|---------------------------------|----------|
| V4JR 40-10M, 5.2M high, no guys | \$99.00  |
| V5JR 80-10M, 6.7M high, no guys | \$165.00 |
| 14AVQ/WB Hy-Gain, 40-10M        | \$109.00 |
| 18AVT/WB Hy-Gain, 80-10M        | \$155.00 |

**DIPOLE KITS**

|                      |         |
|----------------------|---------|
| A4VPN 40M dipole kit | \$32.00 |
|----------------------|---------|

**2M ANTENNAS**

|                           |         |
|---------------------------|---------|
| Scalar M22T 1/4 wave whip | \$7.00  |
| Scalar M25T 5/8 wave whip | \$17.50 |
| Bases for above           | \$4.00  |
| Magnetic Bases            | \$19.00 |
| ARX-2 Ringo base antenna  | \$49.00 |

**DISCONE ANTENNAS**

|                                   |         |
|-----------------------------------|---------|
| 9DX-1 80-480 MHz                  | \$84.00 |
| SCAN-X 65-530 MHz (Receiver Only) | \$35.00 |

**DIP METERS**

|                            |          |
|----------------------------|----------|
| TRIO DM800, ideal for hams | \$145.00 |
|----------------------------|----------|

**70cm BEAMS (JAYBEAM)**

|                                            |          |
|--------------------------------------------|----------|
| 88/70cm, 18.5 dBd gain, 88el, length 3.98M | \$102.00 |
| 48/70cm, 15.7 dBd gain, 48el, length 1.83M | \$79.00  |
| PBM18/70, 18el, 14.9 dBd gain, length 2.8M | \$71.00  |
| D8/70cm, twin 8el, 70cm, 12.3 dBd, 1.1M    | \$62.00  |

**antennas**

**SWR/PWR METERS**

|                                       |          |
|---------------------------------------|----------|
| VC2 twin meters, 3-150 MHz cal. chart | \$34.00  |
| SWR200 Osckerblock 2-200 MHz          | \$75.00  |
| SW410A 140-500 MHz, direct reading    | \$129.00 |
| SW210A 1.8-150 MHz, direct reading    | \$96.00  |
| SWX777 up to 30 MHz, professional     | \$131.00 |

**LOW PASS FILTERS**

|                                      |         |
|--------------------------------------|---------|
| FD30M 32 MHz Fc, 1 Kw max, 3 stages  | \$35.00 |
| FD30LS 32 MHz Fc, 200w max, 3 stages | \$20.00 |

**NOISE BRIDGES**

|                            |         |
|----------------------------|---------|
| Omega TE7-01 up to 100 MHz | \$49.00 |
| Palomar up to 100 MHz      | \$79.00 |

**BALUNS**

|                                     |         |
|-------------------------------------|---------|
| AS-BL for beams                     | \$31.50 |
| BL50A 50 ohm 4 Kw model for dipoles | \$26.00 |
| BL70A 70 ohm 4 Kw model for dipoles | \$27.00 |

**VALVES**

|                                  |         |
|----------------------------------|---------|
| 6146B for Uniden, Kenwood, Yaesu | \$13.00 |
| 6KD6 for early Yaesu linears     | \$13.00 |
| 6JS6C for FT101 series           | \$13.50 |
| 572B for Yaesu linears           | \$59.00 |

**2M BEAMS**

|                                             |         |
|---------------------------------------------|---------|
| 5Y/2M Jaybeam, 7.8 dBd, length 1.6M, 8el    | \$39.00 |
| 8Y/2M Jaybeam, 9.5 dBd, length 2.8M, 8el    | \$47.00 |
| 10Y/2M Jaybeam, 11.4 dBd, length 4.4M, 10el | \$79.00 |

**VICOM**

68 Eastern Road  
SOUTH MELBOURNE VIC 3205  
PH (03) 699.6700 Telex AA30566

|            |          |           |          |
|------------|----------|-----------|----------|
| Perth      | 446.3232 | Sydney    | 681.3544 |
| Adelaide   | 43.7981  | Brisbane  | 38.4480  |
| Gold Coast | 32.2644  | Hobart    | 43.6337  |
| Canberra   | 82.3581  | Melbourne | 836.8635 |



# AMATEUR RADIO

The convention site will be a rural area out of town, with caravan sites available. There are also on-site vans available in town. The whole accommodation of one motel has been reserved for visitors.

The program will include an 80 metre contest for those enroute to the convention on Saturday. Contacts must be within the novice licence segment of the band.

Talk-in facilities on 80 metres, channel 3 repeater, and 10 metres will be maintained continuously throughout Saturday and most of Sunday.

There will be VHF and HF scrambles, two and ten-metre talk-in events, and VHF transmitter hunts.

Events will also be held for the ladies and children.

Trade displays have been arranged, and there will be demonstrations of RTTY and amateur TV.

The official convention dinner will be held at the Wagga Leagues Club on Saturday night. Baby sitting facilities have been arranged for young children during the dinner.

Do not leave accommodation bookings to the last minute. Send details of your requirements to the

Secretary, Wagga Amateur Radio Club, PO box 71, Koorlingal, Wagga 2650

**CAPRICORNIA AMATEUR RADIO FESTIVAL:** The Central Queensland Branch, WIA is holding this festival on the 16th and 17th September, 1978, at Rockhampton. The venue is the National Fitness Centre, Northern End of Fitzroy Bridge, Rockhampton.

If you are looking for an excuse to visit that area of Queensland then go to the Springtime Festival in Rockhampton from the 9th to 17th September, 1978.

The CARF program commences at 1030 Saturday 16th September with registration, arrangement and acceptance of competitive entries and displays; 1300 lunch, barbeque facilities available; 1400 official opening; 1430 female fun hour, film lecture, hidden transmitter hunt, mobile frequency check, 1700 free time; 1830 smorgasbord dinner; 1930 guest speaker; 2000 - 2200 entertainment.

Sunday 17th WIA news broadcast; 0930 judging competitive items, ladies and gents; \$000 swap and sell, ladies interest segment, disposals auction; 1030 hidden transmitter hunt, technical talk, scramble; 1200 presentation of prizes; 1300 barbeque; 1400 conclusion. For further information write to:— WIA, CQ Branch, PO Box 496, Rockhampton Q. 4700.

**WORKED-ALL-QUEENSLAND AWARD:** Issued by Queensland Division of the WIA.

1. zthis award is divided into two sections — Worked all Cities and Towns, and Worked all Shires.

2. Any amateur or shortwave listener may apply for the award, provided that applications comply with the rules.

3. Only one award is issued to an individual station but this will be updated upon receipt of further contacts.

4. Worked all Cities and Towns: There are 20 incorporated cities and towns in Queensland. The initial award: 15 contacts with radio amateurs operating from these cities or towns. A silver sticker will be issued if all 20 are worked.

5. Worked all Shires: There are 111 shires in Queensland. For this award the 1976 listing is considered to be the correct one. The population figures in these shires range from 250 to well over 25000. Initial award; 51 contacts, with stickers for 61, 71, 81, 91, 101 shires, with a gold sticker if all shires have been contacted.

6. Modes and bands: All legitimate modes and bands may be used, LF, HF, VHF, UHF, OSCAR, EME etc., but cross-band contacts are now allowed.

7. Special VK-rules: As a number of areas are not very active, DX-peditions to these areas are encouraged ... to help the award hunter to get that rare Queensland shire, town or city. The following will apply: a. The Queensland awards manager or his appointed delegate shall be advised in writing of the intended VK/P operation in those areas which are not too active or are non-active. If approximate operation dates are available, advance publicity could be given and you may become a much sought after rare DX station.

b. A copy of the VK/P log shall be forwarded to the Queensland awards manager for use as a check list. The VK/P operator will automatically be credited with "having worked" that particular area, if: (I) At least 50 contacts were made with a minimum of four VK call areas, or (II) at least 30 overseas contacts are logged.

8. Method of application: A certified list of contacts, as per CHC rules, to be sent to: The WIA (Q) Awards Manager, GPO Box 638, Brisbane, Queensland 4001, Australia. Together with either \$1.00 (Aust) or 10 IRCs for the initial award. Subsequent stickers will be issued free, although return postage will be appreciated.

9. Contacts made as from 1st January 1976 will be valid for this award.

10. Queensland amateurs, as a matter of courtesy, should include the town, city or shire in which they reside on their QSL cards.

Space does not permit the inclusion of the list of cities, towns and shires. However, the details are available from the address given above.

## TRIAL NOVICE EXAMINATION

The next P & T Department examination for the amateur novice licence will

## BRIGHT STAR CRYSTALS PTY LTD

35 EILEEN ROAD, CLAYTON, VICTORIA, 546 5076. TELEX AA36004  
(ALL MAIL TO:— P.O. BOX 42, SPRINGVALE, VIC. 3171)




With more than 36 years experience BRIGHT STAR can supply your Crystal needs.

### ALSO AVAILABLE

- Wideband Amplifiers.
- Crystal Oscillators.
- Crystal Clock and Decade Counters, C-MOS, TTL.
- Pre Scalars to 250MHz.
- (See previous advertisements.)
- Send S.A.E. for new catalogue

Crystal Clock and Decade Counter

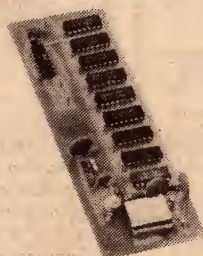

Wideband Amplifier



HOSE & EQUIPMENT CO. PTY. LTD. SYDNEY. PHONE 666-8144

WESTEST ELECTRONICS,  
PERTH. 337 6392.

FRED HOE & SONS PTY. LTD.  
BRISBANE. PHONE 277 4311

ROGERS ELECTRONICS  
ADELAIDE. PHONE 42 6666

DILMOND INSTRUMENTS  
HOBART. PHONE 47 9077



# AMATEUR RADIO

be in October, 1978. To give candidates first hand examination experience, the WIA Education Service has organised a trial examination on Saturday 16th September, 1978, from 2.00 pm to 4.30 pm.

The theory paper will be based on the syllabus recently approved by the P & T Department.

An examination fee of \$1.00 will apply. Instructors or individual candidates who wish to take advantage of this project may obtain full details from the — Education Officer, WIA (NSW) Education Service, PO Box 109, Toongabbie, 2146.

## WICEN & "CITY TO SURF"

As these notes went to press, Sydney members of WICEN were preparing for their biggest exercise to date; providing radio communication for the famous "City to Surf" race on August 13.

The exercise planned to use some 40 WICEN members, with about as many sets, to provide the following services.

Within the Town Hall, pre-race, a low power base station and four pedestrian mobiles, one for each of four senior officials. These were to use 145MHz simplex, on low power.

Outdoors, two repeaters; channel 1 (main) and channel 2 (reserve). These were to cover the administration centre at the Town Hall, nine intermediate (medical) points en route, and a medical centre and the official finishing point (VIP stand) at Bondi.

In addition, a lead vehicle to provide position reports on the lead runners, and a tail vehicle to pick up stragglers.

At Bondi, another local (pedestrian) net on 146MHz for four first aid attendants and five officials.

Backup circuits were also planned, in case of traffic congestion, using HF, six metres, and UHF.

**AN APPRECIATION:** Amateur radio provided valuable communication for David Gosden, VK7HG during a voyage from Hong Kong to Lae in Papua New Guinea, with the Aston family on their 46 foot sailing cutter.

Using the call sign P29GD/maritime mobile, he was initially in contact with Keith Ford, P29EJ, who provided a welcome voice from the destination port.

As the yacht approached Papua New Guinea contact was lost with Keith on 14MHz. A lower frequency could not be used because the loading unit would not work into the short antenna on the stern of the yacht. However, a 14MHz relay was provided by Lin Rhodes, VK2IB, Tuross Heads, with Morice Burleigh, VK7JU, Launceston, standing by if needed.

Two other networks provided very useful services.

## IONOSPHERIC PREDICTIONS FOR SEPTEMBER

Reproduced below are radio propagation graphs based on information supplied by the Ionospheric Prediction Service Division of the Department of Science. The graphs are based on the limits set by the MUF (Maximum Usable Frequency) and the ALF (Absorption Limiting Frequency). Black bands indicate periods when circuit is open.

9.78

| 7MHz EAST    |                   | 01        | 02 | 03 | 04 | 05 | 06 | 07 | 08 | 09 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 |
|--------------|-------------------|-----------|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|
| EAST AUST TO | BARBADOS (SRI)    |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | JOHANNESBURG      |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | McMURDO SOUND     |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | NEW DELHI         |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | NEW YORK          |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | RIO DE JANEIRO    |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | TOKYO             |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | VANCOUVER         |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | WELLINGTON        |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | WEST AFRICA       |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | WEST EUROPE (SRI) |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | WEST EUROPE (LRI) |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | ADELAIDE TO       | SYDNEY    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | BRISBANE TO       | MELBOURNE |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              |                   | PERTH     |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
| DARWIN TO    | SYDNEY            |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
| MELBOURNE TO | PERTH             |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | SYDNEY            |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
| 14MHz GMT    |                   | 15        | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 01 | 02 | 03 | 04 | 05 | 06 | 07 | 08 | 09 | 10 | 11 | 12 | 13 |
| EAST AUST TO | BARBADOS (SRI)    |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | JOHANNESBURG      |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | McMURDO SOUND     |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | NEW DELHI         |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | NEW YORK          |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | RIO DE JANEIRO    |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | TOKYO             |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | VANCOUVER         |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | WELLINGTON        |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | WEST AFRICA       |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | WEST EUROPE (SRI) |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | WEST EUROPE (LRI) |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | ADELAIDE TO       | SYDNEY    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | BRISBANE TO       | MELBOURNE |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              |                   | PERTH     |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
| DARWIN TO    | SYDNEY            |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
| MELBOURNE TO | PERTH             |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | SYDNEY            |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
| 21MHz EAST   |                   | 01        | 02 | 03 | 04 | 05 | 06 | 07 | 08 | 09 | 10 | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 |
| EAST AUST TO | BARBADOS (SRI)    |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | JOHANNESBURG      |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | McMURDO SOUND     |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | NEW DELHI         |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | NEW YORK          |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | RIO DE JANEIRO    |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | TOKYO             |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | VANCOUVER         |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | WELLINGTON        |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | WEST AFRICA       |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | WEST EUROPE (SRI) |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | WEST EUROPE (LRI) |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | ADELAIDE TO       | SYDNEY    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | BRISBANE TO       | MELBOURNE |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              |                   | PERTH     |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
| DARWIN TO    | SYDNEY            |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
| MELBOURNE TO | PERTH             |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|              | SYDNEY            |           |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |

One was the Pacific Maritime Mobile Network co-ordinated by Ted Mulholland, VK4AEM and Noel Curtis, ZL1CU. The yacht checked in each day to report its position and course. It was reassuring to know that help could be provided if required.

The other network was the Pacific Inter-island Network which operates mainly in the USA administrated groups of Mariana, Marshall and Caroline Islands.

### NOVICE STUDY PACKAGE

The review of this package, on page 108 in the August issue, unfortunately omitted the address of the publisher. This is: Ann Davis Publications, P.O. Box 200, Alderly, Queensland 4051.

However, it also provides communications with other Pacific islands and amateur radio equipped vessels. Dixie, KG6JIO on Guam provided regular weather forecasts and Dick KC6AQ on Palau gave the yacht crew much assistance during their visit to Palau. As the yacht approached Palau, Dick advised the best passage through the narrow coral reef entrance and also where they could get supplies and a hot shower; very welcome information after a week at sea.

David, VK7HG is convinced that

amateur radio is more than just a hobby and wishes to thank all those who assisted with the communications.

### AMATEUR RADIO STAMP

In 1976 Japanese amateurs celebrated the 50th anniversary of the Japan Amateur Radio Leabue, which was established on 12th June, 1926. However, it was not until 10th September, 1927 that the first government licence was issued.

In commemoration of this genuine 50th anniversary of amateur radio, Japan issued a 50 yen postage stamp featuring a horn shaped speaker and a telegraph key on 24th September, 1977.

### SO YOU WANT TO BE A RADIO AMATEUR?

To achieve this aim, why not undertake one of the Courses conducted by the Wireless Institute of Australia? Established in 1910 to further the interests of Amateur Radio, the Institute is well qualified to assist you to your goal. Correspondence Courses are available at any time. Personal classes commence in February each year.

For further information write to

**THE COURSE SUPERVISOR,  
W.I.A.  
14 ATCHISON STREET,  
CROWS NEST, N.S.W. 2065**



## FDK Multi-800D 2-metre transceiver

Sideband Electronics Imports, of Springwood, NSW, have submitted a sample of the FDK Multi-800D 2-metre transceiver made by the Fukuyama Electronics Co, Ltd, of Japan. Many Australian amateurs are already familiar with this company's products, particularly the "Multi-7" 2-metre transceiver of a few years ago.

The standard of modern transceivers is so high that, in terms of basic performance, it is difficult to pick one unit over another. Receiver sensitivity, for example, and for all practical purposes, turns out to be almost identical for units in the same class.

The same applies to most other basic specifications, so that the final choice is more likely to be based on the features which a particular unit offers.

Having said that, it will come as no surprise when I say that the Multi-800D performs very much as we have come to expect modern 2-metre transceivers to perform; the effective sensitivity is excellent, there is complete freedom from spurious signals, and there was no sign of cross modulation effects. Similarly, the transmitter performed well in every way.

So let us look first at the features which this transceiver has to offer. As is common practice, it uses a phase locked loop synthesiser for frequency selection, and covers the full 4MHz of the 2-metre band in 5kHz steps.

The novelty in this case is the method of frequency selection. It is by an internal counter which is activated by a panel knob with a choice of three different counting speeds, plus a one (5kHz) step-at-a-time facility.

The knob is spring loaded and is turned clockwise for an increase in frequency and anti-clockwise for a decrease. The first position in each direction gives the one step at a time, or notching, facility.

The second position steps across the band at a rate of 20kHz/sec., which is quite slow, the next position at 100kHz/sec., and the final position at a fast 500kHz/sec. This last covers the entire band in approximately four seconds. When the counter reaches either end of the band it skips back to the opposite end, and commences over again. While counting, the set emits an audible tone every 100kHz.

A memory circuit allows any selected frequency to be held while another frequency is selected and used. Any frequency which has been selected, or stored in the memory, is retained when the set is switched off, provided this is by means of the panel knob only.

The frequency is read out on a four digit LED display, giving the last MHz figure, followed by the 100kHz, 10kHz and 5kHz figures. It is a bright red display, readable in any reasonable ambient light condition.

A feature associated with this is an external display unit, available as an optional extra. It connects to a multi-pin socket on the back of the set via a cord about two metres long and mounts by



an adjustable bracket. It is intended primarily for mobile use, to allow the frequency readout to be presented in the most convenient place, such as the top of the dashboard. The figures are slightly larger than the main display, and are green rather than red.

An auxiliary switch provides for simplex or repeater operation, with +600kHz and -600kHz splits, and a free split position. This permits any combination of transmit/receive frequencies to be used, in conjunction with the memory circuit. When split frequencies are being used the digital display changes with the change from receive to transmit.

The transmitter is rated at 25W output, rather than the more common 10W rating, yet the set is not significantly larger than other makes. The power output is continuously adjustable from 1W to 25W by means of a panel knob — a feature not found on many other sets.

A small panel meter serves as an "S" meter for receive, and as an RF power indicator on transmit, but is a relative indicator only in the latter mode, without calibrations.

There are two auxiliary speaker sockets on the rear panel. One drives the external speaker only; the other allows both the internal and external speakers to function.

The set is sturdily built and well finished. It is provided with a handle which doubles as a stand for bench use, and a versatile mounting bracket. It fits in runners in the side of the set, thus simplifying fitting it to, or removing it from, the vehicle.

Tested on the air, in a typical amateur situation, the set performed extremely well. Effective receiver sensitivity, as judged subjectively, was at least as good as others in its class or, in some case, marginally better. However, the difference was more academic than practical.

The method of frequency selection takes a little getting used to but, once the strangeness wears off, it can be used very effectively. Naturally, the fast count is used for major moves and the slower ones as the required frequency is approached. The last few 5kHz steps are notched up.

Reports on the transmission were all

favourable, with some spontaneous comments on "... a nice audio quality."

The instruction manual contains a circuit diagram and a block diagram, as well as normal set description and operating instructions. The circuit diagram has been reduced considerably, but is still quite legible. However, the instructions suffer badly from "Japanese English" in places, to the point where some would be confusing if taken literally. However, we doubt whether this would worry many amateurs.

For the amateur who needs one set for both base and mobile use, the external readout, the extra power, and convenient mounting arrangement are worthwhile features. The extra power may also appeal to the poorly sited amateur, as an aid to working distant repeaters.

Details of price and availability of both the basic unit and the optional extra display unit may be obtained from Sideband Electronic Imports, PO Box 23, Springwood, NSW 2777. Phone (047) 51 1395. (PGW)



# bail



DOES YOUR ANTENNA TURN IN THE WIND?

DOES YOUR CONTROL UNIT  
'CUT-OUT' AFTER ONLY A FEW REVOLUTIONS?



... then step-up to a RELIABLE EMOTO ROTOR.

Bail Electronics are pleased to announce ...  
... an exciting range of ANTENNA ROTATORS  
by EMOTO ANTENNA Co. of Japan



**EMOTO FEATURES**  
• ROBUST DESIGN  
• HEAVY DUTY STAINLESS HARDWARE  
• 100v. SUPPLY TO MOTOR REDUCES VOLTAGE/POWER-LOSS

**COMPARISON OF ROTOR BRAKE TORQUE FIGURES (kg./cm.)**

| CDE model   | Torque |
|-------------|--------|
| CD44        | 1,152  |
| HAM-2       | 4,025  |
| Emoto model |        |
| 103 LBX     | 1,500  |
| 502 CXX     | 4,000  |
| 1102 MXX    | 10,000 |


We have been in the business long enough to know your requirements for a first class antenna rotor, and we have gone "over-board" for the EMOTO range! There are many brands of antenna rotors, some of them completely unsuitable for the majority of amateur applications, and for this reason we do not stock them.

Most likely your present antenna rotor will turn your antenna and hold satisfactorily, but it just will not hold it stationary under strong wind conditions; i.e. YOUR ROTATOR LACKS SUFFICIENT BRAKE TORQUE, the ability to hold the antenna still whilst a gale is blowing. **HERE IS WHERE THE EMOTO SCORES.** Take a close look at the comparison figures

above. Then compare the prices of all the rotors and you will have to agree that the EMOTO 103 LBX, EMOTO 502 CXX and EMOTO 1102 MXX are the best value. Finally, EMOTO ANTENNA CO., is not a new company. They have been making rotors for many years. Have no fears about this being a new and untried product!
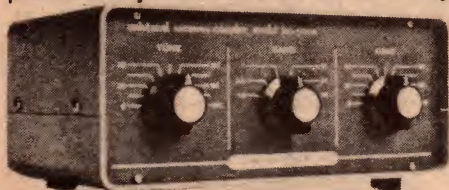
## Universal<sup>®</sup> antenna couplers

Extremely important, especially with modern all-solid state transceivers, is the maintenance of a very low SWR to avoid destruction of costly high-power P.A. transistors. An antenna coupler enables precise adjustment with almost any antenna.



(SW. or co-ax.)

**HC 500A — 160-10m, up to 500w pep**

(also available — not illustrated)

**HC 2500 — 160-10m, up to 2.5kw pep**

**HC-75 — 80-10m, up to 75w pep**

**HC 250 — 80-10m, up to 200w pep**

**KW E-ZEE Match — 80-10m, up to 400w pep**

**FC 301 Yaesu — 160-10m, up to 500w pep**

Now an addition  
to YAESU'S range  
of measuring instruments ...

## QTR-24

24 hour  
World  
Clock



QTR-24

Yaesu has now made an addition to their already well known range of measuring instruments, it is the QTR-24, a 24 hour World Clock. With a glance the time in any principal city or time zone can be simultaneously co-ordinated with local time on a 24 Hour basis. The QTR-24 is powered by a 1.5V dry cell, which has a normal life of approximately one year. No amateur or SWL station could be complete without one.

Our years of handling and specializing in this equipment have enabled us to build up a fund of knowledge and technical experience, backed by a comprehensive range of spare parts and service facilities. We don't just sell a set, our concern extends throughout the life of your equipment.

Contact us for details of other Yaesu equipment plus the accessories required to complete your station.

All equipment from Bail's carries a 90-day warranty and complete service back-up.

JAS 7879-1

# bail

## ELECTRONIC SERVICES

FRED BAIL VK3YS  
JIM BAIL VK3ABA

60 Shannon St., Box Hill North, Vic., 3129.  
Ph. (03) 89 2213

Yaesu Agents in Australia since 1963

Radio amateur equipment from B.E.S. also sold by —

|        |                                                                                   |              |
|--------|-----------------------------------------------------------------------------------|--------------|
| W.A.   | Radio Communication Services, H. R. PRIDE, 26 Lockhart St., Como, 6152            | Ph. 450 4379 |
|        | WILLIS TRADING CO., 429 Murray Street, Perth 6000                                 | Ph. 21 7609  |
| S.A.   | FARMERS RADIO PTY. LTD., 20 Stanley St., Plympton 5038                            | Ph. 293 2155 |
| TAS.   | G. T. ELECTRONICS, 131 Westbury Rd., South Launceston 7200                        | Ph. 44 4773  |
|        | J. P. ELECTRONICS 64 Wentworth St., Launceston 7200.                              | Ph. 44 5000  |
|        | PRINS RADIO, 123 Argyle Street, Hobart 7000                                       | Ph. 34 6912  |
| N.S.W. | Aviation Tooling, STEPHEN KUHLE, 104 Robey St., Mascot 2020                       | Ph. 667 1650 |
|        | Amateur & Novice Comm. Supplies, W. E. BRODIE, 23 Dalray Street, Seven Hills 2147 | Ph. 624 2691 |
|        | DIGITRONICS, 186 Parry St., Newcastle West 2302                                   | Ph. 69 2040  |
|        | RIVERCOM, Sid Ward, 9 Copland St., Wagga Wagga 2650                               | Ph. 21 2125  |
| QLD.   | H. C. BARLOW, 92 Charles St., Aitkenvale, Townsville 4814                         | Ph. 79 8179  |
|        | MITCHELL RADIO CO., 59 Albion Rd., Albion 4010                                    | Ph. 57 6830  |
| A.C.T. | QUICKTRONIC, Jim Bland, Shop 11, Altree Crt., Phillip 2606                        | Ph. 81 2824  |
|        |                                                                                   | 82 2864      |





# YAESU from DICK SMITH

WHEN YOU REALLY CONSIDER THE ALTERNATIVES — THERE ARE NONE!



## Fabulous FRG-7 Communications Receiver

- \* 0.5 to 30MHz continuous reception
- \* Wadley loop circuitry for stability
- \* Mains or 12 volt operation — portable.
- \* BFO for sideband or CW reception
- \* 0.7uV sensitivity (for 10dB signal/noise)
- \* 2 IC's, 22 transistors and 16 diodes
- \* Comes with full instructions plus guide

### EXCLUSIVE!

With every FRG-7 from Dick Smith or dealers, you receive this exclusive 6 page guide to short wave listening — written by Arthur Cushen, MBE — world famous short-wave correspondent and broadcaster.



CAT. D-2850

only  
**\$350**

Terms available


See the review in MAY 1978 E.A.

\*\*\*\*\*

NOW: A short wave antenna kit for the FRG-7 receiver (and any other shortwave receiver...)

Designed specifically for Dick by a short-wave expert, this antenna kit needs no soldering, is complete and ready to assemble and has full instructions. Get the most out of your receiver with a good antenna.

**\$9<sup>50</sup>**

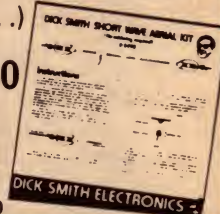


VALUE! Cat K-3490



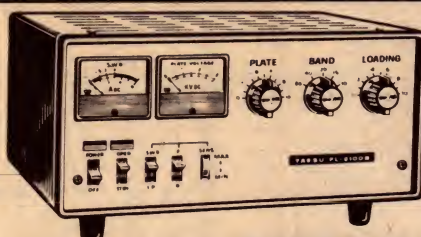**FT101E \$895**

The most popular HF rig in the world! The FT-101E offers full 160 through 10 metre operation on CW, SSB & AM. Rated at 260 watts PEP — with a receiver more sensitive and with less IM distortion than the TS-520S (see our ad last month for comparison). 240V and 12V supplies built in. Join the Yaesu family — soon. Cat D-2860



**FL2100 \$585**

Here it is: the magnificent FL-2100B heavy duty linear amplifier for amateurs. It covers the 80 through 10 metre amateur bands, and is conservatively rated at 1.2kW. Offers the punch to get through when the QRM & QRN are trying their hardest to stop you! Can be used with any HF transceiver rated at 50W PEP or more. Cat D-2546



**FT901D \$1375**

Tomorrow's transceiver — today. It really is the ham's dream: full HF coverage (160 — 10 metres) on all modes (yes, even FM and FSK). Gives digital AND analogue readout, has rugged 6146B finals (90% solid state). This beautiful unit has features others can only dream of! Cat D-2854  
Optional memory unit: Cat D-2858 \$149.50  
Optional DC/DC conv.: Cat D-2856 \$75.00

## SAVE \$100 ON FT301



### FP301: Matching Power Supply

Heavy duty 13.5V @ 25A regulated supply to match the FT-301, FT-7, etc (also an ideal workshop supply). Cat. D-2872.

STILL ONLY  
**\$170<sup>00</sup>**

**\$895**

Factory saving passed on to YOU! Yes — was \$995 (last shipment... All solid state (inc. finals), 200W PEP on all HF amateur bands with AM, CW, SSB & FSK. 12V operation (ideal for mobile or base) with RF speech processor & marker, effective noise blanker. Cat D-2870

\*\*\*\*\*  
Easy terms available to approved applicants on all purchases over \$111

## NEW!

### YAESU ANTENNA TUNER FC301

Cat D-2896



- \* Huge 500 watt rating
- \* Inbuilt power meter
- \* Inbuilt SWR meter
- \* Inbuilt 4 position co-ax switch
- \* 160 — 10 metres & direct

Special introductory price:

**\$249**

## STOP PRESS!

### HEAVY DUTY CO-AX RELAY NOW REDUCED!

Yes! Now you can save over 10% on this quality co-ax relay. Save the high cost of an extra run of co-ax. Make instant band switches or antenna comparisons. Handles 2500W PEP to 60MHz, 1500W PEP to 500MHz. 52 ohm impedance with an insertion loss of less than 0.1dB

~~\$49<sup>50</sup>~~  
**\$44<sup>50</sup>**



Cat D-5210



# AT LAST! THE YAESU FRG-7000

Yes! It's been a long time coming — but the wait was well and truly worth it . . . .  
The Yaesu FRG-7000 offers the serious SWL the ultimate in a communications receiver.



**\$695**


Cat D-2848

Terms are available to approved customers (personal shoppers only) on any item priced \$111 or more, from 10% deposit and easy payments. Mail order customers: We'll send you purchase anywhere in Australia for \$5.00 extra — by Comet.

- Digital frequency readout for accuracy (and allow absolute certainty in returning to a previously logged station)
- Full band coverage — from 0.25MHz (yes, 0.25) up to 29.9MHz — with provision for AM, SSB and CW reception
- Digital clock built-in displays local OR GMT (at the flick of a switch) plus allows the receiver to be turned on at any time (eg for recording when you're not there!)
- Wadley Loop circuitry for rock-solid stability plus FET front end for sensitivity
- Operates from 100 to 240V AC 50/60Hz (easy modification allows portable 12V use)
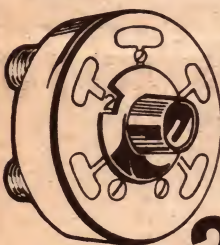
## NEW! High Quality 5position co-ax switch

- \* Grounds all unused inputs
- \* 52 ohm impedance
- \* 2000W SSB
- \* Low SWR and crosstalk
- \* Fitted with a UHF connector



Why take chances with your finals? A proper co-ax switch also reduces TVI, increases efficiency. Insertion loss is negligible, VSWR less than 1.2:1. Up to 150MHz.

**\$29<sup>50</sup>**

Cat. D-5208

## Why not build your whole station around YAESU?




The QTR24 World Clock. Work out at a glance what the time is in any time zone in the world. Every ham should have one. Cat X-1054 . . . . \$33.00

YD-844A desk microphone. 500 ohm/50k switch makes this ideal for all YAESU transceivers. Complete your base station with a YAESU microphone. Cat. C-1116 . \$44.50




## NEW YAESU ANTENNAS

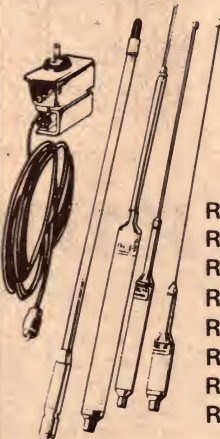

Here's the brilliant Yaesu mobile antenna system for HF and VHF. You buy the gutter mount base and 2m stub, and you're on the air on 2m immediately. As you want the HF bands, simply buy that band resonator/antenna whip and screw it into the 2m stub. You only have to buy the whips you want for the bands you want. Now there's no excuse to stay base . . . go mobile with Yaesu!

|         |              |       |         |
|---------|--------------|-------|---------|
| RSE-M-2 | gutter mount | D4100 | \$32.50 |
| RSE-2A  | 2M stub      | D4102 | \$10.95 |
| RSL-145 | 6M/2M ant    | D4104 | \$23.95 |
| RSL-3.5 | 80M antenna  | D4110 | \$19.95 |
| RSL-7   | 40M antenna  | D4112 | \$19.95 |
| RSL-14  | 20M antenna  | D4114 | \$20.95 |
| RSL-21  | 15M antenna  | D4116 | \$20.95 |
| RSL-28  | 10M antenna  | D4118 | \$20.95 |

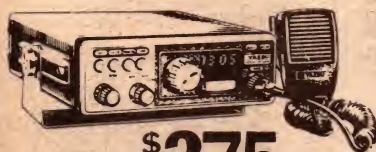EASY TERMS AVAILABLE TO APPROVED APPLICANTS ON ALL ITEMS PRICED \$111 OR MORE.



**FT-227R — FULL 2M RIG**

**\$375**

As reviewed in the March issue of Electronics Australia. Full 2 metre, synthesised FM unit with memory. Ideal for repeaters and duplex operation. Best value rig available today! Cat D-2890



**YC-500S — 500MHz COUNTER**

**\$525**

Fabulous professional quality — 500MHz counter. As reviewed in April E.A. 240V or 12V operation. And it's even cheaper if you have a sales tax exemption! Cat D-2892



**FT-7 — NEW HF MOBILE RIG**

**\$539**

Here it is! The new HF solid state 80 — 10 metre mobile transceiver. It's ideal for novice use, too. The best mobile unit going! Cat D-2866



**FL-110 — 200W LINEAR**

**\$239**

Use the FT-7 or FT-301S as a full-power unit with the 200W linear amplifier. One knob band switching, no tuning required. Cat D-2884

## DICK SMITH ELECTRONICS



**SYDNEY**

125 York Street, SYDNEY. Ph. 29-1126  
147 Hume Hwy, CHULLORA. Ph. 642-8922  
162 Pacific Hwy, GORE HILL. Ph. 439-5311  
30 Grose Street, PARRAMATTA. Ph. 683-1133

**MELBOURNE**

399 Lonsdale Street, MELBOURNE. Ph. 67-9834  
656 Bridge Road, RICHMOND. Ph. 42-1614  
166 Logan Road, BURANDA. Ph. 391-6233  
203 Wright Street, ADELAIDE. Ph. 212-1962

**BRISBANE  
ADELAIDE**

**MAIL ORDERS** P.O. Box 747, Crows Nest, N.S.W. 2065. Post and packing extra.

Dealers across Australia.

SHOPS OPEN 9AM to 5.30PM  
(Saturday 9AM - 12 noon)  
BRISBANE 1/2 Hour earlier.

• ANY TERMS OFFERED ARE TO APPROVED APPLICANTS ONLY


Many lines available from the Dick Smith Electronics Centres at

**GRACE BROS**

Broadway - Bondi - Chatswood - Liverpool  
Murgud - Mt Druitt - Parramatta - Roselands  
and Warringah Mall





|                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                   |                                                                                                                                                                                                                                                                                                                                                                                                                                                                    |                                                                                                                                                                                                                                                                                                                                                               |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                           |
|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| <b>GENUINE AIRCRAFT CLOCKS</b><br><b>8-DAY EX RAAF</b><br><b>\$27.50</b><br>P & P A \$1.60 B \$2.50<br>C \$2.70 D \$2.70                                                                                                                                                                                                                                                                                                                                                                          | <b>SENSITIVE ALTIMETERS</b><br>Ex RAAF Smiths, \$65 each<br>P&P \$1.10                                                                                                                                                                                                                                                                                                                                                                                             | <b>POSTAGE KEY:</b><br>A: NSW<br>B: Vic. Qld. SA<br>C: NT, Tas.<br>D: WA                                                                                                                                                                                                                                                                                      | <b>AIRCRAFT INSTRUMENTS</b><br>Directional Gyros.<br>AN5735-1 Air Operated.<br>Dimensions: 6inx5inx5in.<br>Weight: 2kg<br><b>\$35</b>                                                                                                                                                                                                                                                                                                                                                     |
| <b>GENUINE EX ARMY WRIST WATCHES</b><br>Complete with nylon band <b>\$19.50</b><br>Post \$1.10                                                                                                                                                                                                                                                                                                                                                                                                    | <b>NIFE CELLS</b><br>1.2 volt, fully charged, 4in x 3in x 1in 4 AH.<br><b>\$1.50 each</b> P&P 80c                                                                                                                                                                                                                                                                                                                                                                  | <b>VALVES</b><br>6BM8 <b>\$1.50</b><br>6GV8 <b>\$1.50</b><br><b>BRAND NEW</b> CV850 <b>\$1.50</b><br>65N7GT 95c 1H6G 75c<br>5U4G 95c 832 <b>\$5.00</b><br>EF50 75c 6X4 <b>\$1.80</b><br>5Y3 <b>\$2.25</b> VR65 75c<br>2 X 2 75c<br>P&P 40c                                                                                                                    | Sperry Artificial Horizon.<br>AN5736-1 Air Operated.<br>Dimensions: Length 9in.<br>Diam. 4 1/2in.<br><b>\$45.</b><br>Slip and Turn Indicators<br>Electric. Type Mk. 12.<br>24Vdc.<br>Dimensions: Length 6 1/2in.<br>Diam: 3 1/4in.<br>Weight: 1kg.<br><b>\$17.50.</b><br>P&P A. \$1.60, B. \$2.50, C. \$2.75, D. \$2.75                                                                                                                                                                   |
| <b>P.M.G. TYPE TELEPHONES</b><br>Standard desk type with magneto bell calling device. Range 30 miles. Uses standard batteries at each phone. Any number can be connected together on single line. <b>\$35.00</b><br>(2 TELEPHONE SETS)<br>\$2 Cartage to Rail. Freight payable at nearest attended Railway Station.                                                                                                                                                                               | <b>CENTRE DRILLS 15" / 64 x 5/64</b><br>Carbon Steel, <b>\$3 dozen</b><br>Post 60c                                                                                                                                                                                                                                                                                                                                                                                 | <b>THEODOLITES</b><br>Made by Wilds Microptic, with tripod Model T1, reads down to one minute of ARC <b>\$750.</b><br>(Usual Price <b>\$1750</b> ).<br>Model T2 reads down to one second of ARC <b>\$1000</b> (Usual Price <b>\$3200</b> ).<br>Freight payable at nearest attended R'way Stn.                                                                 | <b>TRANSCIVERS</b><br><b>Ex Army</b><br>No. C45 set. 23 to 38MHz with headphones, mic. 24V power supply, etc. <b>\$95.00</b><br>\$1.00 cartage to rail, freight payable at nearest railway station.                                                                                                                                                                                                                                                                                       |
| <b>TEN CHANNEL VHF TRANSCEIVER</b><br>100 to 125 MHz 28 volt DC operated AM single crystal locks both TX and RX on same channel complete with generator. <b>\$33.00</b>                                                                                                                                                                                                                                                                                                                           | <b>ARTILLERY DIAL SIGHTS MK2</b><br>Can also be adapted as a Dumpy Level or as base for a telescope has full 360° 5 1/2" diam. gunmetal rotating circle. Adjustable elevation and depression. Has top grade 3/4" diam. object lens. F.L. 10" with cross hairs. eyepiece. 1/2" right angle prism — height 10" — weight 3 1/2kgs. With leather carrying case. Original cost \$300. Our Special only <b>\$27.50</b><br>P&P A. \$1.95, B. \$4.25, C. \$5.90, D. \$5.90 | <div data-bbox="572 590 1011 963" data-label="Image"> </div> <b>ZOOM SPOTTING SCOPES</b><br>High grade coated lenses. Ideal for pistol and rifle ranges or general viewing. Zooms in from very low to high powers. Complete with tripods.<br>POST: A. \$1.70, B. \$2.25, C. \$2.40, D. \$2.65.<br><b>TELESCOPES</b><br>25 x 30 <b>\$9.95</b><br>P&P A. \$1.10 | <b>EX-ARMY TWO-WAY FM RADIOS</b><br>                                                                                                                                                                                                                                                                                                                                                                   |
| <b>EX ABC MAGNETIC RECORDING TAPES 1/4"</b><br><b>PROFESSIONAL QUALITY</b><br>5" x 600' ..... <b>\$1.50</b><br>7" x 1200' ..... <b>\$2.75</b><br>P&P A. \$1.10, B. \$2.00, C. \$2.25, D. \$2.25.                                                                                                                                                                                                                                                                                                  | <b>30 x 30</b><br><b>LENGTH 12 1/2", HEIGHT 10"</b><br><b>WEIGHT 1 3/4 lb</b><br><b>\$29.95</b><br>45 x 40<br>Length 16in<br>Height: 10in<br>Weight: 2lb<br><b>\$47.50</b>                                                                                                                                                                                                                                                                                         | <b>CONDENSER LENS</b><br>1 1/2" diam. 4 1/2" F.L. 75c. 2 1/2" diam 2" F.L. <b>\$1.50 each</b> or <b>\$2.50 per pair.</b> P&P 40c                                                                                                                                                                                                                              | <b>1.2 WATTS OUTPUT SUPERHET</b><br>PRC9 AND 9A 27 to 39M/HZ<br>PRC10 AND 10A 38 to 55M/HZ<br>WITH HANDSET ANTENNA \$25 EA.<br><b>UNTESTED</b><br>Battery \$3.50 extra. Harness \$4.50 extra<br>\$2 Cartage to Rail. Freight payable nearest attended Railway Station                                                                                                                                                                                                                     |
| <b>COLLINS INDEPENDENT SIDEBAND TRANSCEIVER TRC/75</b><br>Fully synthesised transceiver with am, upper, lower and independent sideband operation. 1KHz steps from 2MHz to 29.999MHz 1 microvolt sensitivity. 2.5KHz bandwidth ssb. 6KHz bandwidth AM 1 RW. PEP max output. Fully automatic tuning of both transmitter and receiver from remote control unit. Complete with automatic aerial coupling unit, mic, headset, etc. 400Hz supply<br><i>Ideal for amateur use.</i><br><b>PRICE \$750</b> | <b>SPY TELESCOPES</b><br>8 x 17 mag size of a rifle cartridge extends to 8". Only <b>\$6.95 each</b> , post 60c.                                                                                                                                                                                                                                                                                                                                                   | <b>IMPELLER PUMPS</b><br>New gunmetal body, Stainless Steel Shaft, Neoprene Impeller. Up to 15ft. Lift, suitable for almost any type of liquid. Self priming. Ideal boat bilge pump, sillage drains, etc. Approx. size 8" x 5" 3/4" <b>\$30.35</b> , 1/2" <b>\$43.30</b> , 3/4" <b>\$47.60</b><br>P&P A. \$1.90, B. \$2.75, C. \$3.20, D. \$3.95              | <b>16MM SOUND PROJECTORS IN GOOD WORKING ORDER</b><br>240 volts operated complete with Speaker and Amplifier.<br><b>RCA \$275</b><br>\$1 Cartage to Rail. Freight payable at nearest attended Railway Station.                                                                                                                                                                                                                                                                            |
| <b>COLLINS SYNTHESISED 1 SB RECEIVER</b><br>TRC/75 receiver section of transceiver specification as above.<br><b>PRICE \$400</b>                                                                                                                                                                                                                                                                                                                                                                  | <b>BINOCULARS</b><br>PRISMATIC Coated Lenses. Brand new. Complete with case.<br>8 x 30 <b>\$32.50</b> P&P<br>7 x 50 <b>\$43.95</b> A <b>\$1.65</b><br>10 x 50 <b>\$44.95</b> B <b>\$2.75</b><br>12 x 50 <b>\$46.00</b> C <b>\$3.20</b><br>20 x 50 <b>\$47.50</b> D <b>\$3.20</b>                                                                                                                                                                                   | <b>MEGGER Battery Operated</b><br>No cranking — in vinyl case. Ranges. Meg Ohm 0-1000 Megs. Centre 20 meg. Rated voltage 500 volts. Low ohm 0-1000 ohm OH 1 range 0-1 meg ohm on 1k range. AC voltage 0-250 volts. <b>\$79.50</b><br>Post A. \$1.60, B. \$2.50, C. \$2.75, D. \$2.75                                                                          | <b>CB RADIOS</b><br>PMG Approved Famous Pony Brand on 27 Meg.<br>7 transistor model \$55 per set of two (hand held).<br>11 transistor model 1 watt (hand held) <b>\$72 ea.</b><br>5 watt 6 channel <b>\$99 ea.</b><br>Post A. \$1.65, B. \$2.75, C. \$3.20, D. \$3.20                                                                                                                                                                                                                     |
| <b>TELEPHONE WIRE</b><br>1 mile twin (2 miles) genuine ex-Army Don, 8 perfection condition \$35 per drum, \$2.00 cartage to rail freight payable at destination.                                                                                                                                                                                                                                                                                                                                  | <b>SMALL CLIP-ON POCKET TELESCOPE</b><br>15X <b>\$5.40</b> Post 60c                                                                                                                                                                                                                                                                                                                                                                                                | <b>WHIP ANTENNAS</b><br>8ft in 6 tapered sections, copper plated steel no base <b>\$9.50.</b><br>Post <b>\$1.10</b>                                                                                                                                                                                                                                           | <b>COMMUNICATIONS RECEIVER</b><br><b>COLLINS R — 391/URR</b><br>Continuous tuning of range 500 KHz — 32MHz in 32 bands. Receive frequency indicated directly on digital counter type readout to within 300Hz. Selectivity adjustable in six steps. From 100Hz to 16KHz bandwidth. Sensitivity 1 microvolt or better 240 VAC operation — 10 inch rack mount — autotone on eight preset channels available complete with instructions and service manual and tested.<br><b>PRICE \$500.</b> |
| <b>RCA 77DX MICROPHONES</b><br><b>PROFESSIONAL QUALITY \$75</b><br>P&P A. \$1.80, B. \$3.50, C. \$4.55, D. \$4.55.                                                                                                                                                                                                                                                                                                                                                                                | <b>RECEIVER No. 210</b><br>2-16 M/cs <b>\$65.</b><br>Transmitter No. 11 suits 210 <b>\$35.</b><br>24 volt Power supply to suit above <b>\$15.</b><br>Or complete station with Headphones, Mic. Morse Key, Antenna <b>\$110.</b>                                                                                                                                                                                                                                    | <b>MORSE KEY</b>   <b>MORSE KEY BUZZERS</b><br><b>\$1.75</b>   <b>\$4.25</b><br>Post 40c   Post 60c                                                                                                                                                                                                                                                           |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                           |
| <b>KAISE MULTIMETERS</b><br>A compact and handy tester for workshop or lab where quick circuit checks are required.<br>DC Volts 2.5 to 1,000V (20,000 OHMS per volt) AC Volts 10 to 1,000V (10,000 OHMS per volt) DC Current 50 UA 25 MA 250 MA. Resistance 40 K OHM, 4 MEG OHM Decibels minus 20 DB plus 62 DB complete with instructions only <b>\$23.95 ea.</b> P.P. \$1.05. Multimeter similar to above 30,000 OHMS per volt <b>\$29.50 P.P. \$1.05.</b>                                      | <b>SOLENOIDS</b><br>Plunger Type 24V 300MA. Suit electric camera control, miniature trains, radio, etc.<br><b>\$2.50 P&amp;P 20c</b><br>200 MA 24 volt, 1/2in push movement. <b>\$2.50 P&amp;P 20c</b>                                                                                                                                                                                                                                                             | <b>MAGNESIUM DRY CELL BATTERIES</b><br>Suits PRC 25 and dozens of other uses. 15 volts long life only <b>\$1.50 ea.</b><br>P&P A. \$1.65, B. \$2.75, C. \$3.20, D. \$3.20.                                                                                                                                                                                    | <b>Deitch Bros.</b><br><b>70 OXFORD STREET, SYDNEY 2010</b><br>SORRY NO COD                                                                                                                                                                                                                                                                                                                                                                                                               |
| <b>SIEMENS Typing Perforator</b><br>240 Volt Type with Keyboard <b>\$57.50</b>                                                                                                                                                                                                                                                                                                                                                                                                                    | <b>SELSYN MOTORS MAGSLIP</b><br><b>RECEIVERS 2" MK2 \$5.50</b><br><b>TRANSMITTER 3" MK2 \$15.00</b><br>Post Packing A. \$1.75, B. \$2.75, C. \$2.75, D. \$3.65                                                                                                                                                                                                                                                                                                     |                                                                                                                                                                                                                                                                                                                                                               |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                           |
| <b>4 DIGIT RELAY COUNTERS</b><br>50 volt DC, suit slot car Lap counters, etc.<br><b>\$1.25 each, P&amp;P 60c</b>                                                                                                                                                                                                                                                                                                                                                                                  | <b>3000 TYPE RELAYS</b><br>P.M.G. 200 ohms — 1,500 ohm Coils <b>\$2.50 each</b> P&P 60c<br><b>P.M.G. TYPE KEY SWITCHES.</b><br><b>75c P &amp; P 20c</b>                                                                                                                                                                                                                                                                                                            |                                                                                                                                                                                                                                                                                                                                                               |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                           |



# SHORTWAVE SCENE

by Arthur Cushen, MBE



## Radio Nederland links relay bases via satellite

Radio Nederland, with its studios in Hilversum, Holland, and its relay bases on Bonaire and Madagascar, is now broadcasting over these transmitters using a new satellite and undersea cable link.

Both the new Columbus underwater cable (between Holland and the relay station at Bonaire) and the satellite over the Indian Ocean, linking Hilversum and the Madagascar relay base, are now in regular operation. These new communication links mean that programs are now broadcast live simultaneously over all transmitters from the studios in Hilversum.

It has meant that not only is reception of news bulletins of better quality, but all programs are now much more topical than they have been in the past. For instance, DX Jukebox material from the various reporters had to be recorded at least a month in advance so that the tapes could be flown to Holland, the program made up and then the tapes flown back out to the relay base for broadcasting on the scheduled date. This time has now been reduced to 10 days between the time of recording material in Invercargill until its subsequent broadcast from Radio Nederland from the transmitters in Holland, Bonaire and Madagascar.

At present the DX Jukebox program can be heard every Thursday as follows: 0750-0825GMT on 9715 and 9770kHz and 0850-0925GMT on 9715kHz. The Pacific DX Report is heard on the first Thursday of each month, followed by Jan Tuner with a Scandinavian report on the second Thursday, Glen Hauser with the North American report on the third Thursday, and Victor Goonetilleke with an Asian report on the fourth Thursday.

The use of satellite and underwater cable for a continuous broadcast is the first of its type to be undertaken by an international short-wave station. To introduce the new communication



*Radio Nederland's Tom Meyer went on air for 24 hours to celebrate the opening of the new links to the relay bases.*

systems, the Happy Station program of Radio Nederland went on the air for 24 hours with Tom Meyer and this was an outstanding success, as the station received telephone calls from listeners throughout the world. These calls were broadcast live as they were received at the studios in Hilversum.

The most distant call was from Invercargill.

The use of the new links means that programs can be diversified, with many of the programs now only put together the day before their actual broadcast. And, of course, news and current affairs can now be broadcast live.

The BBC has, at times, linked its relay station in Singapore with a satellite link to London. However, this has only been done for news broadcasts when the transmission, which is normally picked up off the short-wave signal and re-broadcast, is suffering from sunspot activity or other disturbances.

### NORWAY SCHEDULE

Radio Norway in Oslo is using some new frequencies for the period up to

November 4. The service to Australia and New Zealand 0700-0830GMT is now on 11850kHz, which replaces 9590kHz. At the same time, the transmission is carried on 15135 and 15175kHz.

The broadcast 1100-1230GMT to Indonesia and Western Australia is now on 17800kHz (replacing 15175), while 21730 carries the same service. For the service to North America 0300-0430GMT 6180 replaces 9645, 9550 replaces 11895, and 9645kHz replaces 11860kHz.

For the transmission 0500-0630GMT, we find that 17800 replaces 17795 and 9645 replaces 11895kHz. The English transmission is heard on Sundays for the last 30 minutes of the broadcast, as well as on Mondays at 0200, 0400 and 0600GMT.

### TURKEY INCREASES POWER

The Voice of Turkey at Ankara is now using a further two 250kW transmitters and has been heard with an English transmission to Europe, the Middle East, Africa and America from 2130GMT. Four frequencies are now used to carry this English broadcast and they are 7170, 7270, 9515 and 9665kHz.

The best frequency for reception in this area is 9665kHz, which suffers only light interference from Radio Moscow on the same channel. The other three frequencies suffer from some degree of interference when the transmission commences: 7170 from the Voice of America, 7270 from Radio Poland and the Italian Radio, and 9515kHz from the Italian Radio.

The new service from Ankara is also being broadcast to South-East Asia on new frequencies. The broadcasts from 1200-1300GMT and to the Middle East from 1300-1500GMT are now on 15145kHz in place of 9665kHz. The English program is 1200-1300GMT.

### LATIN AMERICAN NEWS

**BOLIVIA:** Radio Batallon Colarados, with the call sign CP9, has been heard opening at 1100GMT on 6185kHz. Jack Buckley of Coogee, NSW also reports reception of this station at around 1130GMT. Radio Stentor, which was recently reported on 6173kHz, has returned to 6125kHz and is heard at 1100GMT. Radio Crystal has been heard

Notes from readers should be sent to Arthur Cushen, 212 Earn Street, Invercargill, NZ. All times are GMT. Add 8 hours for WAST, 10 hours for EAST and 12 hours for NZT.



# SHORTWAVE SCENE

on 5050kHz when operating all night during the Bolivian elections. This station is also announcing 6195kHz and is located in La Paz. Brian Dodgson of Melbourne, reporting in "DX Post", states that Radio Emisora Bolivia has been heard at 0930GMT on a slightly higher frequency than the Colombian station Nuevo Mundo on 4755kHz.

**CHILE:** Radio Universidad Concepcion has been heard opening at 1200GMT and the signal, on 6135kHz, is mixed with South Korea. A long news bulletin in Spanish generally follows the opening.

**CUBA:** Radio Moscow is relayed by Radio Havana Cuba at 2315GMT in English and at 2330GMT in Spanish on 7150, 7215, 7400, 7410, 9610, 11790 and 15100kHz, according to "Sweden Calling DXers".

**COLOMBIA:** Radio Mira, in Tumaco, is currently commencing transmission at 1127GMT on 6015kHz with instrumental music, followed by opening announcements and Todelar network news after 1130 in Spanish. Peter Bunn of Melbourne, reporting in "ADXN", says that this is a new sign-on time for Radio Mira, which previously opened transmission at 1100GMT.

Radio Surcolombiana at Neiva, which operates 24 hours a day on 5010kHz, has been heard at 0600GMT. At this time we heard a station announcement and this was followed by news from the Caracol Network.

**COSTA RICA:** Radio Universidad, S. Pedro Montes de Oca, which is listed on 6105kHz, has been heard by Ray Crawford of Invercargill, NZ. The station opened at 1200GMT on the new frequency of 6100kHz.

**DOMINICAN REPUBLIC:** Radio Television Dominicana, in Santo Domingo, has been observed on the new outlet of 5975kHz, with instrumental music after 1000GMT. Peter Bunn of Melbourne, reporting in "ADXN", observes that the station seems to vary its 49m channel almost nightly, using either 5975 or, alternatively, the long-established outlet of 5970kHz. Signals are good on either channel, though 5975 is blocked after 1100GMT when China opens transmission on the frequency.

**VENEZUELA:** Radio Nacional Caracas has been heard opening at 1000GMT on 6170kHz. The station suffers light interference from a Philippine signal on the same frequency.

## NEW AUSTRALIAN FREQUENCIES

Radio Australia's new schedule, effective September 3, lists some new frequencies for the broadcast from the studios in Melbourne. The new channels are: 5955kHz 1730-2030GMT;

5970 1230-2030; 11835 0645-1000; and 11855 2300-0100.

Radio Australia broadcasts around the clock in English, and has transmissions in Indonesian, Standard Chinese, Cantonese, Thai, Vietnamese, Japanese, French and Melanesian.

## JAPAN TESTS FROM SINES

Recently, Radio Japan carried out a series of tests from the transmitters of Trans Europe at Sines in Portugal and these transmissions, both of 30 minutes duration, were received in this area. Radio Japan has had difficulty in serving Europe with its transmissions for some years.

The first broadcast was from 0700-0730GMT on 9685kHz and here interference was experienced from the Armed Forces Radio and Television Service on the same frequency. The second broadcast was between 2200-2230GMT on 9670kHz, and provided much better reception in New Zealand.

## HAVANA BROADCASTS IN ENGLISH

According to the latest schedule of Radio Havana, Cuba, the broadcasts in English are on the air to Europe and South America from 2010-2140GMT on 17855 and 17750kHz. To North America there are transmissions from 0100-0800GMT in English and these are split up into several transmission times: 0100-0450 11930kHz; 0100-0600 11725kHz; 03330-0600 11760; and 0600-0800GMT 9525kHz. The address of the station is PO Box 7026, Havana, Cuba.

## VOICE OF PEACE

One of the last remaining pirate radio stations is the Voice of Peace, which has been broadcasting off the coast of Israel for some years. The station was scheduled to close down in February because a survey conducted by the Israel Broadcasting Authority showed that the pirate radio station had few listeners.

Abie Nathan, owner of the Peace Ship, made a last minute appeal for listeners to meet in a Tel Aviv square. 60,000 people turned up, advertising flooded in, and the Voice of Peace remained on the air.

So far, the station has raised more than \$2 million for worldwide charities. According to the "New Zealand DX Times," transmissions are still being heard on short-wave on 6250kHz and on medium-wave on 1538kHz.

## AUSTRIAN CHANGES

The Austrian Radio at Vienna recently made changes to some of its services, and it is expected that these will remain in force after September 3. The major change for Australian listeners is the service to this area 0700-0900GMT which includes English at 0830GMT. The frequency of 9605kHz has been used, but because of complaints of interference from Radio Morocco on 9615kHz a new frequency had to be found.

The broadcast from Vienna 0700-

0900GMT is now on 9585kHz, while from 0900-1300GMT the new frequency is 17855kHz. For the broadcast to Europe 0500-1900 and 1900-2200GMT, the first transmission remains on 6155kHz, but from 1900 it is on 5945kHz.

## LISTENING BRIEFS EUROPE

**BULGARIA:** Radio Sofia broadcasts in English to the following schedule according to the BBC Monitoring Service: from 0000-0100GMT to North America on 15330kHz; 0430-0500 to North America 11750; 1830-1900 to Africa 15310 and 17825; 1930-2000 to Great Britain and Ireland 9700 and 11720; 2030-2130 to Africa 11735, 11765 and 15310; 2130-2200 to Great Britain and Ireland on 15135 and 11750kHz.

**SWITZERLAND:** "Swiss Radio International" is to be the new slogan of the Swiss Broadcasting Corporation overseas service, according to an announcement from the station. Berne broadcasts to New Zealand and Australia in English daily 0700-0730 and 0900-0930GMT on 9560, 11780, 15305 and 21520kHz. Italian is broadcast at 0730, French at 0800 and German at 0830GMT.

## AFRICA

**SAO TOME:** Signals from Sao Tome on 4807kHz have been observed in New Zealand around 1800GMT, with announcements in Portuguese. The station has also been noted by Barry Williams of Auckland, reporting in the New Zealand DX Times and heard opening at 0530GMT with a weak signal.

**SIERRA LEONE:** Freetown has been heard on 5980kHz, having moved from 3316kHz. According to Peter Bunn, reporting in "ADXN", the station has been noted closing in English at 0002GMT. Signals have been noted on this frequency as early as 2130GMT.

**ANGOLA:** Radio Nacional Luanda now has a daily Spanish transmission for Cubans resident in Angola on 7245 and 9660kHz at 2100-2130GMT, according to Richard Ginbey reporting in "Sweden Calling DXers".

## ASIA

**NEPAL:** According to "DX Digest of India", Radio Nepal is testing on different days between 1220-1520GMT on 15195 and 17795kHz.

**PAKISTAN:** Radio Pakistan at Karachi has been noted on 15405kHz with English news at 1100GMT. This transmission was formerly on 15115kHz. The transmission time of the World Service is 0700-1100GMT, when both 15405kHz and 17665kHz are used. The news bulletin at 1100GMT in English is read at slow-speed.

Radio Pakistan has also been noted on 21730kHz by Tim McSweeney, Mount Isa, Queensland. The station was heard at 0240GMT with a news bulletin in English, and closed at 0245GMT.



# CUSTOM COMMUNICATIONS HAM RADIO SPECIALISTS




WE SELL  
**KENWOOD  
YAESU  
DRAKE  
\* ICOM  
† SWAN  
ATLAS**

\* Sydney distributor for ICOM  
† Australian agent for SWAN



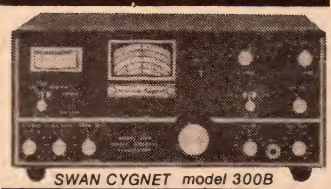RTTY SYSTEMS COMPLETE  
CONSISTS OF  
PAGE PRINTER  
TAPE PERFORATOR  
TAPE DISTRIBUTOR  
DEMULATOR  
LOOP SUPPLY



SPECIAL FEATURE  
FREQUENT HAM AUCTIONS  
PRODUCT NIGHTS  
FULLY EQUIPPED  
"DO IT YOURSELF"  
WORKSHOP



KENWOOD  
Transceiver  
RS-520S  
160 thru  
10M DG-5




KENWOOD  
599D  
Series Receiver

MAIL ORDER SERVICE  
COUNTRY ENQUIRIES  
WELCOME  
ALL LETTERS ANSWERED



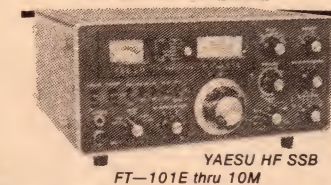USED TEST INSTRUMENTS  
LEVEL METERS  
OSCILLATORS, ETC.,  
V.T.V.M.  
MORSE, KEYS, ELECTRONIC  
KEYERS, MATCHING NETWORK  
HF AND VHF ANTENNAE



YAESU HF SSB  
FT-101E thru 10M

TOP TRADE ON USED  
HF EQUIPMENT

HAM RADIO  
SPECIALISTS

HF-VHF EQUIPMENT

RITTY UNITS

S.S.T.V.

NOVICE EQUIPMENT

ROTATORS

CB RADIO &  
ACCESSORIES

WORKSHOP

• TEST EQUIPMENT  
• Do it yourself workshop

PRODUCT TRAINING  
& ADVICE

\* WE TRADE IN AND  
AUCTION EQUIPMENT

OPEN 6 DAYS  
BANKCARD  
EASY FINANCE

# CUSTOM COMMUNICATIONS

6 ORCHARD LEIGH ST., YENNORA, N.S.W.

**681 3544** AFTER HOURS  
**674 1719**

## ELECTROCRRAFT PTY. LTD.

68 WHITING STREET, ARTARMON 2064

TELEPHONE 438 4308, 433 3266

We have the largest range of  
antenna accessories in Sydney.

(Check our prices)

TRADE AND WHOLESALE SUPPLIED

### CB EQUIPMENT — SPECIALS

**¼ WAVE SPIRAL TUNED BASE STATION AERIAL.** Omnidirectional (top view) radiation pattern with excellent ground wave and sky wave characteristics. Ideal for "point to point" and Skip communications. Sturdy plated base bracket, 4 to telescopic radials and vertical radiator. Spiral tuning stub at base for quick and easy tuning. SWR of 1.1:1 possible. Aerial comes complete with SO 239 socket. U-bolt and saddle and detailed instruction sheet. **\$29.00**

**SWR & POWER METER.** Model ME-11X is SWR & Power Meter with Directional Coupler incorporated. For SWR measurement it uses the Directional Coupler, comparing the power supplied to and reflected from antenna, and this is indicated on the SWR meter. For power detected by Directional Coupler and its frequency range is determined by the figure of Variable Resistor which is for sensitivity adjustment. Specifications: maximum handling power 100W — SWR indication 1:1 to 3:1 — frequency range 3.5 to 150 MHz. **\$16.20.**

**BELLING & LEE HELICAL WHIP** — Model CB 27/GM/T — specially designed to provide maximum performance with reduced length. Helically wound on a resilient fibreglass core 76cm in length with complete base, 3.6m of cable and connector. **\$18.00** — below cost!

## ELECTROPHONE

### Model CB550 AM/ SSB RADIO



★ Built-in S.W.R. & Power

Meter for perfect aerial tuning

★ L.E.D. Digital Channel Readout

★ Special controls for R.F. Gain &  
Noise Blanking

★ Long range reception & transmission

Max Legal Power  
4 Watts A.M.  
12 Watts S.S.B.

|                                                                                                                                                                                                          |         |
|----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---------|
| CB 512 Am CB Receivers Electrophone                                                                                                                                                                      | 7.152   |
| CB 530 AM                                                                                                                                                                                                | 84.81   |
| CB 550 SSB                                                                                                                                                                                               | 197.10  |
| CB 590 SSB Base Station                                                                                                                                                                                  | 248.69  |
| President Grant Receivers SSB 2 only                                                                                                                                                                     |         |
| 23 Channel with 8 Ch Mod Kit                                                                                                                                                                             | 229.00  |
| 1 slightly marked                                                                                                                                                                                        | 220.00  |
| CB UHF Beam 15 el 15 dB Gain 467 to 477 Mz                                                                                                                                                               | 31.00   |
| Rotators C.D.E. AR22XL Fully approved                                                                                                                                                                    | 124.41  |
| <b>BUILD YOUR OWN CB POWER SUPPLY.</b> Ferguson transformers 240V to 18V, 60VA. 3.3A \$8.50. Metal boxes, L2000mm, W135mm, H70mm, Black vinyl covered. Holes drilled on chassis for transformers \$3.50. |         |
| Regulators complete with circuit GH78 CB 13.8v 2.2A                                                                                                                                                      | 2.94    |
| <b>FM ANTENNA'S</b>                                                                                                                                                                                      |         |
| Channelmaster 5 El H. Gain                                                                                                                                                                               | 19.68   |
| Hills FM1 Local                                                                                                                                                                                          | 9.35    |
| Hills 353 3 el Met:                                                                                                                                                                                      | 14.23   |
| Matchmaster FMG/2 Semi fringe                                                                                                                                                                            | 18.30   |
| Matchmaster FMG/6 Outer fringe                                                                                                                                                                           | 40.93   |
| <b>TV ANTENNA'S</b>                                                                                                                                                                                      |         |
| Hills outer fringe CA.16 phase array                                                                                                                                                                     | \$45.94 |
| Hills 215 (Australia's best selling high gain 8 el antenna at a new low price)                                                                                                                           | 25.20   |
| Hills EFC.3 (The best of the colour 75 ohm antennas very high gain, good anti-ghosting)                                                                                                                  | 62.41   |
| Channelmaster 3111A 300-75ohm. (Best metropolitan Anti ghosting antenna)                                                                                                                                 | 41.98   |
| Channelmaster 3100 300-75 ohm local anti ghosting                                                                                                                                                        | 27.96   |
| Belling Lee plugs                                                                                                                                                                                        | .80c    |
| Belling Lee Coaxial wall sockets                                                                                                                                                                         | 1.75    |
| R.F. Amplifiers. Mast-head & Distribution for FM & TV from                                                                                                                                               |         |
| 16dB Ecraft                                                                                                                                                                                              | 45.00   |
| 25dB Ecraft                                                                                                                                                                                              | 53.55   |
| Hills MH 1 Masthead 300 ohms                                                                                                                                                                             | 61.00   |

Please enclose min. \$2 postage with all orders.

WE ARE THE EXPERTS — 30 YEARS  
IN THE ANTENNA BUSINESS





## Charpentier — Louise: new version of a lovely opera

**CHARPENTIER — Louise. Complete Opera.** Ileana Cotrubas (Louise); Plácido Domingo (Julien); Jane Berbie (Mother); Gabriel Bacquier (Father) and countless other minor characters with the New Philharmonia Orchestra and Ambrosian Opera Chorus conducted by George Pretre. CBS Stereo with libretto in English/French and German. S3BR 220614. (Three Boxed Discs).

I never cease to wonder why, outside France, Charpentier's *Louise* has proved such a poor stayer in the opera stakes. It is tuneful in a unique way, for the most part made up of short phrases almost in the Wagnerian leit motif manner — though that is its only likeness to the German's works — and has only one aria, the evergreen and delicious "Depuis le Jour". The composer, by the way, wrote his own first class libretto.

*Louise* was one of the first, if not the very first, of the verismo operas — that is, an opera in a modern setting with the players wearing street clothes and behaving like normal people. There are no gods and goddesses, no dukes and duchesses, no period costuming. Instead *Louise* gives a perfect picture of life in a Parisian working-class family but without the often beautiful tarting up of the atmospheres as in Puccini's *La Bohème*, great work though the latter is.

The period of *Louise* is Paris during *La Belle Époque*. Despite its very large cast it has only five chief characters — a painter (Julien) in love with a young dressmaker who lives opposite, her disapproving "respectable" father and mother, and last but by no means least, the city of Paris.

Frustrated at home the girl runs away to live with her artist lover, and is ecstatically happy with him until she is tricked into returning home by her harsh mother. There she is watched like a prisoner, even by her doting father, until she can stand it no longer and again runs away, this time for good. The final scene is as dramatic as any I can recall in opera and the end of the first act one of the most touching.

The whole is coloured by typical Parisian scenes and characters common at the beginning of this century —

clochards, playboys, street sweepers, hawkers, workgirls and, since it is set for much of the time in Montmartre, feckless but exuberant near-artists. The great Mahler himself regarded the opera as a masterpiece and made a personal friend of the composer, inviting him often to stay with his family. But Frau Mahler was not so keen on his visits, as he was given to spitting on the floor.

It is sparkingly scored for large orchestra and the characters are all presented "in the round". Yet with all this going for it a performance outside Paris is a rare event indeed. This makes the new recording all the more welcome, the more so since it is splendidly sung, well acted vocally, and the whole well held together by the conductor, Georges Pretre. Although the singers are nearly all continental the orchestra is English, the New Philharmonia, and so is the chorus, the Ambrosia Opera Chorus.

I have only one quibble with the production — the voices are often

recorded a little too forward so that the orchestra, which plays such an important role in the work, is sometimes drowned out. I did improve this to an appreciable extent by raising the volume and sitting an extra long way away from the speakers. But I readily forgive its occasional blemishes in gratitude for a new version of this lovely opera.

So far as I know this is only the second time it has been recorded. Philips put out a recording which was far from satisfactory right at the beginning of the LP period. In that version you could hardly hear the orchestra at all.

Charpentier caught to perfection the Paris when it was truly the City of Light, without its present day skyscrapers, traffic snarls, Americanisations and other such degradations. Indeed as you progress through the opera you will realise that the chief character of *Louise* is Paris.

If you enjoy French music, I urge you to buy this record set.

## Isaac Stern: "fastidious musicianship"

**SAINT-SAENS — Violin Concerto No. 3. CHAUSSON — Poème for Violin and Orchestra. FAURE — Berceuse, Op. 16.** CBS Stereo Cassette RC887.

French music of roughly a generation earlier than Charpentier's opera, reviewed above, is on this cassette of a violin recital by Isaac Stern. The major work is the Saint-Saens concerto though I enjoyed the other two works more.

Stern plays the concerto with immense authority. He treats this not very weighty work with complete seriousness and without the slightest hint of condescension. His playing of it has the effect of increasing its significance, which I consider no slight feat.

The work has all Saint-Saens' characteristics — immaculate workmanship and tunefulness of the most easily appreciated kind. Stern's style is always masterful, even in moments of the most extreme delicacy. Even if he does sound a little too asser-

tive in the matter of balance with the orchestra in the first movement, he never completely drowns out the orchestra. I think the work would sound commonplace nowadays under any but this type of treatment.

The *Finale* goes with real boyish bounce — and Stern is far from boyhood nowadays. While there is never a jarring bar throughout the entire work there is very little that could be described as exciting anywhere if one excepts Stern's brilliant technique and fastidious musicianship. Daniel Barenboim and the Orchestra de Paris supply a completely satisfactory accompaniment and the sound is first class.

In Chausson's *Poème*, Stern changes his style to a fitting mood of sensitive romanticism. The smoothness of his phrasing demonstrates that the long French legato has no mysteries for him. He never pulls the music about with exaggerated rubatos or use a tone like the tremulant stop on a cinema organ.

Yet his reading is never short of pas-



sion of the most refined kind. He plays Faure's delectable Berceuse with exactly the simplicity that robs it of none of its innocence. And I might add that this is not the innocence of the Christopher Robin kind but that of a supreme master of his art.

☆ ☆ ☆

**LISZT — Annees de Pelerinage. Second year, Italy. Played by Alfred Brendel (piano). Philips Stereo Cassette 7300 404. (Also on disc.)**

Here is another romantic performer but this time in the present day manner. This cassette gave me constant delight, not only in Brendel's playing but also in the beautiful reproduction of the sound by the cassette engineer. The fidelity of the piano tone, the audibility of Brendel's subtlest variations of sonorities, the complete lack of background noise, and perhaps above all, Brendel's playing makes this an enjoyable listening session.

Till I heard this cassette, Arrau has always been my favourite Liszt player. Now I'm not so sure. Let's say I've found in Brendel another to give me equal pleasure.

Liszt's Second Year of Pilgrimages, as he called them, takes in Italy. (The first was about Switzerland.) It is not the country he describes but his response to some of the works of art found there. The items were written at different times over a fairly long period and then revised and issued in the form we have here some years later.

So radical were some of the revisions that many musicians, pianists among them, will be surprised to learn that the three beautiful Petrarch Sonnets were originally composed for high voice.

Until we reach the last of the seven items in this recital there is no showy virtuosity about Brendel's interpretation. If it were possible to prove by comparison I think that this is the way Liszt would have played them himself. Many of them demonstrate the astonishing originality often found in some of Liszt's works. There is one passage at the end of the first item, "Sposalizio", that might well have been written by Debussy a couple of generations later.

Moreover, Brendel plays it as the later composer would have liked to hear it; to quote him "as if the piano had no hammers." Brendel uses this same exquisite touch in others on this cassette with ravishing effect. And you don't even have to go past this first item to appreciate Brendel's superb control in the building of a huge climax.

The second item, "The Thinker", has nothing to do with the great statue by Rodin. Instead, the subject is Michelangelo's brooding statue on the tomb of Guiliamo de Medici in Florence. To quote from Humphrey Searle's perceptive and all too brief annotations that accompany the cassette: "Liszt's music catches the statue's at-

titude of brooding melancholy, and at the end the music dies away with a chromatic descending passage which anticipates Wagner's Tristan of 20 years later."

But then, Wagner's occasional pinching from Liszt has been notorious for years. This item is a study in sombre beauty, its sadness caught to perfection by composer and executant alike.

No. 3, "Canzonetta del Salvatore Rosa," is based on a song written by a Byronic character who caught Liszt's fancy. It is a fairly straightforward setting of the song itself, but demonstrates Brendel's sense of a beautiful smooth melodic line.

Then come the three Petrarch Sonnets. Petrarch was, of course, a famous poet of another age and the combination of Liszt and Brendel brings out all the music's musing poetry of the first and the more agitated mood of the second. The third is again in quieter mood, and includes a marvellously played series of short, almost staccato chords.

The last work, headed "After Reading Dante", and sub-titled "Fantasia quasi Sonata", is perhaps better known as the Dante Sonata and is no stranger to present day concert goers. It is, as one might guess, more overtly dramatic than any of the preceding pieces and demands a full share of the player's virtuosity.

The whole production is another example of the spectacular improvements Philips have made in the cassette recording technique. I advise both Lisztians and even non-Lisztians not to miss it.

☆ ☆ ☆

**THE ART OF MISCHA ELMAN (violinist) — an album of his favourite pieces by various composers. Vanguard Stereo Disc VSD 71173. (Also on cassette).**

I don't know the difference between the ages of Stern and Elman, but there is a generation's difference in their styles. In Elman's recital there is only one piece that is included in Stern's — Faure's Berceuse — and nothing could demonstrate better the different temperaments of the two players. For while Stern's interpretation is strictly though elegantly classical, Elman's is as romantic as you can get. Elman exploits his golden tone, sensuously muted, in this unaffected modest little piece. And he continues in this mood throughout the recital of what could be regarded as a collection of little encore pieces.

Kreisler called his contribution "La Precieuse" (in the style of F Couperin), but Elman's treatment of it is far from what I have always considered to be Couperin le Grand's style.

Technically, Elman can play very fast, but even at that game I'd back Heifetz or Stern at 100 to 1 on. And while speaking of technique, Elman's harmonics at the end of the Espejo work are quite painful to listen to. It is strange to find in a recital of this kind a composition by Australian composer Arthur Benjamin — "From San Domingo". It is not very impressive and sounds to me like a very early work or one commissioned to be finished in a hurry.

Debussy's "La Plus que Lente," also played muted (con sordino), is full of Saccharine phrasing and distortions. And so it goes throughout the recital of 10 items, all played in Elman's swooning style that might well have provided, with the lights dimmed, an invaluable aid to dumb seducers in a less sophisticated age. He is ably accompanied by Joseph Seiger.

Although just issued in Australia the disc was recorded in 1966 and is also offered on cassette.

## RADIO DESPATCH SERVICE

### THE SPECIALIST STORE

869 GEORGE STREET, SYDNEY, NSW 2000 (near Harris Street),  
PHONES 211 0816, 211 0191

Buy the BEST


#### TEXAS CALCULATORS

The Best: TI-59 a card programmable Calculator — 960 program steps or up to 100 memories integrated with the master library module delivering up to 5000 steps. The TI-59 is nearly a computer in itself Blank magnetic cards are available to record your own program whenever you like. Price \$277.00. Students with Tax Exemption \$249.00. Please note the PC100A Thermal Printer works with the TI-59. Best quality available \$236.00.  
Slide Rule Calculator for students TI-30 \$20.85.
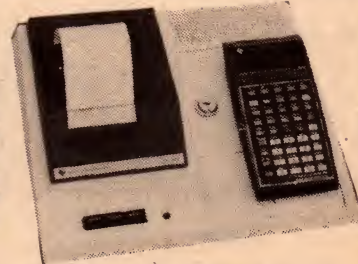
#### C90 LOW NOISE HITACHI CASSETTES



C60 LN ..\$1.72  
C90 LN ....\$2.18  
C120 LN ...\$2.88




TI programmable 29 with PC-100A printer.

Open: Mon-Fri 8.00 am-5.30 pm.  
Thursday late night shopping until 8.30 pm.  
Saturday 8.00 am-11.45 am.



# SPECIAL PURCHASES

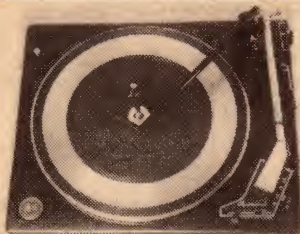

## GARRARD Model SL65B

RECORD CHANGER AT LESS THAN 1/3 LIST PRICE —

(RECOMMENDED RETAIL PRICE \$110.00)

**\$35.00**

SUPPLIED WITH SHURE M75-6s MAGNETIC CARTRIDGE AND DIAMOND STYLUS.

Also available with ceramic cartridge and \$30  
All changers new in original cartons

Send S.A.E. for full specifications

A precision automatic and manual record-playing unit fitted with Garrard Synchro-Lab4 pole shielded motor to provide constant speed conditions for the 10½ inch aluminium turntable.

The low resonance tubular pickup arm is counter-balanced with a resiliently mounted weight to permit light sensitive tracking, and the slide-in cartridge carrier enables styles inspection and the interchange or replacement of cartridges to be carried out simply and quickly.

Fine stylus force adjustment and bias compensation are both calibrated for accurately setting the arm to give optimum playing conditions for the chosen cartridge.

The fluid-damped level-type cue and pause control ensures gentle lowering of the pickup to the surface of the record.

A short spindle is supplied for single record play records.

Precision engineering is reflected in the styling of the SL65B, which is elegantly finished in black and silver.

**POST AND PACKING EXTRA** Send SAE for details  
NSW \$3.75 Vic., SA & Qld \$5.75  
Tas., WA & NT \$7.00 (Reg. post \$2.00 extra)

BASE & PERSPEX COVER FOR GARRARD OR B.S.R. UNITS \$29.50 EXTRA PLUS FREIGHT.

## NEW STANDARD PM-403 W-24 WATT STEREO AMPLIFIER AT LESS THAN TRADE PRICE

MANUFACTURED BY STANDARD RADIO CORPORATION — A MAJOR JAPANESE ELECTRONIC MANUFACTURER.



**\$59.00**

plus post & packing

NSW \$3.50

VIC., QLD, SA \$5.00

WA, TAS. \$6.50

(Reg. post \$2.00 extra)

### SPECIFICATIONS:

Continuous power 12 watts R.M.S. per channel at 8ohms. (24 watts) at 1KHz

Harmonic distortion at 1KHz 0.5% to 10 watts

Power bandwidth 20-20,000Hz at 8ohms

Frequency response 15-40,000Hz

Signal to noise ratio Aux. 70db Mag. 60db.

Bass control ±10db at 100Hz Treble control ±10db at 10,000Hz

Input sensitivity Mag. 2.5mv, Cer. 150mv. Aux 100mv, Tape 500mv.

● TAPE MONITOR SWITCH ● LOUDNESS CONTROL ● SPEAKER SELECTOR SWITCH

● HEADPHONE JACK ● SEPARATE BASS & TREBLE CONTROLS ● BALANCE CONTROL

Dimensions 13½" by 8" by 4" high SUPPLIED IN WALNUT FINISHED CABINET WITH OPERATION INSTRUCTIONS & SCHEMATIC DIAGRAM

READ REVIEW ON THE STANDARD PM-403W AMPLIFIER IN NOV. 77 ISSUE OF E.A.

Send SAE for full specifications.

### SPECIAL PACKAGE OFFER

STANDARD PM-403W AMPLIFIER — TWO GOODMAN-FOSTER SPEAKER KITS AND GARRARD SL65B CHANGER WITH SHURE MAGNETIC CARTRIDGE \$155.00.

(Cabinets for speakers and changer not supplied.) Freight and packing extra per rail or air freight.

### NEW GOODMAN-FOSTER 3-WAY 4-SPEAKER HI-FI SYSTEM

**\$39.00** PER KIT

Frequency Range 45 to 22,000 cycles. Power rating 25 watts. RMS Imp-8ohms. Supplied in kit form (less cabinet) each kit comprises two English Goodman 8" bass units. Foster 5" mid range. Foster 1" dome tweeter crossover components Ocodensers and inductance innabond, speaker fabric and plans of cabinet. Cabinet dimensions 23" x 13" x 10". CABINETS AVAILABLE.

Post & packing extra: NSW \$2.70; VIC. SA, QLD, \$4.70; WA \$5.70.  
(REGISTERED POST \$2.00 EXTRA IF REQUIRED) cabinets available.

### NEW MAGNAVOX — MV50 — 50 WATT SPEAKER SYSTEMS

As featured in Feb. 1976 Issue of Electronics Today

Complete kit of parts (less cabinet) comprising Magnavox 10-40 10" bass unit. 625 mid range 6" two XJ3 dome tweeters, crossover network, innabond, speaker silk and plans of cabinet.

**\$82.00** freight extra per rail or air freight.  
PER KIT Cabinet available.  
830 System also available.

### NEW STANDARD B.S.R. C123 RECORD CHANGERS

**\$25.00** Incl. spare cartridge and stylus **LESS THAN 1/2 LIST PRICE**

Fully automatic turntable plays up to six records automatically and single records automatically or manually as required. 11" turntable. Bias compensation. Cue & pause control. Record speeds 33 1/3, 45 and 78

rev./min. Finished in black with silver trim. Player and changer spindles supplied. Fitted with ceramic cartridge. Post & packing extra. NSW \$2.70; Vic., Qld., SA \$3.70; WA \$4.70 (registered post \$2 extra if required).

Spare cartridge and stylus for above \$3.50 (list price \$10.00).

### B.S.R. STEREO PLAYER MODEL

LESS THAN 1/2 LIST PRICE

**P-128B \$39.00 WITH SHURE M75CS MAGNETIC CARTRIDGE**

PROFESSIONAL SERIES



Auto or manual operation. 3 speed. 11½" diecast turntable 4 pole shielded motor. Slide-in cartridge carrier. Counter-balanced pick-up arm. Fine stylus force adjustment & bias compensation. Damped lever type cue & pause control. Diamond styles. Post and Packing extra.


NSW \$2.75. VIC. SA & QLD \$4.75: Tas. WA & NT \$6.00 (reg. post \$2.00 extra)

### AWA 8in BASS SPEAKER

Type 8wac impedance 8 ohm power handling 20 watts RMS.  
\$9.50. P and P NSW \$2.00, Interstate \$2.50.
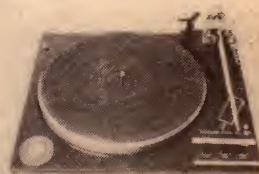
### GARRARD M.82 \$60.00 TRANSCRIPTION CHANGER

Supplied with Pickering Cartridge with Diamond Stylus. Post & Packing (Reg. Post \$2.00 extra). NSW \$3.60. Vic., SA, Qld \$4.74. Tas. \$5.50. WA & NT \$5.80.



## CLASSIC RADIO

245 PARRAMATTA RD, HABERFIELD 2045. PHONES 798-7145, 798-6507.





# Lighter Side

Reviews of other recordings

## Devotional Records

**FRED FIELD And Friends. Stereo, Maranatha HS-031. (From S. John Bacon Pty Ltd, (PO Box 345) 12-13 Windsor Ave, Mt Waverley, 3149.)**

Fred Field, pictured as a young man with a wife and young son, must have been a very busy person during the production of this album in 1976. He wrote most of the lyrics and most of the music, did most of the vocals and took a turn on guitar, fiddle, mandolin, banjo and piano — sometimes on the same tracks, and presumably with the aid of multi-recording.

The lyrics are fringe Gospel with environmental and sociological overtones, and are set out in full on an inner sheet: Warms Away The Coldest Night — The Last Train To Heaven — Falling — Building A House — He Lives — Good Ol' California — Suffer the Little Ones — Country Life — That Morning — Home.

The Music varies widely from rock, through C & W to touches of Hawaiian, but all of it performed by the young for the young. If you like the very modern Gospel idiom, Fred Field could well gain you as yet another friend; if you don't, then look elsewhere. (W.N.W.).

☆ ☆ ☆

**MESSIAH. George Frederick Handel. The Choirs of the Hood College and the US Naval Academy, conducted by John Talley. Stereo, Richardson, RRS-2. (From M. R. Acoustics, PO Box 110, Albion, Qld. 4010.)**

Recorded by Charles A. Richardson in 1976, this is one of a series of albums that aims to preserve, as closely as possible, the character and acoustics of the original performance. While still mastered on tape, it involves a single special microphone and a minimum of console manipulation.

The result is very clean sound, wide dynamic range, and choruses with organ and orchestra that would seldom be equalled in weight and clarity. And, if you have the facilities, a spot of 4-channel ambience will envelop you in the massive sound of the "Hallelujah Chorus". Thrilling indeed!



But, against this, some of the solo work sounds unduly remote, perhaps because, in a sound-only re-creation, the visual is not there to reinforce the audio image. Could not this vital difference be a fundamental subjective gap in the purist argument for a single microphone? Add to it a sprinkling of incidental and audience noises and you have the basis for a counter-argument favouring additional closer mikes, at least for the solos.

Musically, the performance covers what the jacket notes describe as the "Christmas section" of the Messiah:

## Instrumental, Vocal and Humour

**L'ENFANT ROI. FRANCK POURCEL And His Grand Orchestra World Record Club WRC R 03709**

Franck Pourcel's Grand Orchestra is certainly well named. As a group of experienced musicians, they produce a sound that is very pleasing, with renditions of twelve mainly modern tunes: L'Enfant Roi — Mamy Blue — Don't Let It Die — "Opus 35" — We Shall Dance — Io E Te — Jesus Christ SuperStar — Venise Va Mourir — Charlie — Comme Juliette Et Romeo — The Fool — Butterfly.

The sound quality and exploitation of the stereo image is superb, putting the record into the "demo disc" class without a doubt. But it would also be ideal for a quiet evening's relaxation or for that special dinner party. (N.J.M.)

recitatives, plus "And the Glory of the Lord", "For Unto Us A Child" Pastoral Symphony, "Glory To God", "His Yoke Is Easy" and "Hallelujah".

When it comes to "Messiah" this Richardson recording has a lot of competition, particularly in terms of the performance itself. But its claim to attention lies in the "purist" approach to the recording. (W.N.W.)

☆ ☆ ☆

**SCHWEITZER PLAYS BACH. Mono, World Record Club Retrospect series. WRC-3178.**

For anyone at all interested in the late Albert Schweitzer as a person, or as an authority and exponent on the works of J. S. Bach, this record should commend itself automatically. Compiled from the EMI archives by Bryan Crimp, it contains eight tracks as under:

Side 1: Toccata and Fugue in D Minor, BWV 565; Prelude and Fugue in C Major, BWV 545; Fantasia and Fugue in G Minor, BWV 542. These were recorded during 1935 at the organ of All Hallows Church, Barking-by-the-Tower, London.

Side 2, Choral Preludes: Jesus Christus, Unser Heiland; O Mensch Bewein Dein Sunde Gross; Christ Lag In Todesbanden; Liebster Jesu, Wir Sind Hier; Prelude and Fugue in E Minor. These were recorded in 1936 at the organ of Ste Aurelie, Strasbourg.

Side 1 is the better of the groups, with a clean though somewhat dated sound. Side 2 lacks the clarity and definition but not to the extent that will prevent you from appreciating the playing of the famous organist.

The cover carries a portrait of Schweitzer at the console (he would have been 60 in 1935), while there are biographical notes on the back. Retrospect, indeed. (W.N.W.)

**FRANCK POURCEL. SHE'S A LADY. World Record Club WRC R 03317**

Fourteen modern hits from such pens as George Harrison, Paul Anka, Cat Stevens and Bert Bacharach, get the big orchestra treatment from Franck Pourcel and his Grand Orchestra in this very enjoyable album. Originally from the Columbia list, it is released here by the World Record Club.

The Titles are: My Sweet Lord — If You Could Read My Mind — She's A Lady — For All We Know — Sad Lisa — To Sir With Love — Let It Be Me — Love Story — Close To You — Lara's Theme — Je T'Aime Moi Non Plus — I'll Never Fall In Love Again — Theme From Borisalino — Raindrops Keep Falling on My Head.

It is interesting the difference such treatment makes to tunes that one hears ad nauseum on radio in their pop form. (N.J.M.)

Reviews in this section are by Neville Williams (W.N.W.), Jamieson Rowe (J.R.), Leo Simpson (L.D.S.), Norman Marks (N.J.M.), David Edwards (D.W.E.), Greg Swain (G.S.), and Danny Hooper (D.H.).



## THE LIGHTER SIDE — continued

### SERENADE. RON GOODWIN AND HIS ORCHESTRA World Record Club WRC S/2459

Ron Goodwin's big British orchestra does a splendid job on twelve "serenade" type numbers on this Parlophone recording released by World Record Club, with such titles as: Sunrise Serenade — Theme from "Romanoff & Juliet" — Elizabethan Serenade — London Serenade — Clair de Lune — March from "Serenade For Strings" — India — Puppet Serenade — Elizabeth & Essex Love Theme — Serenade to Double Scotch.

This is music in the tradition of Mantovani and Pourcel and ideal for the easy listening situation. The overall quality is excellent. (N.J.M.)

World Record Club recordings reviewed in these columns can be obtained only through the Club, membership of which involves purchasing not less than one record per year. For details: World Record Club Pty Ltd, 605 Camberwell Road, Hartwell 3124. Tel. (03) 29-3636.

### HAPPY HOFBRAUHAUS. The Jo Ment Orchestra. Stereo, World Record Club W.R.C. R-04250.

If you have ever responded to the happy communal sound of hofbrauhaus or a variety of other central European situations, here's your chance to re-awaken the experience with a generous album of orchestra, chorus and audience, unbroken except for the break between sides. There are no separate tracks as such.

The numbers are listed but don't expect to repeat them; the titles are all in German and there's twenty-eight of them, all told! The two lonely English titles are "Beer Barrel Polka" and "Clarinet Polka".

An Ariola recording, released in Australia through the W.R.C., the quality is notably clean and relaxed with good balance and wide stereo separation. But, of course, these qualities will be wasted on you, if you don't like the "happy hofbrauhaus" kind of sound. (W.N.W.)

☆ ☆ ☆

### BODY LOVE, Klaus Schulze. Island L 36491 Festival release.

This is one of those records that is hard to define. The first side consists of one track and the second of two only, of synthesizer music written as additional material for a movie of the same name. It tends to grow on you, something like Ravel's Bolero. The tracks are: Nowhere Now Here — Stardancer — Moogetique.

The cover one would tend to hide from sensitive eyes, with its naked

ladies cavorting through uncomfortable poses. There is a fair amount of rumble in the recording but, apart from that, the quality is okay. (N.J.M.)

☆ ☆ ☆

### LOVE'S UPS AND DOWNS. Barbara Mandrell. ABC Dot stereo DO 2098. Distributed by RCA Ltd.

Barbara Mandrell is a C & W artist who can belt out the numbers in best Nashville style but without the exaggerated nasality that has become associated with this idiom. This latter feature will make Barbara acceptable to a wider audience. The instrumental backing is good with a strong rhythm section. Recording quality is good so it adds up to enjoyable listening.

There are ten tracks in all: Your Love Has Lifted Me Higher And Higher — Don't Hand Me No Hand Me Down Love — If I Were A River — The Magician — Woman To Woman — Tonight — Let The Rain Out — A Fancy Place To Cry — Walking Home In The Rain — How Long. (L.D.S.)

☆ ☆ ☆

### LOUIS ARMSTRONG At The Pasadena Civic Auditorium. GNP Crescendo L45785/6 Festival release

There is no evidence of recording dates on this double album, but Armstrong fans certainly get their money's worth with 16 of Louis' favourites: Sleepy Time Down South — Indiana — Someday — Ole Miss — Tin Roof Blues — My Bucket's Got A Hole In It — Perdido — Dardanella — How High The Moon — The Gypsy — Undecided — Blues — That's My Desire — Kokomo — Sleepy Time Down South — Didn't He Ramble.

Vocals are handled by Louis and



### AN EVENING WITH JULIE ANDREWS. Live concert recording. Stereo, RCA JPL1-1230.

Recorded live, in September 1977, in the Festival Hall at Osaka, Japan, this performance was enjoyed thoroughly by the huge audience.

And I hasten to add: it was enjoyed no less by my own family audience when I reviewed it. Perhaps it was because it had not been put together

Velma Middleton with Trummy Young Edmond Hall, Billy Kyle, Arvell Shaw, Barrett Deems and the Teddy Buckner Band. The record quality is good and captures the sounds and sensations of a live performance before a large and enthusiastic audience. One of the photos inside the cover shows Louis before a huge birthday cake with "70" on the top; perhaps it was a birthday concert. (N.J.M.)

☆ ☆ ☆

### LYNN ANDERSON CBS SBP 237044

If you like your ballads with an upbeat country flavour, you could do much worse than listen to this record, made in Nashville. The quality is really good, with a competent backing from the Lea Jane Singers, together with Janie Frick, Buddy Skipper and Lisa Silver.

They put together ten tracks: He Aint You — Desperado — The Angel In Your Arms — It's Your Love That Keeps Me Going — My World Begins And Ends With You — I Love What Love Is Doing To Me — We Got Love — Right Time Of The Night — Sunshine Man — Will I Ever Hear Those Church Bells Ring.

If you become bored with the record, you can get to work on the sleeve with a pair of scissors as it is printed in the form of paper doll cut-outs of Lynn Anderson, complete with horse and four changes of costume! (NJM)

☆ ☆ ☆

### SHIRLEY BASSEY, YESTERDAYS. United Artists L36516. Festival Release.

Shirley Bassey fans get their money's worth in this album, no doubt released to coincide with her visit to this country.

There are twelve titles on the disc, all old favourites: My Melancholy Baby —

from multiple takes but flowed, rather, as an unbroken display of the Julie Andrews talent; from the sentimental and the saccharine, through stage musicals to belting jazz.

Full marks must be given also to the principal accompanists, to the "String Fantastic Orchestra" and to "Nabuo Hara with his Sharps And Flats."

Track titles are: I'll Play For You — I'm Old Fashioned — Wouldn't It Be Lovely — This Is My Beloved — Being Alive — Medley (jazz, etc) — Whistling Away In The Dark — Medley (Sound of Music, etc) — Medley (musicals) — The Sound Of Music — I'd Rather Leave While I'm In Love.

Allowing for the fact that the whole performance was recorded before a very live and a very enthusiastic audience, the sound quality is very good indeed. This is one that I can heartily recommend. (W.N.W.)



# Plessey components. The complete range. (Well almost).

## Switches

Rotary, lever key, toggle, thumb wheel, touch activated including illuminated.




## Optoelectronic devices

Including LDR's, LED's photodiodes, phototransistors, photocouplers and 7 segment, alphanumeric and cold cathode displays.


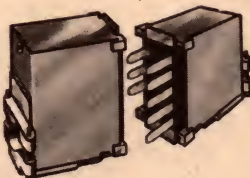
## "E" Cell

The "E" Cell device suitable for a number of applications such as repetitive timing and control, pulse counting and memory, timing, current-time integration, use-time measurement.



## Connectors

A multitude of connectors including the Multicon range consisting of 2, 4, 6, 8, 10, 12, 18, 24, and 33 pole. Also the 159 range of plugs and sockets ranging from 7 to 71 poles. Gold flash on contacts and solder tags for long term protection against tarnishing. Also the 22 range of marine and aviation connectors.

## Dry reed inserts and relays

Suitable for most switching functions the inserts have proven extreme reliability, long life, and the ability to operate in grossly unfavourable environments.




## Batteries - Saft

Nickel cadmium (rechargeable) cells and batteries, for domestic, heavy industrial, emergency power, military and aviation.



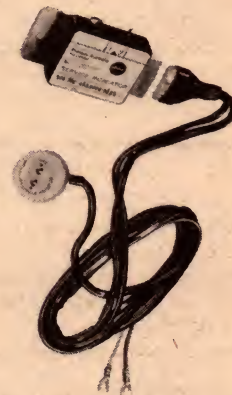
## Capacitors

Capacitors for a wide variety of applications, ranging from tantalum, chip ceramic, long-life and electrolytic.


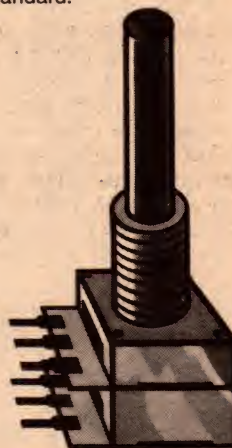
## Potentiometers

Moulded carbon track and wire-wound of both commercial and professional standard.



## Speakers - Foster & Fostex

Speakers ranging from guitar, woofers, mid range, tweeters, horns, full range and elliptical, all are available.



## Sonalerts - Mallory

Electronic audible signals providing a startling innovation in warning devices, producing a penetrating sound by purely electronic means. Circuitry is all solid state for maximum efficiency, lowest current requirements, and highest reliability.



## Lamps and indicators

Consisting of filamentary, neon and LED styles designed for all general illumination applications.



## Speaker Enclosures

One of the range of Plessey Foster and Fostex speaker enclosures.

## Service and elapsed time indicator

For trucks and other vehicles, trains and stationary engines - where ever there's a suitable power source to indicate elapsed time and when service is due.

# PLESSEY

Plessey Australia Pty. Limited  
Components Division  
Christina Road,  
Villawood NSW 2163  
Telephone 72 0133 Telex 20384  
VIC: Plessey Australia Pty. Ltd.  
North Melbourne 329 0044;



# SEMICONDUCTORS AT DISPOSALS PRICES

limited quantities only

|                  |        |
|------------------|--------|
| ASZ 16           | \$1.50 |
| BC 107           | \$0.15 |
| BC 108           | \$0.15 |
| BC 109           | \$0.15 |
| BU 208           | \$3.04 |
| BYX21L-200       | \$0.72 |
| ByX21L-200R      | \$0.72 |
| BZX79C24         | \$0.10 |
| C 103Y           | \$0.46 |
| C 122D           | \$1.36 |
| DTS 410          | \$6.00 |
| GIGI             | \$0.10 |
| LM 309K          | \$1.20 |
| LM 320T-6        | \$0.60 |
| LM 320T-12       | \$0.60 |
| LM 723CN         | \$0.62 |
| LM 741CN8        | \$0.20 |
| LM 741CH         | \$0.35 |
| MM 2102-450ns    | \$1.20 |
| MM 5017N         | \$1.50 |
| PN 3565          | \$0.09 |
| NE 555CN         | \$0.35 |
| OA 91            | \$0.04 |
| PB 40            | \$2.22 |
| SC 245D          | \$4.45 |
| TIC 44           | \$0.39 |
| TIC 126D         | \$1.26 |
| TIC 226D/sc 141D | \$0.60 |
| TIL 112          | \$0.50 |
| TIL 220          | \$0.17 |
| TIL 222          | \$0.19 |
| TIP 31A          | \$0.31 |
| TIP 32A          | \$0.33 |
| TIP 2955         | \$0.55 |
| TIP 3055         | \$0.57 |
| ua 706           | \$0.99 |
| ua 796H          | \$0.60 |
| V 413            | \$0.15 |
| VK 1048          | \$1.85 |
| 1N 914           | \$0.04 |
| 1N 4004          | \$0.08 |
| 1N 4006          | \$0.09 |
| 1N 4148          | \$0.04 |
| 1N 5060          | \$0.13 |
| 1N 5405          | \$0.19 |
| 2N 2646          | \$0.67 |
| 2N 2913          | \$1.12 |
| 2N 3055          | \$0.45 |
| 2N 3819          | \$0.28 |
| 2N 6027          | \$1.10 |
| 1702 E-ROM       | \$5.50 |
| 8 pin ic skt     | \$0.19 |
| 14 PIN ic skt    | \$0.22 |
| 16 PIN ic skt    | \$0.25 |

PRICES PLUS TAX IF APPLICABLE

Other products available on request

## ELECTRONIC and SEMICONDUCTOR DISPOSALS

Post Office Box 72, Parkville 3052

## THE LIGHTER SIDE — continued

I'm In The Mood For Love — I've Got You Under My Skin — Time After Time — Don't Get Around Much anymore — There I've Said It Again — You Made Me Love You — Over The Rainbow — Taking A Chance On Love — As Time Goes By — I Only Have Eyes For You — Love Is Here To Stay.

The sound quality is excellent. If you have seen any of the current series on ABC television, you can appreciate the exuberance the lady puts into every performance. In a word, enjoyable. (N.J.M.)

☆ ☆ ☆

**JIVE TO STAY ALIVE. Dennis Garcia. Indigo. DG/IN001. Astor release.**

This album can be introduced by Dennis Garcia:— "I am currently exploring the field of bio-feedback combining I.B.M. 5100, Roland MC 8 and Digital Synthesizer, also using a number of analogue and digital musical instruments. The purpose of my musical experimentation is to combine bio-feedback devices, computers and synthesizers to create bio-electronic music."

The result is an album somewhere between Rick Wakeman and Giorgio Moroder, possessing a disco appeal.

All of the eight tracks were composed by Dennis Garcia and recorded in Melbourne. A listen to this new bio-electronic music is recommended. (D.H.)

☆ ☆ ☆

**STAN GETZ PRESENTS, Jimmy Rowles, The Peacocks. CBS SBP 237106**

Stan Getz gets together with some of the top names in the business to provide thirteen tracks of enjoyable, restrained jazz.

Others appearing are Jimmy Rowles,

piano; Buster Williams, bass; Elvin Jones, drums; John, Judy and Michelle Hendricks and Beverly Getz on vocals. The tracks are: I'll Never Be The Same — Lester Left Town — Body And Soul — What Am I Here For — Serenade To Sweden — The Chess Players — The Peacocks — My Buddy — The Hour Of Parting — Rose Marie — This Is All I Ask — Skylark — Moaic/Would You Like To Take A Walk.

The quality is excellent, particularly that of the solo piano tracks, but I do wish they would re-work the sleeve design; it tends to be rather off-putting. (N.J.M.)

☆ ☆ ☆

**ERUPTION. Eruption. RCA. VPL1 4067.**

These five black musicians — four males and one female (namely Precious Wilson) have recorded a brilliant album. The musical arrangement and vocals are excellent.

The opening track on the album is a 6½ minute version of the smash hit single — "I Can't Stand The Rain" that erupted it's way into the National Top 3 in Australia and London.

Seven out of the ten tracks can be categorised as disco. The remaining three tracks were slower, including a brilliant version of "The Way We Were".

In summary, this album is excellent. Every song possesses very clear vocals with dynamic music accompanying the vocals. A listen to this album, if not a purchase, is a must for disco followers. (D.H.)

☆ ☆ ☆

**FORMALLY OF THE HARLETTES. Sharon Redd, Ula Hedwig, Charlotte Crossley. CBS SBP 237129.**

These three ladies have released an album which is predominantly soft-



**BLESS THIS HOUSE. Stuart Burrows (Tenor) with Eurfryn John (Piano and Organ). Stereo, World Record Club WRC-S/5313.**

Born in 1933, Welsh tenor Stuart Burrows made his operatic debut with the Welsh National Opera Company, singing Ishmael in Verdi's "Nabucco". Subsequently he filled engagements in Ireland, America, England and Europe.

In this album he is quite a different

role with a mix of songs of faith, songs from Ireland and drawing room ballads: Passing By — Oft In The Stilly Night — Thora — Macushla — Roses of Picardy — I'll Walk Beside You — Bless This House — Because — Gortnamona — I Hear You Calling Me — Maire My Girl — Trees — The Holy City — Ave Maria.

The performance is straightforward — well known solos and traditional piano accompaniments — but so capable that it can scarcely fail to appeal to anyone who would respond to the track titles. Organ is used, by the way, in "The Holy City" and "Ave Maria", again in the usual settings.

While the recording may have a slightly dated sound, it is nevertheless completely clean and as "honest" as the performance which it carries. Playing time is over 40 minutes. (W.N.W.)





**RECKLESS. The Sports Mushroom. L 36571. Festival release.**

The Sports are a Melbourne based band with a predominant sixties background but, although the roots of this band do lie truly in early rock 'n' roll rhythm and blues, they capably translate their influences into songs which possess a genuine '78 sound.

This album contains the single "Boys (What Did The Detective Say)", which received considerable air play throughout Australia. Ten out of the eleven tracks are Australian compositions. All songs contain strong guitar backings and a thumping rhythm — no wonder Sports are basically a good-time dance band.

This album is very good and, with further releases, Sports could become one of Australia's top bands. (D.H.)

**Continued from previous page . . .**

centred, with some disco. Two well-known solo performers make appearances on the album — Bette Midler and Peter Allen.

Bette Midler's contribution has fairly obviously influenced the harmony, as some of the songs on the album are very similar to her own work.

However, despite the contributions of Bette Midler and Peter Allen, the album is not more than routine. The vocals in all cases are excellent but the musical arrangements could be better.

Three out of the eight tracks on the album that do appeal are: Can't Dance — Ain't No Man Worth It — Now (Sweet Lover Man). (D.H.)

★ ★ ★

**I HAD TO FALL IN LOVE. Jean Terrel. A&M Records Inc L 36506. Festival Release.**

Jean Terrel is a former lead singer of the now legendary Supremes (she replaced Diana Ross), so it comes as no surprise to discover that this album is styled largely on the "Mowtown sound".

There are, in my opinion, two outstanding tracks on this album. These are the title track "I Had to Fall in Love," a ballad with a country & western flavour and "That's the Way Love Grows", a powerful up-tempo disco number.

The remaining tracks are rather too stylised for my liking: Don't Stop Reaching for the Top — No One Like My Baby — Rising Cost of Love — Change — How Can You (Life Without Love) — You've Been So Good For Me — No Limit.

My advice is to listen before buying. Recording quality is excellent, with negligible surface noise. (G.S.)

★ ★ ★

**EL TORO, Music Of The Bullring. IMAGE ILP-4978. Astor release.**

Featuring La Banda Taurina, this record of Spanish bullfight music, although excellent in quality, becomes boring after a few tracks, with the sameness of the content and the clockwork precision of the percussion. There are 12 titles, including: El Gato Montes — El Relicario — Paso Doble Te Quiero — Espana Cani — Mi Jaca — Pepita Greus.

My opinion of bull-fighting does not bear repeating in public so perhaps I'm biased but this is one record I would pass up. (N.J.M.)

**ARLEC**

PROUDLY ANNOUNCE

**21**  
**TODAY**

**Not in age, for our origins go back further than that, but in Transformer Voltage Taps.**

**Yes 21 Voltage Taps!**

Just think of the advantages offered by a single transformer that provides a choice of 21 different output voltages including 3 centre tapped configurations.

**FOR EXAMPLE: TRANSFORMER No. 2155A VOLTAGES AVAILABLE**

1.0, 1.2, 2.0, 2.2, 2.4, 3.1, 3.2, 3.5, 4.1, 5.1, 5.5, 6.3, 7.5, 8.5, 8.7, 9.5, 12.6, 15.0 Volts  
2.0V CT, 12.6V CT, 15V CT

**But that's not all!**


With 5 such transformers in our range there is a choice of output currents as well.

**And just in the way of a bonus!**

We are able to offer these new transformers for a price considerably lower than comparable single tapped units while still maintaining the high standards of quality for which we are renowned.

**Like to know more?**

Just ring your local Arlec branch.

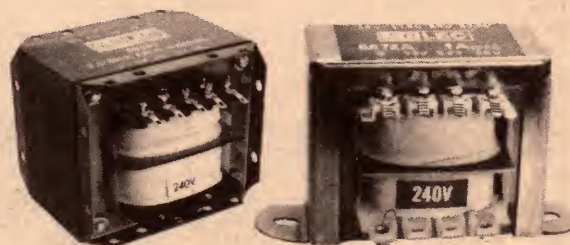

**What do we call them?**

**ARLEC  
MULTI-TAP TRANSFORMERS  
of course!**

**A+R ELECTRONICS PTY. LTD.**

A MEMBER OF THE A+R-SOANAR ELECTRONICS GROUP

30 Lexton Road, Box Hill, Vic., 3128, Australia. Telex: 32286.

SALES OFFICES PHONES  
VICTORIA: 89 0661  
N.S.W.: 78 0281  
S. AUST.: 51 6981  
QUEENSLAND: 52 5421  
W. AUST.: 81 5500



# New Products

## YAESU FRG-7000 PERFORMS WELL

A new and interesting release from the Yaesu Musen Company is the FRG-7000 communications receiver, which features digital readout of the frequency to which the receiver is tuned. It also includes a digital clock displaying local time and GMT, and doubling as an off-on equipment timer.

The FRG-7000 has obviously been developed from the well known and popular FRG-7, which was reviewed, in its latest form, in the May issue. The two receivers will presumably continue in the Yaesu range at their quite different price levels.

Physically, the FRG-7000 is a little wider at 360mm than the FRG-7, a little deeper at 295mm, but not quite so high, at 125mm. The weight is the same, at about 7kg.

Like the FRG-7, the new receiver is a triple-change superhet using the Wadley loop principle.

Incoming signals pass through an initial low-noise FET RF amplifier stage to an up-converter, which shifts them into an IF channel 1MHz wide, centred on 55MHz. They are then down-converted to a second IF amplifier, also 1MHz wide, centred on 2.5MHz. The locally generated frequencies necessary to effect these two conversions are synthesised from a crystal-locked system, with the further refinement that any residual drift tends to cancel rather than add in the end result.

In effect, this front-end serves to shift all desired incoming signals into the range 2MHz to 3MHz, substantially drift-free. This makes it relatively simple for the "back end" of the receiver to convert, amplify and demodulate the signals, using a precision single-range oscillator, a 455kHz IF channel, BFO, product detector and audio system.

The wording in the foregoing paragraphs is very similar to what we said about the FRG-7, for the simple reason that both use similar circuitry. In fact, many of the specifications are identical: modes, AM, AM with ANL, USB, LSB, CW; AM sensitivity, better than 2 $\mu$ V at S/N 10dB; SSB sensitivity, better 0.7 $\mu$ V at S/N 10dB; drift, less than  $\pm$ 500Hz at any 30 minutes after warm-up; speaker impedance 4 ohms; audio power output 2W.



There are, however, significant differences. The FRG-7000 has an extra filter in the 455kHz IF channel which halves the original bandwidth when it is switched to CW or SSB: ie. to  $\pm$ 1.5kHz at -6dB and  $\pm$ 4kHz at -50dB.

The upper frequency limit remains at just above 30MHz but the lower limit has been extended downwards to 250kHz. This has necessitated the provision of five rather than four channels on the RF preselector, with a system of color coding to minimise possible confusion.

Again, the analog scale on the main tuning dial has been replaced by a clearly visible digital readout which shows the frequency to which the receiver is tuned directly into MHz (or kHz on the low range) readable to 1kHz. In effect the "MHz selector" knob sets the figures 0 to 30, to the left of the decimal point, while the main tuning knob sets the figures to the right of the decimal point.

The other notable addition is a digital clock panel to the right of the main frequency readout. It operates from the main 1MHz crystal in the front end and remains operative while ever the receiver is plugged into an active power point — even when the remainder of the circuitry is switched

off. It shows hours to 24, minutes and seconds, and has the usual "Fast", "Slow" and "Hold" switches to permit very accurate setting of the time against standard broadcast signals.

The clock can be set to display local time and GMT, at the flick of a switch, while it can also be set to switch the receiver on and off at pre-set times. An in-built low-voltage switch, operating in conjunction with the timer, can be used to activate external relays and to switch other equipment as, for example, a tape recorder.

One other major point of difference is that the option for an external 12V supply or internal D-cell supply has been deleted, the FRG-7000 being equipped only for mains operation at a power drain of 25W; this compares with 14W for the FRG-7 — a difference of almost 2:1.

Other facilities and the method of tuning are basically the same as detail-

ed for the FRG-7 in the May issue. Perhaps because we were used to the earlier receiver, it took a little longer to react intuitively to the digital display. On the other hand, it might have helped if we had looked at the instruction book before — rather than after — putting the receiver into operation!

Sufficient to say that it didn't take long to come to terms with the new receiver and to appreciate the precision with which it could be set to specific frequencies. Nor was there any doubt about the operation of the narrow filter for the SSB and CW modes, in producing a true "single signal" effect.

Some may argue for a slower tuning rate to facilitate SSB tuning but this would have made the receiver tedious for general listening to other signals. As it was, we found no special difficulty in tuning SSB stations by means of the main knob and without resource to the "fine tune" knob similar to that fitted to the latest FRG-7s.

And, once tuned, they stayed put!

The FRG-7000 was submitted for review by Bail Electronic Services of 60 Shannon St, Box Hill North, Vic. 3129. Phone (03) 89 2213. See their advertisement in the July issue for specifications, warranty details and interstate representatives. (W.N.W.)



# Seif DM-2000 3½-digit DMM

A new arrival in the digital multimeter market is the Seif DM-2000 Digi-tester. It is a low cost 3½-digit unit, and can measure AC and DC volts, alternating and direct currents, as well as resistance. It operates from internal dry cells or an external DC supply.

The DM-2000 is mounted in a black plastic case, measuring 66 x 147 x 161mm. Weight without batteries is 650g. A four digit LED display is provided, along with 6 discrete LEDs to serve as range indicators. The display character height is 11mm.

Power supply is by four AA cells, or an external 6V/300mA DC source. No provision has been made for the use of rechargeable batteries. A pair of red and black test leads are supplied, as well as an instruction manual.

The DC voltage ranges have full scale readings of 199.9mV, 1.999V, 19.99V, 199.9V and 1999V. On this last range, however, readings are restricted to 1000V max. Input impedance is better than 100 megohms on the 199mV range, and better than 10 megohms on the higher ranges.

Rated accuracy is  $\pm 0.2\%$  of the reading  $\pm 0.1\%$  fsd and  $\pm 1$  digit. The input is protected to 1000V DC or peak AC on all ranges by a zener diode network. The resolution is 100uV on the lowest range, rising progressively to 1V on the 1000V range.

The AC voltage ranges are basically similar to the DC voltage ranges, except that on the highest range, the maximum input voltage is 700V. The bandwidth on all ranges is from 16Hz to 10kHz. Rated accuracy is slightly poorer, at  $\pm 0.6\%$  rdg,  $\pm 0.3\%$  fsd and  $\pm 1$  digit. The resolution, input impedance and overload rating are the same as on the DC ranges.

Five DC current ranges are provided, with full scale readings of 199.9uA, 1.999mA, 19.99mA, 199.9mA and 1.999A. Resolution is 100nA on the lowest range, rising to 1mA on the highest range. Overload protection is via a 2A fuse on all ranges, and the maximum voltage drop across the meter is 2V. Accuracy is stated as  $\pm 0.3\%$  rdg  $\pm 0.1\%$  fsd and  $\pm 1$  digit on the four lowest ranges, and  $\pm 0.7\%$  rdg  $\pm 0.5\%$  fsd and  $\pm 1$  digit on the 1.999A range.

The AC current ranges are similar to the DC current ranges, but with reduced accuracy. The figures quoted are  $\pm 1.2\%$  rdg,  $\pm 0.5\%$  fsd and  $\pm 1$  digit on the four lowest ranges, and  $\pm 1.5\%$  rdg,  $\pm 0.7\%$  fsd and  $\pm 1$  digit on the 1.999A range.

The five resistance ranges provided have full scale readings of 1.999k, 19.99k, 199.9k, 1.999M and 19.99M.

Resolution is 1 ohm on the lowest range, and 10k on the highest range. The test current is 0.77mA on the lowest range, falling in decade steps to 0.077uA on the highest range. Maximum applied voltage on all ranges is 0.2V.

The quoted accuracy is  $\pm 0.7\%$  rdg,  $\pm 0.1\%$  fsd and  $\pm 1$  digit. As far as we were able to tell with our limited test equipment, the unit met or exceeded all accuracy specifications.

These accuracy figures are quite impressive, and compare very well with other DMMs in the same and slightly higher price brackets.

Automatic polarity indication is provided on all DC voltage and current ranges. The display is updated every 400mS, and input overloads are indicated by blanking the three rightmost digits of the display. This is not in agreement with the instruction manual,

which states that this is done by flashing the display.

Banana jacks are used for the input connectors. A potential safety hazard exists with these, however, as they are not recessed and bare metal is available on both the sockets and the plugs for the unwary operator's fingers to find. This requires extra care on the high voltage ranges, or when measuring lower voltages or currents at a high potential with respect to ground.

To sum up, the Seif DM-2000 is a compact, versatile and solidly made DMM which offers a high order of accuracy. As such it should be suitable for both amateur and professional use.

The DM-2000 is available from Dick Smith Electronics stores and dealers, and has a recommended retail price, including tax, of \$145.00. Further enquiries should be directed to your nearest DSE store or dealer. (D.W.E.).



## Digital readout system for machine tools

The Teledyne Gurley (USA) range of electronic digital readout systems for machine tools is now available in Australia. These complete off-the-shelf systems, trade-marked "Pathfinder", can be easily retrofitted to existing machine tools such as milling machines and lathes etc.

A pre-packaged, linear, glass incremental scale and readout head is attached to the machine worktable for each axis of motion. Scale lengths up to 366cm are available, according to user requirements.

The electronic outputs from the reading head are connected to a keyboard entry and LED display unit. The position of the work table can then be instantly displayed to 0.01mm (0.0005in) using Model 8780, and to 0.002mm (0.0001in) using Model 8775.

Main features of the display unit include bright LED readouts, pushbutton operation, and advanced



microprocessor based circuitry. Leading zeros are suppressed for clarity, and a warning shows in the event of a momentary power failure.

Installed on a machine tool, the Pathfinder will: convert the machine for inch or metric operation; eliminate backlash and leadscrew errors (important for older machines which may be worn); reduce scrap by reducing operator errors; and increase productivity.

For further information contact Demco Machinery Co. Pty Ltd, PO Box M88, Sydney Mail Exchange, NSW 2012.



## NEW PRODUCTS

### Power supply kit




Latest addition to the range of educational kits developed and marketed by Selectronic Components is the 138 power supply kit. This assembles to provide a neat, strong and versatile nominal 12V/2.5A DC supply, suitable for bench or workshop use. It can be used to power CB radio transceivers and also to charge batteries. The output is fully protected and has current limiting. The kit comes complete with all parts and comprehensive instructions.

Typical output voltage is 13.8V, with 0.68% regulation up to 2.5A.

Further information from Selectronic Components Pty Ltd, 17 Barry St Bayswater Vic. 3153. Telephone (03) 729-2992.

### PCB jumpers

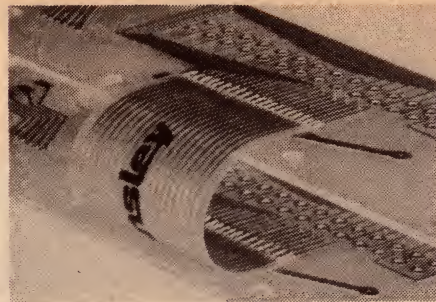

To provide closer spacing of jumper leads on PC boards, Ansley Electronics has added to its range a new series of Flex Strip jumpers on .075in centres. Primarily designed for soldering to PCB pads, the jumpers have flat wires inside the insulation for maximum flexibility, but round ends for easy soldering. The jumpers feature Teflon insulation and come in a range of standard lengths with four different pin end configurations.


Further information and samples from Ansley Electronics, Box 91 P.O. Brookvale NSW 2100. Telephone (02) 938-1713.

### Solid state "buzzers"

A range of miniature piezo ceramic audio indicators is available from Instrument Technics. Low in current drain, they offer freedom from the RFI

and other electrical interference produced by electromechanical buzzers. Typical models offer an acoustic output of 85dBA at 3M distance for 8mA drain (3-30V supply), and feature long life and a wide temperature range.

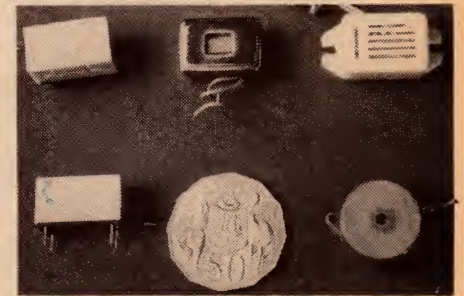Output frequency options are at either 3kHz or 500Hz nominal, both corresponding to peaks in human audio response. Various terminal con-



figurations are available. The devices are available from parts stockists, with prices starting from around \$2.

Further information is available from Instrument Technics (AI information), Box 224 P.O. Doncaster Vic. 3108. Include three 20c stamps to cover cost.

### Digital thermometer

The Digitron 1750 is a pocket-sized battery operated digital thermometer which uses Chromel-Alumel thermocouple sensors to measure over the

## ROD IRVING ELECTRONICS

499 High St, Northcote  
Vic 3070. Tel: (03) 489 8131

| TTL  | 1-9  | 10 up | TTL  | 1-9  | 10 up | TTL   | 1-9  | 10 up |
|------|------|-------|------|------|-------|-------|------|-------|
| 7400 | .25  | .23   | 7432 | .45  | .40   | 7491  | 1.00 | .95   |
| 7401 | .25  | .23   | 7437 | .50  | .45   | 7490  | .75  | .70   |
| 7402 | .25  | .23   | 7438 | .50  | .45   | 7492  | .75  | .70   |
| 7403 | .25  | .23   | 7440 | .30  | .25   | 7493  | .75  | .70   |
| 7404 | .37  | .33   | 7441 | 1.50 | 1.40  | 7496  | 1.25 | 1.20  |
| 7405 | .37  | .33   | 7442 | .70  | .65   | 7497  | 4.00 | 3.50  |
| 7406 | .80  | .75   | 7443 | 2.10 | 1.75  | 74107 | .65  | .60   |
| 7407 | .50  | .45   | 7444 | 2.10 | 1.75  | 74121 | .60  | .55   |
| 7408 | .34  | .28   | 7445 | 1.66 | 1.39  | 74123 | 1.10 | 1.05  |
| 7409 | .34  | .28   | 7446 | 1.50 | 1.40  | 74125 | 1.25 | 1.10  |
| 7410 | .30  | .25   | 7447 | 1.25 | 1.15  | 74126 | .80  | .75   |
| 7411 | .37  | .33   | 7448 | 1.25 | 1.15  | 74132 | 1.75 | 1.65  |
| 7412 | .30  | .25   | 7450 | .35  | .32   | 74137 | 2.10 | 2.00  |
| 7413 | .54  | .47   | 7451 | .35  | .32   | 74141 | 1.35 | 1.30  |
| 7414 | 1.03 | .95   | 7454 | .30  | .25   | 74145 | 2.00 | 1.80  |
| 7416 | .60  | .55   | 7470 | .65  | .60   | 74150 | 1.80 | 1.70  |
| 7417 | .60  | .55   | 7472 | .45  | .40   | 74153 | 1.10 | 1.00  |
| 7420 | .30  | .25   | 7473 | .60  | .55   | 74154 | 1.70 | 1.50  |
| 7421 | .30  | .25   | 7474 | .65  | .60   | 74155 | 1.50 | 1.40  |
| 7423 | .53  | .45   | 7475 | .65  | .60   | 74156 | 2.10 | 1.90  |
| 7425 | .53  | .45   | 7480 | 1.25 | 1.20  | 74162 | 2.70 | 2.50  |
| 7426 | .45  | .40   | 7482 | 1.65 | 1.55  | 74163 | 1.90 | 1.70  |
| 7427 | .45  | .40   | 7485 | 1.45 | 1.35  | 74165 | 2.30 | 2.00  |
| 7430 | .30  | .25   | 7486 | .65  | .60   | 74170 | 4.00 | 3.70  |

| CMOS | 1-9  | 10 up | CMOS | 1-9  | 10 up | CMOS | 1-9  | 10 up |
|------|------|-------|------|------|-------|------|------|-------|
| 4001 | .25  | .23   | 4023 | .25  | .23   | 4052 | 1.20 | 1.10  |
| 4002 | .25  | .23   | 4024 | .90  | .85   | 4053 | 1.20 | 1.10  |
| 4006 | 1.40 | 1.30  | 4025 | .40  | .35   | 4066 | .90  | .85   |
| 4007 | .25  | .23   | 4027 | .80  | .75   | 4068 | .40  | .38   |
| 4008 | 1.25 | 1.20  | 4028 | 1.25 | 1.20  | 4069 | .35  | .30   |
| 4011 | .25  | .23   | 4029 | 1.90 | 1.80  | 4070 | .40  | .35   |
| 4012 | .25  | .23   | 4032 | 1.00 | .90   | 4072 | .40  | .35   |
| 4014 | 1.35 | 1.25  | 4033 | 1.00 | .95   | 4078 | .40  | .35   |
| 4015 | 1.20 | 1.10  | 4034 | 5.40 | 4.90  | 4086 | 1.40 | 1.30  |
| 4016 | .50  | .48   | 4035 | 2.10 | 1.90  | 4510 | 1.50 | 1.45  |
| 4017 | 1.40 | 1.35  | 4040 | 1.30 | 1.20  | 4511 | 1.50 | 1.45  |
| 4018 | 1.40 | 1.35  | 4042 | 1.25 | 1.20  | 4518 | 1.50 | 1.45  |
| 4019 | .75  | .70   | 4043 | 1.50 | 1.45  | 4520 | 1.45 | 1.40  |
| 4020 | 1.60 | 1.50  | 4049 | .60  | .55   | 4523 | 1.45 | 1.35  |
| 4021 | 1.40 | 1.30  | 4050 | .60  | .55   | 4528 | 1.20 | 1.10  |
| 4022 | 1.60 | 1.50  | 4051 | 1.20 | 1.10  | 4553 | 7.50 | 7.20  |
|      |      |       |      |      |       | 4026 | 2.10 | 2.00  |

### REGULATORS

|            |                |            |      |       |        |      |            |        |
|------------|----------------|------------|------|-------|--------|------|------------|--------|
| 7805       | 5v1A           | \$1.30     | 7815 | 15v1A | \$1.30 | 7912 | -12v1A     | \$2.00 |
| 7806       | 6v1A           | \$1.30     | 7818 |       | \$1.30 | 723  | 14 pin DIL | .50    |
| 7808       | 8v1A           | \$1.30     | 7824 | 24v1A | \$1.30 | 723  | (METAL     |        |
| 7812       | 12v1A          | \$1.30     | 7905 | 5v1A  | \$2.00 |      | KC CAN     | \$1.10 |
| uA 78 HGCK | 5 A adjustable | Reg \$8.50 |      |       |        |      |            |        |
| uA H05KC   | 5v 5A          | \$7.90     |      |       |        |      |            |        |

### DIODES & BRIDGES

|        |     |     |        |     |     |         |                   |        |
|--------|-----|-----|--------|-----|-----|---------|-------------------|--------|
| 0A91   | .17 | .15 | IN4148 | .06 | .05 | VJ448   | \$3.65            | \$3.50 |
| 0A95   | .18 | .16 | W02    | .80 | .75 |         | (400v10A Bridge)  |        |
| IN4002 | .08 | .07 |        |     |     | MDA3401 | \$4.75            | \$4.50 |
| IN4004 | .09 | .08 | W04    | .85 | .80 |         | (30A 100v Bridge) |        |
| IN5625 | .50 | .40 |        |     |     |         |                   |        |

### WELLER CORDLESS

#### SOLDERING IRON KIT

Model WC 100DK 15W incl. batteries, solder, four interchangeable tips, battery charger, plus instructions for only

\$29.50

### IC SOCKETS

|            |    |    |
|------------|----|----|
| 8 pin DIL  | 25 | 23 |
| 14 pin DIL | 33 | 30 |
| 16 pin DIL | 35 | 33 |

### OPTOELECTRONICS

|        |         |        |        |                |        |        |            |     |     |
|--------|---------|--------|--------|----------------|--------|--------|------------|-----|-----|
| FND357 | .375"cc | \$1.40 | \$1.30 | FPT100         | \$1.30 | \$1.20 | LED RED    | .25 | .22 |
| FND500 | 5"cc    | \$1.50 | \$1.40 | FPT120A        | \$1.40 | \$1.30 | LED GREEN  | .40 | .35 |
| FND800 | 1"cc    | \$3.50 | \$3.30 | PCD820A        | \$1.50 | \$1.30 | LED YELLOW | .45 | .40 |
|        |         |        |        | (Opto coupler) |        |        |            |     |     |

### LINEARS

|       |        |        |        |        |        |        |        |        |
|-------|--------|--------|--------|--------|--------|--------|--------|--------|
| uA311 | .85    | .80    | uA741  | .40    | .35    | LM301  | .50    | .45    |
| uA339 | .90    | .85    | 9368   | \$1.90 | \$1.75 | LM381  | \$2.20 | \$1.90 |
| uA340 | .90    | .85    | RL4136 | \$3.90 | \$3.60 | LM382  | \$2.20 | \$2.00 |
| uA556 | \$1.20 | \$1.10 | LM380  | \$1.30 | \$1.25 | LM3900 | .95    | .90    |

Also in stock, multimeters, veroboard, solder, solderwick and soldering irons. All components brand new by top companies. Prices current until end August.

Mail orders PO Box 135 Northcote, 3070. Minimum 75c post & pack. Send SAE for free condensed catalogue.






range from  $-50$  to  $+1200$  C. A large bright display indicates temperature with an accuracy of 0.5% of reading  $\pm 0.5$  degree. An advanced auto-ranging system enables a resolution of 0.1 degree between  $-50$  and  $+185$  degrees C.

Also available from the Digitron range is the model 2754 bench-type mains powered digital thermometer. This uses a platinum resistor sensor to cover the range from  $-150$  to  $+800$  degrees C, with an accuracy of 0.2 degrees. An analog output, directly proportional in mV to the temperature reading in degrees C, is provided.

For further information on these and the other instruments in the Digitron range apply to Cortek Instruments, P.O. Box 184, St. Leonards NSW 2065.
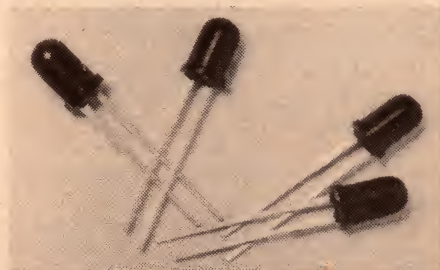
## Low cost LEDs

High quality light-emitting diode lamps in standard diffused-red 5mm diameter packages are available in quantity at attractive prices from Diggerman Electronics. The LEDs offer typically an output of 800 microcandelas at 20mA and 25 degrees C, with peak output centred on 0.65uM.



Unit price for small quantities is 17c, falling to 12c each in 100 lots and 11c each for 1000 off. Mounting bezels are 3c each regardless of quantity.

Further information is available on request, also a sample LED may be obtained by sending a 20c SAE to Diggerman Electronics, Box 33 P.O. Coramba, NSW 2466.

## 360° prism magnifier

The Zi-Tech Inspector is a pocket-sized prism magnifier which shows a full 360-degree inside view of holes. It automatically focuses on contact with the surface and requires no operator

training, allowing potentially costly drilling faults such as spiralling,



roughness and burring to be instantly detected. In electronics production, checks on PCB holes for plating voids, smoothness and solder flow can be made quickly and at low cost.

Further information is available from C & K Electronics (Aust.) Pty Ltd, P.O. Box 101, Merrylands NSW 2160. Telephone (02) 682-3144.

## IC handling tools

Micro Electronic Systems have added a new range of IC insertion and extraction tools to their well-known DIP-A-DIP line. The model 112 insertion tool is designed for 0.4in wide LSI chips, and has stainless steel side plates to allow earthing for MOS devices. Three new extraction tools are also available for 0.4in, 0.5in/24/28 pin and 0.6in/36-40 pin devices.

Further information from Royston Electronics, 22 Firth St, Doncaster, Vic. 3108.

## DEMCO offers New "PATHFINDER"—10 ELECTRONIC LINEAR DIGITAL READOUT SYSTEM

**Technical Features:** Resolution .0001 in./0.02mm Accuracy  $\pm 0.00015$ ins/ft. New Micro-Processor display unit, LEDs 0.6" high, push-button controls, calculator type keyboard, "Preset", inch/mm & floating zero are standard. Inch/mm conversion without loss of position. Flashing 8's indicate power interruption. Standard slew rate 300 in./minute.

**Options Available:** R/D — Radius/Diameter option for lathe cross travel.

M — Memory provides two paralleled count circuits, "recall" displays the distance between present location and the datum line.


A — Absolute zero, & fixed position mark on the glass scale. Further options such as BCD, Remote Reset, also available Axis lengths up to 78 inches.

### Advantages of Use:

- Converts your machine for inch/metric operation, saving replacements and downtime.
- Increases productivity, confidence and accuracy. Operator reads directly from illuminated display.
- Eliminates dial reading errors. No dial setting, dial reading or associated arithmetic errors.
- Eliminates backlash adjustment & leadscrew error. Display shows actual machine table movement regardless of amount of leadscrew wear or inaccuracy.
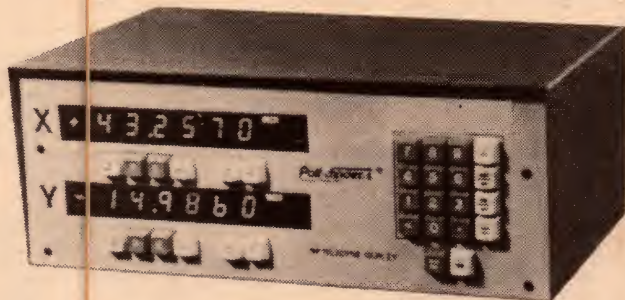
### BACKGROUND OF TELEDYNE GURLEY

Established in 1845, surveying instruments and compasses were among the early products. Now produce navigational instrumentation for NASA and Apollo Moon Ventures.



Other models with accuracy  $\pm 0.00025$ inch/ft.

PATHFINDER-5 to 144in. Resolution .0005/.01mm  
PATHFINDER-105 to 80in. Resolution .0001"/.02mm

### GUARANTEED, ON MAKER'S CONDITIONS

2 years on parts, 1 year on labour

To: DEMCO MACHINERY CO. PTY. LTD.  
Box M88 Sydney Mail Exchange 2012.  
'Phone 699 4121.

or Box 56 Newstead, Queensland 4006.  
or 414 Spencer St., West Melbourne 3003.

Please send me without obligation, brochure and prices for  
AXIS LENGTH X- Y- Z-

OPTIONS REQUIRED  
TO FIT

Name .....  
Address ..... Postcode .....  
'Phone no. ....



# The Trio CO-1303G 75mm CRO: ideal for the amateur "shack"

Designed with an obvious eye to the radio amateur market, the Trio CO-1303G 75mm Oscilloscope is primarily intended for use in checking transmitters. It is a versatile instrument in this field and it should appeal to all who have an interest in monitoring and checking radio transmissions, be they amateur, CB or commercial.

A cathode ray oscilloscope, or CRO for short, is one of the most useful instruments available in the electronics field. With such a device, one is able to actually view many of the waveforms which occur in a wide range of electronic equipment. By so doing, it is often possible to check whether or not a device is functioning normally and to identify possible problems and solutions.


When a CRO is designed with some specific purpose in view, redundant facilities can be eliminated, thus reducing the price tag. At the same time a specialised instrument may have added features so as better to serve the function for which it was designed.

In the context of transmitters, a CRO may be used to view and check the modulation envelope of an AM transmission. By so doing, the percentage of modulation may be ascertained, along with other factors such as whether the modulation is linear or not, whether there is clipping of the positive-going peaks, whether the negative-going cycles are being cut off, etc. Such checks may be made under conditions where a constant tone is fed into the transmitter, or under more

typical conditions where speech is being processed.

Single sideband operation of a transmitter may also be checked. By means of the two-tone technique, the output may be checked for correct linearity, overdrive, bias adjustment, etc. Where CW operation is used, the keying characteristics of the transmitter may be assessed.

As mentioned at the outset, the Trio CO-1303G is a specialised instrument in that it is intended primarily for checking and adjusting radio transmitters. This has resulted in a somewhat simpler unit than some of the more sophisticated general-purpose instruments with dual-trace facilities, wideband calibrated amplifiers and calibrated timebase. On the other hand, the CO-1303G provides direct access to the vertical deflection plates via terminals on the back panel so that transmitter modulation envelopes may be displayed. The sensitivity under these conditions is quoted as being higher than 1W/division with a 50-ohm load. Associated with this facility is an RF attenuator to control the level of RF being fed to the vertical deflection plates.

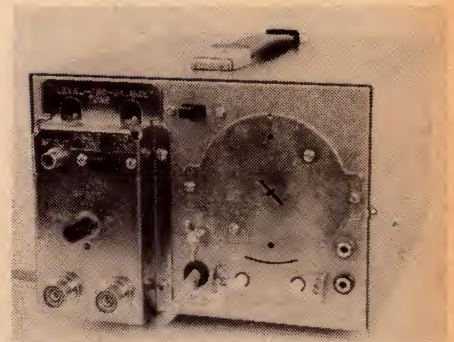

*This rear view of the instrument shows the attachment at the left which provides access for RF to the deflector plates and also houses the two-tone oscillator. To the right are focus and intensity controls, and Z-axis (intensity modulation) facilities, together with a means of rotating the tube slightly for exact vertical and horizontal traces.*

Another feature is a built-in single tone and two-tone audio oscillator. A single tone of 1000Hz is available for testing AM systems, while the two-tone facility includes 1575Hz for testing SSB signals. The inclusion of the audio tones into this instrument makes it virtually self-contained for tests of the sort so far outlined.

It should be pointed out that although transmitter testing is an important function of the CO-1303G, there are many other uses to which it may be put. These include testing of audio amplifiers for frequency response, distortion, square wave performance, etc. Tests involving the use of Lissajous figures may also be made. Also, it is possible to use the CRO for making RTTY tests and adjustments.

In fact, it would not be unreasonable to say that this instrument may be used for most purposes where a general-purpose CRO is used, provided that a dual trace and accurately calibrated amplifiers and time base are not essential.


The unit is supplied with a comprehensive Instruction Manual running to 36 pages. A general description is given of the instrument, together with operating instructions. Maintenance and alignment of the instrument is also covered, along with a complete circuit diagram. The current price is quoted at \$343.85, including tax.

Further information on the CO-1303G may be obtained by contacting Parameters Pty Ltd, 68 Alexander Street, Crows Nest, NSW 2065. (I.L.P.)
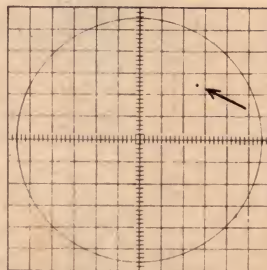
## PARAMETERS/ELECTRONICS AUSTRALIA GRAND INSTRUMENT CONTEST NO. 3

First prize of a TRIO 1303D oscilloscope was won by:  
Mr M. Henry,  
Campbell,  
ACT,  
and second prize of a B&K Digital Multimeter was won by:  
Mr N. Crawford,  
Dulwich Hill,  
NSW.

Our congratulations to Mr Henry and Mr Crawford, and our thanks to the several hundred other readers who participated.




Where was the dot? . . .  
This diagram shows the exact location.



# PARAMETERS/ELECTRONICS AUSTRALIA GRAND INSTRUMENT CONTEST <sup>no. 5</sup>

## TRACE THE TRACE AND WIN...

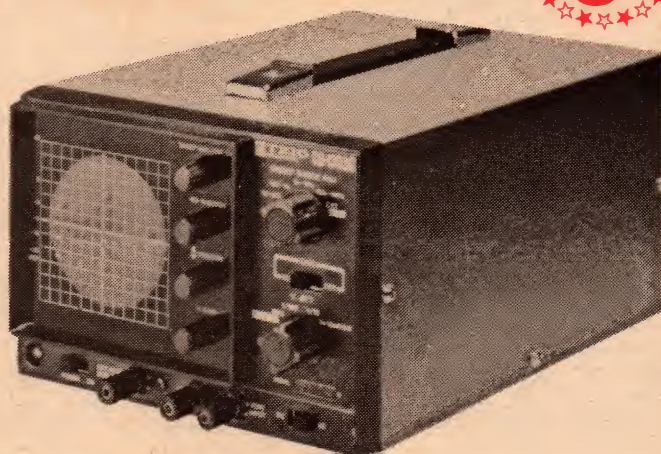

### TRIO 1303G OSCILLOSCOPE

Monitor Frequency Range: 1.8 to 54MHz (1-500W)

Two Tone Generator: 1kHz and 1.575kHz  
(1kHz in single tone)

Oscilloscope capability: DC to 5MHz at 10mV

Designed for the amateur radio enthusiast, the CO1303G is a versatile monitor scope with many useful features. Two M-type connectors on the rear enable the scope to be connected into the antenna coax so that transmitted waveforms may be observed. A built-in two tone generator aids checking and mic gain adjustment etc.

In addition, the 10mV/div vertical sensitivity and broad bandwidth from DC to 5MHz, makes this instrument ideal for general service and lab work.

**Hurry with your entries for Contest 1 — you could win a TRIO 1560A 15MHz scope!!**

### ENTRY COUPON

Parameters/E.A.  
Grand Instrument  
Contest No 5

### TRACE the TRACE

Simply draw the trace as you think it appeared. Fill in your name and address and mail the coupon to:

Parameters/Electronics  
Australia


Grand Instrument  
Contest No 5

P.O. Box 163,  
Beaconsfield, N.S.W. 2014

All entries must be in by  
**October 9th** when the winner  
will be chosen.

The decision of the editor is  
final and no correspondence  
will be entered into.

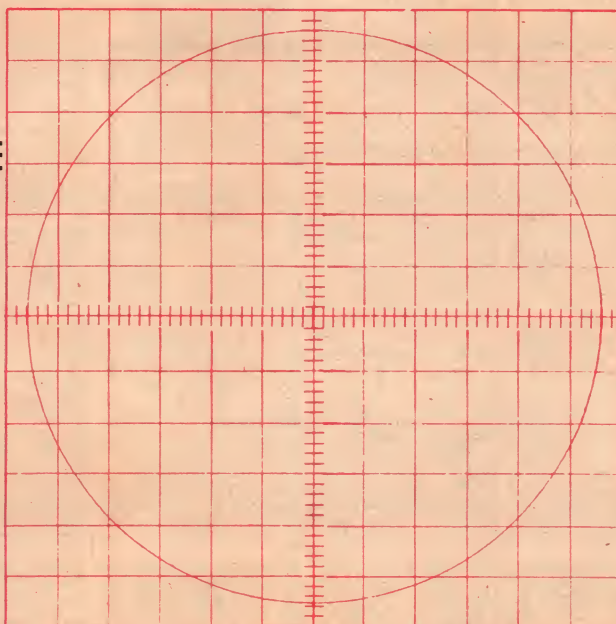Permit No. TC 1209A issued  
under the Lotteries and Art  
Unions Act.



NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

Postcode \_\_\_\_\_

Where do you normally make  
your electronic purchases?

I agree to abide by the rules of  
the contest -

Signed: \_\_\_\_\_




# LEARN ELECTRONICS

with **BOOKS**  
from **DICK!**

Dick has an enormous range of books for beginners, experts, professionals, hobbyists, amateurs. The titles listed here are just a small sample — call into a Dick Smith Store today and see the lot — or write to our Mail Order Centre for a detailed list!

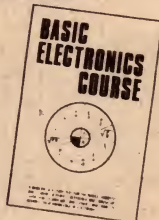
## BOOKS FOR BEGINNERS

**Basic Electronics Course**  
Crowhurst — 361 pages.  
A modern, self-study text for beginners, as well as a useful reference for trained technicians. Illustrated.  
Cat. B-1689 .. .. \$8.95



**Electronics Self-Taught**  
Ashe — 285 pages.  
Ten chapters crammed with everything the beginner in electronics needs to know.  
Cat. B-1684 .. .. \$7.50

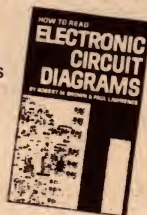**How to Read Electronic Circuit Diagrams**  
Brown & Lawrence - 192 pages  
Describes each circuit part and its function, gives clear pictures of components as well as circuit symbols.  
Cat. B-1650 .. .. \$6.50



**Basic Electronics**  
E.A. Staff — 128 pages  
An easy introduction to radio, hi-fi and electronics. 23 chapters profusely illustrated.  
Cat. B-3620 .. .. \$3.00

**Basic Transistor Course**  
Kenian — 218 pages  
Explains what transistors are, how they work and their relationships with other electronic components.  
Cat. B-1567 .. .. \$7.50



**Fundamentals of Solid State**  
Rowe — 120 pages  
An excellent introduction to semi-conductors and their applications. 17 chapters, many illustrations and drawings.  
Cat. B-3621 .. .. \$3.00

## ANTENNA BOOKS

**ABC's of Antennas**  
Lytel — 96 pages  
Describes basic types of antennas, their radiation characteristics, uses and construction.  
Cat. B-1000 .. .. \$5.50

**Wire Antennas for Radio Amateurs**  
192 pages  
Gives construction details for many types of amateur band antennas including horizontal, vertical, multitrapped and beam antennas, 2-160 metres.  
Cat. B-2302 .. .. \$9.90

**All About Cubical Quad Antennas**  
112 pages  
The world famous 'classic' on quads. Gives dimensions, data for many types of quad antennas.  
Cat. B-2304 .. .. \$7.90

**Beam Antenna Handbook**  
200 pages  
All information you need about construction of triband and compact beams including baluns, matching systems and test instruments.  
Cat. B-2306 .. .. \$9.90

**Amateur Radio Techniques — RSGB**  
Hawker — 300 pages  
Whatever branch of amateur radio you're interested in you'll find loads of information in this book's 300 pages with 700 illustrations. A bargain for the amateur enthusiast.  
Cat. B-2040 .. .. \$6.90

**VHF-UHF Manual — RSGB**  
Evans and Jessop  
This huge manual deals with techniques and equipment for operating above 30 Mhz. Valuable for amateur radio enthusiast.  
Cat. B-2054 .. .. \$15.00

**NBFM Manual — RSGB**  
Hewes and Jessop — 60 pages  
Completely dedicated to narrow band FM systems, this book will answer all your questions on transmitters, receivers and ancillary equipment.  
Cat. B-2052 .. .. \$3.45

## BOOKS FOR AMATEURS (and aspiring amateurs)

**ARRL Handbook**  
1978 edition  
— 704 pages  
The standard reference book for amateurs the world over.  
Cat. B-2218 .. \$12.75



**Radio Handbook**  
Orr — 1080 pages  
Incredibly comprehensive book on amateur communications. Over 30 chapters packed with information.

Cat. B-1106 .. .. \$23.95

**Understanding Amateur Radio**  
ARRL — 218 pages  
Establishes the technical groundwork for all phases of amateur radio.  
Cat. B-2232 .. .. \$8.75

**Getting to Know Oscar**  
From the Ground Up  
QST — 45 pages  
Everything you need to know about working the OSCAR amateur communications satellite.  
Cat. B-2220 .. \$5.50



**Questions and Answers for the Novice License**  
Howard — 104 pages  
Explains the radio theory you need to know to sit for your Novice licence.  
Cat. B-2315 .. .. \$3.95

**ARRL Books**  
So well known they need no description.  
SSB for the Radio Amateur  
Cat. B-2212 .. .. \$6.75  
FM and Repeaters for the Radio Amateur  
Cat. B-2210 .. .. \$6.95  
Specialist Communications Technique  
Cat. B-2230 .. .. \$6.90  
Hints and Kinks. 9th Edition.  
Cat. B-2206 .. Was \$3.75 .. Now \$2.99  
Radio Amateur's Operating Manual  
Cat. B-2208 .. .. \$6.90

## BOOKS FOR CB'ERS

**Citizens Band Radio Handbook**  
Hicks — 192 pages  
Complete CB handbook with dozens of photos and diagrams.  
Cat. B-1268 .. .. \$5.00



**CB Radio Construction Projects**  
Buckwalter — 128 pages  
Shows you how to build many low-cost devices to use with CB radios.  
Cat. B-1220 .. .. \$6.25


**99 Ways to Improve Your CB Radio**  
Buckwalter — 128 pages  
Will help you improve your CB's performance, increase your enjoyment of CB.  
Cat. B-1256 .. .. \$5.75

**What you need to know about CB Antennas**  
Leo G. Sands — 54 pages  
Improve your rig's performance by ensuring your antenna is correctly set up.  
Cat. B-2326 .. .. \$3.00



**CB Radio Antennas**  
Hicks — 136 pages  
A useful guide to all CB'ers who wish to improve the performance of their antenna systems.  
Cat. B-1257 .. .. \$6.50

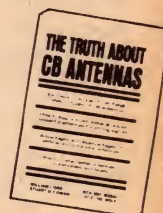**The Truth About CB Antennas**  
Orr & Cowan — 240 pages  
Enables you to build, buy, install and adjust efficient antennas for strongest signals.  
Cat. B-2327 .. .. \$8.50



**CB Radio Installation Handbook**  
Hicks — 178 pages  
Gives you step-by-step instructions on how to install your own base or mobile station.  
Cat. B-1270 .. .. \$7.95

**CB Radio Servicing Guide**  
Sands — 160 pages  
A complete and practical guide to servicing all types of 27 MHz equipment.  
Cat. B-1254 .. .. \$7.50



**CB'ers Handy Atlas/Dictionary**  
— 64 pages  
The most complete CB Dictionary yet, with over 1000 listings.  
Cat. B-1856 .. .. \$3.00

**Dick Smith's Australian CB Radio Handbook**  
128 pages  
The first book written specifically for the Australian CB scene. Tells you everything you want to know about CB.  
Cat. B-2325 .. .. \$3.95



\* SEE OUR DOUBLE PAGE AD FOR FULL LIST OF STORES AND DEALERS

# DICK SMITH ELECTRONICS







# Books & Literature

## Novice exam guide

**MANUAL OF QUESTIONS & ANSWERS FOR THE NOVICE LICENCE**, by Keith Howard, VK2AKX. Sixth edition. A Westlakes Education publication. Soft covers. 100 pages, 240mm x 180mm. Illustrated with numerous diagrams.

The instructional literature produced by Keith Howard and the Westlakes Radio Club has become something of a legend wherever amateur exams and study material is discussed. Produced originally in duplicated form this particular book quickly earned a reputation which resulted in nearly 4000 copies being sold last year.

In the introduction, the author explains that the book has been compiled around questions asked in previous novice examinations, at the same time pointing out that this does not make it a comprehensive guide to all possible questions.

There are 15 sections, under the following headings. (1) Units. (2) Electrons at Work. (3) Circuits. (4) Components. (5) Power Supplies. (6) Propagation. (7) Modulation. (8) Operating (9) Transmitters. (10) Receivers. (11) Meters and Measurements. (12) Calculations. (13) Services (Morse code). (14) Supplement (Tips and facts). (15) Examination (An actual novice paper).

Each section consists of a detailed text covering the particular subject, followed by a series of questions, on that subject, taken from previous examinations. Each question is discussed and the method of arriving at the correct answer shown.

The quality of the instruction material appears to be quite high. Each section starts at an elementary level and, in an easy-to-read style, builds up in logical stages until it is dealing with relatively complex aspects.

At the same time, there are obvious omissions from what one has come to expect from standard text books. There is, for example, no detailed explanation of resonance; only a description of a tuned circuit, and the purpose for which it is used. We imagine that this is deliberate, to avoid confusing the student with material he is unlikely to need at this level.

As well as the technical text, there are notes on applying to sit for the examination, addresses of licensing

branches, and a replica of the application form.

Summing up, this appears to be an excellent book for the aspiring novice, regardless of whether other texts are available or not. And, at the price, extremely good value.

Our copy from Dick Smith Electronics, who quote their price as \$3.75 at all Dick Smith stores, or by mail post free. (PGW)

## ... and for the AOC

**HAM EXAM CRAM BOOK**. By Ivan Botha, VK2B10. Published by the author. Soft covers, 34 pages, 190mm x 160mm, illustrated by circuits and diagrams. Price in Australia \$2.00 postpaid.

It would be unwise to dismiss this booklet on the basis of its modest size and price; on the contrary, the conciseness with which the material is presented is one of the book's features.

As the name implies, it is intended for those studying for the AOC theory exam. It evolved out of the author's studies and notes associated with his own approach to the exam.

One thing the book is not — and the author emphasises this point himself: it is not a substitute for in-depth study, or the classic textbooks normally specified for this exam. Rather it is an additional text to supplement these studies.

In particular, it will help bridge the gap between the formal studies and the exam itself by listing the most vital pieces of information which the student needs to remember.

While there were a couple of points which I felt may mislead a student, perhaps by being over condensed, the material is accurate and pertinent. At the very least this book will be a useful addition to any examinee's library; at the most it may make the difference between passing and failing the first time. Recommended.


Our copy direct from the author at 316 Grey St, Glen Innes, NSW 2370. (P.G.W.)

## Microprocessors

**MICROPROCESSORS: FROM CHIPS TO SYSTEMS**, by Rodney Zaks. 2nd Edition, 1977. Sybex, Inc, Berkeley, California. Soft covers, 139 x 217mm, 416pp. Price in USA \$9.95.

As we have noted before, the way to achieving an understanding of

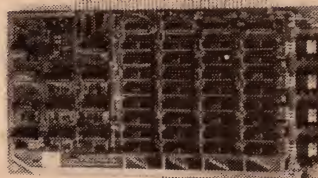**XXX LIMITED OFFER XXX**  
**16K STATIC MEMORY**  
**\$430.00 — \$495.00 Inc. Tax**  
**ASSEMBLED AND TESTED**



### FEATURES:

S-100 Compatible\*, 450nS\*, Memory Mapping\*, Phantom Line Option\*, Ability To Deactivate Any 1K Block\*, Address Select At 16K Boundaries\*, Will Operate With/Without Front Panel\*.

ADD \$5.00 P&P Outside Perth.



**Australian Computer Products Pty Ltd,**  
1300 Hay Street,  
West Perth 6005  
(09) 322 6497

**Authorised Dealers for:** Cromemco — Alpha Micro Systems — Soroc —  
IMS — North Star



# BOOKS

Just some of the books from the biggest range of radio and electronics books in Australia.  
If the book you require is not listed below, it can be ordered from us.

## NEW — NEW — NEW

Latest editions of some of the most popular books on the subject:

|                                                                                                           |         |
|-----------------------------------------------------------------------------------------------------------|---------|
| Just in — New ARRL Handbook 1978 Edition                                                                  | \$12.95 |
| Just in — World Radio TV Handbook 1978                                                                    | \$12.95 |
| RSGB Handbook (New Edition) Volume 1                                                                      | \$21.85 |
| RSGB Handbook (New Edition) Volume 3                                                                      | \$18.90 |
| Reference Data for Radio Engineers (New Edition) ITT                                                      | \$40.50 |
| Radio Handbook (William Orr) 20th Edition                                                                 | \$26.50 |
| How to Build Proximity Detectors and Metal Locators (John Potter Shields)                                 | \$6.35  |
| An Introduction to Microcomputers — Volume 1 — Basic Concepts (Adam Osborne)                              | \$12.55 |
| An Introduction to Microcomputers — Volume 2 — (New Enlarged Edition) — Some Real Products (Adam Osborne) | \$21.55 |
| 6800 Programming for Logic Design (Adam Osborne)                                                          | \$12.55 |
| 8080 Programming for Logic Design (Adam Osborne)                                                          | \$12.55 |
| Weather Satellite Handbook                                                                                | \$7.80  |
| VHF Antenna Handbook                                                                                      | \$7.80  |
| The 73 Test Equipment Library — Volume 1 — Component Testers                                              | \$7.80  |
| The 73 Test Equipment Library — Volume 2 — Audio Frequency Testers                                        | \$7.80  |
| The 73 Test Equipment Library — Volume 3 — Radio Frequency Testers                                        | \$7.80  |
| The 73 Test Equipment Library — Volume 4 — IC Test Equipment                                              | \$7.80  |

## New Books:

|                                                                           |         |
|---------------------------------------------------------------------------|---------|
| 111 Digital and Linear IC Projects (Don Tuite)                            | \$8.50  |
| Unique IC OP-AMP Applications (Walter C. Jung)                            | \$7.00  |
| IC OP-AMP Cookbook (Walter C. Jung)                                       | \$17.50 |
| TTL Cookbook (Lancaster)                                                  | \$12.25 |
| TV Typewriter Cookbook (Lancaster)                                        | \$13.50 |
| RTL Cookbook (Lancaster)                                                  | \$6.60  |
| CMOS Cookbook (Lancaster) 1st Edition 1977                                | \$13.50 |
| Active Filter Cookbook (Lancaster)                                        | \$20.25 |
| IC Timer Cookbook (Jung)                                                  | \$13.50 |
| Transistor Specifications Manual — 8th Edition                            | \$9.50  |
| Transistor Substitution Handbook — New Edition                            | \$6.75  |
| International Transistor Selector (T. D. Towers)                          | \$6.95  |
| Master Tube Substitution Handbook (Tab Books)                             | \$7.00  |
| Australian Electrical Wiring Theory and Practice (Pethebridge & Williams) | \$11.45 |

## CB Radio Books:

|                                                                                  |        |
|----------------------------------------------------------------------------------|--------|
| ABC's of Citizens Band Radio (L. Buckwalter)                                     | \$5.75 |
| Chilton's CB Handbook (New 40 Channel)                                           | \$5.60 |
| CBer's How-To Book (Leo G. Sands)                                                | \$6.95 |
| Citizens Band Radio (Allan Lytel) Revised 2nd Edition                            | \$6.95 |
| Easi-Guide to CB Radio for Truckers (Forest H. Belt)                             | \$4.95 |
| CB Radio Operating Procedures (D. Hicks)                                         | \$5.50 |
| CB Radio Servicing Guide (Leo G. Sands)                                          | \$6.75 |
| Easi-Guide to Citizens Band Radio (Forest H. Belt)                               | \$4.95 |
| CB Radio Construction Projects (Len Buckwalter)                                  | \$5.50 |
| Citizens Band Radio Handbook (David E. Hicks)                                    | \$7.95 |
| CB Radio Operator's Guide (2nd Edition) (Robert M. Brown and Paul L. Dorweiler)  | \$8.50 |
| The Best Book on CB — includes all 40 Channels & 1977 Regulations (Evan Herbert) | \$6.25 |
| CB Bible — The Complete Guide to Citizens Band 2-way Radio                       | \$6.95 |
| The Truth About CB Antennas (William I. Orr)                                     | \$7.00 |

## Microcomputers/Microprocessors Books:

|                                                                                       |         |
|---------------------------------------------------------------------------------------|---------|
| Programming Microprocessors (M. W. McMullan)                                          | \$9.75  |
| Microprocessors: Technology, Architecture and Applications (Daniel R. McGlynn)        | \$18.80 |
| Microprocessors (Electronics Book Series (Hardcover)                                  | \$17.65 |
| Microcomputers/Microprocessing: Hardware, Software and Application (Hilburn & Julich) | \$26.50 |
| Minicomputer Systems: Structure, Implementation and Application (G. Weitzman)         | \$29.55 |
| Microcomputer Primer (Waite & Pardee)                                                 | \$10.75 |
| Minicomputers for Engineers and Scientists (G. Korn)                                  | \$33.15 |
| How to Buy and Use Minicomputers and Microcomputers (W. Barden, Jnr)                  | \$13.50 |

Prices Subject to Alteration

For Mail Orders please add: 80c Local \$1.50 Interstate

**McGILL'S AUTHORISED NEWSAGENCY PTY LTD**

187 Elizabeth Street, Melbourne

Phone: 60 1475-6-7

## American Radio Relay League Publications:

|                                                             |         |
|-------------------------------------------------------------|---------|
| Hints and Kinks for the Radio Amateur                       | \$7.20  |
| The Radio Amateur's VHF Manual                              | \$7.20  |
| ARRL Antenna Handbook                                       | \$8.80  |
| Understanding Amateur Radio                                 | \$8.80  |
| The Radio Amateur's License Manual                          | \$6.20  |
| A Course in Radio Fundamentals                              | \$7.20  |
| Specialized Communications Techniques for the Radio Amateur | \$7.20  |
| FM & Repeater for the Radio Amateur                         | \$7.20  |
| Single Sideband for the Radio Amateur                       | \$7.20  |
| Ham Radio Operating Guide                                   | \$7.20  |
| Electronics Data Book                                       | \$7.20  |
| Solid State Design for the Radio Amateur                    | \$12.80 |
| Learning to Work with Integrated Circuits                   | \$4.00  |
| Getting to Know Oscar from the Ground Up                    | \$6.20  |

## Howard W. Sams Publications:

|                                                                                                                                            |         |
|--------------------------------------------------------------------------------------------------------------------------------------------|---------|
| TV Servicing Guide — Arranged by Trouble Symptoms (Leslie D. Deane & Calvin C. Young Jnr)                                                  | \$6.50  |
| Electric Guitar Amplifier Handbook (Jack Darr)                                                                                             | \$10.20 |
| Transistor Fundamentals — A Programmed Learning Course — Volume 1 Basic Semiconductor and Circuit Principles (Robert J. Brite)             | \$7.75  |
| Transistor Fundamentals — A Programmed Learning Course — Volume 2 — Basic Transistor Circuits (Charles A. Pike)                            | \$7.75  |
| Transistor Fundamentals — A Programmed Learning Course — Volume 3 — Electronic Equipment Circuit (Martin Gersten)                          | \$7.25  |
| Transistor Fundamentals — A Programmed Learning Course — Volume 4 — Digital and Special Circuits (Louis Schweitzer & Reginald H. Peniston) | \$7.25  |
| 101 Easy Audio Projects (Robert Brown & Tom Kneitel)                                                                                       | \$5.10  |
| Video Security Systems (Keith W. Bose)                                                                                                     | \$7.15  |
| Tube Substitution Handbook No. 20                                                                                                          | \$3.95  |
| ABC's of Antenna's (Allan Lytel & Farl J. Waters)                                                                                          | \$5.75  |
| Transistor Radio Servicing Course (Wayne Lemons)                                                                                           | \$11.50 |
| Industrial Electronic Systems (Dale R. Patric & Stephen W. Fardo)                                                                          | \$16.25 |

## RCA Publications:

|                                                                           |        |
|---------------------------------------------------------------------------|--------|
| Electro-Optics Handbook                                                   | \$8.30 |
| RC 30 — Receiving Tube Manual                                             | \$4.50 |
| SC 16 — Solid State Devices Manual (New Edition of RCA Transistor Manual) | \$7.50 |
| RCA Power Devices (RCA Solid State)                                       | \$7.95 |

## Other Titles:

|                                                                                                       |         |
|-------------------------------------------------------------------------------------------------------|---------|
| Colour Television Theory (Hutson)                                                                     | \$10.00 |
| Radio, Valve and Semiconductor Data 10th Edition (Compiled by A. Ball)                                | \$4.25  |
| MOS Digital IC's (G. Flynn)                                                                           | \$8.60  |
| Wind/Solar Energy — For Radio Communications and Low Power Electronic/Electric Applications (E. Noll) | \$10.75 |
| Sound System Engineering (Don & Carolyn Davis)                                                        | \$26.95 |
| Servicing with the Oscilloscope — 2nd Edition (Gordon J. King)                                        | \$12.00 |
| 73 Dipole and Long-Wire Antennas (Edward M. Noll)                                                     | \$6.75  |
| 73 Vertical Beam and Triangle Antennas (Noll)                                                         | \$7.50  |
| Basic Television — Principles and Servicing — 4th Edition (Bernard Grob) New Edition — Soft Cover     | \$15.30 |
| Basic Electronics — 4th Edition (Bernard Grob)                                                        | \$15.75 |
| PAL Colour Television for Servicemen (W. C. Cook)                                                     | \$15.00 |
| Manual of Sound Recording — 2nd Edition (John Aldred)                                                 | \$10.25 |
| Getting the Most out of Your Electronic Calculator (William L. Hunter)                                | \$6.95  |
| Hi-Fi Loudspeakers and Enclosures (A. Cohen)                                                          | \$9.00  |
| Electronics Pocket Book — 3rd Edition (Editor — P. J. McGoldrick)                                     | \$10.10 |
| Simple Low Cost Wire Antennas (William I. Orr & Stuart D. Cowan)                                      | \$5.85  |
| VHF Handbook For Radio Amateurs. (Herbert S. Brier & William I. Orr)                                  | \$7.00  |
| Beam Antenna Handbook — New 5th Edition (William I. Orr)                                              |         |
| All About Cubical Quad Antenna's — 2nd edition (William I. Orr)                                       | \$5.60  |

## Books & Literature

microprocessors is not easy. If you have no understanding of computer concepts at present, no one book — no matter how good — is likely to make you an instant expert. But I must report that this is one of the best introductory books on the subject that I've seen to date.

The author, Dr. Rodney Zaks, is an experienced microprocessor system designer and an established author and lecturer. This book is essentially a distillation of a number of training course texts he has written over the last few years, and as a result it is well polished. The material is well organised and clearly presented, and should go a long way towards helping beginners on their way.

There are 10 chapters, titled as follows. 1 — Fundamental Concepts; 2 — Internal Operation of a Microprocessor; 3 — System Components; 4 — Comparative Microprocessor Evaluation; 5 — System Interconnect; 6 — Microprocessor Applications; 7 — Interfacing Techniques; 8 — Microprocessor Programming; 9 — System Development; 10 — The Future. The book ends with 6 data appendices.

Some of the diagrams and tables have been reduced rather too much, and have become rather difficult to read. However in all it seems a very worthwhile addition to the introductory literature on micros, and one I can recommend.

The review copy came direct from the publisher, but I understand that copies are available from Computerland. (J.R.)

## ... and again

**AN INTRODUCTION TO PERSONAL AND BUSINESS COMPUTING**, by Rodney Zaks. Sybex, Inc, Berkeley, California, 1978. Soft covers, 140 x 217mm, 245pp, many illustrations. Price in USA \$6.95.

Another introductory book by Dr. Rodney Zaks, in this case intended more for the potential hobbyist or business user who needs an introduction to the basic concepts of computers at the system level. It could also be of value to those seeking to go into the subject deeper, but who currently lack the background.

The treatment is pitched at "intelligent layman" (layperson?) level, and does not attempt to give more than a basic familiarity with system concepts and the main items of hardware. But within this realistic context, it is clearly and concisely written, and well illustrated.



There are 14 chapters in all, covering everything from basic definitions to the economics of selecting a business system. There are also six data appendices, covering things like logic concepts, binary notation, communications concepts and lists of manufacturers.

In short, a highly readable introduction to small computing systems for the non-technical hobbyist or business user.

The review copy came direct from the publisher, but I understand that copies are available from Computerland. (J.R.)

## Battery patents

**PRIMARY BATTERIES, Recent Advances.** Edited by Robert W. Graham. Published by Noyes Data Corporation. Hard covers, 363 pages, 230mm x 150mm. Price in US, \$42.00.

**SECONDARY BATTERIES; Recent Advances.** Edited by Robert W. Graham. Published by Noyes Data Corporation. Hard Covers, 398 pages, 230mm x 150mm. Price in US, \$42.00.

We reviewed a forerunner of these books in our August 1975 issue (Storage Batteries and Rechargeable Cell Technology) and the current edition on second batteries is, in fact, an update on this. The one on primary batteries appears to be the first of a new series on this subject.

While the titles of both books sound intriguing to anyone interested in batteries, they are likely to be disappointed if they expect an advanced text book on the subject. In fact, both books are simply reference books, compiled from patent applications lodged with the US Patent Office.

To quote from the foreword, "The US patent literature is the largest and most comprehensive collection of technical information in the world. There is more practical, commercial, timely process information assembled here than is available from any other source."

In this sense these books would undoubtedly be extremely valuable to anyone involved in research at an industrial level, particularly in preventing wasted effort by duplicating work by other researchers, and already on record.

On the other hand, they cannot in any sense be regarded as textbooks which will introduce the student to subject; on the contrary, by their very nature they presuppose that the reader is already deeply involved in the subject, and interested only in the various advances being made.

On this basis, these books must be regarded as being suitable only for a highly specialised market and, particularly by reason of their relatively high price, difficult to justify at any other level.

Our copies direct from the publishers, Noyes Data Corporation, Park Ridge, New Jersey, USA. (PGW).

# You won't want to miss this . . .



**ONLY  
\$3.00\***

+ 60c pack & post

## 27 DO-IT-YOURSELF PROJECTS FROM ELECTRONICS AUSTRALIA

**You can't afford to miss out on this exciting new book from "Electronics Australia". Here are just a few of the projects it contains: loudspeaker protector, digital metronome, active filter, drill speed control, variable power supply, wiper control unit, tach and dwell meters, CDI, digital clock . . . plus many more. Get your copy now!**

### Use this handy order form



**To: Electronics Australia, PO Box 163, Beaconsfield 2014.**

Please send me . . . . . copies of "PROJECTS & CIRCUITS NO. 2" at \$3.60 each. (Price includes packing and postage.)

NAME . . . . .

ADDRESS . . . . .

STATE . . . . . POSTCODE . . . . .

I enclose a cheque/postal order to the value of \$ . . . . .



# A.C.E.

## ELECTRONICS CENTRE

# RADIO

### MUSICOLOUR — NEW IMPROVED MODEL \$85

For the disco, light show, party nights or just relaxing... enjoy your records and tapes more with Organ. Simple to connect to the home stereo or PA system, 3 channels, 1500 watts max. load each.

Fully constructed, ready to operate.



EACH CHANNEL FULLY PROTECTED P.P. \$3.50 Interstate \$5.50.



#### AWA E TONE

15" and 12" speakers

For guitar, organ, bass, disco, rock concert

12" 60W RMS, 8 ohms, 40-7000Hz, Reson. 60Hz, \$49.00 P.P. \$4.50 Interstate \$6.50

15" 100W RMS, 8 ohms, 40-5000Hz, Reson. 60Hz \$99.00 Fon. Road. Rail. Air Send SAE for full tech. data.

### OVER-STOCKED

Plessey Foster 10" speaker, model C250L08, 8 ohms, 40W max res freq 29Hz. Freq response — 4800Hz. Great for HiFi, PA. \$21.95, incl post.

### SUBMINIATURE

#### 2-WAY

#### SPEAKER


#### SYSTEMS

#### 50W MAX



A great rival to systems 10 times their size. Premier high power sound purity guaranteed. A special feature is the one piece aluminium cabinet. Colour mat black. Specs freq response, 75-20,000Hz, 4 ohms, \$133.00 pair. Plessey 20W Max \$112.50 pair. Each model 7 1/2" x 4 1/2" x 4 1/2" p.p. \$3.50 interstate \$5.50.
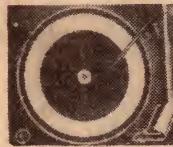
### FACTORY SCOOP — SAVE 66% GARRARD MODEL SL65B CHANGER-PLAYER



#### ONLY \$35.00

#### SHURE MAG.

#### CARTRIDGE

Base and Perspex Cover with hinges, teak or wal nut \$29.00. Freight NSW \$4.50, Interstate \$6.50.

240V 50Hz • Synchro-Lab 4 Pole Motor • 3 speeds • 10 1/2" Aluminium Platter • Slide-in Head • Magnetic Cartridge • Diamond Stylus • Counter-balanced P.U. • Cue and Pause Controls • Stylus Force Adjustment and Calibration • Bias Compensator • Switch Click Suppressor • Auto Set Down • Wow and Flutter better than 0.14% RMS • Rumble better than 46dB • Size 14 3/4" x 12 1/2" x 4 1/2" above and 3" below Mounting Plate PP NSW \$3.75, Vic, SA, Qld \$5.75, WA \$7.00

### PLAYMASTER 40 + 40 STEREO AMPLIFIER

#### GREAT HI-FI PERFORMER TOP VALUE



#### FULLY CONSTRUCTED, GUARANTEED COMPLETE KIT

\$139.95  
\$109.95

Quality components C-core transformer. Easy to build. Full instruction and circuit. Send SAE for technical specs. Freight NSW \$3.50 Interstate \$5.50.

### ● PLESSEY FOSTER ● EXCELLENT QUALITY LOUDSPEAKERS ●

NEW



MODELS

| MOD.    | SIZE   | IMP.<br>OHMS | MAX.<br>POWER W. | FREQ.<br>RANGE Hz | RESONANT<br>FREQ Hz | GAUSS  | MAGNETIC<br>WT OZ | NET<br>WT OZ | PRICE    |
|---------|--------|--------------|------------------|-------------------|---------------------|--------|-------------------|--------------|----------|
| C380K60 | 15"    | 8            | 240W             | 4500              | 40                  | 10,800 | 64                | 300          | \$160.00 |
| C300K60 | 12"    | 8            | 200W             | 5000              | 60                  | 11,200 | 50                | 180          | \$ 89.95 |
| C380L01 | 15"    | 8            | 80W              | 3800              | 28                  | 10,500 | 50                | 210          | \$ 65.00 |
| C300K05 | 12"    | 8            | 50W              | 4000              | 60                  | 9600   | 20                | 88           | \$ 31.00 |
| C200L11 | 8"     | 8            | 40W              | 4000              | 40                  | 9000   | 13                | 58           | \$ 21.00 |
| C200F05 | 8"     | 8            | 80W              | 5000              | 37                  | 9500   | 21                | 125          | \$ 92.00 |
| DO35M13 | 1.4"   | 8            | 40W              | 1500-18,000       | 720                 | 10,000 | 11                | 28           | \$ 13.50 |
| C130M08 | 5 1/4" | 8            | 60W              | 600-8000          | 205                 | 10,000 | 8                 | 32           | \$ 15.00 |
| C130M06 | 5 1/4" | 8            | 30W              | 1200-15,000       | 600                 | 9000   | 4                 | 19           | \$ 9.50  |
| C100M02 | 4"     | 8            | 30W              | 1000-10,000       | 600                 | 10,700 | 6                 | 20           | \$ 9.00  |
| DO25N15 | 1"     | 8            | 30W              | 2600-22,000       | 1300                | 13,000 | 8                 | 19           | \$ 11.00 |
| DO25H03 | 1"     | 8            | 80W              | 4000-20,000       | 2300                | 8100   | 1.2               | 6            | \$ 7.75  |
| C200K12 | 8"     | 8            | 20W              | 7000              | 110                 | 12,000 | 6                 | 26           | \$ 9.00  |

Despatch road, rail, air freight, parcel post. Add freight. Full range available, send SAE for price list.

#### VOLTAGE DOUBLER

9. PF2050 285V 250MA 2X  
24V 1A 6.3V 4.5 A 6.3V 1A  
25V 1A \$12.50

#### 6V to 12V DC CONVERTER

Solid state circuit, instructions, leads, 5 amp fuse included. Size 83 x 57 x 102mm, was over \$20, now \$15. P.p. NSW 95c, Interstate \$1.45.

#### POWER TRANSFORMER SPECIALS

ALL WITH 240V 50Hz PRIMARY  
Type JT25. 40V CT 2A \$10.95  
Type JT256 50V CT 2A \$10.95  
Type JT144 56 V CT 2A \$13.95  
P.p. NSW \$2.00, Interstate \$3.50.

#### C-CORE TRANSFORMERS

240V 50Hz primary  
low noise high efficiency  
Model JT266 0-18V 8A \$22.95  
Model JT235 26-0-26V4A \$21.95  
Model JT249 0-15V  
8.5-0-8.5V 4A  
for micro processor \$23.95  
P.P. NSW \$2.95 Interstate \$3.75

#### VARIABLE CONDENSORS EX AWA

Transmitting types. Double Spaced. 1/4in shaft. Ceramic Insulation. 315pf size 5" x 3 3/4" x 2 1/4". Plates easy to remove. \$7.50 p.p. NSW, \$1.50. Interstate \$2.50. 100pf 2 gang 3 3/4" x 3" x 1 3/4", \$4.50 p.p. NSW, \$1.00. Interstate, \$1.60.

#### CERAMIC INSULATORS

High power, glazed porcelain, stand-off, 4" long, top dia 1 1/2", bottom dia 2", flange dia 3 1/2", \$3.50 p.p. NSW \$1.30. Interstate \$1.60. Feed-through 3 1/2" x 1 1/4" tapered \$1.50. PP NSW 75c. Interstate \$1.10. Each supplied with threaded brass bolt, nuts, gasket, etc. Egg insulators 10 for \$3.99, p.p. 90c.

#### POWER TRANSISTORS

Type 2SD200 + BU205. NPN. 900V. 2.5A. 4 for \$7.00 incl post. 2N3055. 10 for \$7.50 incl post. BD139, BD140. 10 for \$6.00. BD135, BD136. 10 for \$4.50 incl post.  
I-Cs  
UA709, 301, 741, 723. 10 for \$3.00 incl post. 555 Timers, 10 for \$3.00 incl post.

#### POWER TRANSFORMER SALE

All new with 240V 50Hz Primary.

1. 0-12V 1/2 amp \$2.50
2. 0-24V 1/2 amp \$2.50
3. PF201. 225V CT 50MA 6.3V 2A \$4.50
4. A&R 6232 70V CT 75A \$6.50
5. PF 3162 2 separate 20V 1.5A \$7.50
6. 110V 1.8A \$12.50
7. 385 V CT 60MA 5V 2A 6.3 CT 2A \$4.50
8. 385V CT 80MA 5V 2A 6.3 CT 2A \$5.50

#### ISOLATION

10 250, 260 275V, 500VA \$15.00  
11 240V 60MA \$4.50  
P.P. Nos 1-5, 7, 8 11, NSW \$2.00. Interstate \$3.50. Nos. 6, 9 10, Fon., Road, Rial.

#### SOLDER SUCKER

Powerful absorption, miniature, with nonstick Teflon nozzle, \$12.95 p.p. 90c.

#### SERVICE

Moderate charges — Repairs guaranteed. Radios, Tape Recorders, Cassettes, CB Rigs, PA Guitar Amps, Stereos, etc.

WE REGRET THAT PRICES ARE SUBJECT TO CHANGE WITHOUT NOTICE

#### HEAD BOOM-MICROPHONE



600 ohms

With remote footswitch, plugs, cables, quality guaranteed. Both hands are free. Hearing not affected. \$9.95 p.p. \$1.50.

#### RECHARGEABLE BATTERY

6V  
1.2AH



Fully sealed in high impact moulded case. 3 1/2" x 7/8" x 2". Ideal for photographers, cavemen, skindivers, hobbyist. \$4.95 p.p. NSW 80c. Interstate \$1.20. Plug-Pak charger to suit. \$5.50 p.p. 80c. Interstate \$1.20.

#### NEW ELECTROLYTICS

3300uF 50V, suit PCB, 10 for \$11.50  
2200uF, 63V, CMT, 10 for \$6.50  
1000uF, 25V, PCB 10 for \$3.00  
1000uF, 40V, Ax, 10 for \$4.00  
5600uF 40V PCB, 4 for \$11.00  
P.P. NSW \$1.00, Interstate \$1.60.



# INFORMATION CENTRE

**MICROCOMPUTERS:** I am interested in microcomputers. I am a form five student and the school has a Canola SX100 programmable calculator. I have read somewhere that it can produce graphs, parabolic curves, etc but I cannot find how to do it. I have scoured the instruction manual to no avail. Could you help me, as such a facility would be invaluable in physics and chemistry, and I would also gain a greater understanding of programming as such. (I. K., Victoria.)

● Sorry, I.K., but this is the kind of question which is outside the scope of our query service. We have to restrict this service to helping readers who are in trouble with one of our own projects. We simply are not set up to handle queries of a general nature, such as this one. Perhaps a letter to the makers might be more fruitful.

**PLAYMASTER 40/40:** I have constructed two Playmaster 40/40 amplifiers, both of which operate very well. After the two volts drop across the 100 ohm resistors had stabilised, I left the meter connected to the resistor and I placed the lid on the amplifier, running the meter leads under the lid. After the lid was on for only a couple of minutes, I noticed the voltage drop was over four volts and still increasing steadily.

I realise that this occurred due to temperature effects but I wonder what the voltage drop would be after a few hours. Should I use a different setting, depending on whether I operate the unit with lid on or off. I hope I don't sound too confusing but this is bothering me. I am now running both amps with the lids off to avoid doing damage

or at least too much current being drawn with the lids on. (Not signed, Wollstonecraft, NSW.)

● The quiescent current setting in the Playmaster 40/40 is not particularly critical. If you had left the amplifier on for some time you should have found that, after some initial overshoot, the quiescent current would stabilise at some value not too far removed from the initial setting. It is immaterial whether the amplifier is operated with lid on or off, since the quiescent current transistor (T15, T115) is in thermal contact with the output transistors via the chassis.

**LOW COST VDU:** I plan on building your Low Cost VDU and keyboard encoder described in the February and April 1978 editions respectively. As I have a SC/MP microprocessor which requires +5V at 350mA and -12V at 200mA, I was wondering if it is possible to use the VDU power supply for the microprocessor also? (B.F., Winston Hills 2153).

● No extra circuitry can be powered from the VDU power supply, as this is already fully utilised in supplying the VDU. It would be possible to use a larger transformer and a regulator with a higher current capability, although this would involve considerable redesign.

## Notes & Errata

**FET VOLTMETER** (September, 1978, File No. 7/M/55: The printed circuit board No. 78/mv/8 listed in the parts list should read No. 78/vm/8.

**BACK NUMBERS:** Available only until our stocks are exhausted. Within three months of publication, face value. Four months and older, if available, \$2. Post and packing 60c per issue extra.

**OTHER QUERIES:** Technical queries outside the scope of "Replies by Post" may be submitted without fee, for reply in the magazine, at the discretion of the Editor.

**COMMERCIAL, SURPLUS EQUIPMENT:** No information can be supplied.

**COMPONENTS:** We do not deal in electronic components. Prices, specifications, etc., should be sought from advertisers or agents.

**REMITTANCES:** Must be negotiable in Australia and made payable to "Electronics Australia". Where the exact charge may be in doubt, we recommend submitting an open cheque endorsed with a suitable limitation.

**ADDRESS:** All requests to the Assistant Editor, "Electronics Australia", Box 163, Beaconsfield, 2014.

If you are unable to complete an "Electronics Australia" project because you missed out on your regular issue, we can usually provide emergency assistance on the following basis:

**PHOTOSTAT COPIES:** \$2 per project, or \$2 per part where a project spreads over multiple issues. Requests can be handled more speedily if projects are positively identified, and if not accompanied by technical queries.

**METALWORK DYELINES:** Available for most projects at \$2 each, showing dimensions, holes, cutouts, etc., but no wiring details.

**PRINTED BOARD PATTERNS:** Dyeline transparencies, actual size but of limited contrast: \$2. Specify positive or negative. We do not sell PC boards.

**REPLIES BY POST:** Limited to advice concerning projects published within the past two years. Charge \$2. We cannot provide lengthy answers, undertake special research or discuss design changes.

**LATHES.** Pursue your hobby with a good investment

**MYFORD BENCH LATHES ML7 & Super 7** from \$1384 plus 15%

**PRAKASH 3½" LATHES** motorised ½hp, S.P. 2 steadies, faceplate, 2 chucks, etc. \$1140 or \$1311 tax paid  
**HERCUS 4½" & 5" Model V-bed lathes.** Also 11¼" swing x 23" & 33" Bench Lathes from \$1650

Plus 15% sales tax if applicable.

All tools, chucks, engineers' equipment, bench drills, milling machines.



### DEMCO MACHINERY CO PTY LTD

Box M88, Sydney Mall Exchange 2012  
Box 56, Newstead, Queensland 4006  
Box 56, Newstead, Q'land 4006  
484 Spencer St, W Melb, Vic 3003

### PLEASE SEND WITHOUT OBLIGATION BROCHURES & PRICELIST

Name .....

Address .....

Phone .....

I understand that if bought from this coupon, 5% discount applies during the month of issue.

## "Retailers"

**TANDY  
ELECTRONICS  
DEALER**



**NOW  
YOU CAN ADD  
EXTRA PROFIT  
TRAFFIC  
VOLUME**

**TO YOUR ESTABLISHED RETAIL STORE  
AND GET THE BEST OF BOTH WORLDS!**

Our Authorised Sales Centre programme is a proven way to increase retail sales and profits. Choose the famous Tandy products you want to add to your line—and keep your own identity! If you have a successful store (hardware, furniture, appliance, jewellery, photo, chemist, etc.) in a town of under 20,000 contact us NOW. A minimum investment covering inventory and start-up costs can begin a rewarding association with Tandy, a leader in home entertainment and electronics!

Call or Write to:

A.S.C. Area Director: Mr. Ed Epps,  
280-316 Victoria Road, Rydalmere, NSW. 2116.  
Phone (02) 638 6633

**TANDY  
ELECTRONICS**



## DICK SMITH ELECTRONICS

### BRANCH MANAGERS



You've probably heard about us . . . Yes, we're the company that flies Antarctic flights, tows icebergs and sells heated toilet seats.

We also run a successful electronics company and right now we're searching for enthusiastic self-motivated people to train as branch managers for future expansion.

Applicants must be a minimum of 25 years, have retail management experience, a basic knowledge of electronics and also be prepared to move interstate.

Commencing salary will depend on ability. New electronics centres will be opening soon — so why not come and join a "different" Australian company? For further information, call (02) 439 5311

Mr Ike Bain  
General Manager  
Dick Smith Electronics Pty. Ltd.  
24 Carlotta Street,  
Artarmon, NSW 2064

## LANTHUR ELECTRONICS

69 Buchanan Ave, PO Box 162, North Balwyn,  
Vic 3104. Ph. 859 4061.

### BATTERY SAVER KITS

Will supply dc voltages from 2 to 15. Suitable radios, record players, toys, instruments, etc. You get transformer, rectifier, cap and circuit.

|                     |                |
|---------------------|----------------|
| <b>One amp size</b> | <b>\$9.25</b>  |
| Plus post Vic       | \$1.00         |
| Other               | \$2.50         |
| <b>Two amp size</b> | <b>\$12.95</b> |
| Plus post Vic       | \$1.25         |
| Other               | \$3.00         |

### BATTERY CHARGER KITS

Will charge 12 volt wet batteries @ 2 amp. You get transformer, rect., ballast resistor and circuit

|               |        |
|---------------|--------|
| Plus post Vic | \$1.00 |
| Other         | \$2.50 |

Surplus postage refunded

**ELECTRIC MOTOR SPEED CONTROL KITS.** Will control brush type ad/dc motors down to stop without loss of torque. Use with hand tools, lathes, potters' wheels, etc. 10 amp, 2400 watt capacity \$10.95  
Price includes postage.

### LAMP DIMMER KITS

Will control incandescent lamps from full to out. Useful for protection of projection lamps, theatrical, etc. Available with rotary or slider controls. 10 amp, 2400 watt capacity. \$8.95  
Price includes postage.

**CABINETS.** Aluminium suit batt saver kit, 1 amp \$2.95, 2 amp \$3.25. Batt charger kit \$3.25. Speed kits and dimmer kits, Alum \$2.95, Plastic with alum lid, \$1.95.

# Marketplace

## FOR SALE

**PAGE PRINTERS. MOD 15 \$30 to \$60 READERS \$20.**  
Studio 20 Sales 367 Bourke Street, DARLINGHURST  
2010. Tel. 31 3383.

**DUAL TRACE OSCILLOSCOPE,** telequipment, brand new condition, 10 MHz, X-Y MODE, TV line or frame trigg, ext. trigg., Z mod., complete with screened probes, \$490. Phone (03) 878 1537.

**NEAR COMPLETE COLLECTION** of Electronics Australia from Volume 1, No. 1 in good condition. Address offers to F. Kneen, 101 High Street, Brighton, Qld 4014.

**MAKE FRIENDS** with your Tape Recorder. Join ATRA the Australian Tapespondence Club, members in all states and overseas. All welcome. SAE to ATRA, Box 970, GPO Adelaide, 5001.

**DISCONE ANTENNA HUB:** Machined disc and cone only \$30; complete hub (with insulator and 50' coax skt) \$45. J. L. HARLAND, 83 King Edward Ave, Albion 3020.

**AUSTRALIAN RADIO DX CLUB** for 14 years the club for both MW and SW Dxers throughout Australia. Our monthly magazine is packed with the latest DX information. For further details write to P.O. Box 67, Highett Vic. 3190 or P.O. Box 79 Narrabeen NSW 2101. Enclosing a 30c stamp for reply.



**FREE SAMPLE LED** against 20c SAE  
To see is to buy. Best value in LED.  
in Aust. No brag just fact. Quality.  
17c ea. \$12 a 100, \$110 a 1000, 40c P&P  
5mm red well diffused wide viewing angle.  
Clips 3c each all quantities. Diggerman  
Electronics, Box 33, Coramba, NSW 2466.

**LEVEL 1 SOFTWARE** for use with TRS-80  
**DRAUGHTS GAME** (4K Memory required) — You against the Computer Board and pieces displayed on screen. \$7.50.

**LUNAR LANDER (4K)** — Land the Lunar Excursion Module on the Moon, and take off again, if you have enough fuel . . . with animated graphics, (moving LEM, dust, jets, etc). \$10.00.

**STAR TREK (16K)** — You are Captain Kirk of the US Star Ship Enterprise. Your mission is to rid the galaxy of the deadly Klingon menace. With seven commands, including phasers, photon torpedoes and shields. \$15.00.

Send cheques or money order for cassette(s) or \$1 for catalogue and documentation (supplied free with any cassette). Functioning programs and readable cassettes guaranteed. CREATIVE SOFTWARE, 28 Palmerston St., BERWICK, Vic. 3806 (03) 707 2851 AH.

**SPEAKER BOXES.** Hand-made, excellent acoustically  
Write: Sherwood Electronics, PO Sherbrooke 3789.

**DISPLAY ADVERTISEMENTS IN MARKETPLACE** are available in sizes from a minimum of 2cm x 1 col rated at \$11 per col cm. **CLASSIFIED RATES \$2 per line per insertion payable in advance. Minimum two lines.**

**CLOSING DATE** is six weeks prior to the on-sale date. Issues are on sale the first Monday of each month.

**ADDRESS** all classified orders, copy, enquiries, etc., to: The Advertising Manager, **ELECTRONICS Australia**, Box 162, Beaconsfield 2014.

## FUNDAMENTALS OF SOLID STATE

Fundamentals of Solid State provides a wealth of information on the structure, principles, operation and applications of solid state devices. It begins with atomic theory. Successive chapters cover: diode types; unijunction, field-effect and bipolar transistors; thyristor devices; device fabrication; and microcircuits. A glossary of terms and an index complete the 120 pp book. Adopted as a text by many colleges. Fundamentals of Solid State is ideal of amateur, hobbyist, engineer or student.

## EDUC-8 COMPUTER

Still a few copies of this left, but hurry! The computer is now obsolete as a design, but you can still learn a lot about basic computer operation and programming from the hand-book.

**\$3.00 plus 60c  
p & p each**

Use this handy order form

To: Electronics Australia, PO Box 163, Beaconsfield 2014.

Please send me . . . . . copies of Fundamentals of Solid State.

Please send me . . . . . copies of EDUC-8 Computer.

(Price at \$3.60 each includes packing and postage.)

NAME . . . . .

ADDRESS . . . . .

STATE . . . . . POSTCODE . . . . .


I enclose a cheque/postal order to the value of \$ . . . . .




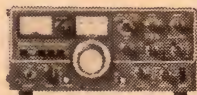
## TS520S

The TS520S Transceiver is designed and engineered for the enthusiast who wants the most professional equipment made. It provides full coverage on all amateur bands from 1.8 to 29.7MHz, with 160 to 2 meters on SSB and CW.



## TS820S

The TS-820S is the rig that is the talk of the Ham Bands. Covers 160 thru to 10 meters. This transceiver has so many features, that there are too many to list.

Write in for further information today.

## DRAKE SSR-1

The SSR-1 Receiver provides precision tuning over the short wave spectrum of 0.5 to 30MHz.

- \*Synthesised
- \*General Coverage
- \*Low Cost
- \*Selectable Sidebands
- \*All Solid State
- \*Built-in AC Power Supply
- \*Excellent Performance



## SWTC

### CT-64 TERMINAL SYSTEM

- \*64 or 32 characters per line
- \*Upper and lower case letters
- \*Full 8 bit memory
- \*128 character ASCII set
- \*Scrolling or page mode operation
- \*Control character decoding — 32 combination
- \*Prints control characters
- \*Usable with any 8 bit ASCII computer



### THE FLUKE 8020A THE DIGITAL MULTIMETER FOR THE PROFESSIONAL

The 8020A is designed for the widest possible range of applications. All accessories available to extend your 8020A measurements. Priced at: \$227.50.



### FM MONITOR MINI

This FM Monitor goes wherever you go. It has a bandwidth as wide as 4MHz (150 MHz band). Priced at: \$125.00 + Crystals.

## Yaesu

WRITE IN FOR  
FURTHER DETAILS

### FT101E



### Bearcat 210 Scanner

The Bearcat 210 super synthesised receiver scans and searches over 16,000 different frequencies without expensive crystals. The Bearcat 210 covers 32-50, 146-174 and 416-512MHz, and has AC/DC operation.

Prices do  
not include  
P & P

ALL ACCESSORIES  
TO COMMUNICATIONS  
EQUIPMENT ARE  
AVAILABLE  
ON REQUEST

# NEW! ELECTRICAL INDUSTRY BIBLE



Published by ELECTRICAL INDUSTRY ADVERTISING

128 PAGES 8 1/4" x 11 3/4"  
**ORDER NOW!**

\$6.40 Post Paid  
To EIA PO Box 139 Glenroy 3046

AVAILABLE AT TECHNICAL BOOK SHOPS  
OR BY MAIL ORDER

INDUSTRIAL and DOMESTIC articles on: Testing methods and equipment • Cable Terminations • Contactors Controls and Relays • Transformers • Basic Refrigeration • Switchboards Domestic and Industrial • MIMS cables • Bus Duct Systems.

Vital Information on: Emergency First Aid for electricians • Electrical Licencing in Australia • Electric Ranges • Hot Water Systems • Safety Hints • Earth Leakage Circuit Breakers • and much more.

Large Reference Section: Formulae — (general • 1 and 3 phase • motors • lighting etc.), Tables • Conversions • Technical Data • Basic Circuit Diagrams. Listings for the Electrical Trade • Publications • Electrical Authorities • Organisations

## an Australian reference book for Electricians, Technicians and Engineers

Published by Electrical Industry Advertising  
Reg. Office 91 Vincent Street Oak Park

To EIA Box 139 Glenroy 3046  
Enclosed is cheque for ..... copies  
at \$6.40 each including packing and postage  
Name .....  
Address .....  
Postcode .....



# PRICES SLASHED!



COMPARE THESE MONEY SAVERS

|      |                   |                                                              |                                                                    |                                                                      |
|------|-------------------|--------------------------------------------------------------|--------------------------------------------------------------------|----------------------------------------------------------------------|
| 7400 | TTL<br>36c<br>28c | 2N3055 <del>\$1.00</del><br>75c<br>Transistor<br>c/w Washers | 7805<br>7806<br>7808<br>7812<br>7815<br>7818<br>7824<br>Regulators | 741 50c<br>Op Amps 35c                                               |
| 7401 |                   |                                                              |                                                                    |                                                                      |
| 7402 |                   |                                                              |                                                                    |                                                                      |
| 7403 |                   |                                                              |                                                                    |                                                                      |
| 7404 |                   |                                                              |                                                                    |                                                                      |
| 7405 |                   |                                                              |                                                                    |                                                                      |
| 7408 |                   | 7442 <del>\$1.00</del><br>65c                                |                                                                    | 4000<br>4001<br>4002<br>4007<br>4011<br>4012<br>4023<br>4025<br>CMOS |
| 7409 |                   |                                                              |                                                                    |                                                                      |
| 7410 |                   |                                                              |                                                                    |                                                                      |
| 7411 |                   |                                                              |                                                                    |                                                                      |
| 7412 |                   |                                                              |                                                                    |                                                                      |
| 7420 |                   | 7446 <del>\$1.40</del><br>\$1.00                             | 555 65c<br>Timers 45c                                              |                                                                      |
| 7430 |                   |                                                              |                                                                    |                                                                      |
| 7440 |                   |                                                              |                                                                    |                                                                      |
| 7450 |                   |                                                              |                                                                    |                                                                      |
| 7451 |                   | 7475 90c<br>65c                                              | 74154 <del>\$2.10</del><br>\$1.50                                  | 4016 85c<br>50c                                                      |
| 7453 |                   |                                                              |                                                                    |                                                                      |
| 7454 |                   |                                                              |                                                                    |                                                                      |
| 7460 |                   |                                                              |                                                                    |                                                                      |

\*\*\* SPECIAL \*\*\* LM309K \*\*\* \$1.30

LOTS MORE \$\$\$ SAVERS JUST WRITE FOR YOUR FREE COPY  
OF OUR CATALOGUE

PACK AND POST 50c MINIMUM — PLEASE ALLOW MORE FOR HEAVIER ITEMS

LINEAR ELECTRONICS

P.O. BOX 254,  
PUNCHBOWL 2196

## ADVERTISING INDEX

|                                           |                                                   |
|-------------------------------------------|---------------------------------------------------|
| A & R Soanar                              | 121                                               |
| ASP Microcomputers                        | 87                                                |
| Ace Radio                                 | 132                                               |
| Adcola Products                           | 37                                                |
| All Electronic Components                 | 78                                                |
| Applied Technology Pty Ltd                | 84                                                |
| Audio Telex Communications Pty Ltd        | 48                                                |
| Australian Computer Products Pty Ltd      | 129                                               |
| Australian General Electric Pty Ltd       | 7                                                 |
| Australian Government Recruiting          | 81                                                |
| BASF (Aust.) Pty Ltd                      | In colour section                                 |
| Bail Electronic Services                  | 107                                               |
| Bright Star Crystals Pty Ltd              | 104                                               |
| Cash-More Sound Systems Pty Ltd           | 57                                                |
| Cema (Distributors) Pty Ltd               | 51                                                |
| Chirnside Electronics                     | 102                                               |
| Classic Radio                             | 116                                               |
| Convoy International Pty Ltd              | 34                                                |
| Customs Communications                    | 113                                               |
| Deitch Bros                               | 110                                               |
| Delta Design Laboratory                   | 93                                                |
| Demco Machinery Co Pty Ltd                | 125, 133                                          |
| Dick Smith Electronic Group               | 28, 29, 46, 58, 59, 89,<br>97, 108, 109, 128, 134 |
| Diggerman Electronics                     | 134                                               |
| E. D. & E. (Sales) Pty Ltd                | 78                                                |
| Electrical Industry Advertising           | 135                                               |
| Electrocraft Pty Ltd                      | 113                                               |
| Electronic Calculator Discounts           | 66                                                |
| Electronics & Semi Conductor<br>Disposals | 120                                               |
| Ellistronics                              | 66                                                |
| Ferguson Transformers Pty Ltd             | 55                                                |
| Hagemeyer (Aust.)                         | IBC, In colour section                            |
| Harman Australia Pty Ltd                  | In colour section                                 |
| In Electronics                            | 69                                                |
| Instant Component Service                 | 88, In colour section                             |
| International Correspondence Schools      | 57                                                |
| Lanthur Electronics                       | 134                                               |
| Linear Electronics                        | 136                                               |
| McGills Newsagency Pty Ltd                | 130                                               |
| National Panasonic (Australia) Pty Ltd    | OBC                                               |
| Nomis Electronics Pty Ltd                 | 17                                                |
| Non-Linear Systems (Australia) Pty Ltd    | 21                                                |
| Parameters Pty Ltd                        | 27                                                |
| Paris Radio Electronics                   | 91                                                |
| Pennywise Peripherals                     | 90                                                |
| Philips                                   | 2, 94, 98, In colour section                      |
| Pitt Street Micro Computer Shop           | 93                                                |
| Plessey Australia Pty Ltd                 | 21, 119                                           |
| RCS Radio                                 | 63                                                |
| Radio Despatch Service                    | 115                                               |
| Radio Parts Group                         | 100                                               |
| Rank Australia Pty Ltd                    | 32                                                |
| Rod Irving Electronics                    | 124                                               |
| S.M. Electronics                          | 91                                                |
| Sanwa Electric Instruments                | 73                                                |
| Scope Laboratories                        | 25                                                |
| Sony Australia Pty Ltd                    | IFC                                               |
| Sovereign City Electronics                | 93                                                |
| Stotts Technical College                  | 65                                                |
| Superscope (A/asia) Pty Ltd               | 30, 40                                            |
| Tandy International Electronics           | 54, 133                                           |
| Technico Electronics                      | 76                                                |
| Television Replacement Service Pty Ltd    | 19                                                |
| Vanfi Pty Ltd                             | In colour section                                 |
| Vicom International                       | 103                                               |
| Video Technics                            | 56                                                |
| Warburton Franki Ltd                      | 18                                                |
| Wentworth Electronics                     | 49                                                |
| Willis Trading Co Pty Ltd                 | 67, 135                                           |
| Wireless Institute of Australia           | 105                                               |

## GETTING INTO MICROPROCESSORS



Can you afford not  
to know about microprocessors?

This book will help you find out what the  
revolution is all about . . .

Available from newsagents, electronic suppliers and also "Elec-  
tronics Australia", 57 Regent St, Sydney. **PRICE \$4.50** OR by mail  
order from "Electronics Australia", PO Box 163, Beaconsfield  
2014. **PRICE \$5.10.**

## SUBSCRIPTION SERVICE



**ELECTRONICS  
Australia**

### Subscription Rates

\$A17.00 per year  
within Australia.

\$A20.00 per year  
elsewhere.

Make sure you receive every copy of the magazine by ordering it from your newsagent or the publisher.  
For publisher subscriptions post this coupon, with your remittance, to Electronics Australia Subscription  
Dept., John Fairfax & Sons Ltd, GPO Box 506, Sydney, 2001. Subscription will start with first available  
issue.

Name . . . . .

Address . . . . .

Postcode . . . . . Enclosed is . . . . . for . . . . . years



# FILL OUT THIS COUPON AND WE'LL SEND YOU 30 NEW WAYS TO ENJOY HI-FI



## FREE! COLOUR HI-FI CATALOGUE

JVC have just released 30 new Hi-Fi products.  
And how many companies in this magazine can make  
that statement?

It's worthy to note that these new JVC Hi-Fi Products are not just a design or cosmetic change, but are the culmination of years of research and development. Resulting in innovations and performance features such as:— Quartz locked turntables with uncanny accuracy; Receivers/Amplifiers, some with built in SEA Graphic Equaliser and DC, class A/B amplification. Cassette decks with the revolutionary Spectro Peak Indicators; Computer designed speaker systems; Separate but matching components designed to complement one another, perfectly. In fact, the finest JVC audio range ever produced.

# JVC

Altogether you'll find out what's available and new in terms of JVC Hi-Fi enjoyment.

And all this know-how is yours... merely for the asking.

Just fill out this coupon and we'll fill you in...

Name .....

Address .....

..... Post Code .....

I am especially interested in...

- |                                           |                                     |
|-------------------------------------------|-------------------------------------|
| <input type="checkbox"/> Cassette Decks   | <input type="checkbox"/> Speakers   |
| <input type="checkbox"/> Amplifiers       | <input type="checkbox"/> Turntables |
| <input type="checkbox"/> Matching Systems | <input type="checkbox"/> Receivers  |

WT51/78

## the right choice

ADDRESS YOUR ENVELOPE TO...JVC ADVISORY SERVICE, POST OFFICE BOX 49, KENSINGTON, N.S.W. 2033



ST-9030

SU-9070

SH-9010

SH-9020

SE-9060



# Technics DC 'Flat Series'. Components literally made for each other.

In creating the 'flat' system, Technics engineers separated the basic amplifier / tuner into five components, researched and developed each, then recombined them into a system of audio excellence.

The system consists of:

Stereo Tuner (ST-9030) with wide and narrow IF bands.

Stereo DC Preamp. (SU-9070) with phono signal-to-noise ratio of 88dB (for 2.5 mV input).

Stereo Universal Frequency Equaliser (SH-9010) for exact response control in any acoustic environment.

Peak/ Average Meter Unit

(SH-9020) for exact response measurement.

Stereo/ Mono DC Power Amplifier (SE-9060) with all-stage direct-coupled pure complementary symmetry circuitry. Total harmonic distortion is 0.02%.

Each individual component offers a degree of fidelity in sound reproduction, and a flexibility and ease of operation that makes it a natural choice for the audio fan who cannot be content with less than the best.

 **Technics**  
hi-fi

For a National Technics Catalogue, please write to:  
National Technics Advisory Service, P.O. Box 49, Kensington, N.S.W. 2033.